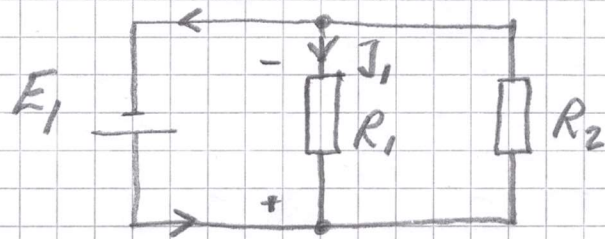


A0.3



$$-J_1 = \frac{E_1}{R_1}$$

$$J_1 = -\frac{E_1}{R_1}$$

$J_1$  GÅR ÅT MOTSATT HÅLL