



$$u_{in} - u + u_o = 0 \quad \dots (1) \quad u_o = 0$$

$$u_{out} + R \cdot i + u_o = 0 \quad \dots (2)$$

$$i = C \cdot \frac{du}{dt}$$

$$(1) \rightarrow u = u_{in} \quad \Rightarrow \quad i = C \cdot \frac{du_{in}}{dt}$$

$$\text{INS } , (2) \Rightarrow$$

$$u_{out} + CR \cdot \frac{du_{in}}{dt} = 0 \quad \Rightarrow \quad u_{out} = -CR \cdot \frac{du_{in}}{dt}$$