

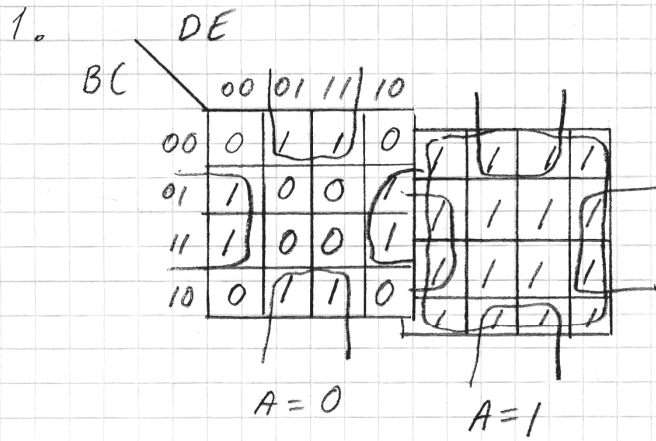


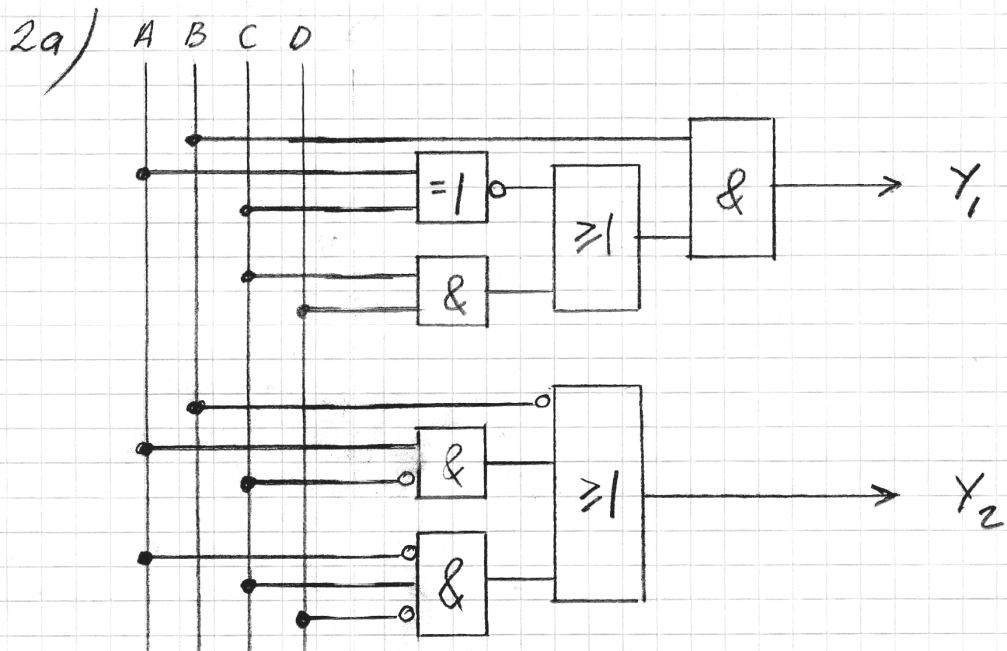Lösningförslag till dugga 2 i TMEL53 Digitalteknik 2015-02-04


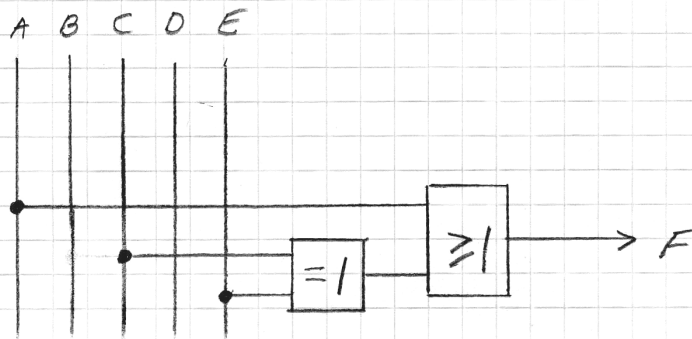
$$F = A + C\bar{E} + \bar{C}E = A + (C \oplus E)$$



2b) STÄLL UPP FUNKTIONSTABELLER FÖR  $Y_1$  OCH  $Y_2$  OCH JÄMFÖR DEM.

A	B	C	D	$\overline{A \oplus C}$	CD	$Y_1$
0	0	0	0	1	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	1	0
0	1	0	0	1	0	1
0	1	0	1	1	0	1
0	1	1	0	0	0	0
0	1	1	1	0	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	0	1	1	1	1	0
1	1	0	0	0	0	0
1	1	0	1	0	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	1

A	B	C	D	$\overline{B}$	$\overline{A \overline{C}}$	$\overline{A \overline{C} \overline{D}}$	$Y_2$
0	0	0	0	1	0	0	0
0	0	0	1	1	0	0	0
0	0	1	0	1	0	1	0
0	0	1	1	1	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	0	1
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	0	1	0	0
1	1	0	1	0	1	0	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	0	1

AV TABELLERNA OVAN FRAMGÅR  
ATT  $Y_2 = Y_1$  V.S.V.

ALTERNATIV : ANVÄND BOOLESK ALGEBRA

$$\begin{aligned}
 Y_2 &= \overline{\overline{B + AC + \overline{ACD}}} = \overline{\overline{B} \cdot \overline{AC} \cdot \overline{\overline{ACD}}} = \\
 &= B(\overline{A+C})(A+\overline{C}+D) = (\overline{A}B + BC)(A+\overline{C}+D) \\
 &= \underbrace{A\overline{A}B}_0 + \overline{A}B\overline{C} + \overline{A}BD + ABC + \underbrace{BCC\overline{C}}_0 + BCD \\
 &= B(\overline{A}\overline{C} + \overline{A}D + AC + CD) = \\
 &= B(\overline{A}\overline{C} + \overline{A}(\overline{C}+C)D + AC + CD) = \\
 &= B(\overline{A}\overline{C} + \overline{A}\overline{C}D + \overline{A}CD + AC + CD) = \\
 &= B(\overline{A}\overline{C}(\underbrace{1+D}_1) + CD(\underbrace{\overline{A}+1}_1) + AC) = \\
 &= B(\overline{A}\overline{C} + AC + CD) = \\
 &= B((\overline{A \oplus C}) + CD) = Y_1 \quad \text{V. S. V.}
 \end{aligned}$$