



Dugga 2: Boolesk algebra och kombinatoriska nät

För godkänt på duggan krävs minst 7 poäng av 10 möjliga.

1. Konstruera ett kombinatoriskt nät med valfria grindar som fungerar enligt vidstående sanningstabell. För full poäng får max två grindar användas.

(4 p)

A	B	C	D	E	F
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	1	0	0
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	0	1	0
0	0	1	1	0	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	0
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	1

2a) Rita grindnäten för $Y_1 = B((\overline{A \oplus C}) + CD)$ och $Y_2 = \overline{B + AC + \overline{ACD}}$. (3 p)

2b) Visa att $Y_2 = Y_1$. (3 p)

Boolesk algebra

Satser för en variabel:

$$A + A = A$$

$$A \cdot A = A$$

$$A + \overline{A} = 1$$

$$A \cdot \overline{A} = 0$$

$$A + 1 = 1$$

$$A \cdot 0 = 0$$

$$A + 0 = A$$

$$A \cdot 1 = A$$

$$\overline{\overline{A}} = A$$

Satser för flera variabler:

$$A + (B + C) = (A + B) + C$$

Associativa
lagarna

$$A(BC) = (AB)C$$

$$A + B = B + A$$

Kommutativa
lagarna

$$AB = BA$$

$$A(B + C) = AB + AC$$

Distributiva
lagarna

$$A + (BC) = (A + B)(A + C)$$

$$A + AB = A$$

Absorptions-
lagarna

$$A(A + B) = A$$

$$\overline{AB} + AC = \overline{A}B + AC + BC$$

Consensus-
lagarna

$$(\overline{A} + B)(A + C) = (\overline{A} + B)(A + C)(B + C)$$

$$\overline{\overline{A + B}} = \overline{\overline{A}} \cdot \overline{\overline{B}}$$

de Morgans
lagar

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

$$A \oplus B = \overline{A}B + A\overline{B}$$

Omskrivning av EXOR

$$\overline{A \oplus B} = AB + \overline{A}\overline{B}$$

Omskrivning av EXNOR

Sammanställning av grindar som förekommer inom digitaltekniken

Funktion	Symbol			Funktions- tabell	Logiskt uttryck															
	IEC	Amerikansk	Äldre svensk																	
OCH AND				<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	$Y = A B$ $Y = A \wedge B$
A	B	Y																		
0	0	0																		
0	1	0																		
1	0	0																		
1	1	1																		
ELLER OR				<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	$Y = A + B$ $Y = A \vee B$
A	B	Y																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	1																		
ICKE NOT				<table border="1"> <thead> <tr> <th>A</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	Y	0	1	1	0	$Y = \bar{A}$									
A	Y																			
0	1																			
1	0																			
NAND				<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	$Y = \overline{A B}$
A	B	Y																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
NOR				<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	0	$Y = \overline{A + B}$
A	B	Y																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		
Exklusivt- ELLER Exclusive-OR EXOR			 	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0	$Y = A \oplus B$
A	B	Y																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
Exklusivt- NOR Exclusive-NOR EXNOR			 	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>Y</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1	$Y = \overline{A \oplus B}$
A	B	Y																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	1																		