

# TSEA83 : Datorkonstruktion

## Fö10

VHDL 3/3

# Fö10 : Agenda

- Repetition  
buffer, record, loop  
kombinatoriska processer
- Varning  
latchar, hasard
- uprogCPU  
VHDL-kod för mikromaskin med  
hämtfas
- Minnen i FGPA  
Distributed RAM (LUT)  
Block-RAM
- 3-portars registerfil
- pipeCPU  
VHDL-kod för pipeline-CPU med  
instruktionshämtning
- VGA-labben
- Kravspec + Designspec

# Repetition, sekvensnät

*Buffer, record, loop, kombinatoriska processer*



# Istället för buffer skapa en intern signal och använd out som vanligt

```


library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity counter is
port(clk, clear: in std_logic;
      qout: out unsigned(3 downto 0));
end counter;

architecture simple of counter is
  signal q: unsigned(3 downto 0);
begin
  process(clk)
  begin
    if rising_edge(clk) then
      if clear='0' then
        q <= "0000";
      elsif q=9 then
        q <= "0000";
      else
        q <= q + 1;
      end if;
    end if;
  end process;

  qout <= q;
end simple;


```

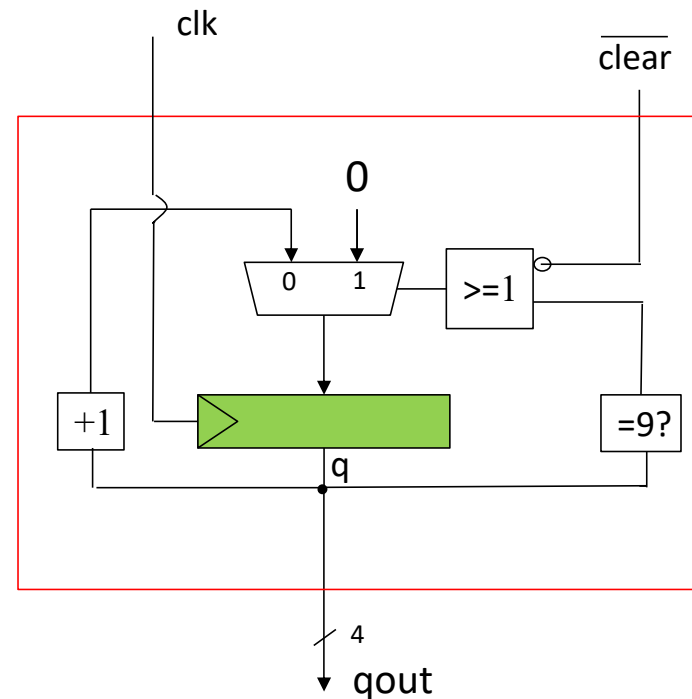

Varför?  
 Modelsim "gillar inte" buffer!

 
# Datorkonstruktion **record**

```
type controlword is record
  alu: unsigned(3 downto 0);
  tobus: unsigned(2 downto 0);
  halt: std_logic;
```



```
end record;
```
 
```
type styrminne is array(0 to 31) of controlword;
```



```
signal styr1, styr2: controlword;
```

```
signal mm: styrminne;
```

```
--
```

```
styr1.halt <= '0';
```

```
styr1.alu <= "1011";
```

```
styr1.tobus <= styr2.tobus;
```

```
--
```


```
mm(3) <= ("1011", "111", '0');
```

# Lite överkurs - loop

Vi har en buss  $x$ , med 32 ledningar. Vi vill bilda paritet mellan alla ledningarna. Loopen beskriver på ett kompakt sätt det kombinatoriska nätet!

```
entity parity is
    port ( x : in  UNSIGNED (31 downto 0);
          pout : out  STD_LOGIC);
end entity;

 
architecture func of parity is
begin
    -- kombinatoriskt nät
    process (x)
        variable p: std_logic := '0';
    begin
        for i in 31 downto 0 loop
            p := p xor x(i);
        end loop;
        if p='1' then
            pout <= '1';
        else
            pout <= '0';
        end if;
    end process;
end architecture;
```


 
# Kombinatoriska processer

Vi kan använda `process` för att göra kombinatorik  
 + `if`- och `case`-satarna blir tillgängliga  
 - varning för latchar!

Exempel:  $\delta/\lambda$ -nätet i ett sekvensnät



```
process (clk)
begin
  if rising_edge (clk)
    q <= qplus;
  end if;
end process;
```

```
process (x, q)
begin
  u <= "00";
  qplus <= idle;

  -- sats för delta/lambda
  -- nu räcker det att beskriva
  -- när det inte ska va default
  ...
end;
```

alla insignaler, ej clk

Default-värden  
för alla utsignaler



# Kombinatoriska processer lämpar sig inte alltid

```
process (b)
begin
  y <= '0';
  if b='1' then
    y <= '1';
  end if;
end process;
```

betyder

```
process (b)
begin
  if b='1' then
    y <= '1';
  else
    y <= '0';
  end if;
end process;
```

Blir KN

```
y <= b;
```

Det lämpar sig inte alltid med en kombinatorisk process.

# Ett varningsord : Önskade latchar

Vid **select-sats** och **case-sats** kräver VHDL att alla fall täcks!

Det är inte nödvändigt vid **if-sats** och **when-sats**!


Ibland är detta bra och ibland är det förskräckligt dåligt.

**För de fall som inte täcks bibehålls föregående utsignal.**

	Sekvensnät (inuti klockad process)	Kombinatorik?
Ofullst.	<pre> <b>if</b> count='1' <b>then</b>   q &lt;= q+1; <b>end if</b>; </pre>	<pre> u &lt;= y <b>when</b> s(1) = '1' <b>else</b>   x <b>when</b> s(0) = '1'; </pre>
Fullst.	<pre> <b>if</b> count='1' <b>then</b>   q &lt;= q+1; <b>else</b>   q &lt;= q; <b>end if</b>; </pre>	<pre> u &lt;= y <b>when</b> s(1) = '1' <b>else</b>   x <b>when</b> s(0) = '1' <b>else</b>   '0' <b>when others</b>; </pre>

# Ett varningsord : Önskade latchar


Latch = asynkront minneselement

 



$s$	$u$
1	$x$
0	$x$
2	$y$
0	$y$
 
# Ett varningsord : Önskade latchar


- Önskat (oklockat) minneselement pga kombinatorisk loop
- Ihopkoppling av Mealy-nät kan ge kombinatorisk loop!  
Använd hellre Moore-nät!



 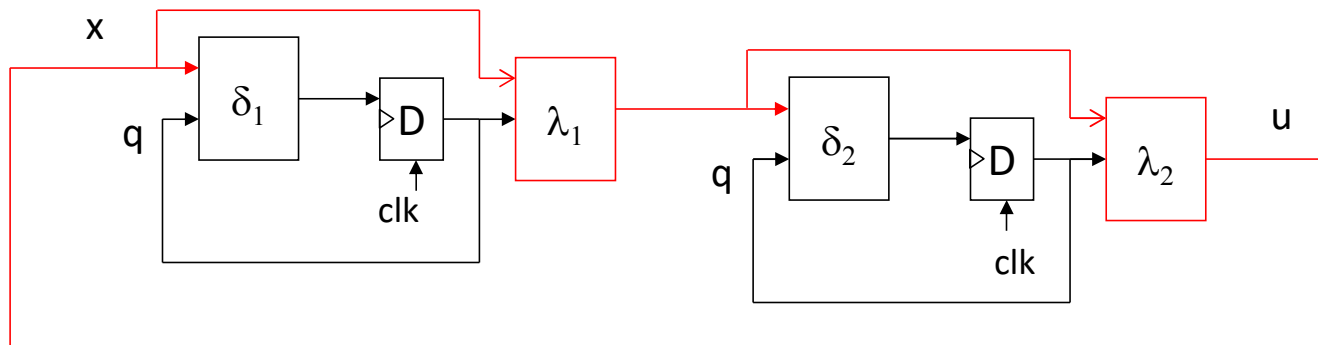Kombinatorisk återkoppling kan även orsaka självsvängning, t ex om signalen inverteras ett ojämnt antal gånger.




# Synkronisering + enpulsning. Bra!

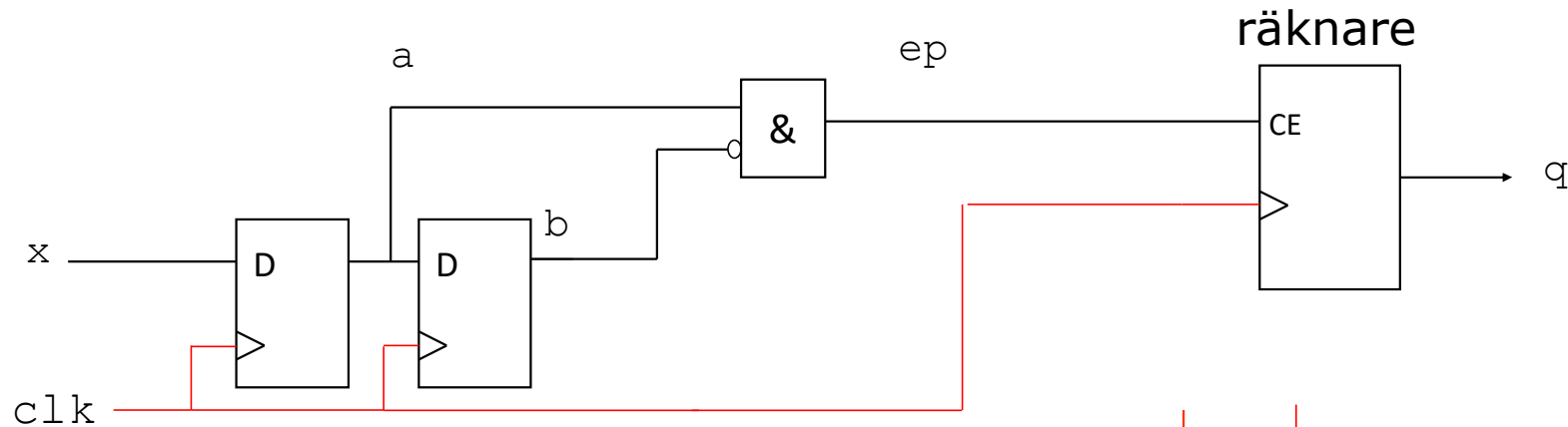

```

sep: process (clk)
begin
  if rising_edge (clk) then
    a <= x;
    b <= a;
  end if;
end process sep;
-- till räknaren
ep <= a and not b;


```

 

# Datorkonstruktion **Hasard**


Def: Kortvariga värden på utgångarna från ett K-nät när någon insignal byter värde.

Exempel:

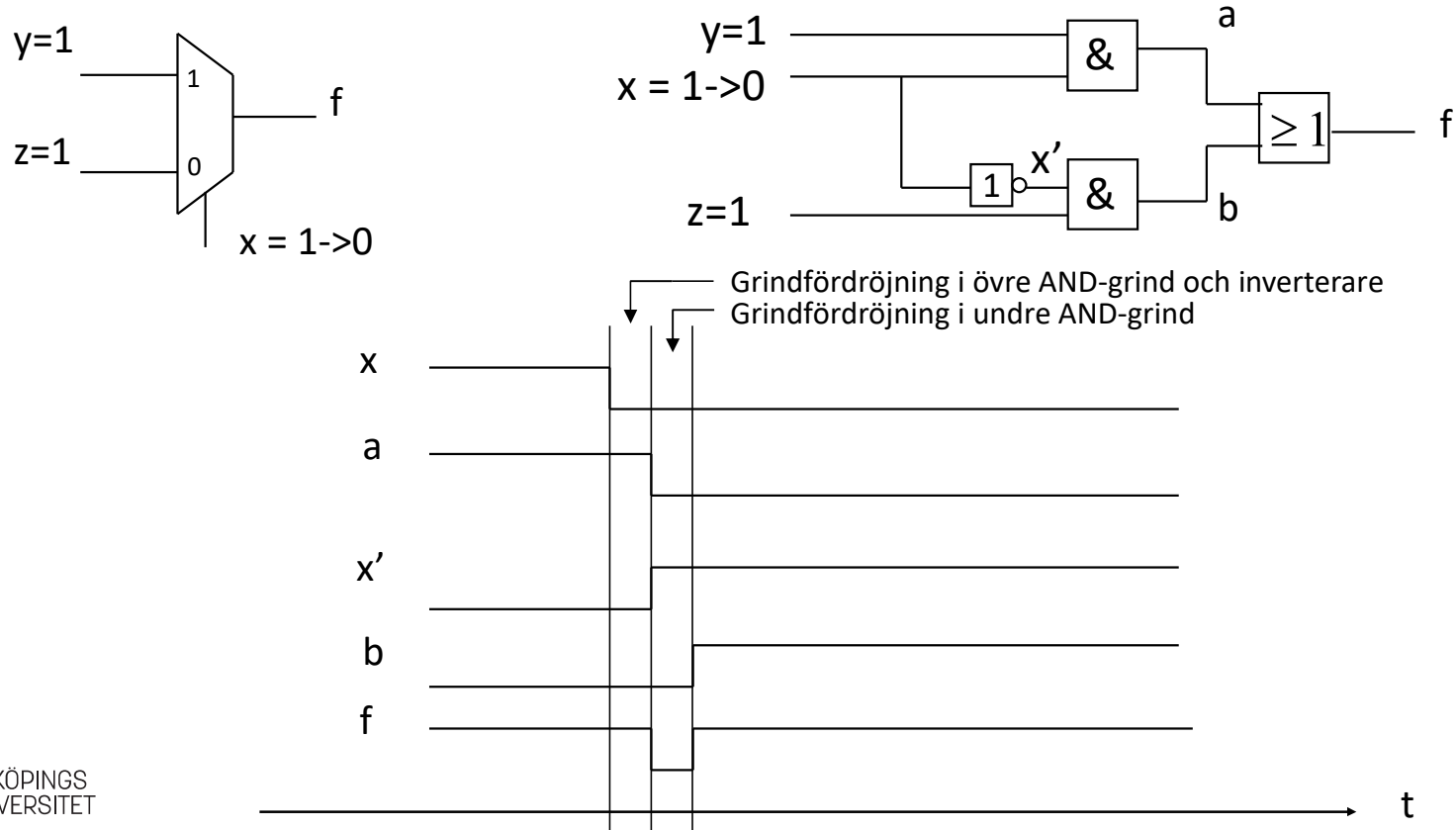
 
# Datorkonstruktion **Hasard**

Om f kopplas till en asynkron ingång, så fungerar inte nätet (som det var tänkt) !



Dvs, varning för asynkron reset!

Studera övergången i ett KD,

$$f = xz + x'y$$

	00	01	11	10
x			1	1
0			1	1
1		1	1	

Hasarden kan elimineras

- 1) genom att lägga till termen yz,  
 $f = xz + x'y + yz$
- 2) Synkronisera f
- 3) Undvika asynkrona ingångar


# uprog CPU

*VHDL-kod för mikromaskin med hämtfas*



Datorkonstruktion **Uprog CPU**

Vi börja med en enkel skiss ...

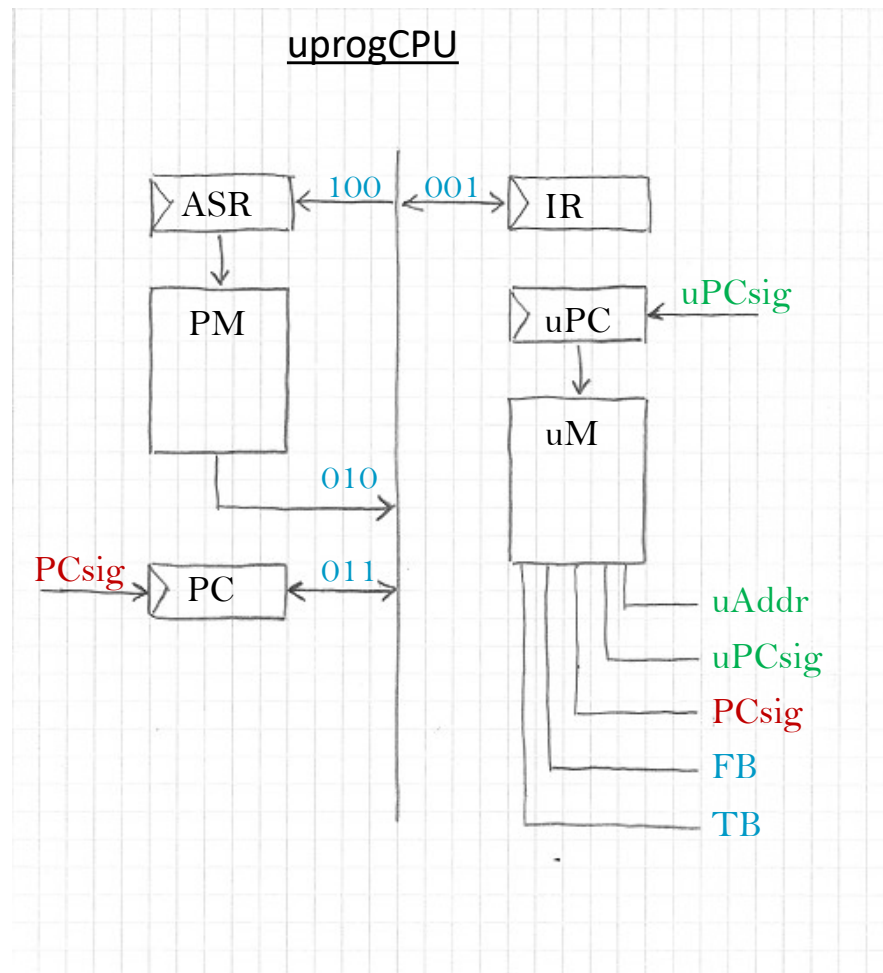

# Datorkonstruktion **Uprog CPU**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;


-- CPU interface
entity cpu is
    port(clk      : in std_logic;
          rst     : in std_logic);
end entity;

architecture func of cpu is

    -- micro Memory component
    component uMem
        port(uAddr      : in unsigned(5 downto 0);
             uData      : out unsigned(15 downto 0));
    end component;

    -- program Memory component
    component pMem
        port(pAddr      : in unsigned(15 downto 0);
             pData      : out unsigned(15 downto 0));
    end component;

end architecture;
```

 

# Datorkonstruktion Uprog CPU

## -- micro Memory signals

```
signal uM      : unsigned(15 downto 0); -- micro Memory output
alias TB       : unsigned(2 downto 0) is uM(13 downto 11);
alias FB       : unsigned(2 downto 0) is uM(10 downto 8);
alias PCsig    : std_logic is uM(7);      -- (0:PC=PC, 1:PC++)
alias uPCsig   : std_logic is uM(6);      -- (0:uPC++, 1:uPC=uAddr)
alias uAddr    : unsigned(5 downto 0) is uM(5 downto 0);
```

## -- program memory signals


```
signal PM      : unsigned(15 downto 0); -- Program Memory output
```

## -- local registers

```
signal uPC     : unsigned(5 downto 0); -- micro Program Counter
signal PC      : unsigned(15 downto 0); -- Program Counter
signal IR      : unsigned(15 downto 0); -- Instruction Register
signal ASR     : unsigned(15 downto 0); -- Address Register
```
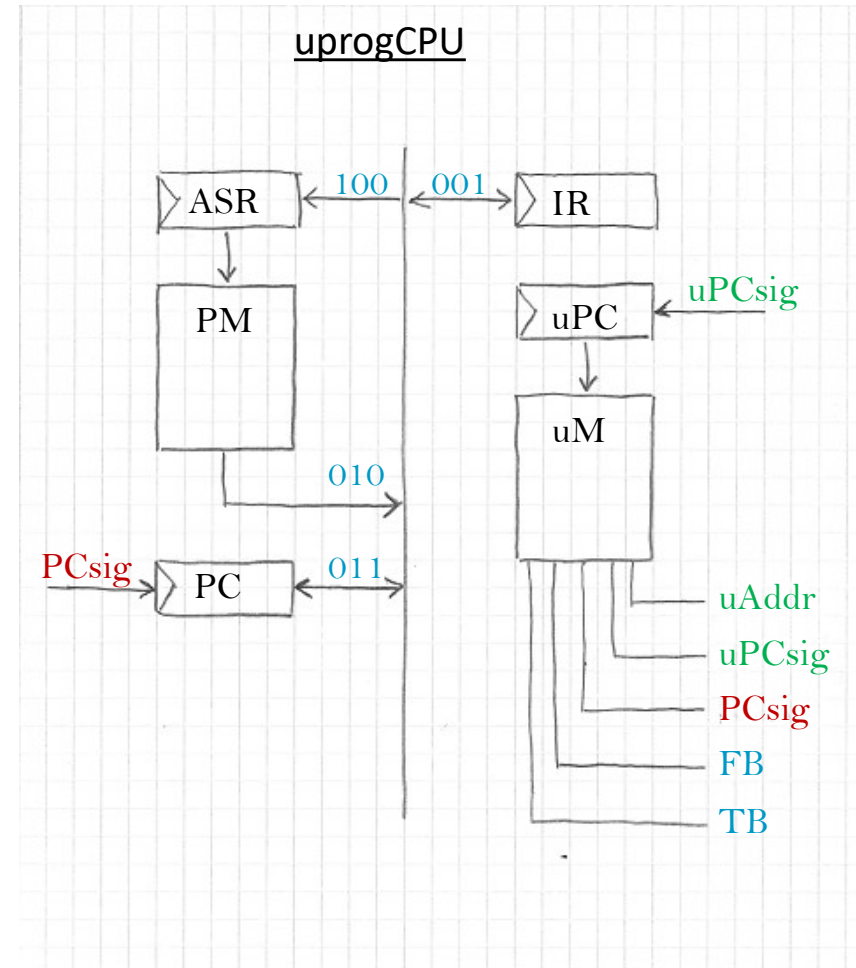
## -- local combinatorials

```
signal DATA_BUS : unsigned(15 downto 0); -- Data Bus
```




```

begin
-- mPC : micro Program Counter
process(clk)
begin
  if rising_edge(clk) then
    if (rst = '1') then
      uPC <= (others => '0');
    elsif (uPCsig = '1') then
      uPC <= uAddr;
    else
      uPC <= uPC + 1;
    end if;
  end if;
end process;

-- IR : Instruction Register
process(clk)
begin
  if rising_edge(clk) then
    if (rst = '1') then
      IR <= (others => '0');
    elsif (FB = "001") then
      IR <= DATA_BUS;
    end if;
  end if;
end process;

```

# uprog CPU

 

```

-- PC : Program Counter
process(clk)
begin
  if rising_edge(clk) then
    if (rst = '1') then
      PC <= (others => '0');
    elsif (FB = "011") then
      PC <= DATA_BUS;
    elsif (PCsig = '1') then
      PC <= PC + 1;
    end if;
  end if;
end process;


```

```

-- ASR : Address Register
process(clk)
begin
  if rising_edge(clk) then
    if (rst = '1') then
      ASR <= (others => '0');
    elsif (FB = "100") then
      ASR <= DATA_BUS;
    end if;
  end if;
end process;

```

# uprog CPU

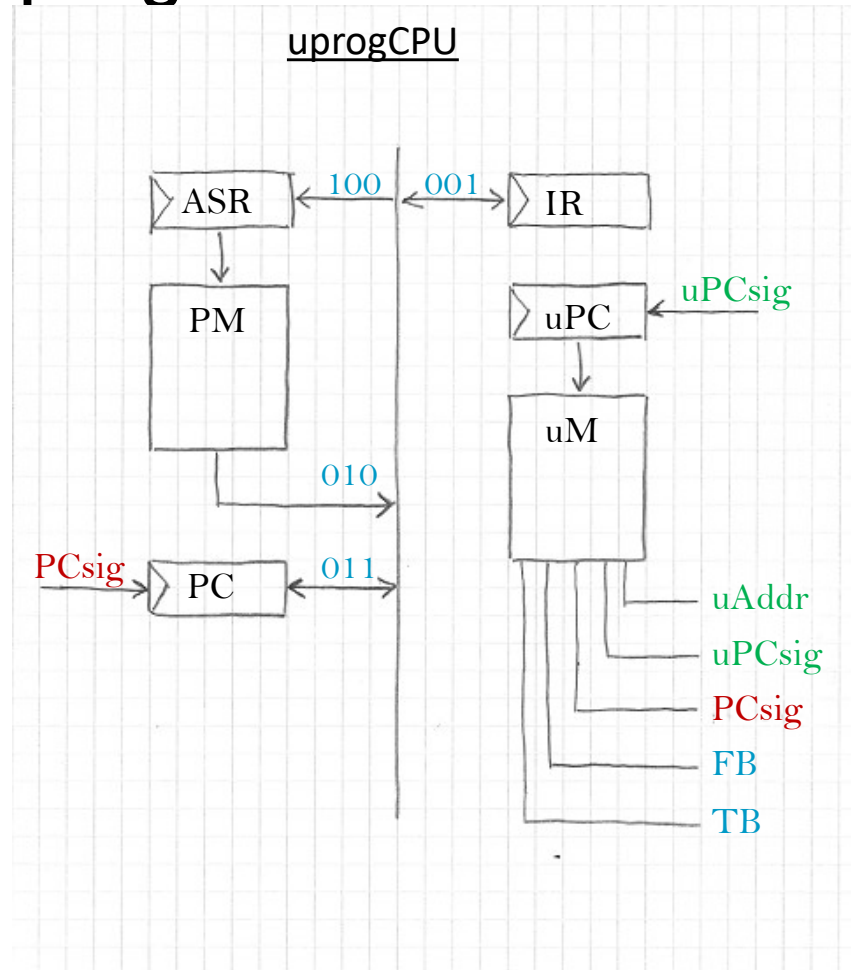

# Datorkonstruktion **Uprog CPU**

```
-- micro memory component connection
U0 : uMem port map(uAddr=>uPC, uData=>uM);


-- program memory component connection
U1 : pMem port map(pAddr=>ASR, pData=>PM);

DATA_BUS <= IR when (TB = "001") else
           PM when (TB = "010") else
           PC when (TB = "011") else
           ASR when (TB = "100") else
           (others => '0');

end architecture;
```
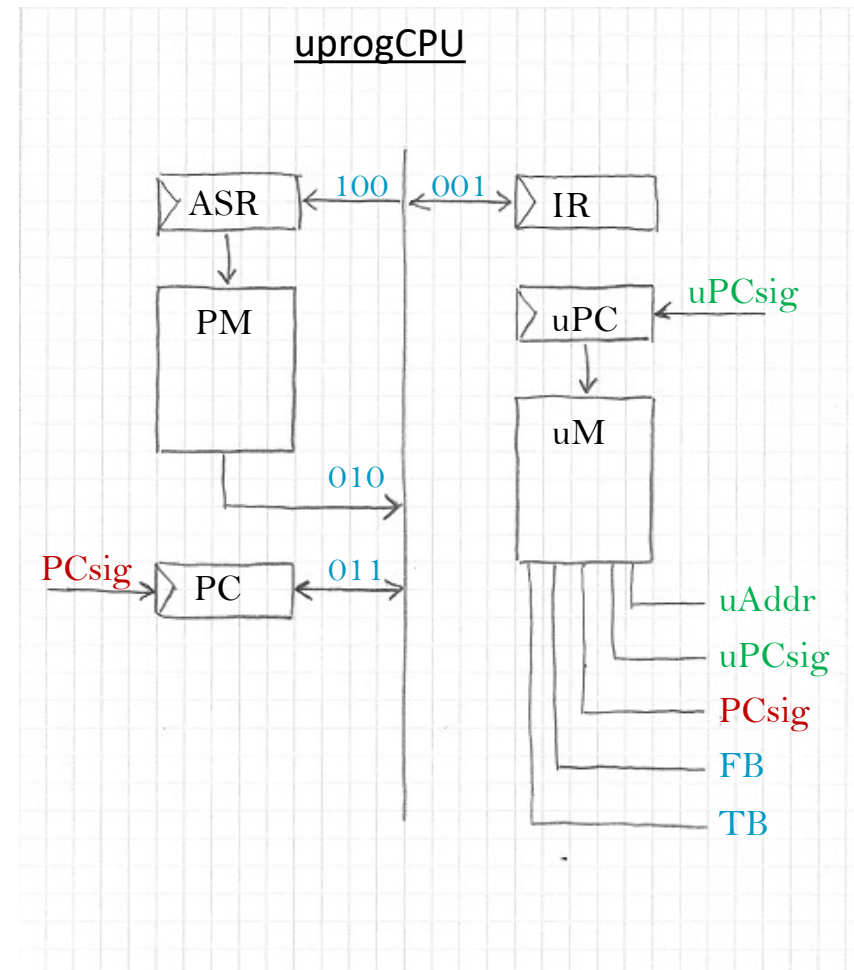
## Makefile

```
...
proj.:%: S=uprogCPU.vhd uMem.vhd pMem.vhd
proj.:%: T=uprogCPU_tb.vhd
proj.:%: U=Nexys3_Master.ucf
...
```



# Datorkonstruktion uMem.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity uMem is
    port(uAddr      : in unsigned(5 downto 0));
        uData      : out unsigned(15 downto 0));
end entity;

architecture func of uMem is
    -- micro Memory
    type u_mem_t is array (0 to 15) of unsigned(15 downto 0);
    constant u_mem_c : u_mem_t :=
        --ALU_TB_FB_PC_uPC_uAddr
        (b"00_011_100_0_0_000000",
         b"00_010_001_1_1_000000",
         b"00_000_000_0_0_000000",
         . . .
         b"00_000_000_0_0_000000");

    signal u_mem : u_mem_t := u_mem_c;


begin
    uData <= u_mem(to_integer(uAddr));
end architecture;

```

```

-- ASR:=PC
-- IR:=PM, PC:=PC+1, uPC:=uAddr

```

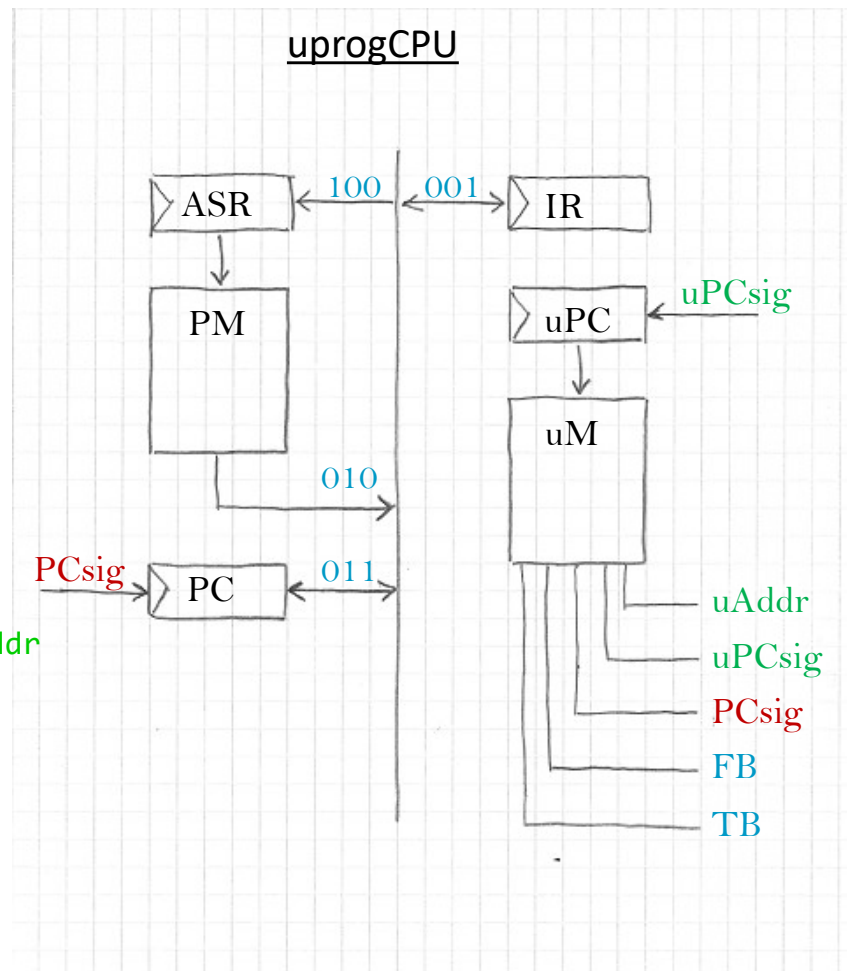

# Datorkonstruktion pMem.vhd


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity pMem is
    port(pAddr      : in unsigned(15 downto 0);
         pData      : out unsigned(15 downto 0));
end entity;

Architecture func of pMem is
-- program Memory
type p_mem_t is array (0 to 15) of unsigned(15 downto 0);
constant p_mem_c : p_mem_t :=
    (x"0042", --
     x"00A0", --
     x"0000", --
     x"0000",
     . . .
     x"0000");


signal p_mem : p_mem_t := p_mem_c;

 begin
    pData <= p_mem(to_integer(pAddr));
end architecture;
```




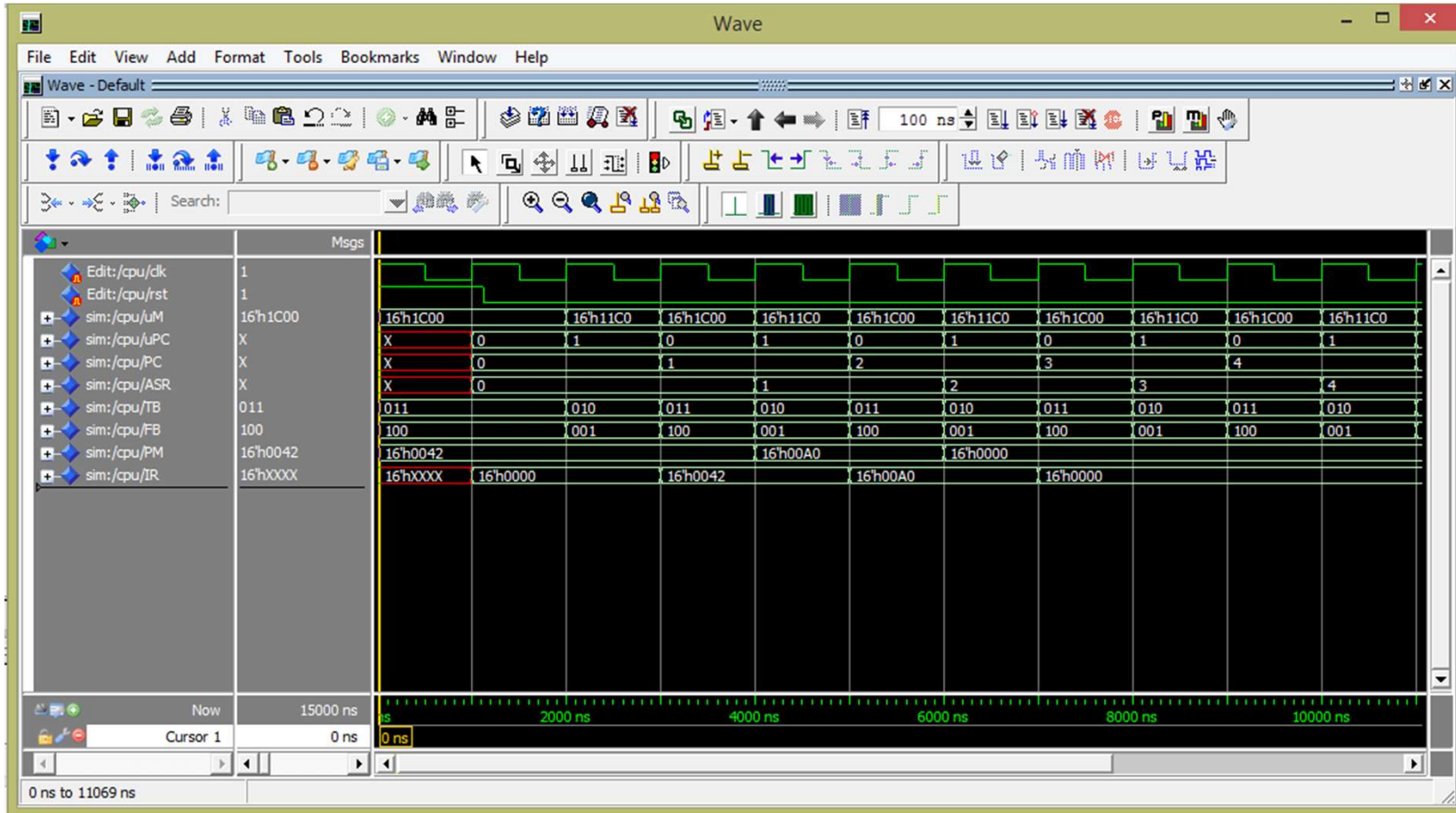
# Datorkonstruktion Uprog CPU simulering med Modelsim



# Datorkonstruktion **uprogCPU\_tb.vhd** testbänken

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;  
USE IEEE.NUMERIC_STD.ALL;
```

```
ENTITY uprogCPU_tb IS  
END uprogCPU_tb;
```

```
ARCHITECTURE func OF uprogCPU_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT uprogCPU
```

```
PORT(  
  clk : IN  std_logic;  
  rst : IN  std_logic  
);
```

```
END COMPONENT;
```


```
--Inputs
```

```
signal clk : std_logic := '0';
```

```
signal rst : std_logic := '0';
```

```
-- Clock period definitions
```
 
```
constant clk_period : time := 1 us;
```



# Datorkonstruktion **uprogCPU\_tb.vhd** testbänken

BEGIN

-- Instantiate the Unit Under Test (UUT)

```
 uut: uprogCPU PORT MAP (  
     clk => clk,  
     rst => rst  
 );
```

-- Clock process definitions

```
 clk_process :process
```

```
 begin
```

```
   clk <= '0';
```

```
   wait for clk_period/2;
```


```
   clk <= '1';
```

```
   wait for clk_period/2;
```

```
 end process;
```

```
 rst <= '1', '0' after 1.5 us;
```

END;

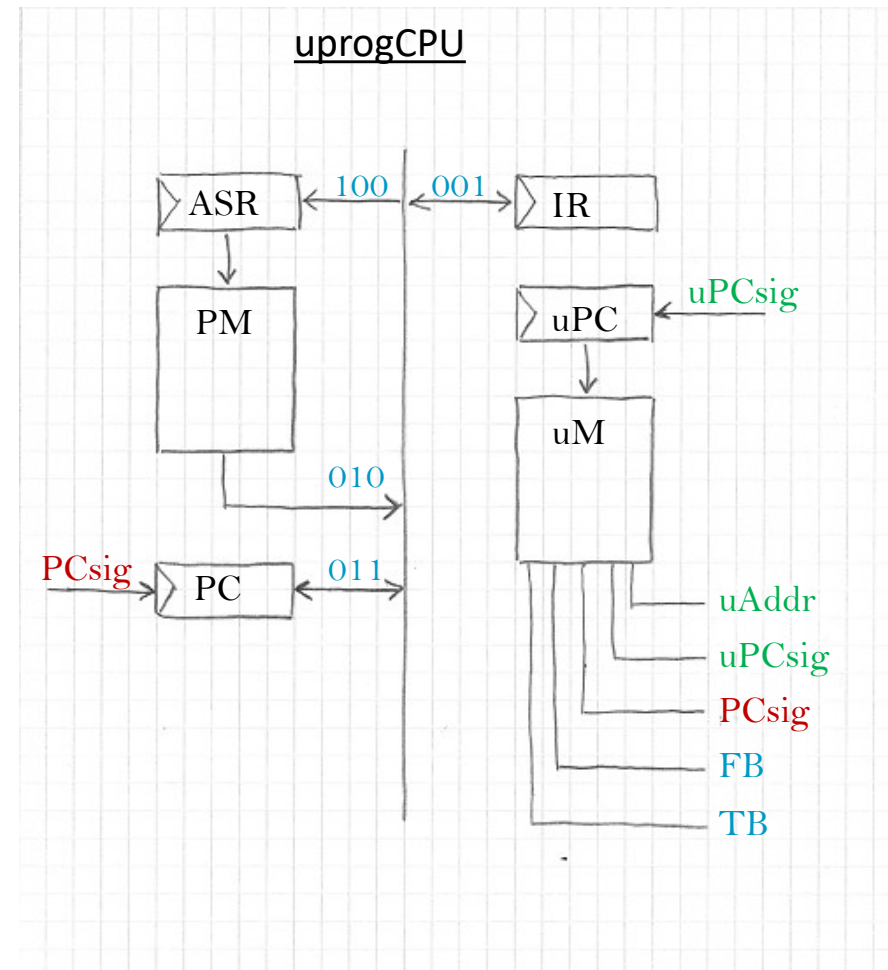

# Minnen i FPGA

*Distributed RAM*  
*BlockRAM*

# Minnen i FPGA

- Distributed RAM (LUT) : passar till K1, K2, registerfil, programminne, mikrominne (ROM)
  - Kombinatorisk läsning
  - Klockad skrivning
  
- Block RAM: passar till bildminne, (programminne), ...
  - Klockad läsning
  - Klockad skrivning

Man kan påverka vilken minnestyp det blir med sin VHDL-kod, men i båda fallen rekommenderas att syntesverktyget får avgöra


# Datorkonstruktion LUT-RAM deklarerar i separat fil

```
entity L_RAM is
port(clk : in std_logic;
     -- port
     we   : in std_logic; -- write enable
     data_in : in std_logic_vector(7 downto 0);
     data_out : out std_logic_vector(7 downto 0);
     addr  : in unsigned(10 downto 0));
end entity;

architecture func of L_RAM is
-- RAM type
type ram_t is array (0 to 2047) of std_logic_vector(7 downto 0);
-- RAM init : address 0 = x"1F", other addresses = 0
signal lram : ram_t := (0 => x"1F", others => (others => '0'));

process(clk)
begin
if rising_edge(clk) then
if (we = '1') then
lram(to_integer(addr)) <= data_in;
end if;
end if;
end process;

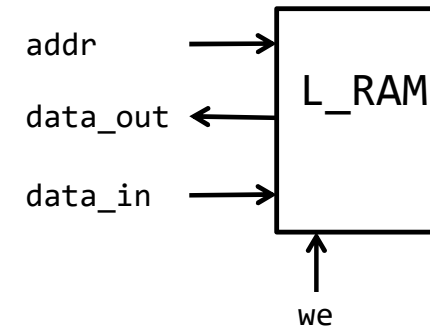data_out <= lram(to_integer(addr));
end architecture;
```



- "En-ports-RAM"
- Synkron skrivning
- ASynkron läsning

Access av minnet, ska **ENDAST** förekomma inne i RAM-komponenten. Detta för att undvika multipla instanser av minnet.

```

entity B_RAM is
port(clk : in std_logic;
    -- port 1
    we1 : in std_logic;
    data_in1 : in std_logic_vector(7 downto 0);
    data_out1: out std_logic_vector(7 downto 0);
    addr1 : in unsigned(10 downto 0);
    -- port 2
    we2 : in std_logic;
    data_in2 : in std_logic_vector(7 downto 0);
    data_out2: out std_logic_vector(7 downto 0);
    addr2 : in unsigned(10 downto 0));
end entity;


architecture func of B_RAM is
    -- RAM type
    type ram_t is array (0 to 2047) of std_logic_vector(7 downto 0);
    -- RAM init : address 0 = x"1F", other addresses = 0
    signal bram : ram_t := (0 => x"1F", others => (others => '0'));

    process(clk)
    begin
        if rising_edge(clk) then
            if (we1 = '1') then
                bram(to_integer(addr1)) <= data_in1;
            end if;
            data_out1 <= bram(to_integer(addr1));

            if (we2 = '1') then
                bram(to_integer(addr2)) <= data_in2;
            end if;
            data_out2 <= bram(to_integer(addr2));
        end if;
    end process;

end architecture;
    
```


# Block-RAM deklarereras i separat fil

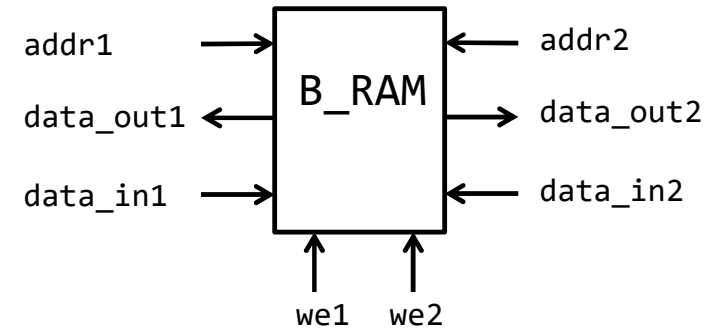

- "Två-ports-RAM"
- Synkron skrivning
- Synkron läsning


Access av minnet, ska **ENDAST** förekomma inne i RAM-komponenten. Detta för att undvika multipla instanser av minnet.
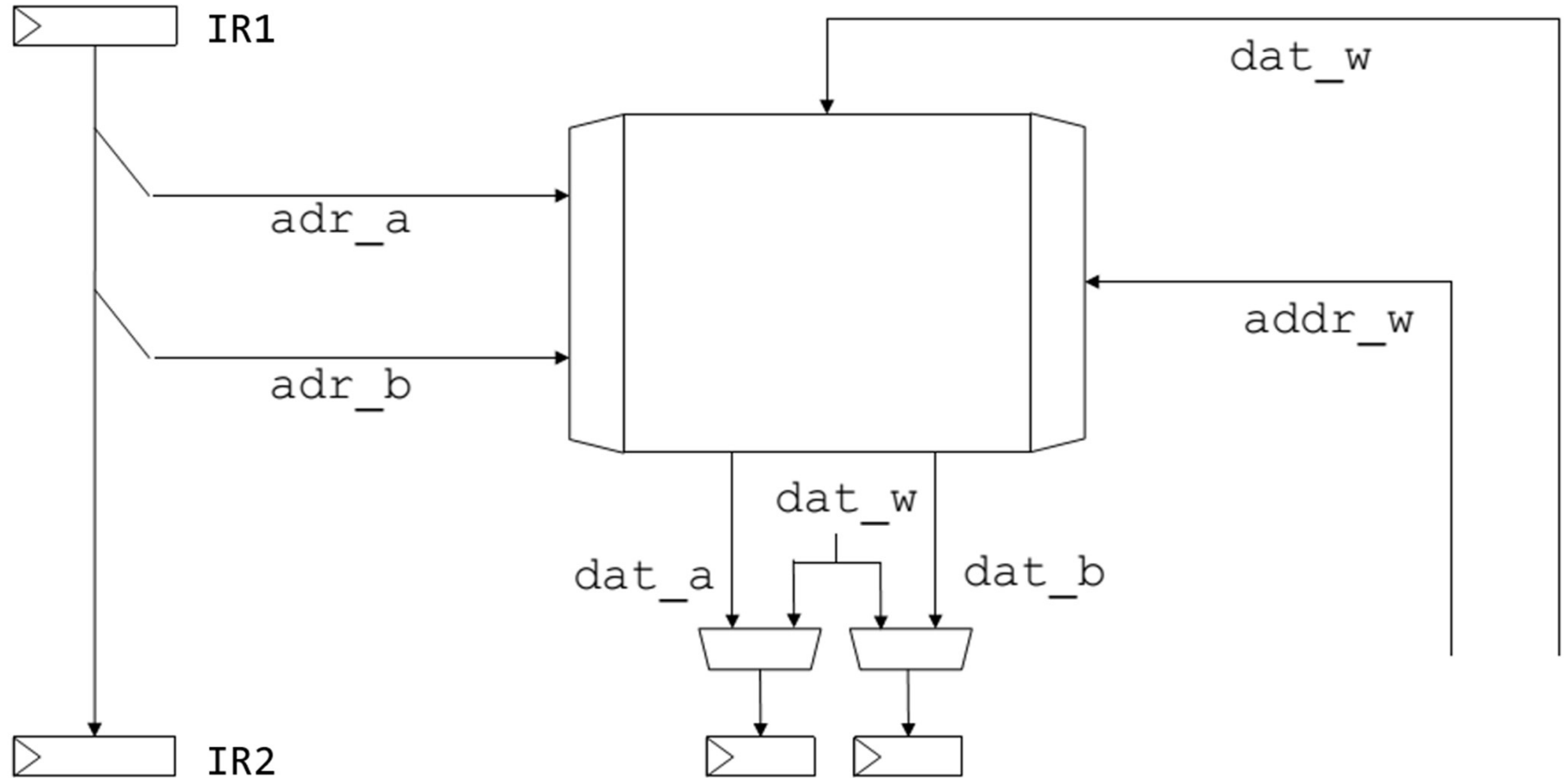
# Registerfil i pipelinad dator "3-ports-minne"




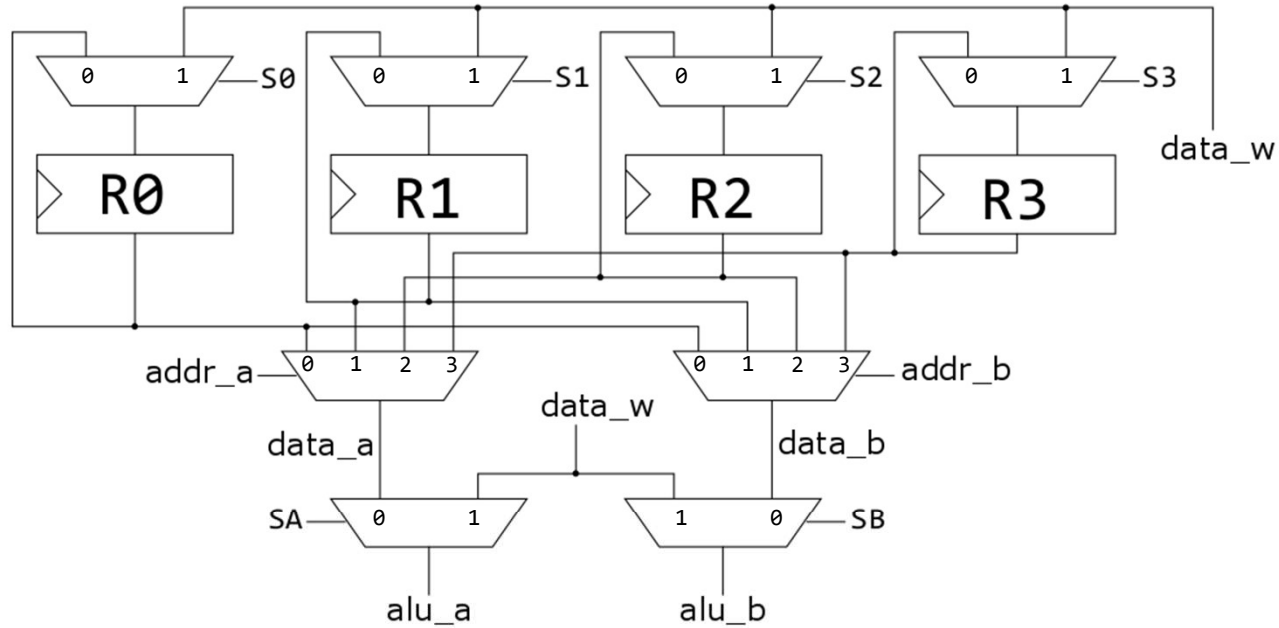
# Registerfil i pipelinad dator "3-ports-minne"



S0 : (addr\_w = "00") and (w\_d = '1')

S1 : (addr\_w = "01") and (w\_d = '1')

S2 : (addr\_w = "10") and (w\_d = '1')

S3 : (addr\_w = "11") and (w\_d = '1')

SA : (addr\_a = addr\_w) and (r\_a = '1') and (w\_d = '1')

SB : (addr\_b = addr\_w) and (r\_b = '1') and (w\_d = '1')

# RF.vhd : Registerfil i pipelinad dator "3-ports-minne"

```


LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

```

```

entity register_file is
  port(clk : in std_logic;
        r_a : in std_logic; -- read source register A signal
        r_b : in std_logic; -- read source register B signal
        addr_a : in unsigned(1 downto 0); -- source A address
        addr_b : in unsigned(1 downto 0); -- source B address
        w_d : in std_logic; -- write destination register signal
        addr_w : in unsigned(1 downto 0); -- destination address
        data_w : in unsigned(7 downto 0); -- destination data
        alu_a : out unsigned(7 downto 0); -- alu A data
        alu_b : out unsigned(7 downto 0) -- alu B data
  )
end entity;

```

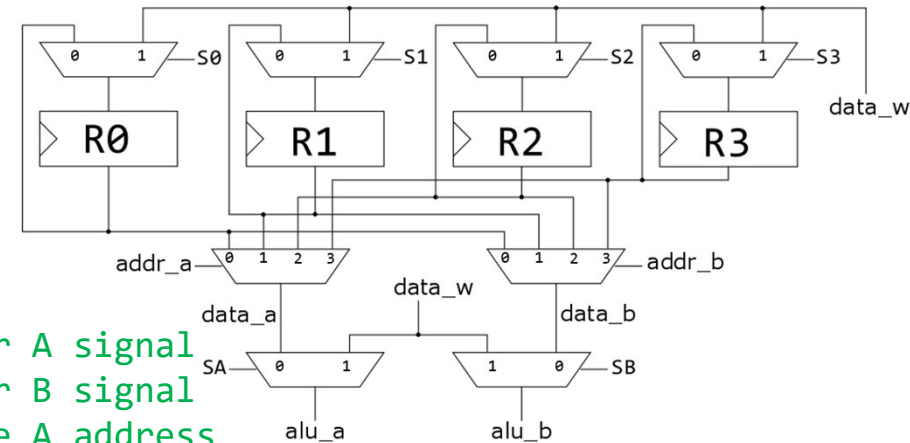

# RF.vhd : Registerfil i pipelinad dator "3-ports-minne"

architecture func of register\_file is

```
signal R0, R1, R2, R3 : unsigned(7 downto 0);
signal data_a, data_b : unsigned(7 downto 0);
```

begin

```
process(clk)
```

```
begin
```

```
  if rising_edge(clk) then
```

```
    if (w_d = '1') then
```

```
      case addr_w is
```

```
        when "00" => R0 <= data_w;
```

```
        when "01" => R1 <= data_w;
```

```
        when "10" => R2 <= data_w;
```


```
        when "11" => R3 <= data_w;
```

```
      end case;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

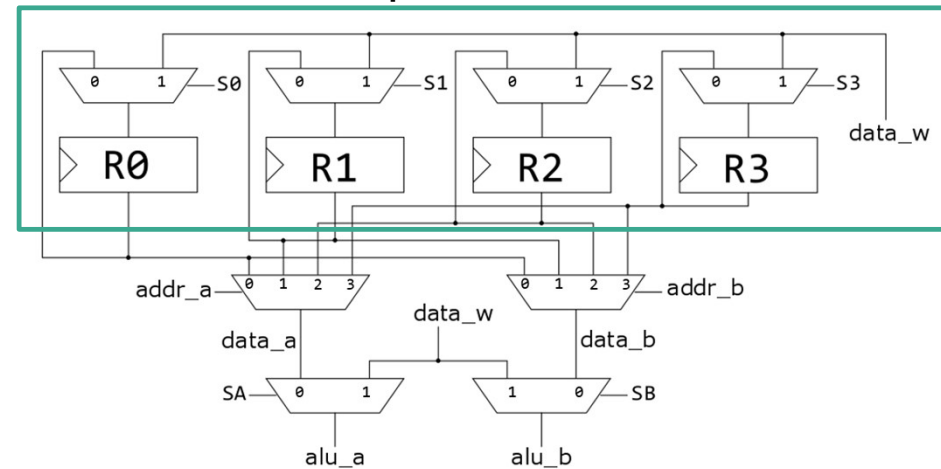

# RF.vhd : Registerfil i pipelinad dator "3-ports-minne"


```
data_a <= R0 when (addr_a = "00") else
R1 when (addr_a = "01") else
R2 when (addr_a = "10") else
R3;
```

```
data_b <= R0 when (addr_b = "00") else
R1 when (addr_b = "01") else
R2 when (addr_b = "10") else
R3;
```

```
alu_a <= data_w when ((addr_a = addr_w) and
(w_d = '1') and
(r_a = '1')) else
data_a;
```

```
alu_b <= data_w when ((addr_b = addr_w) and
(w_d = '1') and
(r_b = '1')) else
data_b;
```

```
end architecture;
```

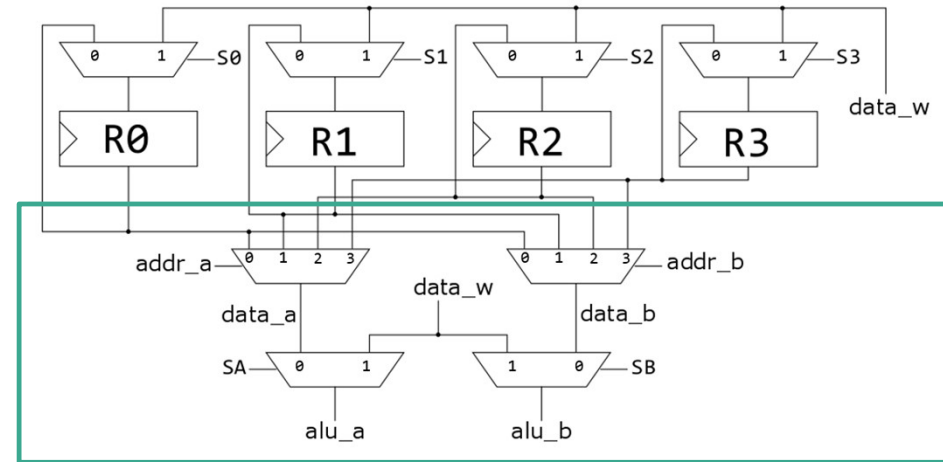


# pipelinad CPU

*VHDL-kod för pipeline-CPU med instruktionshämtning*
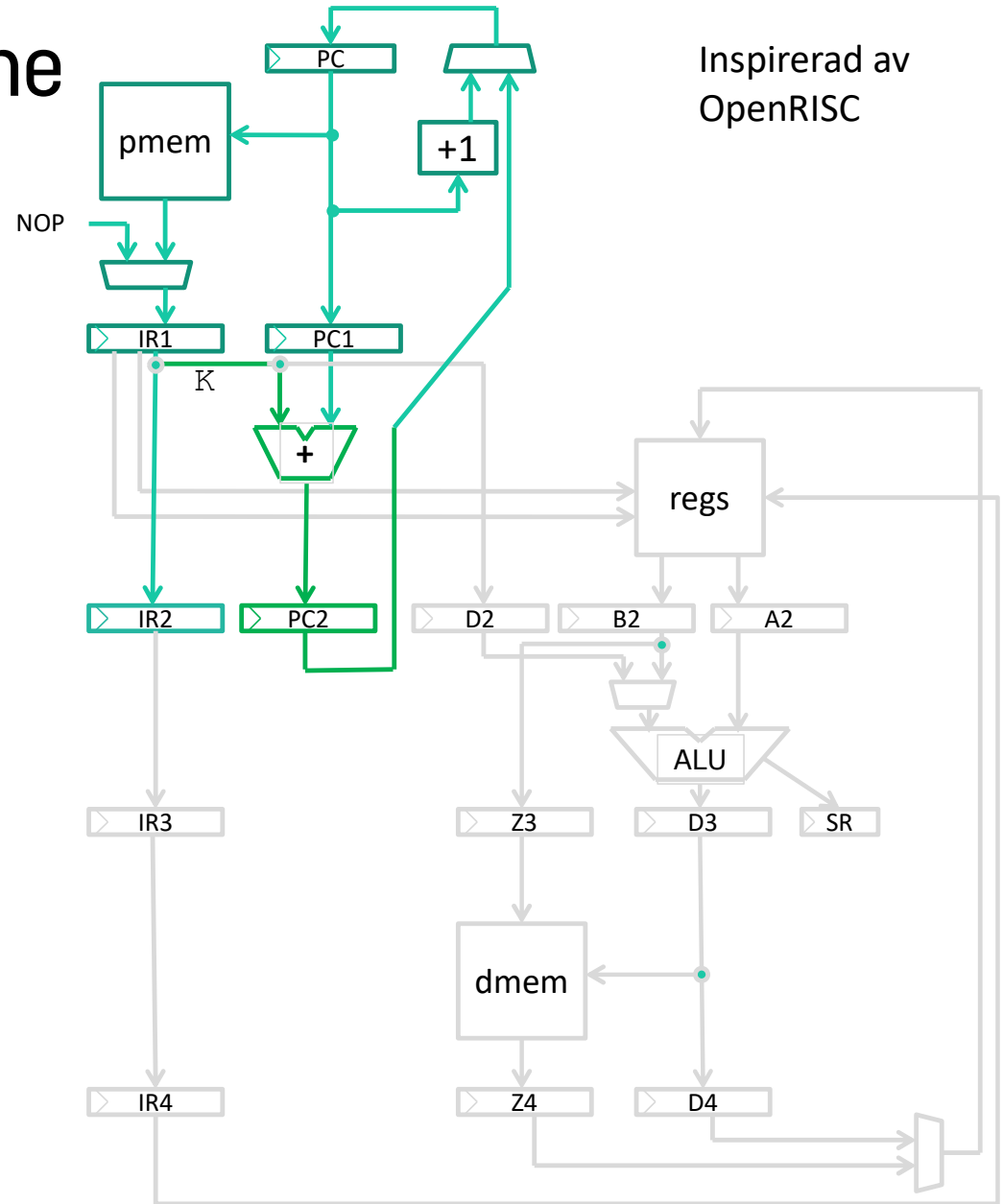
# Klassisk 5-steps pipeline

- **IF:** instruction fetch  
hämta instr och ny PC
- **RR:** register read  
läs reg/beräkna hopp
- **EXE:** execute  
kör ALU
- **MEM:** read/write dmem  
läs/skriv/ingenting
- **WB:** write back register  
skriv reg/ingenting









Datorkonstruktion **pipeCPU.vhd**

```

component PM_comp is
  port(addr : in unsigned(8 downto 0);
        data_out : out unsigned(31 downto 0));
end component;

```


begin

```

U1 : PM_comp port map(
  addr => pm_addr,
  data_out => PMdata_out
);

```

Inspirerad av  
OpenRISC

 

# Datorkonstruktion pipeCPU.vhd

```

process(clk)
begin
  if rising_edge(clk) then
    if (rst='1') then
      PC <= (others => '0');
    elsif (IR2_op = iJ) then
      PC <= PC2;
    else
      PC <= PC + 1;
    end if;
  end if;
end process;

```

```

pm_addr <= PC(8 downto 0);

```

```


process(clk)
begin
  if rising_edge(clk) then
    if (rst='1') then
      PC1 <= (others => '0');
    else
      PC1 <= PC;
    end if;
  end if;
end process;

```

```

process(clk)
begin
  if rising_edge(clk) then
    if (rst='1') then
      PC2 <= (others => '0');
    else
      PC2 <= PC1 + IR1_c;
    end if;
  end if;
end process;

```

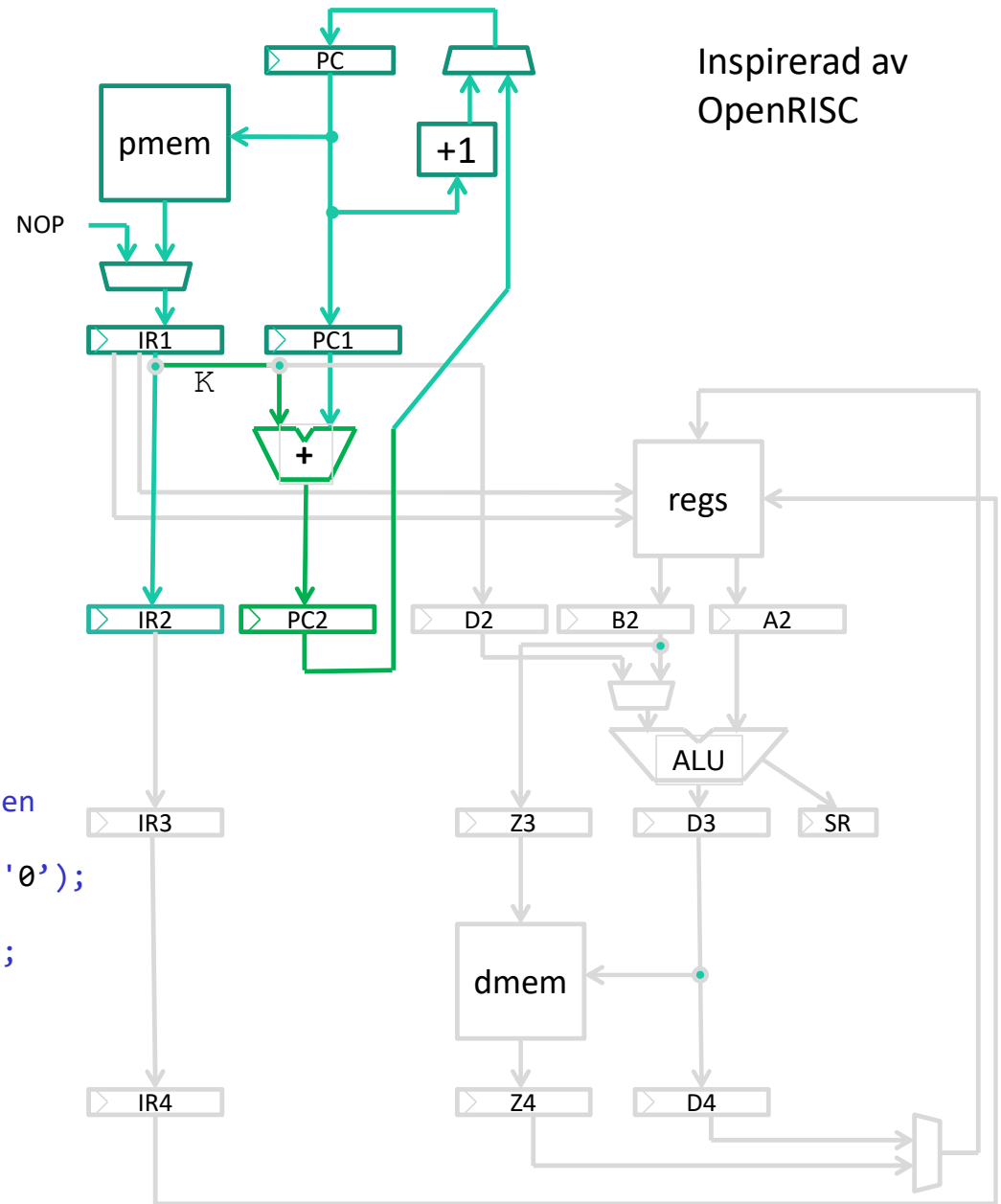

Datorkonstruktion **pipeCPU.vhd**

```

process(clk)
begin
  if rising_edge(clk) then
    if (rst='1') then
      IR1 <= (others => '0');
      IR1_op <= iNOP;
    elsif (IR2_op = iJ) then
      IR1_op <= iNOP;
    else
      IR1 <= PMdata_out(31 downto 0);
    end if;
  end if;
end process;

```

```

process(clk)
begin
  if rising_edge(clk) then
    if (rst='1') then
      IR2 <= (others => '0');
      IR2_op <= iNOP;
    else
      IR2 <= IR1;
    end if;
  end if;
end process;


```

```

end architecture;

```

Inspirerad av  
OpenRISC

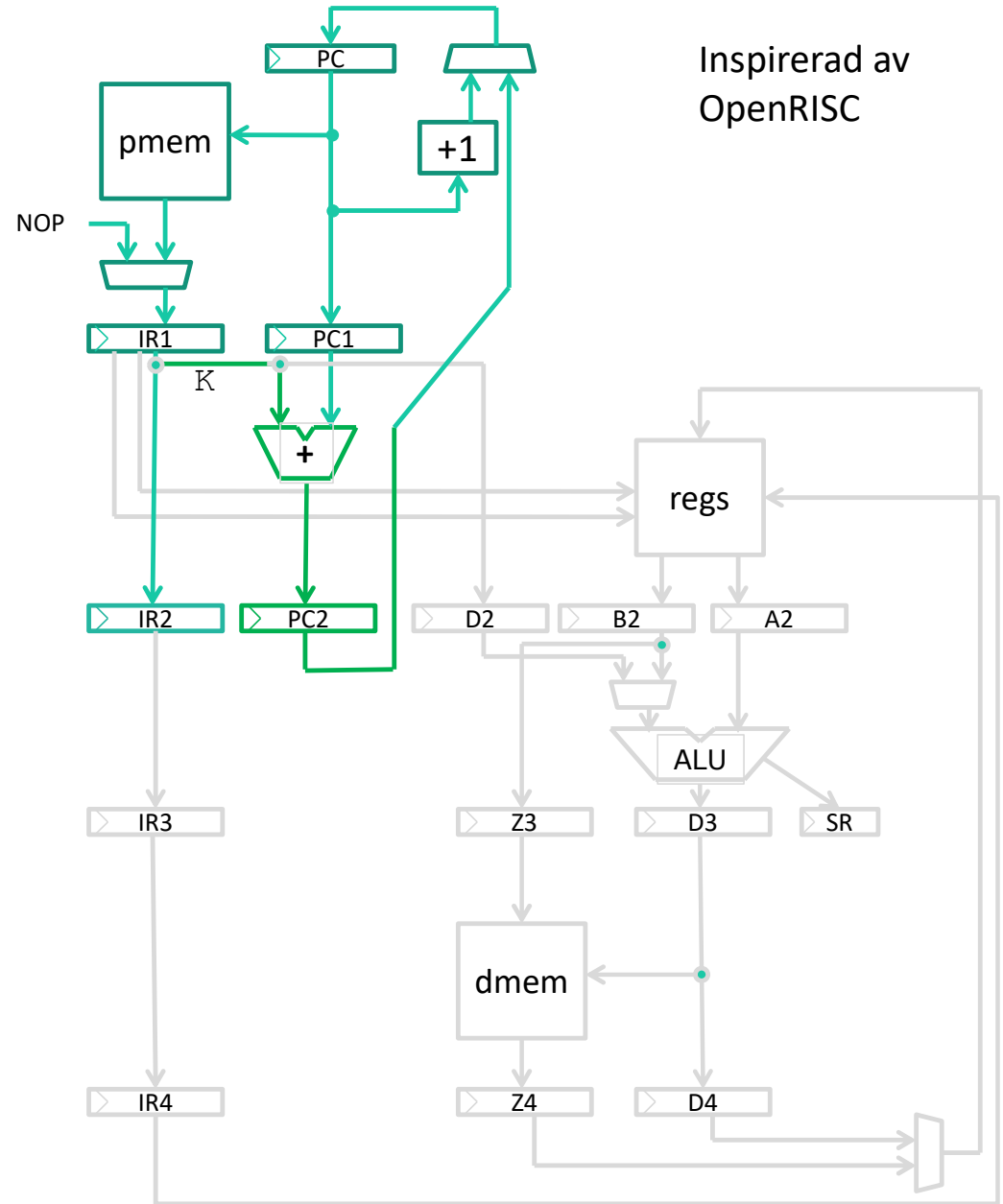

Datorkonstruktion

# PM.vhd deklarerar i separat fil

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity PM_comp is
  port(
    addr : in unsigned(8 downto 0);
    data_out : out unsigned(31 downto 0)
  );
end entity;

architecture func of PM_comp is


  type PM_t is array(0 to 511) of unsigned(31 downto 0);
  constant PM_c : PM_t := (
    X"04000000",      -- dummy
    X"08000000",      -- dummy
    X"540007FE",      -- J 0
    X"0C000000",      -- dummy
    X"10000000",      -- dummy

    others => (others => '0')
  );


  signal PM : PM_t := PM_c;

begin
  data_out <= PM(to_integer(addr));
end architecture;

```

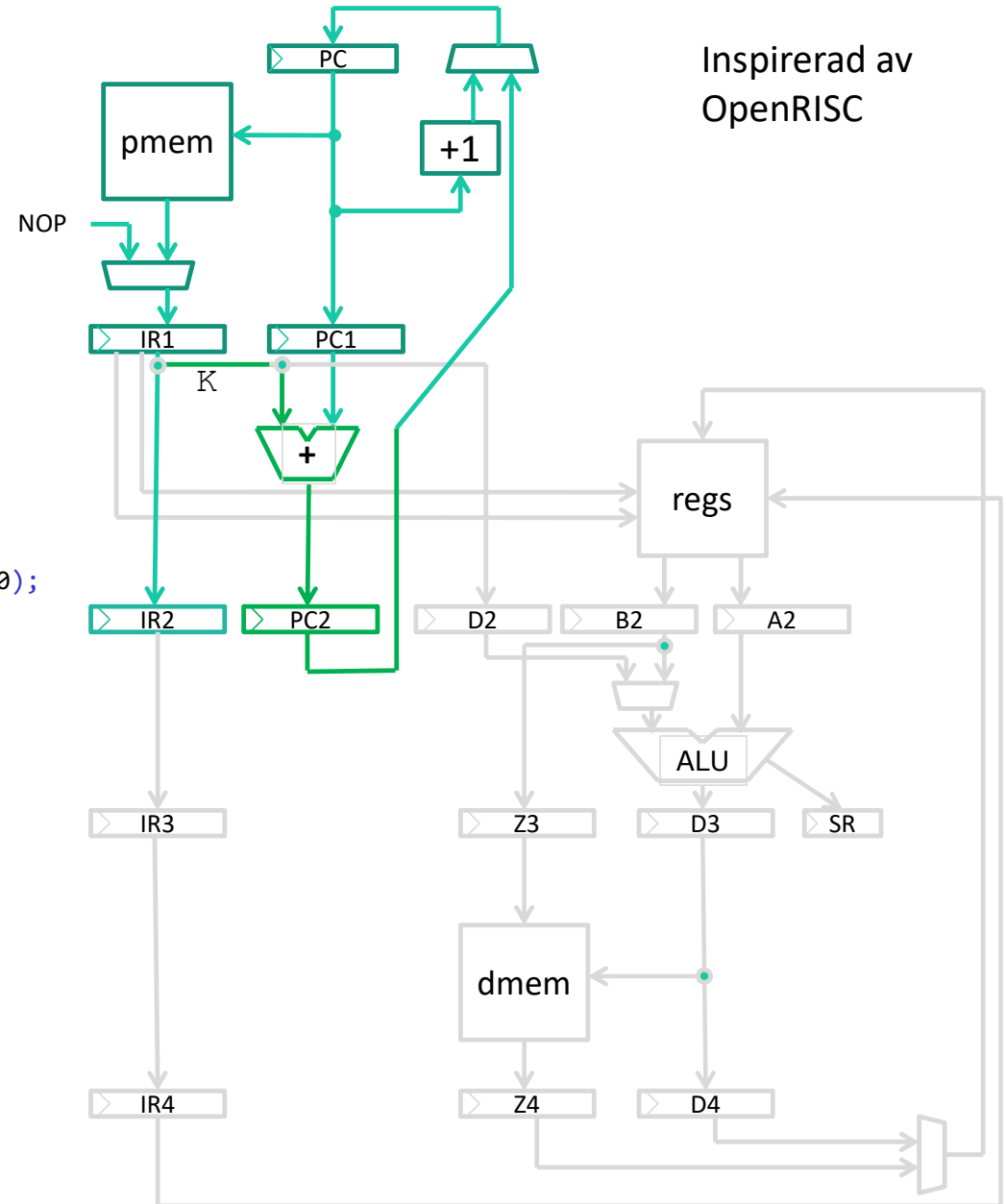

# Datorkonstruktion Simulering

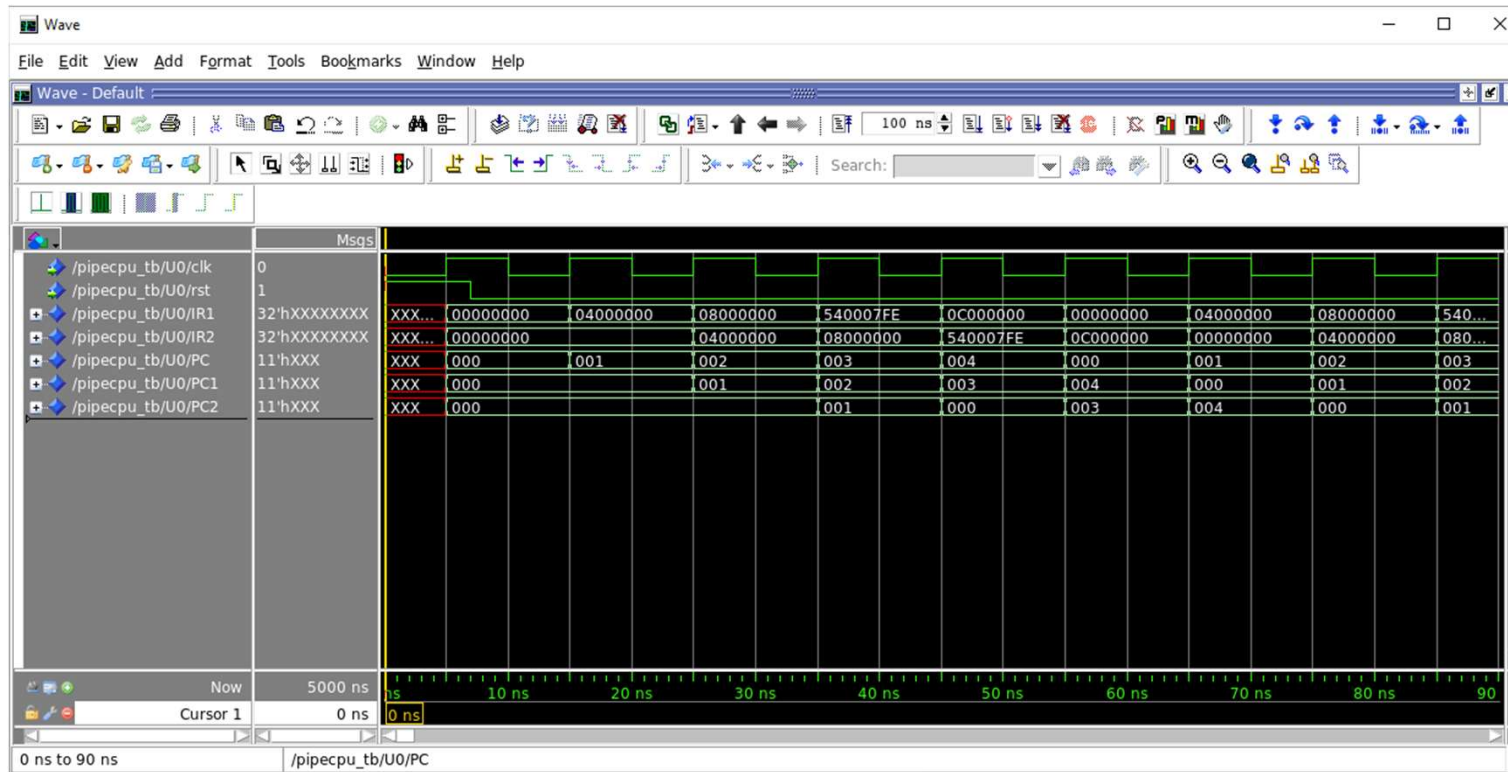

## Datorkonstruktion Lab4 : VGA

- VGA-labben
  - Makefile
  - VHDL-filer
  - Nexys3.ucf
- Kravspec - påminnelse
- Designspect – hur ska datorn byggas?

Anders Nilsson

[www.liu.se](http://www.liu.se)