

Written Test

TSEI30, Analog and Discrete-time Integrated Circuits

Date: August 21, 2000

Time: 14 – 18

Place: Garnisonen

Max. no of points: 70;
50 from written test,
15 for project and 5 for oral test.

Grades: 30 for 3, 42 for 4, and 56 for 5.

Allowed material: No laptops. No text books, such as Johns & Martin "*Analog Integrated Circuit Design*". No dedicated compendia, such as Eriksson "*Aktiva RC-filter och SC-filter*". Pocket calculators are allowed. Written material, tables, downloaded web-material, etc., are allowed.

Examiner: Lars Wanhammar

Responsible teacher: J. Jacob Wikner.
Tel.: 0705915938

Correct (?) solutions: Solutions and results will be displayed in Sept. 2000.

Good Luck!

Instructions

The CMOS transistor operation regions, small signal parameters, and noise characteristics are found on the last page of this test.

Generally, do not just answer yes or no on a brief question. Always motivate your answer with figures, formulas, etc., otherwise no or fewer points will be given.

Basically, there are few numerical answers to be given in this test.

You may answer in Swedish, German, or English.

Exercises — “Favorit i repris”

1. CMOS Building Blocks

Consider the CMOS building block in Figure 1. This is a gain-boosting circuit and from the name we obviously understand that the gain is increased. The current sources have an infinite output resistance.

- Express the small-signal gain from the input to the output (V_{in} to V_{out}) as a function of the bias currents, transistor sizes and process parameters. (4p.)
- Describe how to choose the DC voltages on M2 and M3 to get maximum DC gain (6p.)

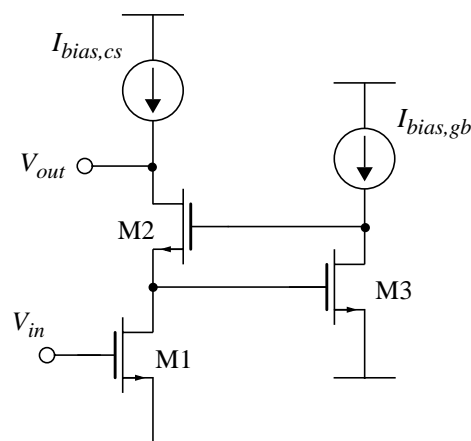


Figure 1 Gain-boosting circuit.

10 points

2. Operational Amplifier

Consider the operational amplifier in Figure 2 (a). Assume that its transfer function is given by

$$A(s) = \frac{A_0}{\left(1 + \frac{s}{p_1}\right) \cdot \left(1 + \frac{s}{p_2}\right)}$$

The poles are well separated but we do not know how p_2 relates to the unity-gain frequency.

a) In open-loop configuration, how much larger must p_2 be than the unity-gain frequency in order to get a phase margin of 60 degrees? (3p.)

a) Assume the OP is used in a feedback loop with the feedback factor β as shown in Figure 2 (b). Derive the total transfer function and find a closed expression on the phase margin. Make reasonable approximations. Sketch the phase margin as a function of the feedback factor β . For which β is the phase margin smallest? (7p.)

 


Figure 2 Operational amplifier in (a) open-loop and (b) closed-loop.

10 points

3. Surprise - CMOS building block

Consider the circuit in Figure 3. The input voltage source has an output resistance R_s .

a) Find the transfer function of the circuit. What is the DC gain? (3p.)

b) Under what circumstances will the output impedance of the circuit become approximately inductive? Do not forget the parasitic capacitances. (7p.)

 


Figure 3 CMOS circuit.

10 points

4. Noise

Consider the three-stage circuit in Figure 4. Only consider thermal noise from each transistor. The current sources are noiseless. Let the output load capacitance be C_L and parasitic capacitances are only given by gate-source capacitances.

a) Derive the total output noise power. (5p.)

b) Discuss – by using relevant circuit parameters – how you should minimize the output noise power and how it affects the gain and bandwidth of the circuit. (5p.)

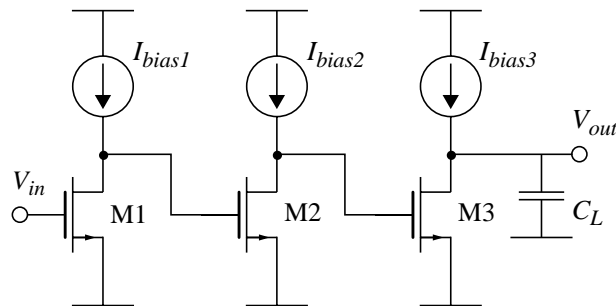


Figure 4 Noisy multi-stage circuit.

10 points

5. Switched Capacitor

Consider the switched-capacitor circuit in Figure 5. Assume that the operational amplifier has a finite DC gain, A , and an input voltage offset error, V_{os} . To simplify your formulas, assume that $C_0 = C_1 = C_2 = C$.

a) Find the transfer function of the circuit. (6p.)

b) How do the finite DC gain and input offset voltage affect the result? (4p.)

 


Figure 5 Switched-capacitor circuit.

10 points

Transistor formulas and noise

CMOS transistors

Current formulas and operating regions

Cut-off:

$$V_{GS} < V_T \quad I_D \approx 0$$

Linear:

$$V_{GS} - V_T > V_{DS} > 0 \quad I_D \approx \frac{\mu_0 C_{ox}}{2} \cdot \frac{W}{L} \cdot (2(V_{GS} - V_T) - V_{DS}) \cdot V_{DS}$$

Saturation:

$$0 < V_{GS} - V_T < V_{DS} \quad I_D \approx \frac{\mu_0 C_{ox}}{2} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda V_{DS})$$

Small-signal parameters

Linear region:

$$g_m \approx \mu_0 C_{ox} \cdot \frac{W}{L} \cdot V_{DS} \quad g_{ds} \approx \mu_0 C_{ox} \cdot \frac{W}{L} \cdot (V_G - V_T - V_D)$$

Saturation region:

$$g_m = \frac{dI_D}{dV_{GS}} = \sqrt{2\mu_0 C_{ox} \frac{W}{L} I_D} \quad g_{ds} = \frac{dI_D}{dV_{DS}} \approx \lambda I_D$$

MOS transistor noise

Thermal noise

The thermal noise spectral density at the gate is $\frac{\overline{v^2}}{\Delta f} = \frac{8kT}{3} \cdot \frac{1}{g_m}$

Flicker noise

The flicker noise spectral density at the gate is $\frac{\overline{v^2}}{\Delta f} = \frac{K}{WLC_{ox}f}$

Parasitics

In the saturation region, the parasitic capacitances on the MOS transistor are approximately given by

$$C_{gs} \approx \frac{2}{3} \cdot W \cdot \left(L + \frac{3}{2} \cdot L_{ov} \right) \cdot C_{ox}, \quad C_{gd} \approx WL_{ov} \cdot C_{ox}$$