

Written Test
TSEI30,
Analog and Discrete-time Integrated Circuits

Date	August 16, 2001
Time:	14 - 18
Place:	Garnisonen
Max. no of points:	70; 50 from written test, 15 for project, and 5 the assignment.
Grades:	30 for 3, 42 for 4, and 56 for 5.
Allowed material:	All types of calculators except Lap Tops. All types of tables and handbooks. Written material and downloaded web-material except old exams. No textbooks are allowed.
Examiner:	Lars Wanhammar.
Responsible teacher:	Robert Hägglund. Tel.: 013 - 28 16 76 (3).
Correct (?) solutions:	Solutions and results will be displayed in House B, entrance 25 - 27, corridor C, ground floor.

Good Luck!

Student's Instructions

The CMOS transistor operation regions, small signal parameters, and noise characteristics are found on the last page of this test.

Generally, do not just answer yes or no on a short question. You always have to answer with figures, formulas, etc., otherwise no or fewer points will be given.

Basically, there are few numerical answers to be given in this test.

You may write down your answers in Swedish or English.

Exercise

1. Basic CMOS building block

a) Assume that V_{b3} is connected to ground. Determine the gain and the dominating pole of the circuit shown in Figure 1.1. (4p)

b) Derive the expression for the possible input and output swing for the circuit shown Figure 1.1. Use relevant design parameters such as W , L , ... (4p)

c) Which node has the largest parasitic capacitance? Find an expression for that capacitance. (2p)

 


Figure 1.1 CMOS building blocks

2. Operational amplifier

Assume that C_c smaller than C_L and $W_6 > W_2$.

- Draw the small signal scheme for the amplifier shown in Figure 2.1. Do not forget the most important parasitics. (2p)
- Derive the gain, poles, and zeros of the amplifier. Motivate all the approximations you are doing. (4p)
- Determine two ways to increase the unity-gain frequency of the amplifier. What will happen to the phase margin, common-mode range and the DC voltage at node x? (4p)

 


Figure 2.1 Operational transconductance amplifier

3. Noise in CMOS circuits

A good model for the thermal noise in a transistor is to add a noise source in parallel with the transistor as shown in Figure 3.1. The noise in the drain is given by

$$I_d^2(f) = 4kT\left(\frac{2}{3}\right)g_m$$

Use this model in this exercise.

 


Figure 3.1 Thermal noise model for a MOS transistor

- Derive the total output noise power of the circuit in Figure 3.2. All parasitics are much smaller than the load capacitor. Assume that the resistor is not noisy. (4p)
- Describe one way to decrease the thermal output noise power of the circuit shown in Figure 3.2 by changing design parameters. What will happen to the gain and the unity-gain frequency? (2p)
- Add a large capacitor $C_1 \gg C_L$ in parallel with the resistor. Derive the output noise power caused by thermal noise? (4p)

 


Figure 3.2 A noisy common source gain stage

4. Switched capacitor

The operational transconductance amplifier suffers from finite gain, A .

a) Derive the transfer function, i.e. $V_2(z)/V_1(z)$, of the circuit shown in Figure 4.1. (4p)

b) Is the circuit insensitive to parasitics? Motivate your answer carefully. (2p)

c) Find the settling time constants, i.e. the speed of the circuit, for both clock phases. Neglect the influence of the switches. (4p)

 


Figure 4.1 A switched capacitor circuit

5. CMOS Building blocks

a) Sketch the output signal of the circuit in Figure 5.1 as a function of the input signal, when the input signal ramps from ground to V_{DD} . Determine the operation region of the transistor in the diagram. Assume $R_L = R_S$.

(3p)

 


Figure 5.1 An analog building block

b) Determine the output resistance of the circuit shown in Figure 5.2. (3p)

 


Figure 5.2 A current mirror

c) Derive the minimal input and output voltages of the current mirror shown in Figure 5.2 (2p)

d) Explain the difference between an operational amplifier, OP, and an operational transconductance amplifier, OTA. Draw a macro model of both amplifiers. (2p)

Transistor formulas and noise

CMOS transistors

Current formulas and operating regions

Cut-off:

$$V_{GS} < V_T \qquad I_D \approx 0$$

Linear:

$$V_{GS} - V_T > V_{DS} > 0 \qquad I_D \approx \frac{\mu_0 C_{ox}}{2} \cdot \frac{W}{L} \cdot (2(V_{GS} - V_T) - V_{DS}) \cdot V_{DS}$$

Saturation:

$$0 < V_{GS} - V_T < V_{DS} \qquad I_D \approx \frac{\mu_0 C_{ox}}{2} \cdot \frac{W}{L} \cdot (V_{GS} - V_T)^2 \cdot (1 + \lambda V_{DS})$$

Small-signal parameters

Linear region:

$$g_m \approx \mu_0 C_{ox} \cdot \frac{W}{L} \cdot V_{DS} \qquad g_{ds} \approx \mu_0 C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_T - V_{DS})$$

Saturation region:

$$g_m = \frac{dI_D}{dV_{GS}} \approx \sqrt{2\mu_0 C_{ox} \frac{W}{L} I_D} \qquad g_{ds} = \frac{dI_D}{dV_{DS}} \approx \lambda I_D$$

Circuit noise

Thermal noise

The thermal noise spectral density at the gate of a CMOS transistor is

$$\frac{\overline{v^2}}{\Delta f} = \frac{8kT}{3} \cdot \frac{1}{g_m}$$

Flicker noise

The flicker noise spectral density at the gate of a CMOS transistor is

$$\frac{\overline{v^2}}{\Delta f} = \frac{K}{WLC_{ox}f}$$