

Tutorial 2: LNA

Problem 1

It is preferred in current RF designs that the input of LNA be matched to 50- Ω . The easiest way is to shunt the gate with a resistor of 50- Ω .

a) Calculate the gain A_0 , input impedance and noise figure (NF) in absence of gate noise. Assume that $R_{sh} = R_s$ and the resistances R_L and R_{sh} noiseless for NF derivation.

b) What are the disadvantages of shunt resistor with reference to gain and NF?

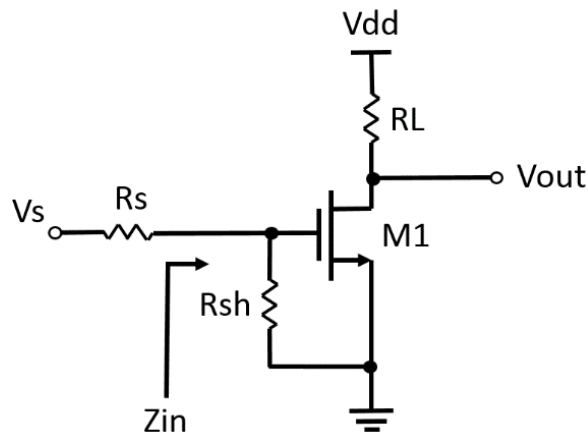


Fig. 1. Common-source amplifier with shunt input resistance

Problem 2

The inductor source degenerate amplifier shown below presents a noiseless resistance of 50- Ω for input power match.

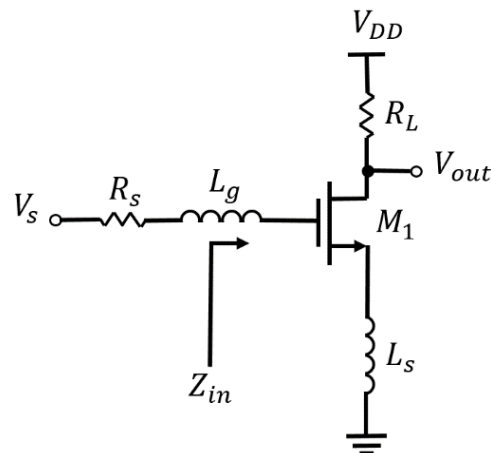


Fig. 2. Inductor source degenerated amplifier

- Calculate the input impedance. How can we cancel the imaginary part of the complex input impedance so that the LNA presents 50-Ω real input resistance at input port? Neglect gate-drain, gate-bulk capacitance.
- Calculate the NF. Neglect gate-drain, gate-bulk and gate-source capacitance.
- C_{gd} bridges the input and the output ports. The reverse isolation of this LNA is very poor. Why is reverse isolation important? Suggest a modification to improve the reverse isolation.

Problem 3

A common-source low noise amplifier (LNA) with feedback is shown in the figure below. R_S is the input source resistance. Assume that the transistors are long-channel devices and $\lambda = 0$.

- Determine the input impedance R_{in} of the LNA.
- Calculate the voltage gain, $A_0 = V_{out}/V_{in}$ of the LNA after matching if $R_F = 10R_S$.
- Derive an expression for the output noise contributed by R_S after matching. Assume $R_F \gg R_S$.

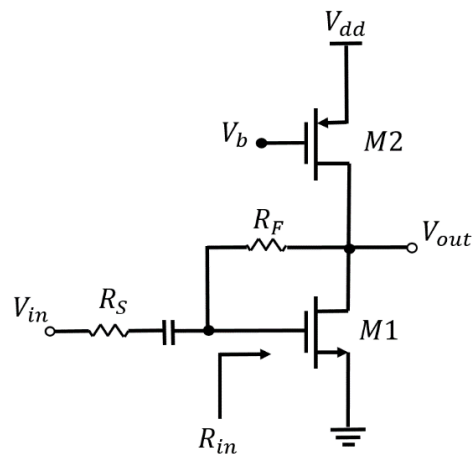


Fig. 3. CS stage with resistive feedback

Problem 4

In the common-source stage in Fig. 3, determine

- Input impedance
- Closed-loop gain and
- Noise Figure.

Assume $\lambda \neq 0$ and matching at the input.

Homework

Determine the noise figure of the common-gate (CG) circuits shown below. Neglect channel-length modulation and the body effect. Assume that R_1 is the loss of inductance L_1 .

