

Tutorial 3: Mixer

Problem 1

Consider the active mixer shown in the figure below where the LO has abrupt edges and a 50% duty cycle. Also, channel-length modulation and body effect are negligible. The load resistors exhibit mismatch, but the circuit is otherwise symmetric. Assume $M1$ carries a bias current of I_{SS} . Determine the output offset voltage.

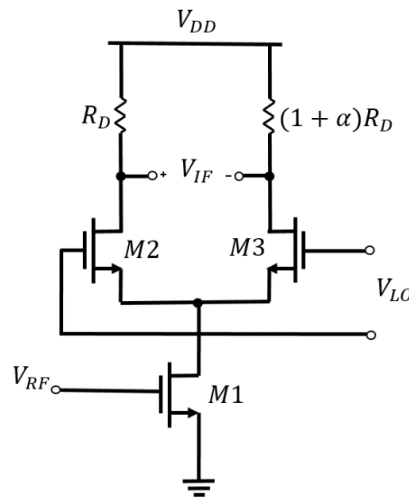


Fig. 1. Active mixer with load mismatch

Problem 2

Shown below is the front-end of a 1.8-GHz receiver. The LO frequency is chosen to be 900 MHz and the load inductors and capacitances resonate with a quality factor Q at IF. Assume $M1$ is biased at a current I_1 , and the mixer and LO are perfectly symmetric. Also assume $M2$ and $M3$ are ideal switches (they switch abruptly and completely). Compute (a) the measured level of the 900-MHz at the output in the absence of an RF signal, (b) the LO-IF feedthrough with the presence only of the gate-drain capacitance C_{GD} . Neglect gate-source and gate-bulk capacitance.

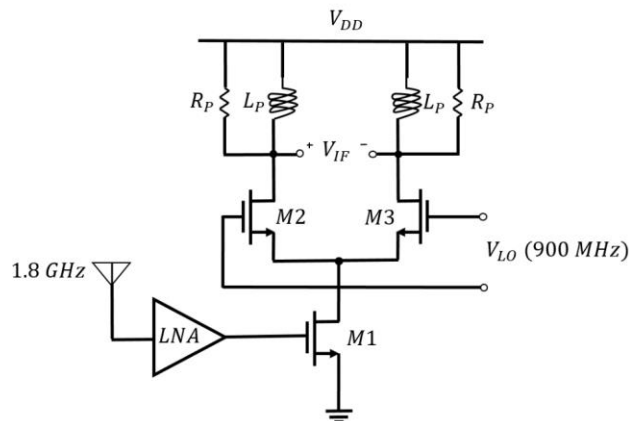


Fig. 2. Receiver front-end

Problem 3

The circuit shown below is a dual-gate mixer used in traditional microwave design. Assume abrupt edges and a 50% duty cycle for the LO and neglect channel-length modulation and body effect.


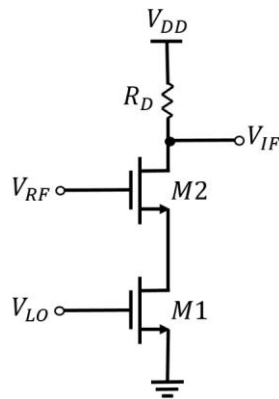


Fig. 3. Dual-gate mixer

- Assume that $M1$ is an ideal switch. Determine the frequency components which appear at the mixer IF port.
- Assume when $M1$ is on, it has an on-resistance of R_{on1} . Compute the voltage conversion gain of the circuit. Assume $M2$ does not enter the triode region and denote its transconductance by g_{m2} .
- Assume when $M1$ is an ideal switch. Compute the voltage conversion gain of the circuit.

Homework 1

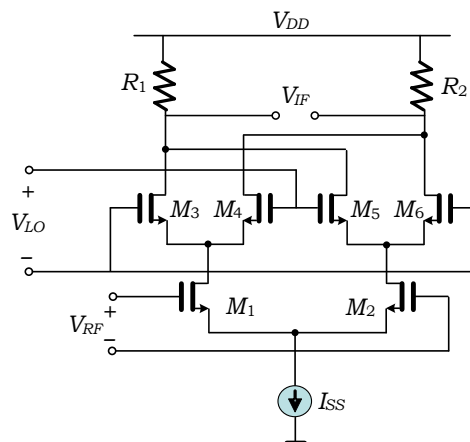Gilbert mixer and its variants are one of the most popular types of mixers used in today's designs due to its good conversion gain, NF, linearity, and isolation.



- Derive the expression for the conversion.
- Derive the expression to identify the frequency components at the output spectrum of the mixer IF port.
- Derive the expression for the noise figure.

Homework 2

In the circuit of Fig. 6.67 of the course book, we place a parallel RLC tank in series with the source of M_4 such that at resonance, the noise contribution of M_4 is reduced. Recalculate Eq. (6.116) if the tank provides an equivalent parallel resistance of R_p . (Bear in mind that R_p itself produces noise).

