

Tutorial 4: Oscillator

Problem 1

Suppose $H(s)$ in the negative feedback system shown below satisfies the following conditions at a frequency of ω_1 : $|H(s)| = 1$, and $\angle H(s) = 170^\circ$.

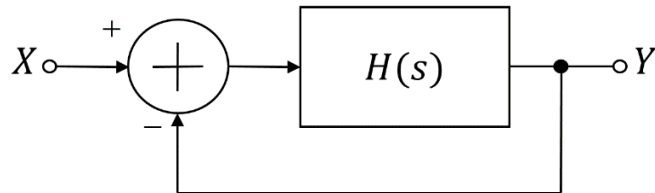


Fig. 1. Negative feedback system

Explain what happens to the phase and the amplitude of the output signal.

Problem 2

Prove that the series combination of the two tanks in Fig. 2(a) can be replaced by one tank as shown in Fig. 2(b).

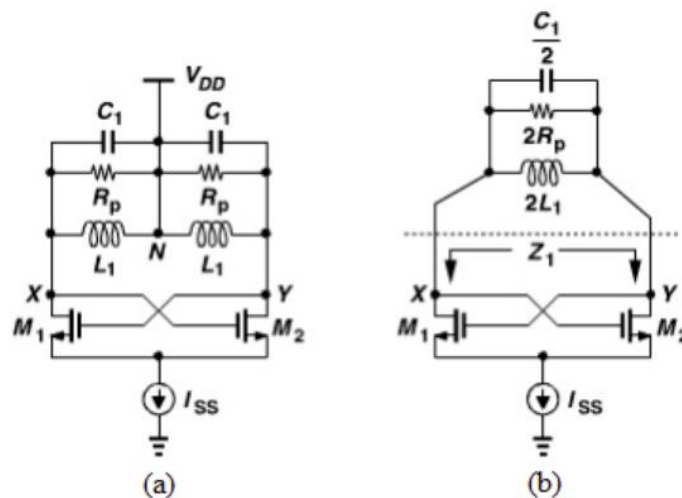


Fig. 2 (a) Cross-coupled oscillator. (b) with tanks merged

Problem 3

A negative resistance LC oscillator is shown in Fig. 3. The component values are $L=5$ nH, $C = 2.5$ pF, Inductor $Q = 5$ and $\mu_n C_{ox} = 110$ $\mu\text{A}/\text{V}^2$.

- Calculate the frequency of oscillation, without and with losses in the inductor.
- Calculate the value of negative resistance provided by the cross-coupled NMOS transistor pair to support oscillation.
- What is the W/L ratio of $M1$ and $M2$ to achieve the required negative resistance.

- d) To cover 40 MHz frequency band, the RFIC-designer would like to use a varactor, replacing the C in the schematic with a C_{var} , a varactor with a tuning range from C_{min} to C_{max} . Calculate the tuning range of the capacitor (%). Is the required tuning range possible to achieve with a conventional CMOS varactor?

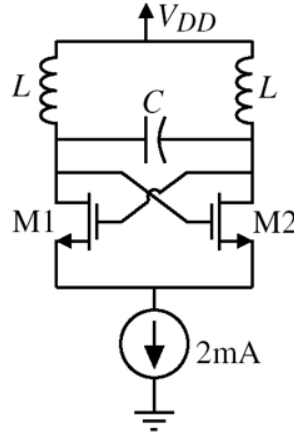


Fig. 3. Negative resistance LC oscillator

Problem 4

A single-transistor inductor-feedback oscillator is shown in Fig. 4.


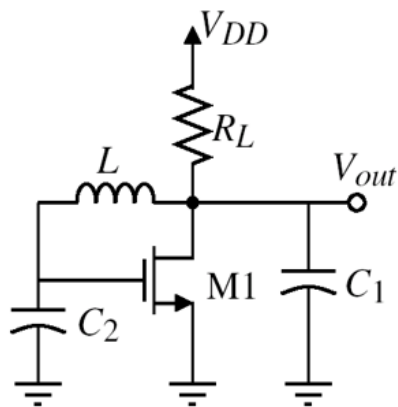


Fig. 4. Single-transistor inductor-feedback oscillator


Find an expression for the frequency of oscillation and the value of $g_m R_L$ necessary for oscillation. Assume that output resistance of the transistor is negligible.

Homework 1

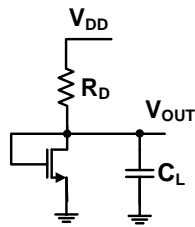
Which of the following (a), (b), and (c) circuit oscillates? State the reason in terms of frequency dependent phase shift and DC phase shift.



(a)

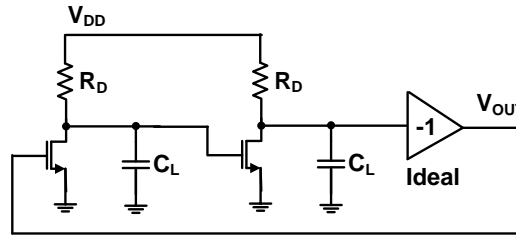

(b)

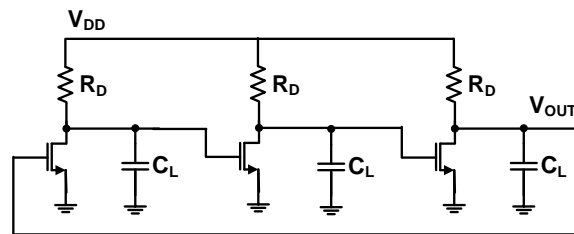

(c)

Answer:

(a) DC phase shift = 180° (frequency $\rightarrow 0$)

Open loop circuit contains one pole

\Rightarrow Frequency dependent phase shift = 90° (at frequency $\rightarrow \infty$)

Total phase shift = $90^\circ + 180^\circ = 270^\circ \Rightarrow$ No oscillation.

(b) DC phase shift = 180° (frequency $\rightarrow 0$)

Open loop circuit contains two poles

\Rightarrow Frequency dependent phase shift = $90^\circ + 90^\circ = 180^\circ$ (at frequency $\rightarrow \infty$)

Total phase shift = $180^\circ + 180^\circ = 360^\circ$

But as frequency $\rightarrow \infty$ the loop gain vanishes \Rightarrow No oscillation.

(c) DC phase shift = 180° (frequency $\rightarrow 0$)

Open loop circuit contains three poles

\Rightarrow Frequency dependent phase shift = $90^\circ + 90^\circ + 90^\circ = 270^\circ$ (at frequency $\rightarrow \infty$)

Total phase shift = $180^\circ + 270^\circ = 450^\circ$ or 90°

However at $f = f_{p1,2,3} < \infty$, where f_p is the cut-off frequency of a stage, the frequency dependent phase shift = $45^\circ + 45^\circ + 45^\circ = 135^\circ$

Therefore for some $f_p < f < \infty$ the circuit may oscillate with a sufficient loop gain.

Homework 2

A Colpitts oscillator is shown in figure below. Find the oscillation frequency, ω_{osc} and the value of g_m necessary for oscillation, in terms of L , C_1 , C_2 and R . Neglect channel-length modulation and the body effect.

Answer:

$$\omega_0 = \sqrt{\frac{1}{L \frac{C_1 C_2}{C_1 + C_2}} + \frac{1}{R \frac{C_1 C_2}{g_m}}}$$

$$g_m R_L = \left(\frac{C_1 + C_2}{C_1 C_2 L} + \frac{g_m}{C_1 C_2 R} \right) L (C_1 + C_2)$$

$$g_m = \frac{R(C_1 + C_2)^2}{R^2 C_1 C_2 - L(C_1 + C_2)}$$

