

Tutorial 4: Oscillator Solutions

Problem 1

Suppose $H(s)$ in the negative feedback system shown below satisfies the following conditions at a frequency of ω_1 : $|H(s)| = 1$, and $\angle H(s) = 170^\circ$.

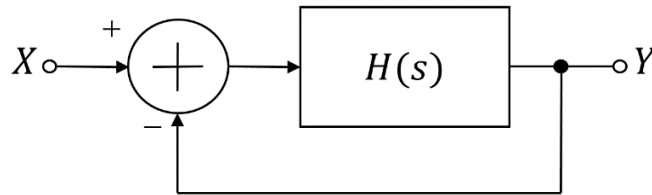


Fig. 1.1. Negative feedback system

Explain what happens to the phase and the amplitude of the output signal.

Solution:

The transfer function of the negative feedback system is expressed as

$$\frac{Y(s)}{X(s)} = \frac{H(s)}{1 + H(s)} \quad (1.1)$$

where the function $H(s)$ can be decomposed through the Euler's identity as

$$H(s) = 1 \cdot e^{j170^\circ} = \cos 170^\circ + j \sin 170^\circ \quad (1.2)$$

Elaborating more for (1.1), we have

$$\begin{aligned} \frac{Y(s)}{X(s)} &= \frac{H(s)[(1 + H(s))^*]}{[(1 + H(s))][(1 + H(s))^*]} \\ \Rightarrow \frac{Y(s)}{X(s)} &= \frac{H(s) + |H(s)|^2}{1 + H(s) + H(s)^* + |H(s)|^2} \end{aligned} \quad (1.3)$$

Substituting for $|H(s)|$ and $\angle H(s)$ in (1.3), we have

$$\begin{aligned} \frac{Y(s)}{X(s)} &= \frac{(1 + \cos 170^\circ) + j \sin 170^\circ}{2(1 + \cos 170^\circ)} \approx 0.5 + j5.76 \\ \Rightarrow \frac{Y(s)}{X(s)} &\approx 5.78 \angle 85.04^\circ \quad \blacksquare \end{aligned} \quad (1.4)$$

So, if $x(t)$ is a sinusoid signal at ω_1 , then the amplitude of the output signal $y(t)$ will be multiplied by 5.78 and the phase changed by 85.04 degrees approximately.

Problem 2

Prove that the series combination of the two tanks in Fig. 2.1(a) can be replaced by one tank as shown in Fig. 2.1(b).

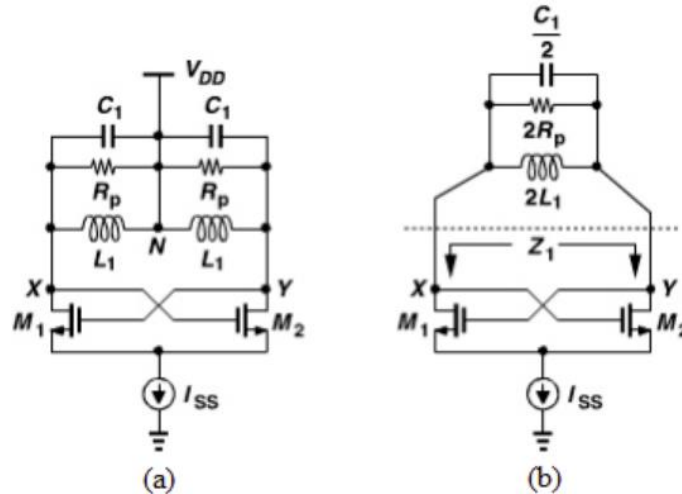


Fig. 2.1. (a) Cross-coupled oscillator. (b) with tanks merged

Solution:

The impedance observed from the nodes X and Y is equal to

$$Z_{eq} = 2(Z_{L1} || Z_{C1} || R_P) \quad (2.1)$$

Generally speaking, if we have two impedances Z_A and Z_B , then the resultant parallel impedance from Z_A and Z_B multiplied by a factor N is equal to multiply each individual impedance by the same factor N and then calculate for the resultant parallel impedance. This can be expressed as

$$N \cdot (Z_A || Z_B) \triangleq N \cdot Z_A || N \cdot Z_B \quad (2.2)$$

Demonstration:

$$\begin{aligned} N \cdot (Z_A || Z_B) &= \frac{NZ_A Z_B}{Z_A + Z_B} \\ N \cdot (Z_A || Z_B) &= \frac{N^2 Z_A Z_B}{NZ_A + NZ_B} = \frac{(NZ_A)(NZ_B)}{NZ_A + NZ_B} \\ &\Rightarrow N \cdot (Z_A || Z_B) = N \cdot Z_A || N \cdot Z_B \end{aligned}$$

This result can be applied for more than two impedances. Then, (2.1) can also be expressed as

$$\begin{aligned} Z_{eq} &= 2Z_{L1} || 2Z_{C1} || 2R_P \\ \Rightarrow Z_{eq} &= 2sL || 2/sC || 2R_P \quad \blacksquare \end{aligned} \quad (2.3)$$

Notice that (2.3) coincide with the impedances connected in parallel in Fig. 2.1(b).

Problem 3

A negative resistance LC oscillator is shown in Fig. 3.1. The component values are $L=5$ nH, $C = 2.5$ pF, Inductor $Q = 5$ and $\mu_n C_{ox} = 110$ $\mu\text{A}/\text{V}^2$.

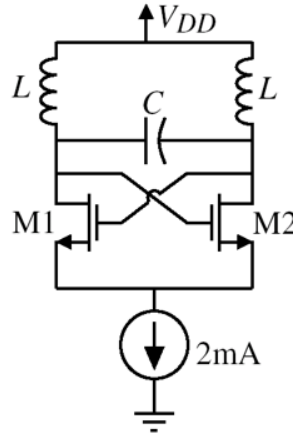


Fig. 3.1. Negative resistance LC oscillator

- Calculate the frequency of oscillation, without and with losses in the inductor.
- Calculate the value of negative resistance provided by the cross-coupled NMOS transistor pair to support oscillation.
- What is the W/L ratio of $M1$ and $M2$ to achieve the required negative resistance.
- To cover 40 MHz frequency band, the RFIC-designer would like to use a varactor, replacing the C in the schematic with a C_{var} , a varactor with a tuning range from C_{min} to C_{max} . Calculate the tuning range of the capacitor (%). Is the required tuning range possible to achieve with a conventional CMOS varactor?

Solution:

- a) The model of the resonant circuit is shown in Fig. 3.2.

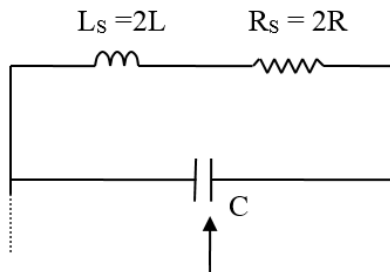


Fig. 3.2. Resonant circuit RLC

Without losses in the circuit $R_s = 0$. The resonance frequency in the system is equal to:

$$f_0 = \frac{1}{2\pi\sqrt{L_s C}} = \frac{1}{2\pi\sqrt{2(5\text{nH})(2.5\text{pF})}} \approx 1.007 \text{ GHz} \quad (3.1)$$

With losses in the circuit $R_s \neq 0$. To simplify the analysis in the circuit, we transform the RL network in series into a parallel network as shown in Fig. 3.3.

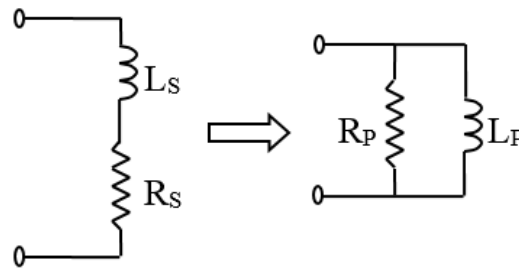


Fig. 3.3. Transformation from series to parallel RL network

In this case the, the resonant frequency can be calculated as follows

$$f_0 = \frac{1}{2\pi\sqrt{L_p C}} \quad (3.2)$$

where the inductance L_p is expressed as

$$L_p = L_s \left(1 + \frac{1}{Q^2}\right) \quad (3.3)$$

Details of the L_p derivation can be found in chapter 3 of Thomas H. Lee book: “The design of CMOS Radio Frequency Integrated Circuits”, 2nd edition. Substituting (3.3) into (3.2) and then evaluating for the resonant frequency, we have

$$f_0 = \frac{Q}{2\pi\sqrt{L_s C(Q^2 + 1)}} = \frac{5}{2\pi\sqrt{2(5\text{nH})(2.5\text{pF})(5^2 + 1)}} \approx 0.987 \text{ GHz} \quad (3.4)$$

b) The parallel resistance R_p can be expressed as

$$R_p = Q\omega_0 L_p \quad (3.5)$$

The negative resistance R_{neg} is equal to $-R_p$. So, substituting (3.3) into (3.5) and solving for $-R_p$, we have

$$R_{neg} = -(5)(2\pi \cdot 0.987 \text{ GHz})(10 \text{ nH}) \left(1 + \frac{1}{5^2}\right) \approx -322.4 \Omega \quad (3.6)$$

c) R_{neg} seen by the RLC network can be found through the circuit shown in Fig. 3.4.

The current i_{in} can be expressed as

$$i_{in} = g_{m1}V_{gs1} \quad (3.7)$$

$$-i_{in} = g_{m2}V_{gs2} \quad (3.8)$$

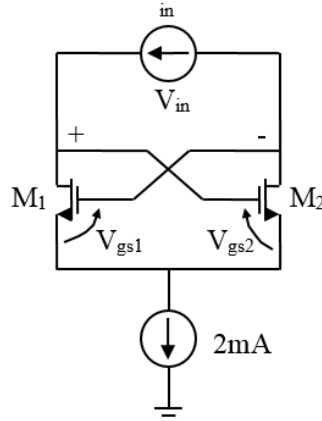


Fig. 3.4. Negative resistance seen by the RLC network

On the other hand, the voltage V_{in} can be expressed as

$$V_{in} = V_{gs2} - V_{gs1} = -i_{in} \left(\frac{1}{g_{m2}} + \frac{1}{g_{m1}} \right) \quad (3.9)$$

Assuming that g_{m1} and g_{m2} are both identical, then R_{neg} seen by the RLC network equals to

$$R_{neg} = \frac{V_{in}}{i_{in}} = - \left(\frac{1}{g_{m2}} + \frac{1}{g_{m1}} \right) = - \frac{2}{g_m} \quad (3.10)$$

Since the transconductance g_m is also expressed as $\sqrt{2\mu_n C_{ox} I_D (W/L)}$, where $\mu_n C_{ox} = 110 \mu\text{A}/\text{V}^2$ and $I_D = 1 \text{ mA}$, $-R_p$ is

$$-R_p = - \frac{2}{\sqrt{2\mu_n C_{ox} I_D (W/L)}} \quad (3.11)$$

Solving for the ratio W/L , we have

$$\frac{W}{L} = \frac{2}{\mu_n C_{ox} I_D R_p^2} \approx 175 \quad (3.12)$$

d) The tuning range of the capacitor, $T = C_{max} - C_{min}$, can be expressed in terms of the frequency band through the equation 8.53 in Razavi's book as

$$\Delta\omega_{osc} \approx \frac{1}{\sqrt{L_1 C_1}} \frac{C_{var2} - C_{var1}}{2C_1} = \frac{1}{\sqrt{L_1 C_1}} \frac{T}{2C_1} \quad (3.13)$$

Therefore, solving for T in (3.13), we have

$$\begin{aligned} T &= \Delta\omega_{osc} \sqrt{L_1 C_1} 2C_1 \\ \Rightarrow T &= 2\pi(40 \text{ MHz}) \sqrt{(10 \text{ nH})(2.5 \text{ pF})(5.0 \text{ pF})} \approx 0.2 \text{ pF} \end{aligned} \quad (3.14)$$

Problem 4

A single-transistor inductor-feedback oscillator is shown in Fig. 4.1.

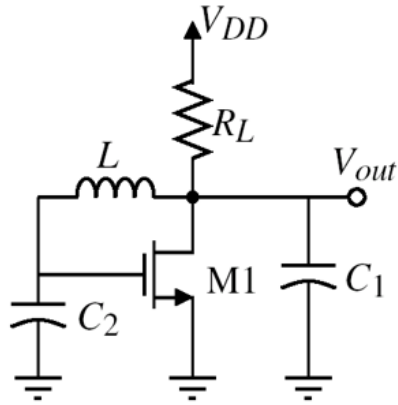


Fig. 4.1. Single-transistor inductor-feedback oscillator

Find an expression for the frequency of oscillation and the value of $g_m R_L$ necessary for oscillation. Assume that output resistance of the transistor is negligible.

Solution:

Write the node equations at the input and output.

$$g_m V_{gs} + \frac{V_{out}}{R_L} + sC_1 V_{out} + \frac{V_{out} - V_{gs}}{sL} = 0$$

and

$$\frac{V_{out} - V_{gs}}{sL} = sC_2 V_{gs} \Rightarrow V_{out} = V_{gs} (1 + s^2 LC_2)$$


$$g_m V_{gs} + \left(\frac{1}{R_L} + sC_1 + \frac{1}{sL} \right) V_{out} - \frac{V_{gs}}{sL} = 0$$

$$g_m V_{gs} + \left(\frac{1}{R_L} + sC_1 + \frac{1}{sL} \right) (1 + s^2 LC_2) V_{gs} - \frac{V_{gs}}{sL} = 0$$

$$V_{gs} \left[g_m + \left(\frac{1}{R_L} + sC_1 + \frac{1}{sL} \right) (1 + s^2 LC_2) - \frac{1}{sL} \right] = 0$$

Assuming that $V_{gs} \neq 0$ we find the oscillation condition
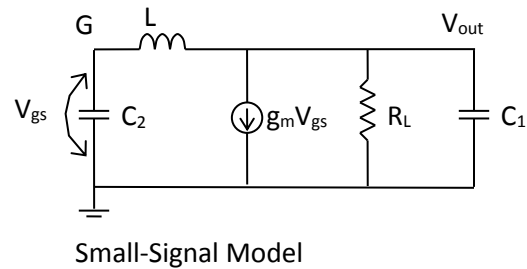
$$g_m + \left(\frac{1}{R_L} + sC_1 + \frac{1}{sL} \right) (1 + s^2 LC_2) - \frac{1}{sL} = 0$$



$$\left(g_m + \frac{1}{R_L} - \frac{\omega^2 LC_2}{R_L} \right) + j\omega (C_1 - \omega^2 LC_1 C_2 + C_2) = 0$$



$$\begin{aligned} g_m + \frac{1}{R_L} &= \frac{LC_2}{R_L} \omega_{osc}^2 \\ &= \frac{1}{R_L} \left(1 + \frac{C_2}{C_1} \right) \end{aligned}$$

$$g_m R_L = \frac{C_2}{C_1}$$

$$C_1 - \omega^2 LC_1 C_2 + C_2 = 0$$

$$\omega_{osc} = \sqrt{\frac{C_1 + C_2}{LC_1 C_2}} = \frac{1}{\sqrt{LC_{eq}}}$$