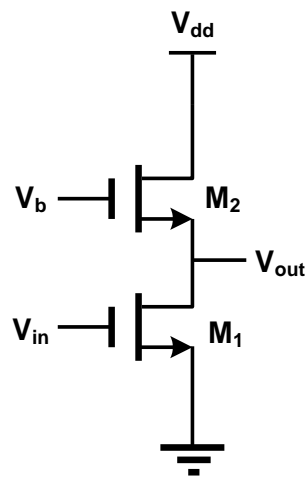


Tutorial 6: Repetition

Problem 1. Noise

A cascode amplifier stage is shown in figure below. Assume that both transistors are long-channel devices and V_b is the bias voltage for M_2 . Furthermore, assume that $g_{m1} \neq g_{m2}$ and $\lambda \neq 0$.


Determine the input-referred noise voltage. Consider only the thermal noise sources and ignore the gate noise of the transistors.



A cascode stage.


Problem 2. LNA

For the common-gate LNA shown below, matched to 50 Ohm, compute the noise figure at the output resonance frequency.

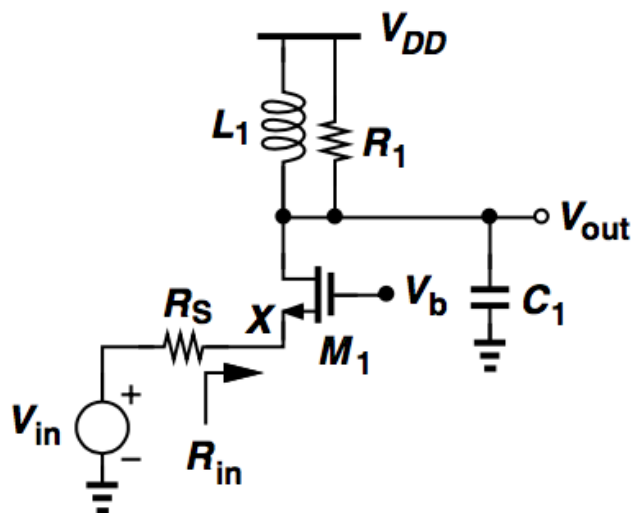

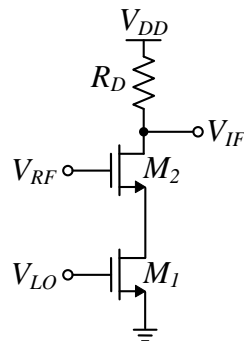Problem 3. Mixer

The circuit shown below is a dual-gate mixer used in traditional microwave design. Assume abrupt edges and a 50 % duty cycle for the LO and neglect channel-length modulation and body effect. Also assume M_1 is an ideal switch and has no noise contribution.



- Compute the voltage conversion gain of the circuit.
- Derive the expression for the noise figure of the mixer.

Problem 4. Oscillator

4) A negative-resistance oscillator operating at 2.4 GHz frequency is shown in Fig. 4. The resonant circuit is implemented using inductor $L = 5$ nH with $Q = 10$ and a variable capacitor C . Assume that we can neglect all parasitics associated with the transistors.

- What is the minimum width of two identical transistors M_1 and M_2 to ensure the oscillation? (2 p)
- How much should the variable capacitance C be varied to enable tuning from 2.4 GHz to 2.5 GHz? (1 p)
- For a capacitance corresponding to 2.4 GHz oscillation frequency, if an additional inductor of 5 nH is connected in parallel with the capacitor C , how much will the oscillation frequency change (in percentage)? (2 p)

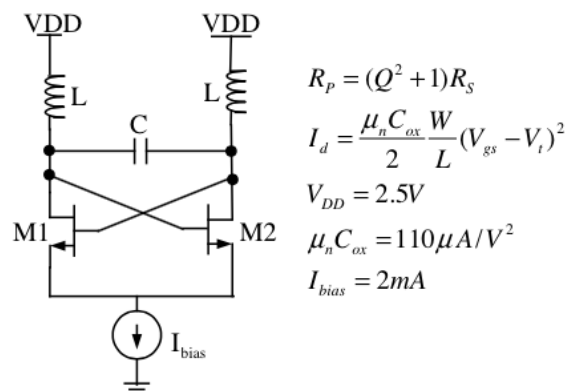


Fig. 4. A negative-resistance oscillator.