

**EXAMINATION IN**  
**-**  
**TSEK03/TEN1**  
**RADIO FREQUENCY INTEGRATED CIRCUITS**

Date: 2013-03-14  
Time: 14-18  
Location: TER1  
Aids: Calculator, Dictionary  
Teachers: Behzad Mesgarzadeh (5719)  
Amin Ojani (2716)

12 points are required to pass.

12-16 : 3

16-20 : 4

20-24 : 5

**Please start each new problem at the top of a page!**  
**Only use one side of each paper!**

---



- 1) Figure 1 shows an amplifier schematic. Determine the input-referred noise voltage. Consider only the thermal noise sources and ignore the gate noise of the transistor. ( $\lambda = \gamma_{body\ effect} = 0$ ) (4 p)

**Hint:**  $\overline{i_{n,M1}^2} = 4kT\gamma g_m$

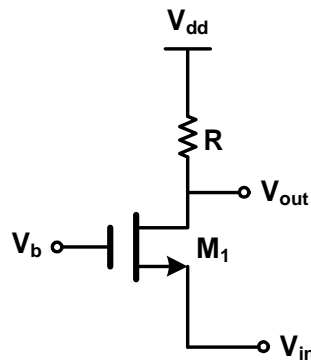


Fig. 1. An amplifier schematic.

- 2) A common-source low noise amplifier (LNA) with feedback is shown in Fig. 2.  $R_S$  is the input source resistance. Assume that the transistors are long-channel devices and  $\lambda = 0$ .

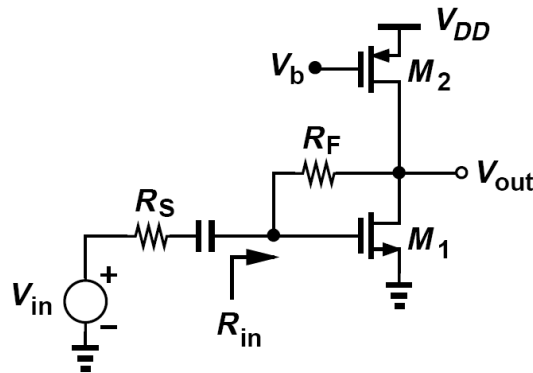


Fig. 2. A CS low-noise amplifier (LNA).

- (a) Determine the input impedance ( $R_{in}$ ) of the LNA. (1 p)  
 (b) Calculate the voltage gain of the LNA (i.e.,  $V_{out}/V_{in}$ ) after matching if  $R_F = 25R_S$ . (2 p)  
 (c) Derive an expression for the output noise of the LNA contributed by  $R_S$  after matching. Assume  $R_F \gg R_S$ . (2 p)

- 3) A single-balanced mixer is shown in Fig. 3. Assume that the switching transistors  $M_1$  and  $M_2$  are ideal switches with zero on-resistance and  $\lambda = 0$ .

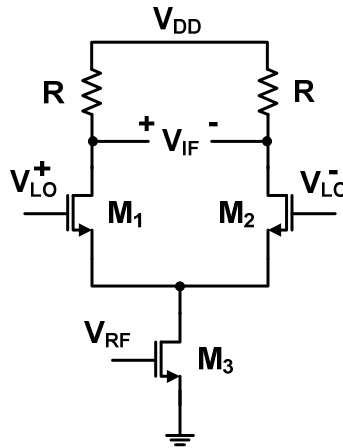


Fig. 3. A single-balanced mixer.

- (a) Derive an expression for the conversion gain of this mixer. (2 p)
- (b) Derive an expression for the noise figure of this mixer. Assume the switching transistors do not generate noise. The total noise is contributed by transistor  $M_3$ , load resistors  $R$  and source resistor  $R_S$  connected to the RF input (is not shown in the figure). Consider only the thermal noise sources and ignore the gate noise of the transistor. (3 p)

**Hints:**

- i)  $\overline{i_{n,M}^2} = 4kT\gamma g_m$
- ii)  $V_{LO}(t) = \frac{4}{\pi} \cos \omega_{LO}(t) - \frac{4}{3\pi} \cos 3\omega_{LO}(t) + \frac{4}{5\pi} \cos 5\omega_{LO}(t) - \dots$

4) Two identical ideal integrators are connected in a feedback loop as shown in Fig. 4. The transfer function of each integrator is  $H(s) = k/s$ .

- (a) Determine the closed-loop transfer function (i.e.,  $\frac{Y}{X}(s)$ ). (1 p)
- (b) Using Bode plot, show the relationship between the phase and the magnitude for different frequencies. (2 p)
- (c) Write a differential equation describing the closed-loop system and show that the system oscillates generating a sinusoidal output. Determine the oscillation frequency with respect to  $k$ . (2 p)

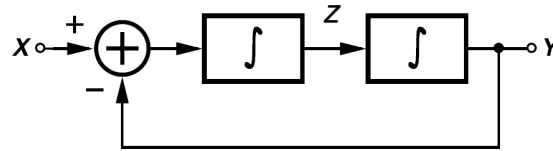


Fig. 4. Two integrators in a feedback loop.

5)

- (a) Explain how a type-I PLL operates as a FSK demodulator, if the VCO control voltage is considered as the output. (2 p)
- (b) Figure 5 show the waveforms of PFD and charge pump in a type-II PLL. Using this figure, determine the transfer function of this combination (i.e.,  $\frac{V_{out}}{\Delta\phi}(s)$ , where  $\Delta\phi$  is the phase difference between PFD inputs). Assume  $I_1 = I_2 = I_p$ . (3 p)


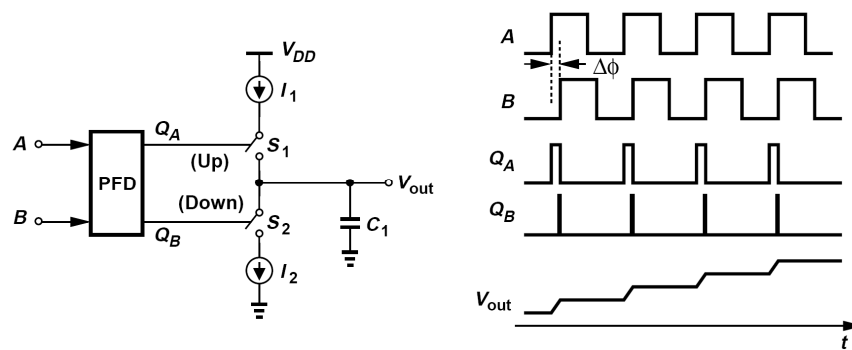


Fig. 5. PFD and Charge Pump.

## TRANSISTOR EQUATIONS

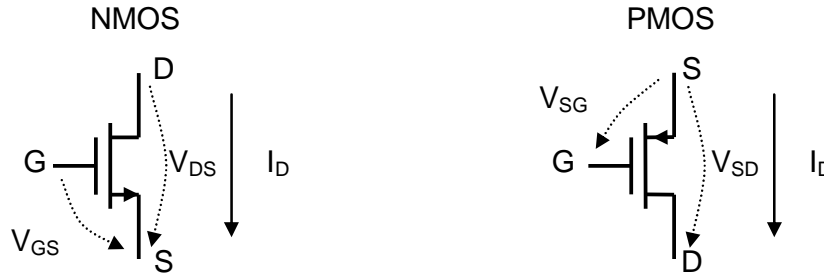

### NMOS

- **Cutoff:**  $I_D = 0$  ( $V_{GS} < V_{TN}$ )
- **Linear mode:**

$$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} < V_{GS} - V_{TN})$$
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} > V_{GS} - V_{TN})$$
- **On-resistance in triode region:**  $R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})}$

### PMOS

- **Cutoff:**  $I_D = 0$  ( $V_{GS} < |V_{TP}|$ )
- **Linear mode:**

$$I_D = \mu_p C_{ox} \frac{W}{L} \left( (V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right) \quad (V_{GS} > |V_{TP}|) \text{ and } (V_{SD} < V_{SG} - |V_{TP}|)$$
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD}) \quad (V_{GS} > |V_{TP}|) \text{ and } (V_{SD} > V_{SG} - |V_{TP}|)$$
- **On-resistance in triode region:**  $R_{on} = \frac{1}{\mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)}$