

# ANSWERS

-

## TSEK03

### RADIO FREQUENCY INTEGRATED CIRCUITS

Date: 2013-03-14  
Time: 14-18  
Location: TER1  
Aids: Calculator, Dictionary  
Teachers: Behzad Mesgarzadeh (5719)  
Amin Ojani (2716)

12 points are required to pass.

12-16 : 3

16-20 : 4


20-24 : 5

**Please start each new problem at the top of a page!**  
**Only use one side of each paper!**

---

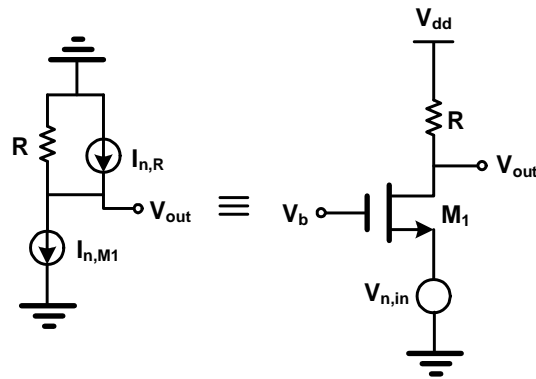1)

There are two thermal noise sources as shown below.



Since:

$$\overline{I_{n,R}^2} = 4kT/R$$

$$\overline{I_{n,M1}^2} = 4kT\gamma g_m$$

The output noise in both circuits should be the same. Then:


$$\overline{V_{n,out}^2} = (4kT\gamma g_m + 4kT/R) \cdot R^2 = \overline{V_{n,in}^2} (g_m R)^2$$

Then we can determine the input referred noise as:

$$\overline{V_{n,in}^2} = \frac{4kT}{g_m^2} (\gamma g_m + 1/R)$$

2)

Small-signal model:

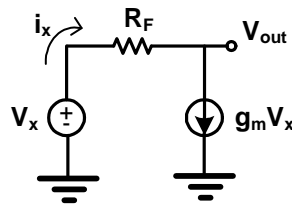

(a)  $i_x = g_m V_x \rightarrow R_{in} = \frac{V_x}{i_x} = \frac{1}{g_m}$

(b) Gain from the gate of the transistor to the output:

$$\frac{V_{out} - V_x}{R_F} + g_m V_x = 0 \rightarrow \frac{V_{out}}{V_x} = 1 - g_m R_F$$

After matching:  $g_m = 1/R_S \rightarrow A = \frac{V_{out}}{V_{in}} = \frac{1/g_m}{R_S + 1/g_m} (1 - g_m R_F) = \frac{1}{2} \left(1 - \frac{R_F}{R_S}\right)$

If  $R_F = 25R_S$ , then:  $A = -12$

(c) The noise of  $R_S$  is multiplied by the gain square to appear at the output. Thus:


$$\overline{V_{n,out,R_S}^2} = 4kTR_S \cdot \frac{1}{4} \left(1 - \frac{R_F}{R_S}\right)^2$$

If  $R_F \gg R_S$ :

$$\overline{V_{n,out,R_S}^2} \approx 4kTR_S \cdot \frac{1}{4} \left(-\frac{R_F}{R_S}\right)^2 = kT \frac{R_F^2}{R_S}$$

3)

(a)

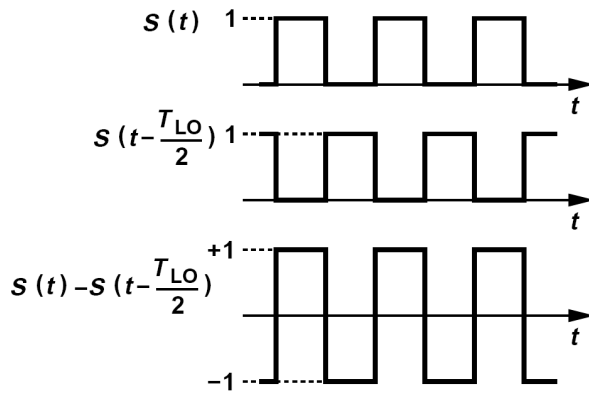

$$V_{out}(t) = I_{RF}R[S(t) - S(t - T_{LO}/2)]$$

If  $V_{RF} = A_{RF} \cos(\omega_{RF}t)$ , then by ignoring the higher order terms:

$$V_{IF} = V_{out} = \frac{4}{\pi} g_{m3} R A_{RF} \cos(\omega_{RF}t) \cos(\omega_{LO}t) = \frac{2}{\pi} g_{m3} R A_{RF} \cos((\omega_{RF} - \omega_{LO})t)$$

Therefore the conversion gain is:

$$G_C = \frac{V_{IF}}{A_{RF}} = \frac{2}{\pi} g_{m3} R$$

(b)

$$\overline{V_{n,out,M_3}^2} = 4kT \gamma g_m R^2$$

$$\overline{V_{n,out,R_S}^2} = 4kT R_S (g_m R)^2$$

$$\overline{V_{n,out,R}^2} = 2 \times 4kT R$$


The noise figure can be written as:

$$NF = \frac{\overline{V_{n,out,M_3}^2} + \overline{V_{n,out,R_s}^2} + \overline{V_{n,out,R}^2}}{G_C^2 \overline{V_{n,out,R_s}^2}} = \frac{\pi^2}{4} \left( 1 + \frac{\gamma}{g_m R_S} + \frac{2}{g_m^2 R_S R} \right)$$

4)

(a)  $\frac{Y}{X}(s) = \frac{k^2}{k^2 + s^2}$

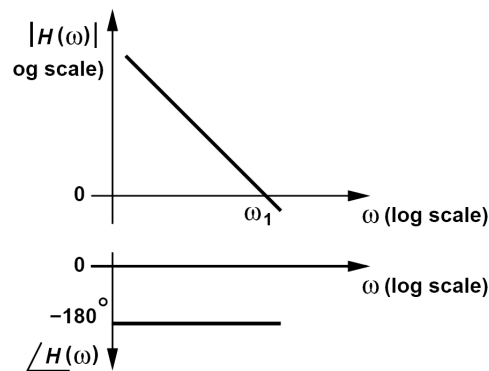(b) The open-loop transfer function is  $k^2/s^2$ . Two poles at origin gives a  $-180^\circ$  constant phase shift and a magnitude with  $-40$  dB/dec slope.



(c) Differential equation:  $\frac{d^2y}{dt^2} + k^2y = kx$ .

For  $x = 0$ ,  $y = A \cos(\omega_1 t + \phi)$  is the solution of the abovementioned equation. If we replace it in the differential equation we get:

$$-A\omega_1^2 \cos(\omega_1 t + \phi) + k^2 A \cos(\omega_1 t + \phi) = 0 \rightarrow \omega_1 = k \quad (\text{oscillation frequency})$$

5)

(a) Refer to the course book Chapter 9.

(b) Refer to the course book Chapter 9.