

**EXAMINATION IN**  
**-**  
**TSEK03/TEN1**  
**RADIO FREQUENCY INTEGRATED CIRCUITS**

Date: 2013-06-05  
Time: 14-18  
Location: TER3  
Aids: Calculator, Dictionary  
Teachers: Behzad Mesgarzadeh (5719)  
Amin Ojani (2716)

12 points are required to pass.

12-16 : 3

16-20 : 4

20-24 : 5

**Please start each new problem at the top of a page!**  
**Only use one side of each paper!**

---



- 1) Figure 1 shows an amplifier schematic. Determine the input-referred  $1/f$  noise voltage. Ignore all the thermal noise sources. Assume  $g_m \gg 1/r_o$ ,  $\gamma = 0$ , and  $\lambda \neq 0$ . (5 p)

**Hint:**  $\overline{V_n^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f}$

 


Fig. 1. An amplifier schematic.

- 2) Consider the wideband common-gate low noise amplifier (LNA) shown in Fig. 2.  $R_S$  is the input source resistance. Assume that the transistors are long-channel devices with  $\lambda_n = 0$ . Also assume that  $\gamma_{body\ effect} = 0$ .

 


Fig. 2. A common-gate LNA.

- (a) Calculate the input impedance of the LNA. Assume that we can neglect all parasitics associated with the transistors. (2 p)
- (b) Derive an expression for the noise figure of the LNA. Only consider the thermal noise sources and ignore the gate noise of the transistors. Also assume that  $R_L$  is a noiseless resistor. (3 p)

**Hint:**  $\overline{i_{n,M}^2} = 4KT\gamma g_m$

- 3) The circuit shown in Fig. 3 is a dual-gate mixer used in traditional microwave design. Assume abrupt edges and a 50% duty cycle for the LO, and neglect channel-length modulation and body effect.


 


Fig. 3. A dual-gate mixer.

- (a) Assume that  $M_1$  is an ideal switch. Determine all the frequency components which appear at the mixer IF port. (2 p)
- (b) Assume when  $M_1$  is on, it has an on-resistance of  $R_{on1}$ . Compute the voltage conversion gain of the circuit. Assume  $M_2$  does not enter the triode region and denote its transconductance by  $g_{m2}$ . (1 p)
- (c) Assume that  $M_1$  is an ideal switch (noise contribution is zero). Derive the expression for the noise figure of the mixer. (2 p)

**Hints:**

 

- i)  $i_{LO}(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) - \frac{2}{3\pi} \cos 3\omega_{LO}(t) + \frac{2}{5\pi} \cos 5\omega_{LO}(t) - \dots$
- ii)  $i_{RF}(t) = I_{bias} + I_{RF} \cos \omega_{RF}(t)$
- iii)  $i_{n,M}^2 = 4KT\gamma g_m$

4) A negative-resistance oscillator operating at 2.4 GHz frequency is shown in Fig. 4. The resonant circuit is implemented using inductor  $L = 5$  nH with  $Q = 10$  and a variable capacitor  $C$ . Assume that we can neglect all parasitics associated with the transistors.

- (a) What is the minimum width of two identical transistors  $M_1$  and  $M_2$  to ensure the oscillation? (2 p)
- (b) How much should the variable capacitance  $C$  be varied to enable tuning from 2.4 GHz to 2.5 GHz? (1 p)
- (c) For a capacitance corresponding to 2.4 GHz oscillation frequency, if an additional inductor of 5 nH is connected in parallel with the capacitor  $C$ , how much will the oscillation frequency change (in percentage)? (2 p)

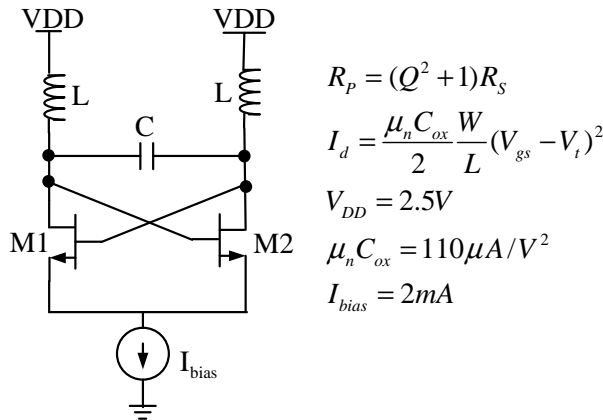


Fig. 4. A negative-resistance oscillator.

5) Figure 5 shows a block level description of a PLL.

- (a) Determine the closed-loop transfer function (i.e.,  $\frac{\Phi_{out}}{\Phi_{in}}(s)$ ) and the type of the PLL. (2 p)
- (b) Prove that for slow input phase variations the output tracks the input. (2 p)


 


Fig. 5. Block level description of a PLL.

## TRANSISTOR EQUATIONS

 

### NMOS

- **Cutoff:**  $I_D = 0$  ( $V_{GS} < V_{TN}$ )
- **Linear mode:**

$$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} < V_{GS} - V_{TN})$$
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} > V_{GS} - V_{TN})$$
- **On-resistance in triode region:**  $R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})}$

### PMOS

- **Cutoff:**  $I_D = 0$  ( $V_{GS} < |V_{TP}|$ )
- **Linear mode:**

$$I_D = \mu_p C_{ox} \frac{W}{L} \left( (V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right) \quad (V_{GS} > |V_{TP}|) \text{ and } (V_{SD} < V_{SG} - |V_{TP}|)$$
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD}) \quad (V_{GS} > |V_{TP}|) \text{ and } (V_{SD} > V_{SG} - |V_{TP}|)$$
- **On-resistance in triode region:**  $R_{on} = \frac{1}{\mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)}$