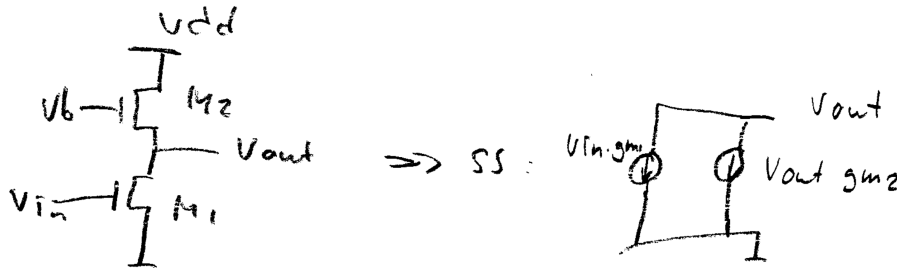


1.

Similar (but not identical) to Tutorial 6, problem 1, also similar (but again not identical) to Example 7.10 in Razavi's "Design of Analog CMOS Integrated Circuits", p. 226.

a.



$$V_{out} g_{m2} + V_{in} g_{m1} = 0$$

$$A_0 = \frac{V_{out}}{V_{in}} = - \frac{g_{m1}}{g_{m2}}$$

Noise-source independent; can be added.

$$M_1: \overline{V_{n1,M1}^2} = \frac{4kT\gamma}{g_{m1}} \quad \text{already at the input}$$

$$M_2: \overline{V_{n1,M2}^2} = \frac{\overline{V_{n0,M2}^2}}{(A_0)^2} = \frac{4kT\gamma}{g_{m2}} \cdot \left(\frac{g_{m2}}{g_{m1}} \right)^2 = \frac{4kT\gamma}{g_{m1}} \cdot \frac{g_{m2}}{(g_{m1})^2}$$


$$\overline{V_{n1,tot}^2} = \overline{V_{n1,M1}^2} + \overline{V_{n1,M2}^2} = \frac{4kT\gamma}{g_{m1}} \left(1 + \frac{g_{m2}}{g_{m1}} \right)$$

* compared to the tutorial and Razavi analog CMOS,
 $\lambda = 0 \Rightarrow$ no CLM \Rightarrow no r_{o1} & r_{o2} !

1 b. To minimize the (input-referred) noise, g_{m2} should be minimized. Since g_m is proportional to the square root of (W/L) , the size of M_2 should be small (small W for fixed L).

2.

Small-signal model:

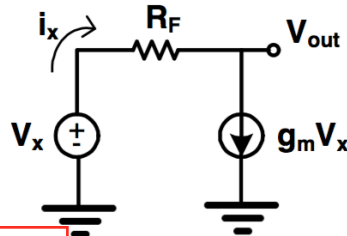

$$(a) i_x = g_m V_x \rightarrow R_{in} = \frac{V_x}{i_x} = \frac{1}{g_m}$$

(b) Gain from the gate of the transistor to the output:

$$\frac{V_{out} - V_x}{R_F} + g_m V_x = 0 \rightarrow \frac{V_{out}}{V_x} = 1 - g_m R_F$$

$$\text{After matching: } g_m = 1/R_S \rightarrow A = \frac{V_{out}}{V_{in}} = \frac{1/g_m}{R_S + 1/g_m} (1 - g_m R_F) = \frac{1}{2} \left(1 - \frac{R_F}{R_S}\right)$$

If $R_F = 10R_S$, then $A = -9/2$ or -4.5

(c) The noise of R_S is multiplied by the gain square to appear at the output. Thus:

$$\overline{V_{n,out,R_S}^2} = 4kTR_S \cdot \frac{1}{4} \left(1 - \frac{R_F}{R_S}\right)^2$$

If $R_F \gg R_S$:

$$\overline{V_{n,out,R_S}^2} \approx 4kTR_S \cdot \frac{1}{4} \left(-\frac{R_F}{R_S}\right)^2 = kT \frac{R_F^2}{R_S}$$

3.

(a) Ignoring higher frequency terms:

$$i_{LO}(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) - \frac{2}{3\pi} \cos 3\omega_{LO}(t) + \dots \quad \text{and} \quad i_{RF}(t) = I_{RF} \cos \omega_{RF}(t) + I_{BIAS}$$

Therefore in case of switching the output voltage at IF is given by:

$$i_{IF}(t) = [I_{RF} \cos \omega_{RF}(t) + I_{BIAS}] \times \left[\frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) \right]$$

$$i_{IF}(t) = \frac{I_{RF}}{2} \cos \omega_{RF}(t) + \frac{I_{BIAS}}{2} + \frac{2I_{BIAS}}{\pi} \cos \omega_{LO}(t) + \frac{I_{RF}}{\pi} \cos(\omega_{LO} - \omega_{RF})t$$

Applying $V_{IF}(t) = -g_m R V_{RF}$, The conversion gain is given by:

$$G_C = \frac{|V_{IF}(t)|}{|V_{RF}(t)|} = \frac{\left| \frac{R \times i_{IF}(t)}{g_m} \right|}{I_{RF}} = \frac{\frac{1}{\pi} g_m R I_{RF}}{I_{RF}} = \frac{1}{\pi} g_m R$$

similar to g_m for our transistors, since long channel devices

(b) $\bar{V}_{nout,M3}^2 = \bar{I}_{n,M3}^2 R^2 = 4KT\gamma g_{d\sigma} R^2 \Delta f$

$$\bar{V}_{nout,R_S}^2 = \bar{V}_{n,R_S}^2 A_V^2 = 4KTR_S (g_m R)^2 \Delta f$$

$$\bar{V}_{nout,R}^2 = 4KTR \Delta f$$

The noise factor is given by:

$$F = \frac{\bar{V}_{nout,M3}^2 + \bar{V}_{nout,R_S}^2 + \bar{V}_{nout,R}^2}{(G_C)^2 \bar{V}_{n,R_S}^2} = \pi^2 \left(1 + \frac{\gamma}{g_m^2 R_S} + \frac{1}{g_m^2 R R_S} \right)$$

The M_3 in this solution is called M_2 for our problem

4.

a. See Example 8.14 and Figure 8.26 in the book. Here instead we have $Q=8$ @ 2.45 GHz
 $\Rightarrow Q*(L1+L2)*\omega = 246 \Omega$.

g_m for the transistors $> 246/2 = 123 \Omega^{-1}$.

b. See the book, pp. 511-512.

5.

Similar to Fig 9.30 in the course book and eq. 9.17 - 9.19.

The solution can also be written as:

Open loop transfer functions of the system is:

$$H_o(s) = K_{PFD} Z_{LPF}(s) \frac{K_{VCO}}{s} = \frac{I_o}{2\pi} \left(\frac{1}{sC_p} + R \right) \frac{K_{VCO}}{s}$$

$$H_o(s) = \frac{I_o K_{VCO}}{2\pi C_p} \frac{1 + sRC_p}{s^2} = k \frac{1 + sRC_p}{s^2}, \text{ where } k = \frac{I_o K_{VCO}}{2\pi C_p}$$

The close-loop transfer function is then:

$$H(s) = \frac{H_o(s)}{1 + H_o(s)} = k \frac{1 + sRC_p}{s^2 + sRC_p k + k}$$

6.

a. B C E D A

b. The "conduction angle" describes how large portion of the total cycle an amplifier is conducting, see book, p. 780.