

1.

The gain of the first stage is $A_1 = g_{m1}R_1$ and the gain of the second stage is $A_2 = g_{m2}R_2$. There are two noise sources contributed by the transistors. Thus the total noise at the output is:

$$4kTR_S\Delta f \times A_1^2A_2^2 + 4kT\gamma g_{m1}\Delta f \times R_1^2 \times A_2^2 + 4kT\gamma g_{m2}\Delta f \times R_2^2$$

The total noise at the output due to the source is: $4kTR_S\Delta f \times A_1^2A_2^2$

Based on these expressions the noise figure is:


$$NF = \frac{4kTR_S\Delta f \times A_1^2A_2^2 + 4kT\gamma g_{m1}\Delta f \times R_1^2 \times A_2^2 + 4kT\gamma g_{m2}\Delta f \times R_2^2}{4kTR_S\Delta f \times A_1^2A_2^2} \Rightarrow$$

$$NF = 1 + \frac{\gamma}{g_{m1}R_S} + \frac{\gamma}{g_{m1}^2g_{m2}R_S R_1^2}$$

2.

- See Example 5.3 in Razavi. New value for $Q = 2450/(2550-2350) = 12.25 \approx 12$.
- On-chip L:s are usually much more lossy than on-chip C:s.
- In the L, the Q value is mainly limited by the series resistance in the metallization and, at higher frequencies, the losses in the substrate.

3. Start by calculating R_{in} and A_v :

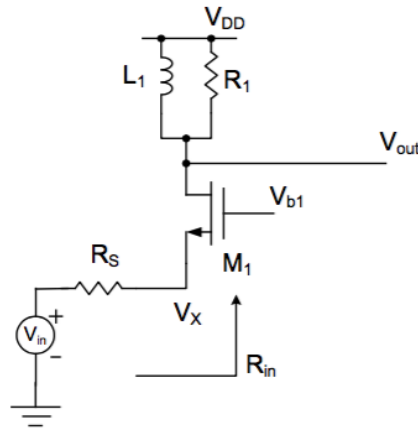

$$R_{in} = \frac{1}{g_{m1}} \text{ and } A_x = g_{m1}R_1$$

Assume input matching, $R_S = \frac{1}{g_{m1}}$ and $A_v = \frac{R_1}{2R_S}$

Now we calculate the noise figure. The noise contributions are from M1, M2, R1, and R_s.

- a. The output noise power of M1.
Similar to Problem 5.8 (or refer to the book on page 277)

$$\overline{V_{n,out}^2} \Big|_{M1} = \frac{4kT\gamma}{g_{m1}} \left(\frac{R_1}{R_S + \frac{1}{g_{m1}}} \right)^2 = kT\gamma \frac{R_1^2}{R_S}$$

- b. Calculate the output noise power from R1

$$\overline{V_{n,out}^2} \Big|_{R1} = 4kTR_1$$

- c. Calculate the output noise power from M2
First, we calculate the noise voltage gain from M2 to output.

$$A_{M2} = -\frac{g_{m2}R_1}{2}$$

Thus, the output noise power of M2:

$$\overline{V_{n,out}^2} \Big|_{M2} = \frac{4kT\gamma}{g_{m2}} \left(\frac{g_{m2}R_1}{2} \right)^2 = kT\gamma g_{m2}R_1^2$$

The noise of R_s is multiplied by the gain when referred to the output, and the result is divided by the gain when referred to the input. We thus have:

$$\begin{aligned} NF &= \frac{1}{4kTR_S} \frac{\overline{V_{n,out}^2}}{A_v^2} \\ &= 1 + \frac{4kTR_1}{4kTR_S \left(\frac{R_1}{2R_S} \right)^2} + \frac{kT\gamma \frac{R_1^2}{R_S}}{4kTR_S \left(\frac{R_1}{2R_S} \right)^2} + \frac{kT\gamma g_{m2}R_1^2}{4kTR_S \left(\frac{R_1}{2R_S} \right)^2} \\ &= 1 + 4 \frac{R_S}{R_1} + \gamma + \gamma g_{m2}R_S \end{aligned}$$

4.

$$\left(\phi_{in}(s) - \frac{\phi_{out}(s)}{M} \right) \cdot K_{PD} \cdot \frac{1}{sRC+1} \cdot \frac{K_{VCO}}{s} = \phi_{out}(s)$$

$$\phi_{in}(s) \left(K_{PD} \cdot \frac{1}{sRC+1} \cdot \frac{K_{VCO}}{s} \right) = \phi_{out}(s) \left(1 + \frac{K_{PD}K_{VCO}}{s(sRC+1)M} \right)$$

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{\frac{K_{PD}K_{VCO}}{s(sRC+1)}}{1 + \frac{K_{PD}K_{VCO}}{s(sRC+1)M}} = \frac{\frac{K_{PD}K_{VCO}}{s(sRC+1)}}{\frac{s(sRC+1)M + K_{PD}K_{VCO}}{s(sRC+1)M}} = \frac{K_{PD}K_{VCO}M}{s(sRC+1)M + K_{PD}K_{VCO}} = \frac{K_{PD}K_{VCO}M}{s^2RCM + sM + K_{PD}K_{VCO}}$$

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{\frac{K_{PD}K_{VCO}M}{RCM}}{s^2 + s \frac{M}{RCM} + \frac{K_{PD}K_{VCO}}{RCM}} = \frac{\frac{K_{PD}K_{VCO}}{RC}}{s^2 + s \frac{1}{RC} + \frac{K_{PD}K_{VCO}}{RCM}}$$


$$s^2 + 2\xi\omega_n s + \omega_n^2 \Rightarrow$$

$$\omega_n = \sqrt{\frac{K_{PD}K_{VCO}}{RCM}} \quad \text{and}$$

$$2\xi\omega_n = \frac{1}{RC} \Rightarrow \xi = \frac{1}{2\omega_n RC} = \frac{1}{2RC \sqrt{\frac{K_{PD}K_{VCO}}{RCM}}} = \frac{1}{2\sqrt{\frac{K_{PD}K_{VCO}RC}{M}}}$$

5.

(a)

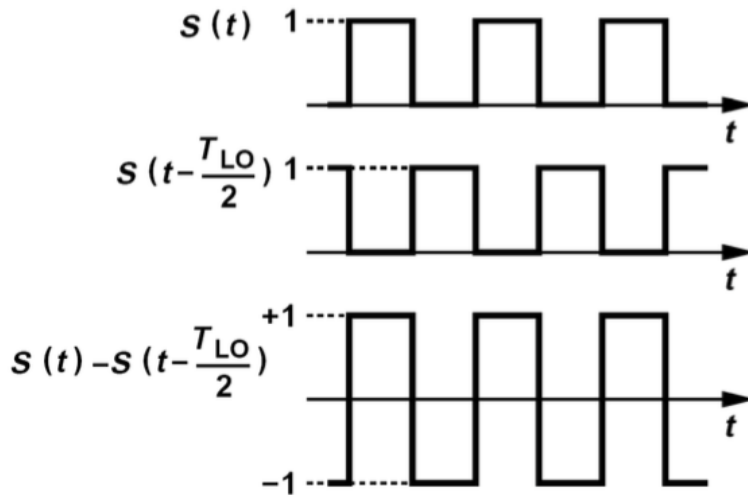

$$V_{out}(t) = I_{RF}R [S(t) - S(t - T_{LO}/2)]$$

If $V_{RF} = A_{RF} \cos(\omega_{RF}t)$, then by ignoring the higher order terms:

$$V_{IF} = V_{out} = \frac{4}{\pi} g_{m3} R A_{RF} \cos(\omega_{RF}t) \cos(\omega_{LO}t) = \frac{2}{\pi} g_{m3} R A_{RF} \cos((\omega_{RF} - \omega_{LO})t)$$

Therefore the conversion gain is:

$$G_C = \frac{V_{IF}}{A_{RF}} = \frac{2}{\pi} g_{m3} R$$

(b)

$$\overline{V_{n,out,M_3}^2} = 4kT\gamma g_m R^2$$

$$\overline{V_{n,out,R_S}^2} = 4kT R_S (g_m R)^2$$

$$\overline{V_{n,out,R}^2} = 2 \times 4kT R$$

The noise figure can be written as:

$$NF = \frac{\overline{V_{n,out,M_3}^2} + \overline{V_{n,out,R_S}^2} + \overline{V_{n,out,R}^2}}{G_C^2 \overline{V_{n,out,R_S}^2}} = \frac{\pi^2}{4} \left(1 + \frac{\gamma}{g_m R_S} + \frac{2}{g_m^2 R_S R} \right)$$

6.

See Example 12.6 in Razavi for the details.

6a: losses in the balun = 0.3 mW

6b: losses in the balun = 300 mW this is more unfavorable