

EXAMINATION IN

TSEK03

**RADIO FREQUENCY INTEGRATED
CIRCUITS**

Date: 2016-08-27

Time: 8-12

Location: TER1

Tools: Calculator, Dictionary

Teachers: Ted Johansson (070-6270237)
alt. 1223


12 points are required to pass.
(12-15: 3, 16-19: 4, 20-24: 5)

Please start each new problem at the top of a page!
Only use one side of each paper!

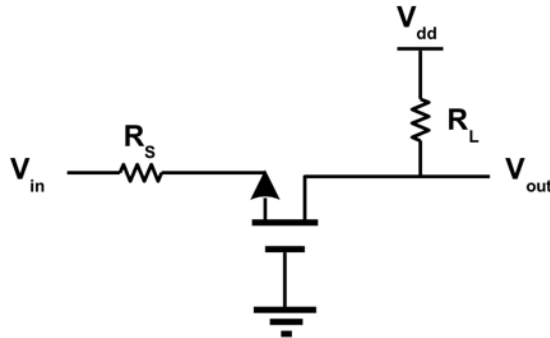1.

Consider the common-gate broadband amplifier below.


- Derive an expression for the noise figure in the absence of gate noise. Select the transistor's g_m for use as an LNA. Neglect transistor capacitances, body effect, and channel-length modulation. (3 p)
- Re-derive the noise figure, now taking gate noise into account. Hint: model the gate noise using a voltage source of $4kTR_G/3$. (1 p)



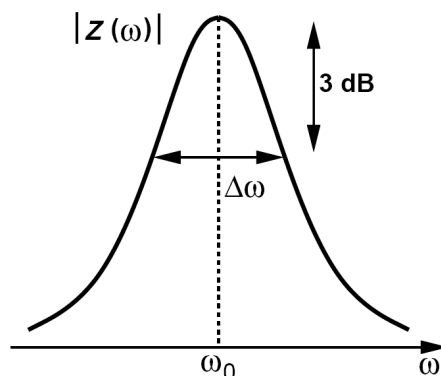2.

A Bluetooth LNA must achieve a 3-dB bandwidth from 2350 to 2550 MHz in order to fulfill a 1-dB bandwidth in the 2400 MHz to 2485 MHz (ISM) band.


- If the LNA incorporates a second-order LC tank as its load, what is the maximum allowable tank Q? (2 p)
- This tank Q is given by the combination of the Q for the L:s and for the C:s. Which component of the L and C typically have the lowest Q (highest losses) when realized on-chip in a typical CMOS process, thus limiting the Q of the tank? (1 p)
- What are the main sources of the losses in this component (give at least one)? (1 p)



3.

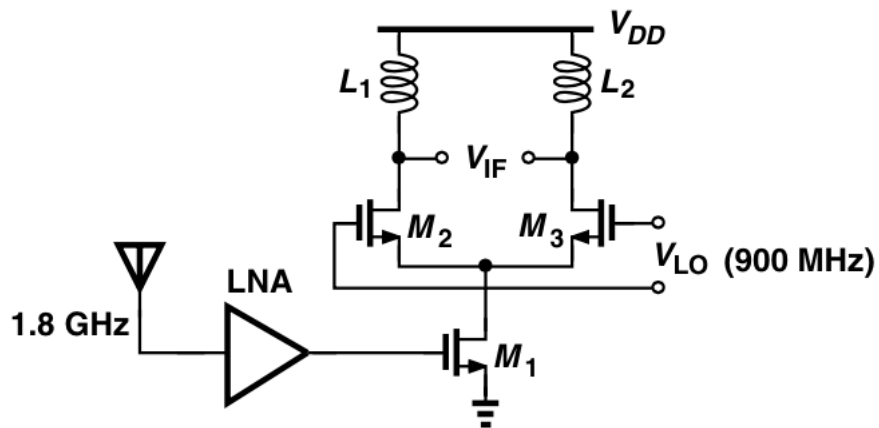- a. Shown in the figure below is the frontend of a 1.8-GHz receiver. The LO frequency is chosen to be 900 MHz and the load inductors and capacitances resonate with a quality factor of Q at IF. Assume M_1 is biased at a current of I_1 , the mixer and the LO are perfectly symmetric, and M_2 and M_3 switch abruptly and completely.

Compute the LO-IF feedthrough, i.e., the measured level of the 900-MHz output component in the absence of an RF signal. Model the inductor losses with parallel resistors, $Q = R_p / (\omega_0 L_p)$. (3 p)




- b. Assuming that all components of this heterodyne mixer are noiseless — except for the equivalent thermal noise from the antenna — what is the noise figure of the mixer (also called SSB noise figure)? (1 p)


4.

The symmetric inductor in the figure below has a value of 2 nH (from port X to port Y) and a Q of 5 at 2.45 GHz. $M_1 = M_2$.

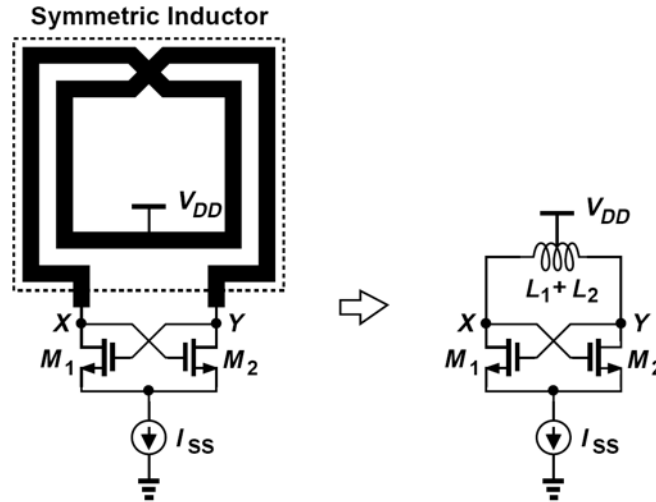- a. What is the minimum required transconductance (g_m) of M_1 and M_2 to guarantee startup? (2 p)



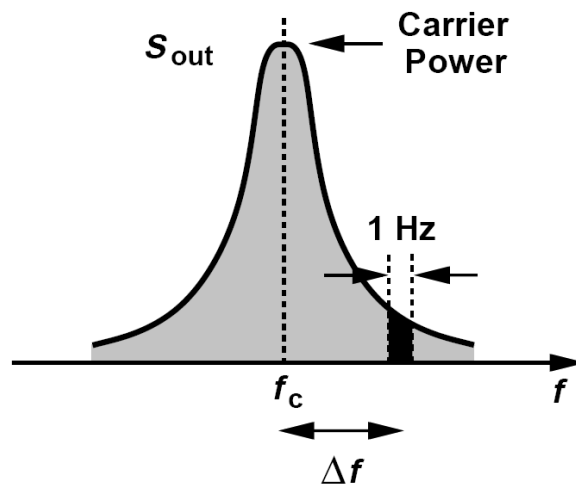
- b. Phase noise: At high carrier frequencies, it is difficult to measure the noise power in a 1-Hz bandwidth. Suppose a spectrum analyzer measures a noise power of -70 dBm in a 1-kHz bandwidth at 1-MHz offset. How much is the phase noise at this offset if the average oscillator output power is -2 dBm? (2 p)



5.

A block level description of a PLL is shown below.

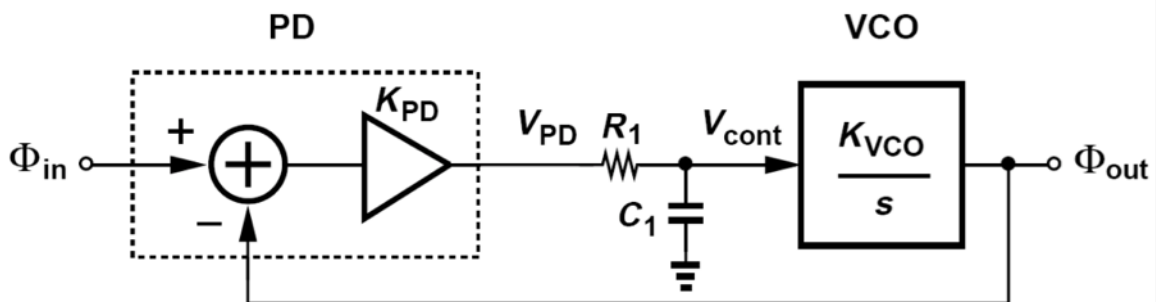- a. Derive an expression for the closed-loop transfer function, $H(s) = \Phi_{out}(s)/\Phi_{in}(s)$. (2 p)
- b. What type of PLL is it? (1 p)
- c. Prove that for slow input phase variations, the output tracks the input. (2 p)



6.

- a. The following table lists three different properties for the A, B, C, D, and E power amplifier classes and their typical values. Identify the power amplifier class for each column. (2.5 p)

Maximum drain efficiency [%]	50	78.5	100	100	100
Peak drain voltage [$*V_{DD}$]	2	2	1	2	3.6
Normalized power output capability [Pout/(max V and I)]	0.125	0.125	0.32	0.125	0.098
Power Amplifier Class					

- b. How do you design a Doherty amplifier with only one amplifier (transistor)? (0.5 p)