
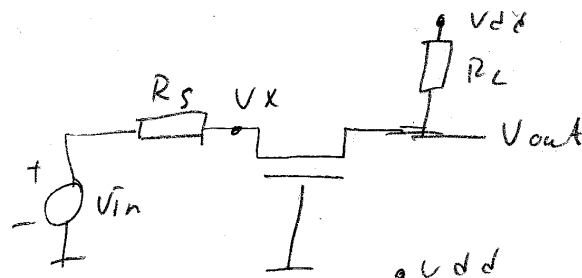


Solutions.

(a) Circuit:

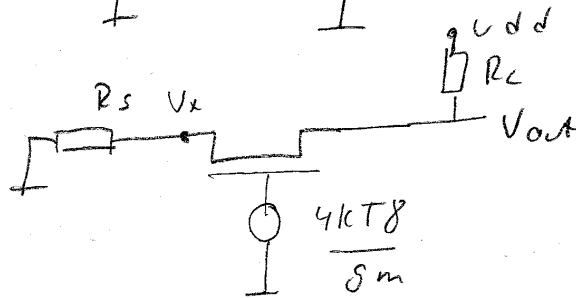

For noise



(c) Gain? $\frac{V_{out}}{V_x} = g_m \cdot R_L$

$$A_v = \frac{V_{out}}{V_{in}} = g_m \cdot R_L \left(\frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_S} \right) = g_m \cdot R_L \left(\frac{1}{1 + g_m \cdot R_S} \right)$$

When used as an LNA, select $g_m = \frac{1}{R_S} \Rightarrow$

$$A_v = \frac{R_L}{2R_S}$$

(i) Noise from MI: $\overline{V_{n,out,MI}^2} = \frac{4kT\gamma}{g_m} \left(\frac{R_L}{R_S + \frac{1}{g_m}} \right)^2 = kT\gamma \frac{R_L^2}{R_S}$

Noise from $R_L = \overline{V_{n,out,RL}^2} = 4kTR_L$

(ii) NF: $1 + \frac{\overline{V_{n,out,MI}^2} + \overline{V_{n,out,RL}^2}}{A_v^2 \cdot \overline{V_{n,RS}^2}} =$

(1 a) cont.

$$= 1 + \frac{KT\gamma \frac{R_L^2}{R_S} + 4KT R_L}{\left(\frac{R_L}{2R_S}\right)^2 \cdot 4KT R_S} = 1 + \frac{KT R_L^2}{R_S}$$

$$\Rightarrow \boxed{1 + \gamma + 4 \frac{R_S}{R_L}} \quad \text{NF}$$

1 b) For gate noise, add another voltage source on the gate: $\overline{V_{n\text{out}, M_3}^2} = \frac{4KT R_G}{3} \cdot \left(\frac{R_L}{2R_S}\right)^2 =$

$$= \frac{KT \cdot R_G \cdot R_L^2}{3 R_S^2}$$

$$\Rightarrow \text{NF} = 1 + \frac{KT\gamma \frac{R_L^2}{R_S} + \frac{KT R_G \cdot R_L^2}{3 R_S^2} + 4KT R_L}{KT \frac{R_L^2}{R_S}} =$$

$$\boxed{1 + \gamma + \frac{R_G}{3R_S} + 4 \frac{R_S}{R_L}} \quad \text{NF}$$

2.

a. See Example 5.3 in Razavi. New value for $Q = 2450/(2550-2350) = 12.5$


b. On-chip L are usually much more lossy than on-chip C.

c. In the L, the Q value is mainly limited by the series resistance in the metallization and, at higher frequencies, the losses in the substrate.

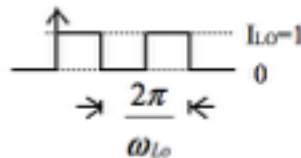3.

a.

LO-IF feedthrough: measured level of the 900-MHz output component in the absence of an RF signal.



$$i_{LO}^+(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) - \frac{2}{3\pi} \cos 3\omega_{LO}(t) + \frac{2}{5\pi} \cos 5\omega_{LO}(t) - \dots$$

$$i_{LO}^-(t) = \frac{1}{2} - \frac{2}{\pi} \cos \omega_{LO}(t) + \frac{2}{3\pi} \cos 3\omega_{LO}(t) - \frac{2}{5\pi} \cos 5\omega_{LO}(t) + \dots$$

$$i_{RF}(t) = I_1 + I_{RF} \cos \omega_{RF} t$$

No RF signal: $I_{RF} = 0 \Rightarrow i_{RF}(t) = I_1$

The output current at IF is given by:

$$i_{IF}^+(t) = i_{LO}^+(t) \times i_{RF}(t) = \left[\frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) - \frac{2}{3\pi} \cos 3\omega_{LO}(t) + \frac{2}{5\pi} \cos 5\omega_{LO}(t) - \dots \right] \cdot (I_1)$$

$$= \frac{I_1}{2} + \frac{2I_1}{\pi} \cos \omega_{LO}(t)$$

$$i_{IF}^-(t) = i_{LO}^-(t) \times i_{RF}(t) = \left[\frac{1}{2} - \frac{2}{\pi} \cos \omega_{LO}(t) + \frac{2}{3\pi} \cos 3\omega_{LO}(t) - \frac{2}{5\pi} \cos 5\omega_{LO}(t) + \dots \right] \cdot (I_1)$$

$$= \frac{I_1}{2} - \frac{2I_1}{\pi} \cos \omega_{LO}(t)$$

$$i_{IF}(t) = i_{IF}^+(t) - i_{IF}^-(t) = \frac{4I_1}{\pi} \cos \omega_{LO}(t)$$

$$v_{IF}(t) = i_{IF}(t) \times R_p = \frac{4}{\pi} I_1 R_p \cdot \cos \omega_{LO}(t)$$

where R_p is the parallel resistance, which models the inductor loss.

$$R_p = Q \omega_o L_p \Rightarrow \text{LO-IF feedthrough} = \frac{4}{\pi} I_1 R_p = \frac{4}{\pi} I_1 Q \omega_{LO} L_p$$

b. The noise figure of a noiseless mixer is 3 dB (SSB), Razavi 6.1.2.

4.

a. See Razavi Example 8.14 and Figure 8.26. Here instead we have $Q=5$ @ 2.45 GHz $\Rightarrow Q*(L1+L2)*\omega = 154 \Omega$. ($L1 = L2 = 1$ nH each!)

g_m for the transistors $> 154/2 = 77 \Omega^{-1}$.

b. See Razavi, Example 8.23: -98 dBc/Hz.

5.

a.
$$H(s) = \frac{\phi_{out}}{\phi_{in}}(s) = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}}$$

b. Type I.

c. For slow variations, $s \approx 0$ and then $H(s) = 1$. The output phase tracks the input.

6.

a.

Maximum drain efficiency [%]	50	78.5	100	100	100
Peak drain voltage [$*V_{DD}$]	2	2	1	2	3.6
Normalized power output capability [Pout/(max V and I)]	0.125	0.125	0.32	0.125	0.098
Power Amplifier Class	A	B	D	C	E

b. You don't! :-)

A Doherty amplifier (Razavi section 12.9) consists of (at least) two amplifiers: a main amplifier (carrier PA) and an auxiliary amplifiers (peaking PA).