

EXAMINATION IN
TSEK03
RADIO FREQUENCY INTEGRATED
CIRCUITS


Date: 2017-03-14
Time: 8-12
Location: TER2
Tools: Calculator, Dictionary
Teachers: Ted Johansson (070-6270237)
alt. 1223
Oscar Morales (070-4023671)

12 points are required to pass.
(12-15: 3, 16-19: 4, 20-24: 5)

Please start each new problem at the top of a page!
Only use one side of each paper!

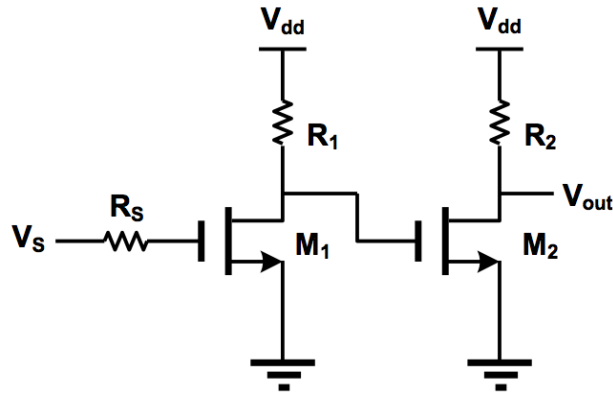
1.

A two-stage amplifier is shown below. Derive the noise factor of this amplifier. Consider only the thermal noise sources and ignore the gate and $1/f$ noise of the transistors. Assume that R_1 and R_2 are noiseless, ignore all the parasitics, and neglect channel-length modulation. (4 p)



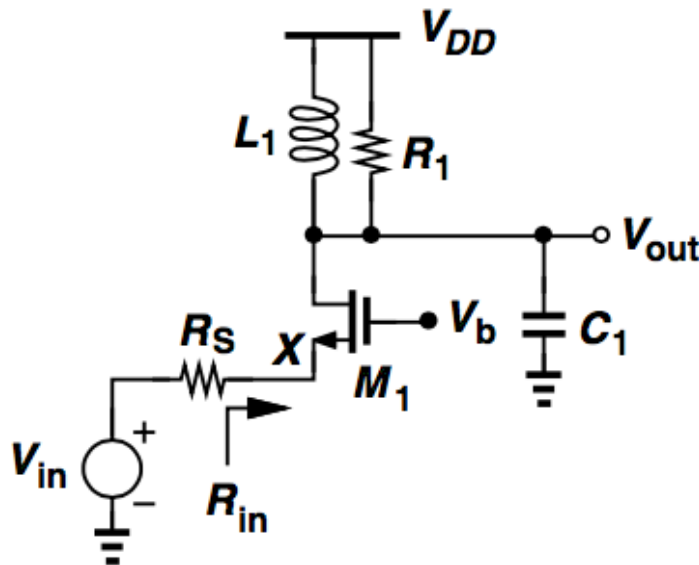
2.

A common-gate LNA is shown below. Derive the noise factor at the output resonance frequency if $g_m \neq R_s$. (4 p)



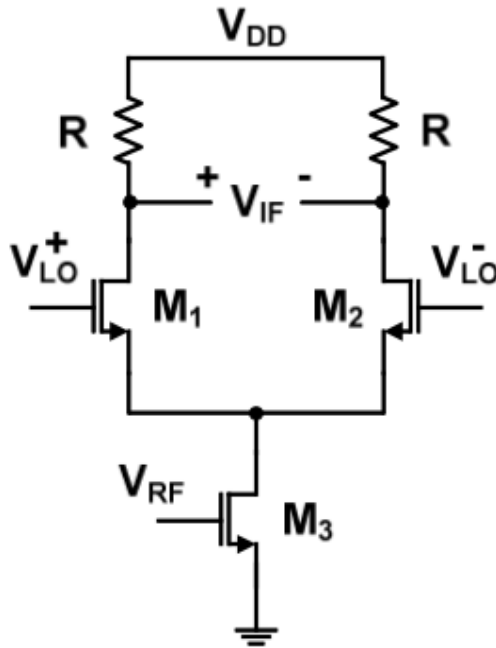3.

A single-balanced mixer is shown below. Assume that the switching transistors M_1 and M_2 are ideal switches with zero on-resistance and there is no CLM.



- a. Derive an expression for the conversion gain of this mixer. (2 p)
- b. Derive an expression for the noise factor of this mixer. (3 p)

Assume the switching transistors do not generate noise. The total noise is contributed by transistor M_3 , load resistors R and source resistor R_S connected to the RF input (not shown in the figure). Consider only the thermal noise sources and ignore the gate noise of the transistor.

Hints:

$$\text{i) } \overline{i_{n,M}^2} = 4kT\gamma g_m$$

$$\text{ii) } V_{LO}(t) = \frac{4}{\pi} \cos \omega_{LO}(t) - \frac{4}{3\pi} \cos 3\omega_{LO}(t) + \frac{4}{5\pi} \cos 5\omega_{LO}(t) - \dots$$





4.

Which of the following circuits oscillate?

(4p)

For each circuit, state the reason in terms (some or all) of:

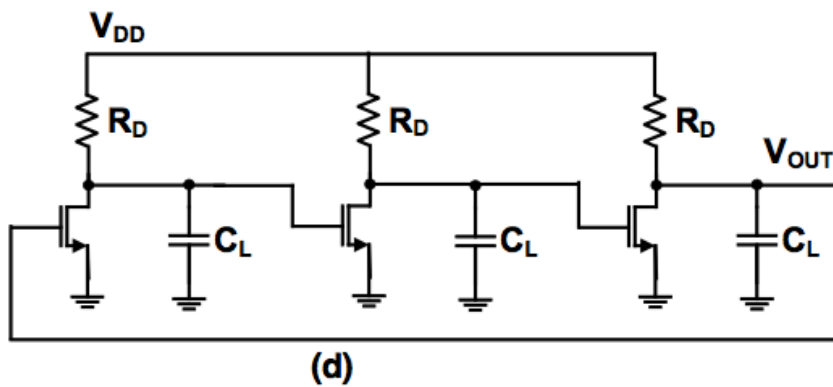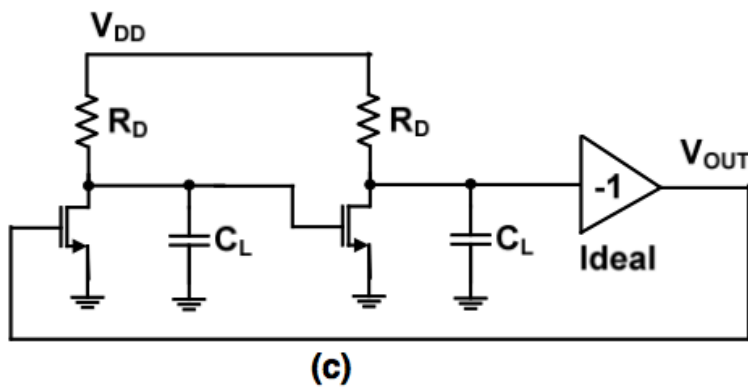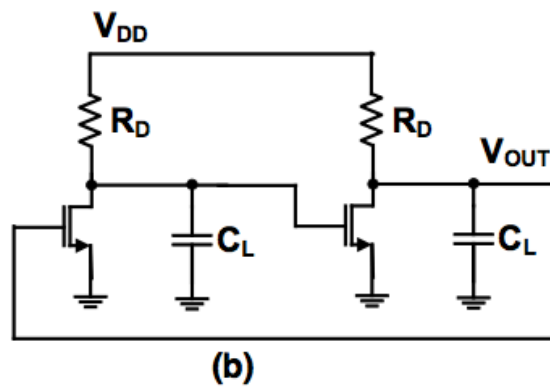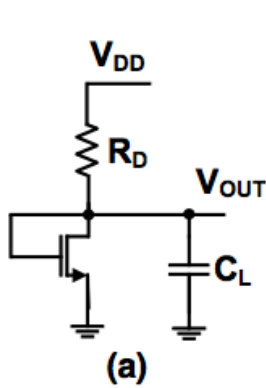
- DC shift,
- frequency dependent phase shift,
- open loop circuit poles,
- total phase shift,
- conclusion: no or possible oscillation.



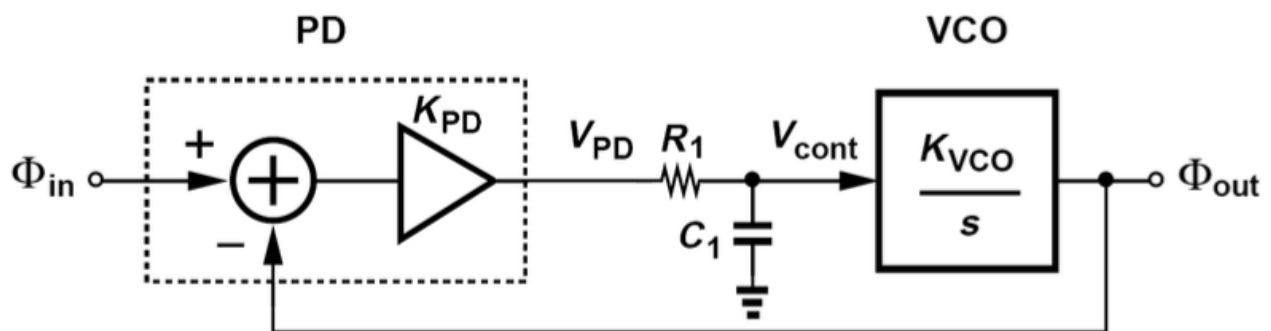5.

A block level description of a PLL is shown below.

- Derive an expression for the closed-loop transfer function, $H(s) = \Phi_{\text{out}}(s)/\Phi_{\text{in}}(s)$. (3 p)
- What type of PLL is it? Motivate! (1 p)
- Prove that for slow input phase variations, the output tracks the input. (1 p)



6.

A couple of power amplifier questions!

- Best class for efficiency? A or B? (0.5 p)
- Best class for efficiency? A or D (inverter-based class-D)? (0.5 p)
- Best class for linearity? A or B? (0.5 p)
- Best class for linearity? A or D? (0.5 p)

Please give short motivations for your answers.
