
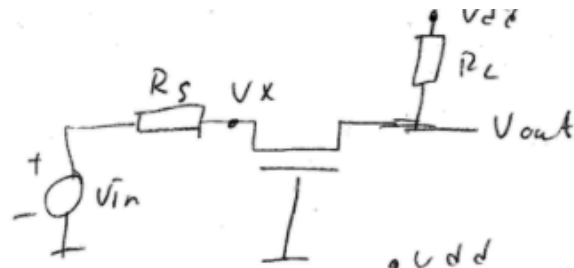


Solutions

(a) Circuit:

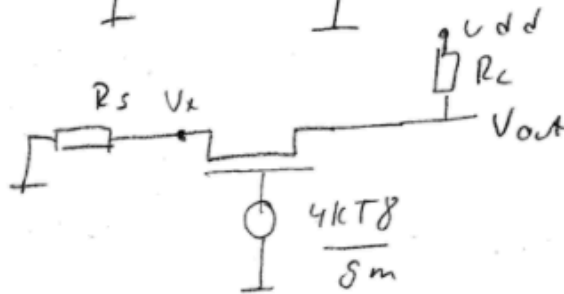

For noise



(i) Gain?  $\frac{V_{out}}{V_x} = g_m \cdot R_L$

$$A_v = \frac{V_{out}}{V_{in}} = g_m \cdot R_L \left( \frac{\frac{1}{g_m}}{\frac{1}{g_m} + R_s} \right) = g_m \cdot R_L \left( \frac{1}{1 + g_m \cdot R_s} \right)$$

When used as an LNA, select  $g_m = \frac{1}{R_s} \Rightarrow$

$$A_v = \frac{R_L}{2R_s}$$

(ii) Noise from  $M_1$ :  $\overline{V_{n,out,M_1}^2} = \frac{4kTg}{g_m} \cdot \left( \frac{R_L}{R_s + \frac{1}{g_m}} \right)^2 = kTg \cdot \frac{R_L^2}{R_s}$

Noise from  $R_L$ :  $\overline{V_{n,out,R_L}^2} = 4kTR_L$

(ii) NF:  $1 + \frac{\overline{V_{n,out,M_1}^2} + \overline{V_{n,out,R_L}^2}}{A_v^2 \cdot \overline{V_{n,R_s}^2}} =$

(1 a) cont.

$$= 1 + \frac{KT\gamma \frac{R_L^2}{R_S} + 4KT R_L}{\left(\frac{R_L}{2R_S}\right)^2 \cdot 4KT R_S} = 1 + \frac{KT R_L^2}{R_S}$$

$$= \boxed{1 + \gamma + 4 \frac{R_S}{R_L}} \quad NF$$

1 b) For gate noise, add another voltage source on the gate:  $\overline{V_{n,out,MIS}^2} = \frac{4KT R_G}{3} \cdot \left(\frac{R_L}{2R_S}\right)^2 =$

$$= \frac{KT \cdot R_G \cdot R_L^2}{3 R_S^2}$$

$$\Rightarrow NF = 1 + \frac{KT\gamma \frac{R_L^2}{R_S} + \frac{KT R_G \cdot R_L^2}{3 R_S^2} + 4KT R_L}{KT \frac{R_L^2}{R_S}} =$$

$$\boxed{1 + \gamma + \frac{R_G}{3R_S} + 4 \frac{R_S}{R_L}} \quad NF$$


1c.

3 dB, see Razavi, chapter 6.1.2

2.

As a start, see Tutorial 6, problem 2. But here not matched,  $g_m \neq R_s$ . This is actually Problem 5.8 from the book.

1. Calculate the voltage gain

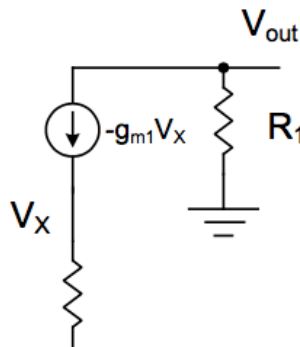

$$V_{out} = g_{m1} V_X R_1 \quad \rightarrow \quad A_X = \frac{V_{out}}{V_X} = g_{m1} R_1$$



Since  $R_{in} = \frac{1}{g_{m1}}$ , we have the voltage gain from  $V_{in}$  to  $V_{out}$ :

$$A_V = \frac{1}{R_S + \frac{1}{g_{m1}}} A_X = \frac{g_{m1} R_1}{1 + R_S g_{m1}}$$

2. Calculate noise figure

The noise contributions are from M1, R1, and  $R_s$ .

a. Calculate output noise from M1

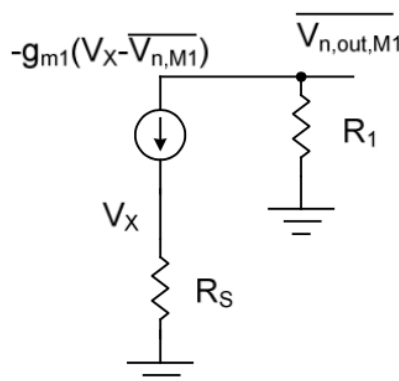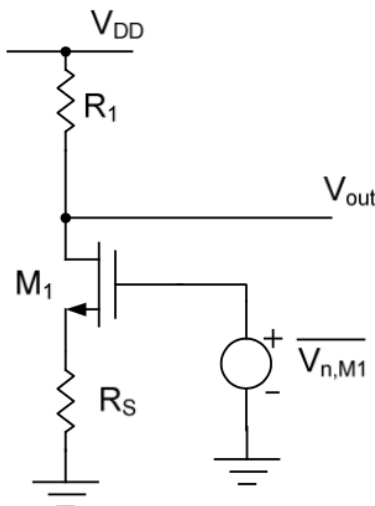

2. (continued)

$$A_{M1} = -\frac{R_1}{R_S + \frac{1}{g_{m1}}}, \text{ hence the output noise of M1 can be obtained from}$$

$$\overline{V_{n,out}^2} \Big|_{M1} = \frac{4kT\gamma}{g_{m1}} A_{M1}^2 = \frac{4kT\gamma}{g_{m1}} \left( \frac{R_1}{R_S + \frac{1}{g_{m1}}} \right)^2$$

b. Calculate output noise from R1

$$\overline{V_{n,out}^2} \Big|_{R1} = 4kTR_1$$

The noise of  $R_S$  is multiplied by the gain when referred to the output, and the result is divided by the gain when referred to the input.

We thus have:

$$NF = \frac{1}{4kTR_S} \frac{\overline{V_{n,out}^2}}{A_V^2}$$

$$= 1 + \frac{4kTR_1}{4kTR_S \left( \frac{g_{m1}R_1}{1 + R_S g_{m1}} \right)^2} + \frac{\frac{4kT\gamma}{g_{m1}} \left( \frac{R_1}{R_S + \frac{1}{g_{m1}}} \right)^2}{4kTR_S \left( \frac{g_{m1}R_1}{1 + R_S g_{m1}} \right)^2}$$

$$= 1 + \frac{(1 + R_S g_{m1})^2}{R_S R_1 g_{m1}^2} + \frac{\gamma}{g_{m1} R_S}$$

3.

- a. See Example 5.3 in Razavi. New value for  $Q = 5400/(5900-4900) = 5.4$
- b. On-chip L:s are usually much more lossy than on-chip C:s.
- c. In the L, the Q value is mainly limited by the series resistance in the metallization and, at higher frequencies, the losses in the substrate.

4.

(a) DC phase shift =  $180^\circ$  (frequency  $\rightarrow 0$ )

Open loop circuit contains one pole

 $\Rightarrow$  Frequency dependent phase shift =  $90^\circ$  (at frequency  $\rightarrow \infty$ )Total phase shift =  $90^\circ + 180^\circ = 270^\circ \Rightarrow$  No oscillation.(b) DC phase shift =  $0^\circ$  (frequency  $\rightarrow 0$ )

Open loop circuit contains two poles

 $\Rightarrow$  Frequency dependent phase shift =  $90^\circ + 90^\circ = 180^\circ$  (at frequency  $\rightarrow \infty$ )Total phase shift =  $0^\circ + 180^\circ = 180^\circ \Rightarrow$  No oscillation.(c) DC phase shift =  $180^\circ$  (frequency  $\rightarrow 0$ )

Open loop circuit contains two poles

 $\Rightarrow$  Frequency dependent phase shift =  $90^\circ + 90^\circ = 180^\circ$  (at frequency  $\rightarrow \infty$ )Total phase shift =  $180^\circ + 180^\circ = 360^\circ$ But as frequency  $\rightarrow \infty$  the loop gain vanishes  $\Rightarrow$  No oscillation.(d) DC phase shift =  $180^\circ$  (frequency  $\rightarrow 0$ )

Open loop circuit contains three poles

 $\Rightarrow$  Frequency dependent phase shift =  $90^\circ + 90^\circ + 90^\circ = 270^\circ$  (at frequency  $\rightarrow \infty$ )Total phase shift =  $180^\circ + 270^\circ = 450^\circ$  or  $90^\circ$ However at  $f = f_{p1,2,3} < \infty$ , where  $f_p$  is the cut-off frequency of a stage, the frequency dependent phase shift =  $45^\circ + 45^\circ + 45^\circ = 135^\circ$ Therefore for some  $f_p < f < \infty$  the circuit may oscillate with a sufficient loop gain.

5.

(a) Ignoring higher frequency terms:

$$i_{LO}(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) - \frac{2}{3\pi} \cos 3\omega_{LO}(t) + \dots \quad \text{and} \quad i_{RF}(t) = I_{RF} \cos \omega_{RF}(t) + I_{BIAS}$$

Therefore in case of switching the output voltage at IF is given by:

$$i_{IF}(t) = [I_{RF} \cos \omega_{RF}(t) + I_{BIAS}] \times \left[ \frac{1}{2} + \frac{2}{\pi} \cos \omega_{LO}(t) \right]$$

$$i_{IF}(t) = \frac{I_{RF}}{2} \cos \omega_{RF}(t) + \frac{I_{BIAS}}{2} + \frac{2I_{BIAS}}{\pi} \cos \omega_{LO}(t) + \frac{I_{RF}}{\pi} \cos(\omega_{LO} - \omega_{RF})t$$

Applying  $V_{IF}(t) = -g_m R V_{RF}$ , The conversion gain is given by:

$$G_C = \left| \frac{V_{IF}(t)}{V_{RF}(t)} \right| = \left| \frac{R \times i_{IF}(t)}{i_{RF}(t)} \right| = \frac{\frac{1}{\pi} g_m R I_{RF}}{I_{RF}} = \frac{1}{\pi} g_m R$$

similar to  $g_m$  for our transistors, since long channel devices

(b)  $\bar{V}_{nout,M3}^2 = \bar{I}_{n,M3}^2 R^2 = 4KT \gamma g_{d0} R^2 \Delta f$

$$\bar{V}_{nout,R_S}^2 = \bar{V}_{n,R_S}^2 A_V^2 = 4KTR_S (g_m R)^2 \Delta f$$

$$\bar{V}_{nout,R}^2 = 4KTR \Delta f$$

The noise factor is given by:

$$F = \frac{\bar{V}_{nout,M3}^2 + \bar{V}_{nout,R_S}^2 + \bar{V}_{nout,R}^2}{(G_C)^2 \bar{V}_{n,R_S}^2} = \pi^2 \left( 1 + \frac{\gamma}{g_m^2 R_S} + \frac{1}{g_m^2 R R_S} \right)$$

6.

- a. A Class-A has the best linearity among the linear classes (A, AB, B, C). By DC-biasing it to half the full output signal, any frequency signal would just swing around this middle point, with no limitations (unless very large). Class-B is off half the cycle, it is very non-linear.
- b. A Class-A: see above.  
Class-D is a switching amplifier, it has only on/off levels, and therefore very bad linearity.
- c. AB Class-A has 50 % maximum theoretical efficiency, class-B 78.5 %, and the class AB somewhere between.
- d. A Both class-A and class-E have voltage peaks (on the drain of the transistor above V<sub>dd</sub>, but A no more than about 2, while class-E is over 3.5).
- e. DE = RF-power out / DC power in.  
PAE = (RF-power out - RF-power in) / DC power in

So PAE also takes into account the input power. With high gain, then DE >> PAE, with high gain DE ≈ PAE, but PAE can never be higher than the DE.

From the lecture notes:

• Drain (collector) efficiency [%]	$\eta_D = \frac{P_{RF}}{P_{DC}}$
• Power-added efficiency [%]	$PAE = \frac{P_{RF} - P_{IN}}{P_{DC}}$
• PAE can also be expressed as	$PAE = \eta_D \frac{G-1}{G}$
• PAE: when gain is low, it takes some power to drive the PA, must be accounted for!	