

EXAMINATION IN
TSEK03
RADIO FREQUENCY INTEGRATED
CIRCUITS


Date: 2017-08-26
Time: 8-12
Location: TER3
Tools: Calculator, Dictionary
Teachers: Ted Johansson (070-6270237)
Oscar Morales (070-4023671)

12 points are required to pass.
(12-15: 3, 16-19: 4, 20-24: 5)

Please start each new problem at the top of a page!
Only use one side of each paper!

1.

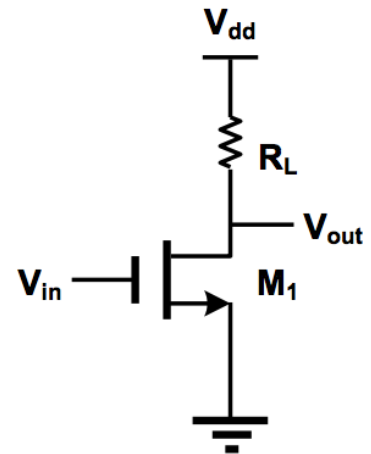a. In the amplifier schematic shown to the right, determine the total input-referred noise voltage. Consider the thermal noise sources and the noise from the gate resistance of the transistor. Neglect flicker noise, channel-length modulation and body effect. (3 p)




b. Now also add the effect of flicker noise. (1 p)
Hint: It can be model it as another current source in the transistor channel as:

$$\bar{I}_n^2 = g_m^2 \frac{K}{WLC_{ox}} \frac{1}{f}$$

c. Explain "Friis' equation" in words! What is the practical implication for the noise in a receiver chain ? (1 p)

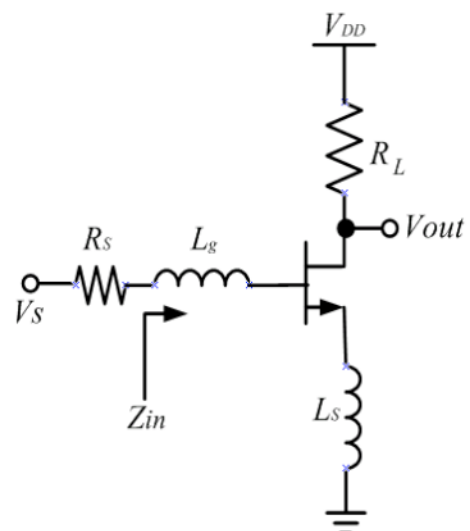2.

The inductor source degenerated amplifier shown to the right can be designed to present a noiseless resistance of 50 Ω for matching the input (Z_{in}) to a 50 Ω source.




a. Calculate the input impedance. (3 p)

b. How do we select the component values (from the derived input impedance) to achieve matching to a 50 Ω source? (1 p)

4.


The symmetric inductor in the figure below has a value of 2 nH (from port X to port Y) and a Q of 5 at 2.45 GHz. $M_1 = M_2$.

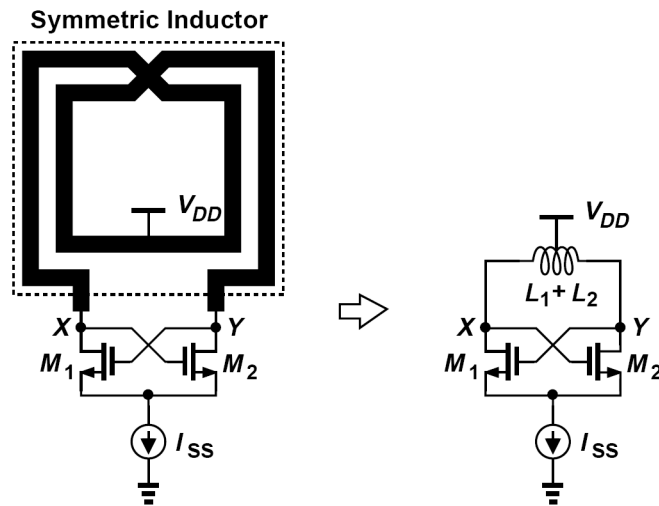a. What is the minimum required transconductance (g_m) of M_1 and M_2 to guarantee




startup? (2 p)

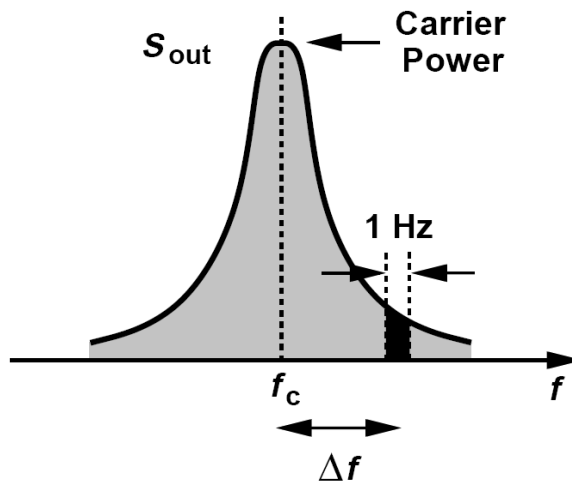b. Phase noise: At high carrier frequencies, it is difficult to measure the noise power in a 1-Hz bandwidth. Suppose a spectrum analyzer measures a noise power of -70 dBm in a 1-kHz bandwidth at 1-MHz offset. How much is the phase noise at this offset if the average oscillator output power is -2 dBm? (2 p)



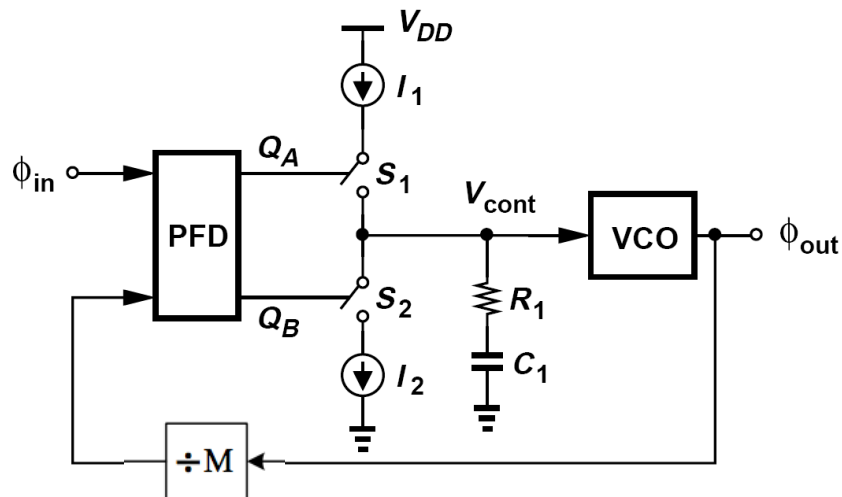5.

Derive an expression for the closed-loop phase transfer function, $H(s) = \Phi_{out}(s)/\Phi_{in}(s)$, of the CP-PLL shown below. The transfer function of the VCO is K_{VCO}/s and the transfer function of the PFD/CP is $I_0/(2\pi)$ (I_0 is the charge pump current). (4 p)



6.

Please answer the following power amplifier questions and with (short) motivations for your answers.

- Best class for linearity? AB or B? (0.5 p)
- Best class for linearity? AB or D (inverter-based class-D)? (0.5 p)
- Best class for efficiency? AB or C? (0.5 p)
- Best class for lowest voltage peaks? AB or E? (0.5 p)

Please give short motivations for your answers.
