

3.17. Sketch  $V_{out}$  versus  $V_{in}$  for the circuits of Fig. 3.69 as  $V_{in}$  varies from 0 to  $V_{DD}$ . Identify important transition points.

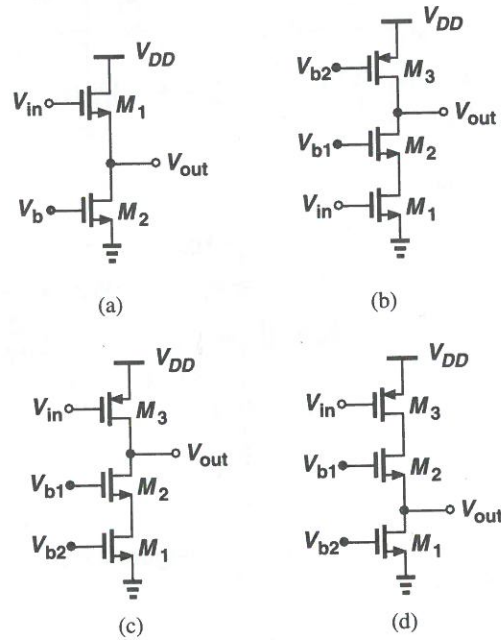


Figure 3.69

3.18. Sketch  $I_X$  versus  $V_X$  for the circuits of Fig. 3.70 as  $V_X$  varies from 0 to  $V_{DD}$ . Identify important transition points.

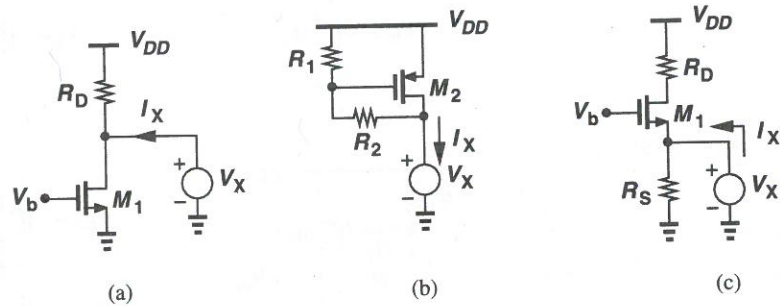


Figure 3.70

3.19. Sketch  $I_X$  versus  $V_X$  for the circuits of Fig. 3.71 as  $V_X$  varies from 0 to  $V_{DD}$ . Identify important transition points.

3.20. Assuming all MOSFETs are in saturation, calculate the small-signal voltage gain of each circuit in Fig. 3.72 ( $\lambda \neq 0, \gamma = 0$ ).

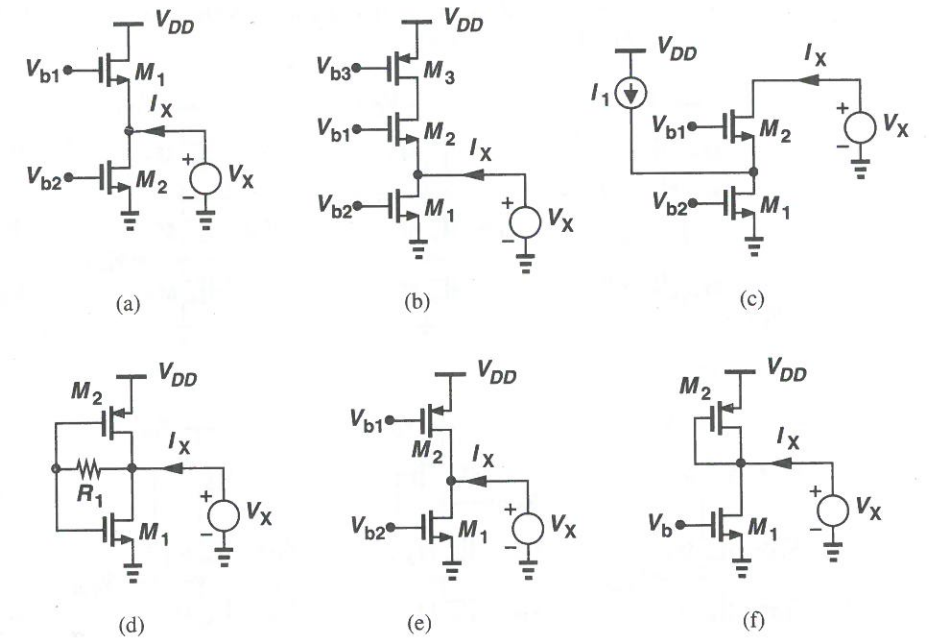


Figure 3.71

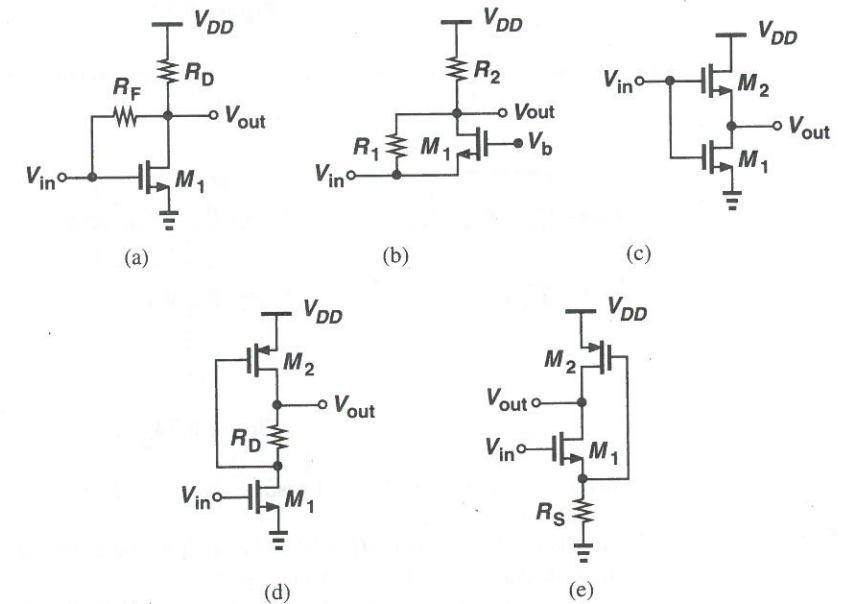


Figure 3.72

3.21. Assuming all MOSFETs are in saturation, calculate the small-signal voltage gain of each circuit in Fig. 3.73 ( $\lambda \neq 0, \gamma = 0$ ).

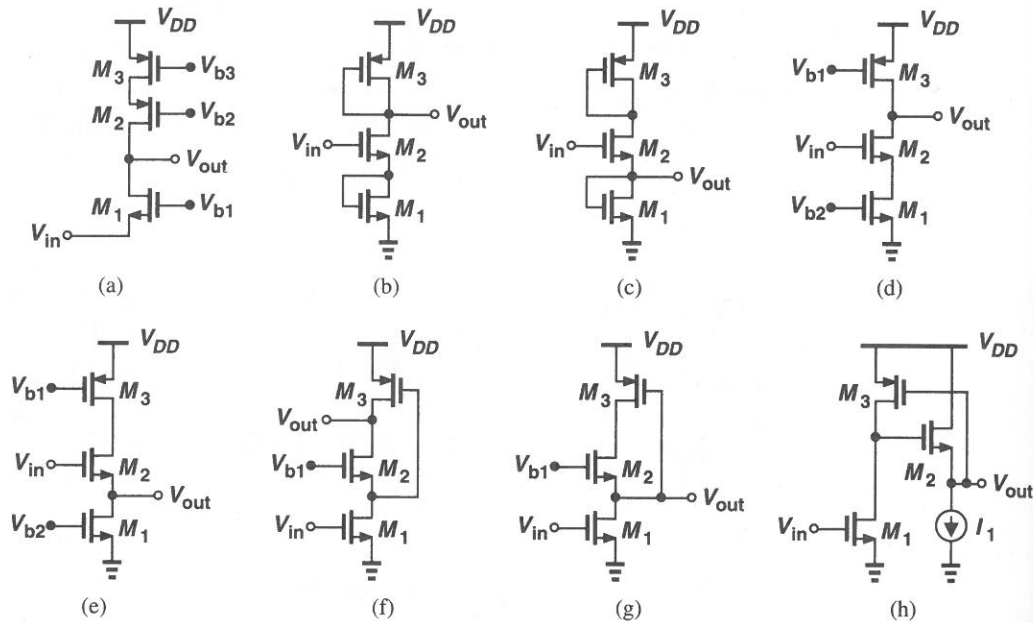


Figure 3.73

3.22. Sketch  $V_X$  and  $V_Y$  as a function of time for each circuit in Fig. 3.74. The initial voltage across  $C_1$  is equal to  $V_{DD}$ .

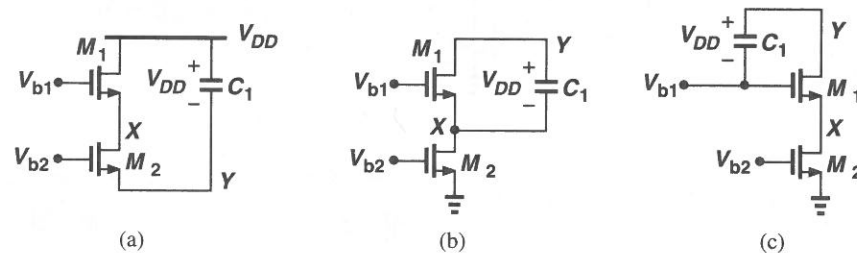


Figure 3.74

3.23. In the cascode stage of Fig. 3.50, assume  $(W/L)_1 = 50/0.5$ ,  $(W/L)_2 = 10/0.5$ ,  $I_{D1} = I_{D2} = 0.5$  mA, and  $R_D = 1$  k $\Omega$ .  
 (a) Choose  $V_b$  such that  $M_1$  is 50 mV away from the triode region.  
 (b) Calculate the small-signal voltage gain.  
 (c) Using the value of  $V_b$  found in part (a), calculate the maximum output voltage swing. Which device enters the triode region first as  $V_{out}$  falls?  
 (d) Calculate the swing at node X for the maximum output swing obtained above.

3.24. Consider the circuit of Fig. 3.16 with  $(W/L)_1 = 50/0.5$ ,  $R_D = 2$  k $\Omega$ , and  $R_S = 200$   $\Omega$ .  
 (a) Calculate the small-signal voltage gain if  $I_D = 0.5$  mA.  
 (b) Assuming  $\lambda = \gamma = 0$ , calculate the input voltage that places  $M_1$  at the edge of the triode region. What is the gain under this condition?

3.25. Suppose the circuit of Fig. 3.15 is designed for a voltage gain of 5. If  $(W/L)_1 = 20/0.5$ ,  $I_{D1} = 0.5$  mA, and  $V_b = 0$  V.  
 (a) Calculate the aspect ratio of  $M_2$ .  
 (b) What input level places  $M_1$  at the edge of the triode region. What is the small-signal gain under this condition?  
 (c) What input level places  $M_2$  at the edge of the saturation region? What is the small-signal gain under this condition?

3.26. Sketch the small-signal voltage gain of the circuit shown in Fig. 3.15 as  $V_b$  varies from 0 to  $V_{DD}$ . Consider two cases: (a)  $M_1$  enters the triode region before  $M_2$  is saturated; (b)  $M_1$  enters the triode region after  $M_2$  is saturated.

3.27. A source follower can operate as a level shifter. Suppose the circuit of Fig. 3.30(b) is designed to shift the voltage level by 1 V, i.e.,  $V_{in} - V_{out} = 1$  V.  
 (a) Calculate the dimensions of  $M_1$  and  $M_2$  if  $I_{D1} = I_{D2} = 0.5$  mA,  $V_{GS2} - V_{GS1} = 0.5$  V, and  $\lambda = \gamma = 0$ .  
 (b) Repeat part (a) if  $\gamma = 0.45$  V $^{-1}$  and  $V_{in} = 2.5$  V. What is the minimum input voltage for which  $M_2$  remains saturated?

3.28. Sketch the small-signal gain,  $V_{out}/V_{in}$ , of the cascode stage shown in Fig. 3.50 as  $V_b$  goes from 0 to  $V_{DD}$ . Assume  $\lambda = \gamma = 0$ .

3.29. The cascode of Fig. 3.60 is designed to provide an output swing of 1.9 V with a bias current of 0.5 mA. If  $\gamma = 0$  and  $(W/L)_{1-4} = W/L$ , calculate  $V_{b1}$ ,  $V_{b2}$ , and  $W/L$ . What is the voltage gain if  $L = 0.5$   $\mu$ m?