

Exercises for Tutorial 1: Single Ended Amplifiers

1. Problem 3.20 in the course book

a) KCL at v_{out} :

$$\frac{v_{out} - v_{in}}{R_F} + g_{m1}v_{gs1} + \frac{v_{out}}{r_{o1} \parallel R_D} = 0 \Rightarrow v_{gs1} = v_{in} / \Rightarrow$$

$$v_{out} \left(\frac{1}{R_F} + \frac{1}{r_{o1} \parallel R_D} \right) = -v_{in} \left(g_{m1} - \frac{1}{R_F} \right) \Rightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = - \frac{g_{m1} - \frac{1}{R_F}}{\frac{1}{R_F} + \frac{1}{r_{o1} \parallel R_D}}$$

b) KCL at v_{out} :

$$g_{m1}v_{gs1} + \frac{v_{out} - v_{in}}{r_{o1} \parallel R_1} + \frac{v_{out}}{R_2} = 0 \Rightarrow v_{gs1} = -v_{in} / \Rightarrow$$

$$v_{out} \left(\frac{1}{r_{o1} \parallel R_1} + \frac{1}{R_2} \right) = v_{in} \left(g_{m1} + \frac{1}{r_{o1} \parallel R_1} \right) \Rightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = \frac{g_{m1} + \frac{1}{r_{o1} \parallel R_1}}{\frac{1}{r_{o1} \parallel R_1} + \frac{1}{R_2}}$$

c) KCL at v_{out} :

$$g_{m1}v_{gs1} - g_{m2}v_{gs2} + \frac{v_{out}}{r_{o1} \parallel r_{o2}} = 0 \Rightarrow v_{gs1} = v_{in} \quad v_{gs2} = v_{in} - v_{out} / \Rightarrow$$

$$v_{out} \left(\frac{1}{r_{o1} \parallel r_{o2}} + g_{m2} \right) = -v_{in} (g_{m1} - g_{m2}) \Rightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = - \frac{g_{m1} - g_{m2}}{g_{m2} + \frac{1}{r_{o1} \parallel r_{o2}}}$$

d) KCL at v_x and v_{out} .

$$v_x: g_{m1}v_{in} + \frac{v_x}{r_{o1}} + \frac{v_x - v_{out}}{R_D} = 0 \Leftrightarrow v_x \left(\frac{1}{r_{o1}} + \frac{1}{R_D} \right) = -g_{m1}v_{in} + \frac{v_{out}}{R_D} \quad (1)$$

$$v_{out}: \frac{v_{out} - v_x}{R_D} + g_{m2}v_x + \frac{v_{out}}{r_{o2}} = 0 \Leftrightarrow v_{out} \left(\frac{1}{R_D} + \frac{1}{r_{o2}} \right) = v_x \left(-g_{m2} + \frac{1}{R_D} \right) \quad (2)$$

Insert (1) into (2):

$$v_{out} \left(\frac{1}{R_D} + \frac{1}{r_{o2}} \right) \left(\frac{1}{r_{o1}} + \frac{1}{R_D} \right) = \left(-g_{m1}v_{in} + \frac{v_{out}}{R_D} \right) \left(-g_{m2} + \frac{1}{R_D} \right) =$$

$$g_{m1}g_{m2}v_{in} - \frac{g_{m1}}{R_D}v_{in} - \frac{g_{m2}}{R_D}v_{out} + \frac{v_{out}}{R_D^2} \Leftrightarrow$$

$$v_{out} \left(\frac{1}{R_D r_{o1}} + \frac{1}{R_D^2} + \frac{1}{r_{o2} r_{o1}} + \frac{1}{r_{o2} R_D} - \frac{1}{R_D^2} + \frac{g_{m2}}{R_D} \right) = v_{in} \left(g_{m1}g_{m2} - \frac{g_{m1}}{R_D} \right) \Leftrightarrow$$

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{R_D}{r_{o1} r_{o2}} + \frac{1}{r_{o2}} + g_{m2} \right) = v_{in} (g_{m1}g_{m2}R_D - g_{m1}) \Leftrightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = \frac{g_{m1}(g_{m2}R_D - 1)}{\frac{1}{r_{o1}} + g_{m2} + \frac{1}{r_{o2}} \left(1 + \frac{R_D}{r_{o1}} \right)}$$

e) KCL at v_x and v_{out} .

$$(v_x): \frac{v_x}{R_S} - g_{m1}(v_{in} - v_x) + \frac{v_x - v_{out}}{r_{o1}} = 0 \Leftrightarrow v_x \left(g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \right) = g_{m1}v_{in} + \frac{v_{out}}{r_{o1}} \quad (1)$$

$$(v_{out}): g_{m1}(v_{in} - v_x) + g_{m2}v_x + \frac{v_{out} - v_x}{r_{o1}} + \frac{v_{out}}{r_{o2}} = 0 \Leftrightarrow$$

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) = v_x \left(g_{m1} - g_{m2} + \frac{1}{r_{o1}} \right) - g_{m1}v_{in} \quad (2)$$

Insert (1) into (2):

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) = \frac{\left(g_{m1}v_{in} + \frac{v_{out}}{r_{o1}} \right) \left(g_{m1} - g_{m2} + \frac{1}{r_{o1}} \right)}{g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}}} - g_{m1}v_{in} \Leftrightarrow$$

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) \left(g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \right) = \left(g_{m1}v_{in} + \frac{v_{out}}{r_{o1}} \right) \left(g_{m1} - g_{m2} + \frac{1}{r_{o1}} \right) - g_{m1}v_{in} \left(g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \right) \Leftrightarrow$$

$$v_{out} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o2}} \right) \left(g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \right) = -v_{in}g_{m1} \left(g_{m2} + \frac{1}{R_S} \right) + \frac{v_{out}}{r_{o1}} \left(g_{m1} - g_{m2} + \frac{1}{r_{o1}} \right) \Leftrightarrow$$

$$v_{out} \left(\frac{g_{m1}}{r_{o1}} + \frac{1}{r_{o1}R_S} + \frac{1}{r_{o1}^2} + \frac{g_{m1}}{r_{o2}} + \frac{1}{r_{o2}R_S} + \frac{1}{r_{o1}r_{o2}} - \frac{g_{m1}}{r_{o1}} + \frac{g_{m2}}{r_{o1}} - \frac{1}{r_{o1}^2} \right) = -v_{in}g_{m1} \left(g_{m2} + \frac{1}{R_S} \right) \Leftrightarrow$$

$$v_{out} \left(g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \left(1 + r_{o2} \left(g_{m2} + \frac{1}{R_S} \right) \right) \right) = -v_{in}g_{m1} \left(g_{m2} + \frac{1}{R_S} \right) r_{o2} \Leftrightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = - \frac{g_{m1} \left(g_{m2} + \frac{1}{R_S} \right) r_{o2}}{g_{m1} + \frac{1}{R_S} + \frac{1}{r_{o1}} \left(1 + r_{o2} \left(g_{m2} + \frac{1}{R_S} \right) \right)}$$

2. Problem 3.21(h) in the course book

KCL at v_x and v_{out} :

$$(v_x): g_{m1}v_{in} + g_{m3}v_{out} + \frac{v_x}{r_{o1}} + \frac{v_x}{r_{o3}} = 0 \Leftrightarrow v_x = -(g_{m1}v_{in} + g_{m3}v_{out})r_{o1} \parallel r_{o3} \quad (1)$$

$$(v_{out}): -g_{m2}(v_x - v_{out}) + \frac{v_{out}}{r_{o2}} = 0 \Leftrightarrow v_{out} \left(g_{m2} + \frac{1}{r_{o2}} \right) = g_{m2}v_x \quad (2)$$

$$(1) \text{ in } (2): v_{out} \left(g_{m2} + \frac{1}{r_{o2}} \right) = -g_{m1}g_{m2}(r_{o1} \parallel r_{o3})v_{in} - g_{m2}g_{m3}(r_{o1} \parallel r_{o3})v_{out} \Leftrightarrow$$

$$v_{out} \left(g_{m2} \left(1 + \frac{g_{m3}}{\frac{1}{r_{o1}} + \frac{1}{r_{o3}}} \right) + \frac{1}{r_{o2}} \right) = -v_{in} \frac{g_{m1}g_{m2}}{\frac{1}{r_{o1}} + \frac{1}{r_{o3}}} \Leftrightarrow$$

$$v_{out} \left(g_{m2} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}} + g_{m3} \right) + \frac{1}{r_{o1}r_{o2}} + \frac{1}{r_{o2}r_{o3}} \right) = -v_{in}g_{m1}g_{m2} \Leftrightarrow$$

$$\begin{aligned} A_V = \frac{v_{out}}{v_{in}} &= - \frac{g_{m1}g_{m2}}{g_{m2} \left(\frac{1}{r_{o1}} + \frac{1}{r_{o3}} + g_{m3} \right) + \frac{1}{r_{o1}r_{o2}} + \frac{1}{r_{o2}r_{o3}}} \\ &= - \frac{g_{m1}g_{m2}r_{o1}r_{o2}r_{o3}}{g_{m2}g_{m3}r_{o1}r_{o2}r_{o3} + g_{m2}r_{o2}r_{o3} + g_{m2}r_{o1}r_{o2} + r_{o3} + r_{o11}} \\ &= - \frac{g_{m1}g_{m2}r_{o1}r_{o2}r_{o3}}{(r_{o1} + r_{o3})(1 + g_{m2}r_{o2}) + g_{m2}g_{m3}r_{o1}r_{o2}r_{o3}} \end{aligned}$$

3. Problem 3.27 in the course book. Assume $\mu_n C_{ox} = 200 \mu A/V^2$, $V_{t0,n} = 0.5 V$, $|2\Phi_f| = 0.9 V$ and $V_{DD} = 3 V$. Also assume that in part (a) both transistors are in saturation region.

a) $\lambda = \gamma = 0$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{GS1} - V_{t0,n})^2 = 0.5 \text{ mA} \Leftrightarrow \frac{W_1}{L_1} = \frac{2 \times 0.5 \text{ mA}}{\mu_n C_{ox} (V_{GS1} - V_{t0,n})^2}$$

$$\frac{W_2}{L_2} = \frac{2 \times 0.5 \text{ mA}}{\mu_n C_{ox} (V_{GS2} - V_{t0,n})^2}$$

$$V_{GS1} = V_{in} - V_{out} = 1 V \text{ and } V_{GS2} = V_{GS1} = 0.5 V \Rightarrow V_{GS2} = 1.5 V$$

$$\frac{W_1}{L_1} = \frac{2 \times 0.5 \times 10^{-3}}{200 \times 10^{-6} (1 - 0.5)^2} = 20$$

$$\frac{W_2}{L_2} = \frac{2 \times 0.5 \times 10^{-3}}{200 \times 10^{-6} (1.5 - 0.5)^2} = 5$$

b) $\gamma = 0.45 \text{ } 1/\sqrt{V}$ and $V_{in} = 2.5 V \Leftrightarrow M_1$ has body effect, $V_{SB1} = V_{out} = V_{in} - 1 V = 1.5 V$

$$\frac{W_1}{L_1} = \frac{2I_{D1}}{\mu_n C_{ox} (V_{GS1} - V_{t1})^2}, V_{t1} = V_{t0,n} + \gamma \left(\sqrt{|2\Phi_f + V_{SB1}|} - \sqrt{|2\Phi_f|} \right) = 0.77 V$$

$$\frac{W_2}{L_2} = \frac{2I_{D2}}{\mu_n C_{ox} (V_{GS2} - V_{t0,n})^2} = 5 \text{ (Same as in a)}$$

$$\frac{W_1}{L_1} = \frac{2 \times 0.5 \times 10^{-3}}{200 \times 10^{-6} (1 - 0.77)^2} = 94.5$$

M_2 is at the edge of saturation when $V_{out} = V_{GS2} - V_{t0,n} = 1.5 V - 0.5 V = 1 V$

M_2 keeps current 0.5 mA so:

$$\left\{ \begin{array}{l} V_{t1} = V_{t0,n} + \gamma \left(\sqrt{|2\Phi_f + V_{out}|} - \sqrt{|2\Phi_f|} \right) = 0.69 V \\ V_{in} = V_{out} + V_{GS1} = V_{out} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W_1}{L_1}}} + V_{t1} = 1 + 0.23 + 0.69 = 1.92 V \end{array} \right.$$

$$V_{in,min} = 1.92 V$$

4. A two-stage single-ended amplifier is shown in Figure 1. Calculate the small-signal voltage gain and the output resistance. Assume $g_m \gg 1/r_{o1}$ and $R_D \ll r_{o2}$. ($\lambda \neq 0$ and $\gamma = 0$).

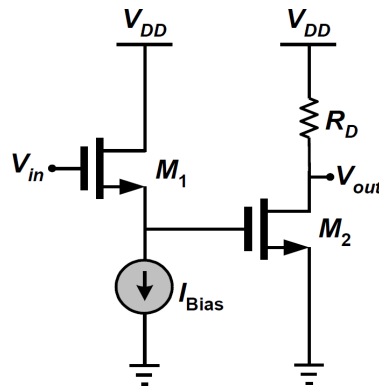


Figure 1 A two-stage amplifier

KCL at v_x and v_{out} :

$$(v_x): \frac{v_x}{r_{o1}} = g_{m1}(v_{in} - v_x) \Leftrightarrow v_x \left(g_{m1} + \frac{1}{r_{o1}} \right) = g_{m1} v_{in} \Leftrightarrow v_x = v_{in} \frac{g_{m1}}{g_{m1} + \frac{1}{r_{o1}}} \quad (1)$$

$$(v_{out}): g_{m2} v_x + \frac{v_{out}}{r_{o2}} + \frac{v_{out}}{R_D} = 0 \Leftrightarrow v_{out} \left(\frac{1}{r_{o2}} + \frac{1}{R_D} \right) = -v_x g_{m2} \quad (2)$$

(1) in (2):

$$v_{out} \left(\frac{1}{r_{o2}} + \frac{1}{R_D} \right) = -v_{in} \frac{g_{m1} g_{m2}}{g_{m1} + \frac{1}{r_{o1}}} \Leftrightarrow$$

$$A_V = \frac{v_{out}}{v_{in}} = - \frac{g_{m1} g_{m2}}{\left(g_{m1} + \frac{1}{r_{o1}} \right) \left(\frac{1}{r_{o2}} + \frac{1}{R_D} \right)} \approx -g_{m2} R_D$$

$$R_{out} = \frac{V_Z}{I_Z} = \frac{I_Z (r_{o2} \parallel R_D)}{I_Z} = r_{o2} \parallel R_D \approx R_D \quad (R_D \ll r_{o2})$$

5. Using the small-signal model, calculate the voltage gain of the cascode stage shown in Figure 2 For both transistors we assume $g_m \gg g_{mb}$ and $r_o \rightarrow \infty$.

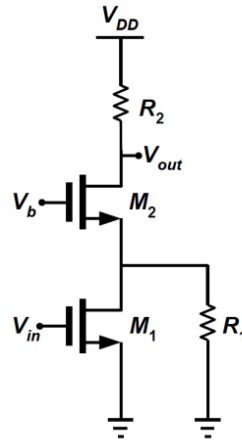


Figure 2 A cascode amplifier stage

$$g_{m1}v_{in} + g_{m2}v_x + \frac{v_x}{R_1} = 0 \Leftrightarrow v_x = -v_{in} \frac{g_{m1}}{g_{m2} + \frac{1}{R_1}} \quad (1)$$

$$-g_{m2}v_x + \frac{v_{out}}{R_2} = 0 \Leftrightarrow v_{out} = v_x g_{m2} R_2 \quad (2)$$

$$(1) \text{ and } (2): A_V = \frac{v_{out}}{v_{in}} = -\frac{g_{m1} g_{m2} R_2}{g_{m2} + \frac{1}{R_1}}$$