

## Exercises for Tutorial 5: Interconnect

1. Consider the circuit shown in Figure 11. A voltage source with a  $Z_s = 200 \Omega$  output impedance drives a transmission line with a characteristic impedance of  $Z_0 = 50 \Omega$  terminated in a load impedance of  $Z_L = 12.5 \Omega$ . The transmission line has a propagation delay of  $t_d = 2 \text{ ns}$ . For a unit step on the voltage source, how long does it take before the reflected wave on the line has an amplitude less than  $10 \text{ mV}$ ?

12 ns

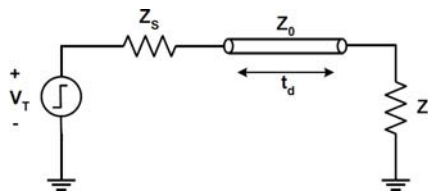


Figure 11 A voltage source driving a terminated transmission line.

2. If a lossless transmission line of characteristic impedance  $Z_0$  and length  $l$ , driven sinusoidally, is terminated in an arbitrary impedance  $Z_L$ , show that the impedance at the drive end is  $Z(l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$  where  $\beta = \omega\sqrt{LC}$ . The term  $\beta$  determines the rate at which the phase changes along the line and is equal to  $2\pi/\lambda$ , where  $\lambda$  is the wavelength of the excitation frequency.
3. In problem 2, what is the input impedance as a function of load impedance when the length of the line is  $\lambda/4$ . For this case what is the input impedance when the line is shorted? What is the input impedance when the line is open?

Short:  $Z\left(\frac{\lambda}{4}\right) = \frac{Z_0^2}{Z_L}$  → if shorted:  $Z\left(\frac{\lambda}{4}\right) = \infty$  and if open:  $Z\left(\frac{\lambda}{4}\right) = 0$

4. Estimate the delay of the wire with a high frequency  $Z_0 = 50 \Omega$ , resistance  $r = 14 \text{ k}\Omega / \text{m}$  and dielectric constant  $\epsilon_r = 4$ .
  - a) Length  $d = 1 \text{ mm}$ .

$t_d = 6.7 \text{ ps}$

- b) Length  $d = 25 \text{ mm}$ .

$t_d = 443 \text{ ps}$

5. An RC-wire with length of  $d$  is divided into  $N$  equal-length sections and between each section repeaters are inserted as shown in Figure 12. To get the optimal delay through the wire, what section length should be chosen? How many repeaters are needed? Assume that the propagation delay of each repeater is  $t_p$  and the wire resistance and wire capacitance per unit length is  $r$  and  $c$ , respectively.

$$\text{Optimal section length} = \sqrt{\frac{t_p}{0.38rc}}, \text{ and optimal number of repeaters} = d \sqrt{\frac{0.38rc}{t_p}}$$

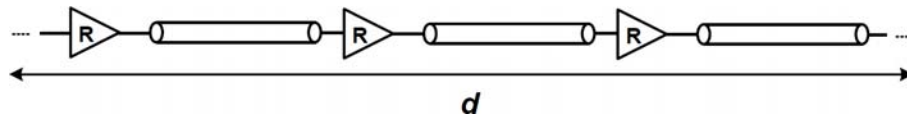


Figure 12 Inserting repeaters into an RC line.