

Exercises for Tutorial 6: Timing issues

1. Assume that an inverter stage can be approximated as a first-order circuit with a single pole at ω_0 and a stage gain of $-A$. Determine the open-loop transfer function of a 5-stage ring oscillator. Calculate the minimum required voltage gain per stage in order to have oscillation.

$$H(s) = -\frac{A^5}{\left(1 + \frac{s}{\omega_0}\right)^5}, A_{\min} = 1.23$$

2. A voltage-controlled oscillator with linear tuning characteristic has a gain of $2\pi \times 10^8 \frac{\text{rad}}{s} / V$. The control voltage varies between 0 and 3 V. When the control voltage is 0.5 V, the oscillation frequency is 1 GHz. Calculate the required control voltage to get 1.25 GHz oscillation frequency.

$$V_{\text{cont}} = 2.5 \text{ V}$$

3. Consider the PLL loop filter circuit shown in Figure 13. Determine the transfer function $G(s)$ of this filter. The op-amp is ideal.

$$G(s) = -\frac{1 + sR_1C}{sR_2C}$$

 


Figure 13 Loop filter circuit.

4. A block diagram of a PLL is shown in Figure 14. ϕ_{in} is the reference phase and ϕ_{out} is the output of the oscillator. The following relations can be identified:

$$V_1 = K_{PD}(\phi_{in} - \phi_{out})$$

$$\frac{d\phi_{out}}{dt} = K_{VCO}V_2$$

- a) Determine the closed-loop transfer function of the PLL from ϕ_{in} to ϕ_{out} . Use the loop filter transfer function $G(s)$ in problem 3.

$$H(s) = -\frac{K_{PD}K_{VCO}(1 + sR_1C)}{s^2R_2C - K_{PD}K_{VCO}(1 + sR_1C)}$$

- b) What are the necessary conditions on K_{PD} and K_{VCO} for stability?

$$K_{PD}K_{VCO} < 0$$

 


Figure 14 PLL block diagram.