

ANSWERS

-

TSEK37 ANALOG CMOS INTEGRATED CIRCUITS

Date: 2012-04-13
Time: 14-16
Location: TER2
Aids: Calculator, Dictionary
Teachers: Behzad Mesgarzadeh (5719)
Ali Fazli (2794)
Daniel Svärd (8946)

8 points are required to pass.

Please start each new problem at the top of a page!
Only use one side of each paper!

1)

(a) For M_1 to be in saturation we have:

$$V_{GS1} - V_{TH1} \leq V_{DS1} \Rightarrow V_{GS1} - V_{TH1} \leq V_b - V_{GS2}$$

For M_2 to be in saturation we have:

$$V_{GS2} - V_{TH2} \leq V_{DS2} \Rightarrow V_b - V_{TH2} \leq V_{GS1}$$

So combining these two expressions we get the following bounds on V_b :

$$V_{GS2} + (V_{GS1} - V_{TH1}) \leq V_b \leq V_{GS1} + V_{TH2}$$

A solution to this relation only exists if

$$V_{GS2} + (V_{GS1} - V_{TH1}) \leq V_{GS1} + V_{TH2} \Rightarrow V_{GS2} - V_{TH2} \leq V_{TH1}$$

This means that we must size M_2 such that its overdrive voltage is less than one threshold voltage.

(b) For M_4 to be in saturation we have:

$$V_{GS4} - V_{TH4} \leq V_{DS4} \Rightarrow V_b - V_{TH4} \leq V_P$$

So for the lowest V_P and the lowest V_b we have:


$$V_P = V_b - V_{TH4} = V_{GS2} + V_{GS1} - V_{TH1} - V_{TH4}$$

If $M_3 = M_1$ and $V_{GS4} = V_{GS2}$, then:

$$V_P = (V_{GS3} - V_{TH3}) + (V_{GS4} - V_{TH4})$$

So the minimum voltage headroom consumed by the current mirror is two overdrive voltages.

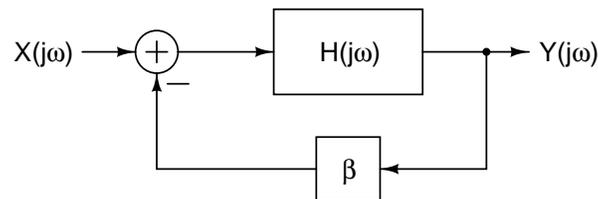2) The figure below shows a general feedback system.



The closed-loop transfer function of this system can be found to be

$$\frac{Y(j\omega)}{X(j\omega)} = \frac{H(j\omega)}{1 + \beta H(j\omega)}$$

From the problem description we have that $\beta=1/4$ and

$$H(j\omega) = \frac{A_0}{\left(1 + j\frac{\omega}{\omega_{p1}}\right)\left(1 + j\frac{\omega}{\omega_{p2}}\right)},$$

where $\omega_{p1} = 2\pi \times 1$ Mrad/s and $\omega_{p2} = 2\pi \times 450$ Mrad/s.

To find the phase margin we need to look at the loop transfer function $\beta H(j\omega)$. To make calculations easier we first rewrite the loop transfer function on complex exponential form:

$$\begin{aligned} \beta H(j\omega) &= \frac{\beta A_0}{\sqrt{1 + \left(\frac{\omega}{\omega_{p1}}\right)^2} \exp\left(j \arctan \frac{\omega}{\omega_{p1}}\right) \sqrt{1 + \left(\frac{\omega}{\omega_{p2}}\right)^2} \exp\left(j \arctan \frac{\omega}{\omega_{p2}}\right)} = \\ &= \frac{\beta A_0}{\sqrt{1 + \left(\frac{\omega}{\omega_{p1}}\right)^2} \sqrt{1 + \left(\frac{\omega}{\omega_{p2}}\right)^2}} \times \exp\left[-j \left(\arctan \frac{\omega}{\omega_{p1}} + \arctan \frac{\omega}{\omega_{p2}}\right)\right] \end{aligned}$$

We now look at the phase response to find the frequency (ω_u) at which the phase has shifted $60^\circ - 180^\circ = -120^\circ$. Here we use the identity from the hint.

$$\begin{aligned} -\arctan \frac{\omega_u}{\omega_{p1}} - \arctan \frac{\omega_u}{\omega_{p2}} = -120^\circ &\Leftrightarrow -\arctan \left(\frac{\omega_u(\omega_{p1} + \omega_{p2})}{\omega_{p1}\omega_{p2} - \omega_u^2}\right) = -120^\circ \\ &\Rightarrow \frac{\omega_u(\omega_{p1} + \omega_{p2})}{\omega_{p1}\omega_{p2} - \omega_u^2} = -\sqrt{3} \end{aligned}$$

Solving this equation for ω_u and plugging in the values for the poles gives:

$$\omega_u = \frac{(\omega_{p1} + \omega_{p2}) \pm \sqrt{(\omega_{p1} + \omega_{p2})^2 + 12\omega_{p1}\omega_{p2}}}{2\sqrt{3}} = \begin{cases} 1646834563 \text{ rad/s} \\ -10787536.48 \text{ rad/s} \end{cases}$$

Since the second solution is negative, we use the first solution for the frequency of -120 degrees phase shift. Now we can look at the magnitude of the loop transfer function to find the value of A_0 that yields a unity gain frequency of ω_u .

$$|\beta H(j\omega)| = \frac{\beta A_0}{\sqrt{1 + \left(\frac{\omega_u}{\omega_{p1}}\right)^2} \sqrt{1 + \left(\frac{\omega_u}{\omega_{p2}}\right)^2}} = 1$$


Solving this equation for A_0 and plugging in the values for β , ω_u , ω_{p1} and ω_{p2} gives:

$$A_0 = \frac{1}{\beta} \sqrt{1 + \left(\frac{\omega_u}{\omega_{p1}}\right)^2} \sqrt{1 + \left(\frac{\omega_u}{\omega_{p2}}\right)^2} \approx 1213$$

The DC gain of the amplifier must therefore be 1213 V/V or 61.7 dB.

3)

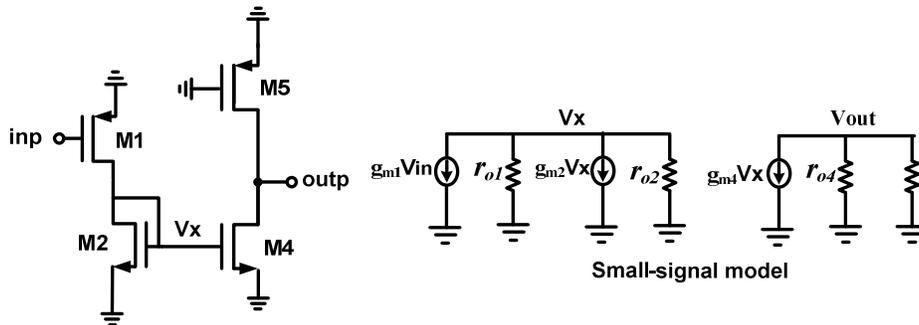(a) The half-circuit and corresponding small-signal model is shown below.



Writing two KCLs at nodes V_x and V_{out} and noting that $g_{ds} = r_o^{-1}$ we get:
 at node V_x :

$$g_{m1} V_{in} + (g_{ds1} + g_{m2} + g_{ds2}) V_x = 0 \Rightarrow \frac{V_x}{V_{in}} = \frac{-g_{m1}}{g_{ds1} + g_{ds2} + g_{m2}} \quad (1)$$


at node V_{out} :

$$g_{m4} V_x + (g_{ds4} + g_{ds5}) V_{out} = 0 \quad (2)$$

Combining (1) and (2) we obtain

$$\Rightarrow \text{DCgain} = \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{ds1} + g_{ds2} + g_{m2}} \cdot \frac{g_{m4}}{g_{ds4} + g_{ds5}} \quad (3)$$

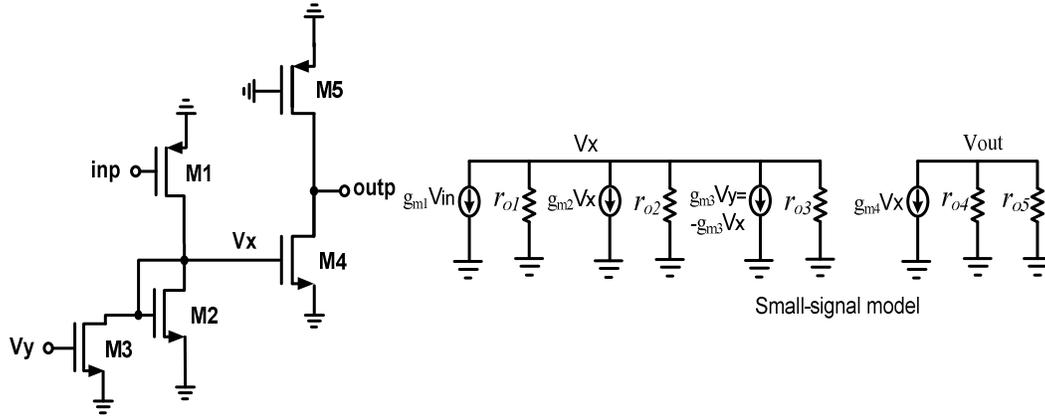(b) The half-circuit and corresponding small-signal model is shown below.



Due to transistor M_3 , two more terms appers in equation (1) as given

$$g_{m1} V_{in} + (g_{ds1} + g_{m2} + g_{ds2} + g_{ds3} - g_{m3}) V_x = 0 \Rightarrow$$

$$\frac{V_x}{V_{in}} = \frac{-g_{m1}}{g_{ds1} + g_{ds2} + g_{m2} + g_{ds3} - g_{m3}} \quad (4)$$

at node V_{out} : similar to part (b)

$$g_{m4} V_x + (g_{ds4} + g_{ds5}) V_{out} = 0 \quad (5)$$

Combining (4) and (5) we obtain

$$\Rightarrow \text{DCgain} = \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{g_{ds1} + g_{ds2} + g_{m2} + g_{ds3} - g_{m3}} \cdot \frac{g_{m4}}{g_{ds4} + g_{ds5}} \quad (6)$$

As can be seen from (6), the transistor M_3 can be sized such that the transconductance g_{m3} to be 70-80% of the term $g_{ds1} + g_{ds2} + g_{m2} + g_{ds3}$. This method enhances the DC gain.

(c) The dominate pole due to load capacitance C_L :

$$P_1 = \frac{1}{2\pi \cdot (r_{o4} // r_{o5}) \cdot C_L} \quad (7)$$

The 2nd pole due to parasitic capacitance C_C at the gate of M_2 , M_3 , and M_4 , mainly because of the gate-source capacitance of the devices.

$$P_2 = \frac{1}{2\pi \cdot (1/g_{m2}) \cdot C_C} = \frac{g_{m2}}{2\pi \cdot C_C} \quad (8)$$

4)

From A:


$$\Gamma_{r,A} = \frac{Z_1 // Z_2 - Z_0}{Z_1 // Z_2 + Z_0} = -1/3, \quad T_A = 1 + \frac{Z_1 // Z_2 - Z_0}{Z_1 // Z_2 + Z_0} = +2/3$$


From B:

$$\Gamma_{r,B} = \frac{Z_0 // Z_2 - Z_1}{Z_0 // Z_2 + Z_1} = -2/3, \quad T_B = 1 + \frac{Z_0 // Z_2 - Z_1}{Z_0 // Z_2 + Z_1} = +1/3$$

From C:

$$\Gamma_{r,C} = \frac{Z_0 // Z_1 - Z_2}{Z_0 // Z_1 + Z_2} = 0, \quad T_C = 1 + \frac{Z_0 // Z_1 - Z_2}{Z_0 // Z_1 + Z_2} = 1$$

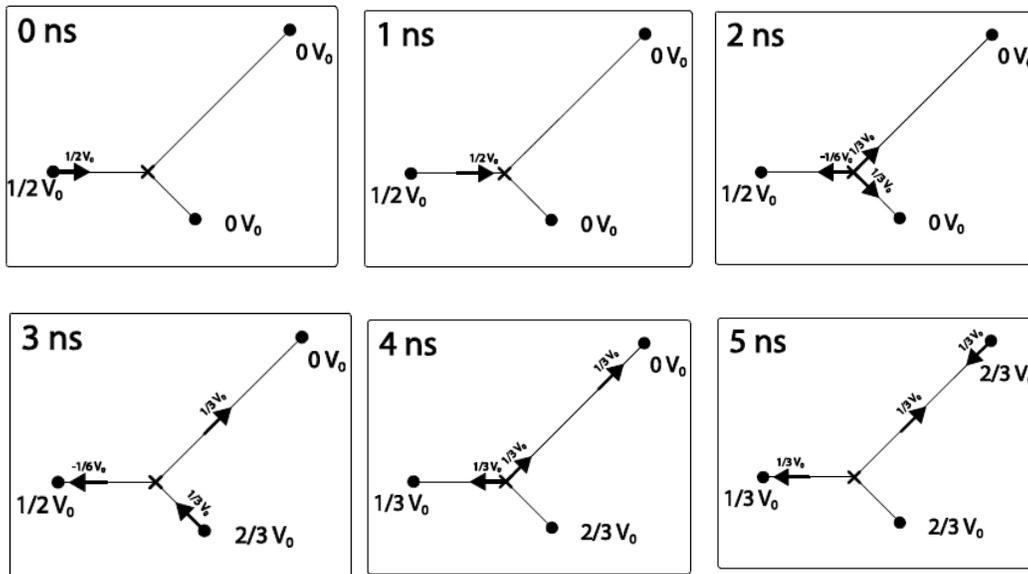

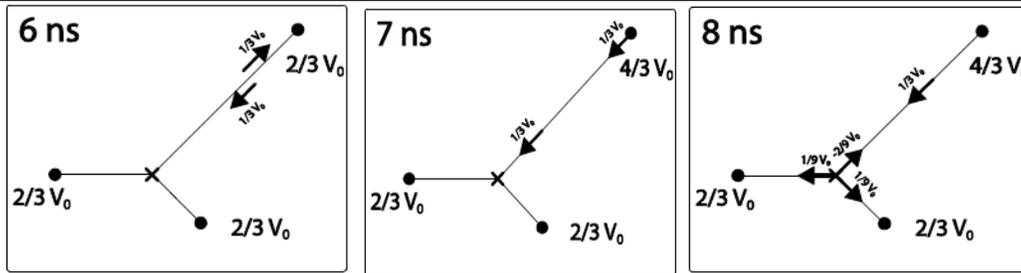

at 7.5ns: $V_A = 2/3V_0$, $V_B = 4/3V_0$ and $V_C = 2/3V_0$

5)

See example 14.17 in the text book and also lecture notes. Spectrum consists of a carrier tone at ω_0 and two tones at $\omega_0 - \omega_m$ and $\omega_0 + \omega_m$.

6)

The PLL experiences a frequency step of 0.5 MHz and the final value of the PLL output frequency change should be within 100 Hz from 0.5 MHz. For the worst-case, we can put the sine function equal to 1. Then:

$$\omega_{out}(t) = \left\{ 1 - \frac{1}{\sqrt{1-\zeta^2}} \cdot e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} t + \theta) \right\} \Delta\omega u(t)$$

$$\frac{1}{\sqrt{1-\zeta^2}} \approx 1 \Rightarrow$$

$$0.5 \times 10^6 - 100 = (1 - e^{-\zeta\omega_n t_s}) \times 0.5 \times 10^6 \Rightarrow e^{-\zeta\omega_n t_s} = \frac{100}{0.5 \times 10^6}$$

$$e^{-\zeta\omega_n t_s} = 2 \times 10^{-4} \Rightarrow \zeta\omega_n t_s = 8.5 \Rightarrow t_s = \frac{17}{\omega_{LPF}} = 94.6 \mu s$$