

**ANSWERS**  
-  
**TSEK37 ANALOG CMOS INTEGRATED  
CIRCUITS**

Date: 2014-01-18  
Time: 8-12  
Location: U1  
Aids: Calculator, Dictionary  
Teachers: Behzad Mesgarzadeh (5719)  
Daniel Svård (8946)

8 points are required to pass.

**Please start each new problem at the top of a page!  
Only use one side of each paper!**

---

1)

(a)

At time  $t_1$ , transistors M1, M5 and M9 have the same bias point. The drain-source voltage drop is therefore equal for all three transistors. The source-gate voltage for transistor M2, M6 and M10 are therefore identical. With ( $\lambda = \gamma = 0$ ), the current through the transistors M2, M6 and M10 will therefore be identical.  $I_D$  for M10 =  $I_{ref} \Rightarrow I_D$  for M2 =  $I_D$  for M5 =  $I_{ref}$ . In a similar manner, transistor M4 and M8 will have identical bias points at time  $t_2$ , resulting in identical gate-source voltages for transistor M3 and M7 giving that  $I_D$  for M3 =  $I_D$  for M7 =  $I_D$  for M6 =  $I_{ref}$ .

So  $I_{out}$  at time  $t_1 = -I_{ref} = -10 \mu A$  and  $I_{out}$  for time  $t_2 = I_{ref} = 10 \mu A$ .

(b)

When the down signal is high, transistor M1 will be in the linear region. From (a) we know that the current  $I_D$  will be  $10 \mu A$ .

Transistor equation for a NMOS transistor in the linear region:

$$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \Rightarrow V_{DS} = (V_{GS} - V_{TN}) \pm \sqrt{(V_{GS} - V_{TN})^2 - \frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$V_{DS} = \begin{cases} 0.83mV \\ (5.799V) \end{cases}$$

Transistor M10 is always in saturation.  $V_{GS}$  is then given from:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \Rightarrow V_{GS} = \sqrt{\frac{I_D}{(1 + \lambda V_{DS}) \mu_n C_{ox} \frac{W}{L}}} + V_{TN} \Rightarrow V_{GS} = 0.4683V$$

which is also the  $V_{GS}$  for transistor M2.

Transistor M2 is in saturation as long as ( $V_{GS} > V_{TN}$ ) and ( $V_{DS} > V_{GS} - V_{TN}$ )

$$V_{DS} = V_{GS} - V_{TN} = 0.4683V - 0.4V = 68.3mV$$

The minimum output voltage is then  $V_{DSM1} + V_{DSM2} = 0.83mV + 68.3mV = 69.1mV$

The same calculation as for transistor M1 gives for transistor M4:

$$I_D = \mu_p C_{ox} \frac{W}{L} \left( (V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right) \Rightarrow V_{SD} = (V_{SG} - |V_{TP}|) \pm \sqrt{(V_{SG} - |V_{TP}|)^2 - \frac{2I_D}{\mu_p C_{ox} \frac{W}{L}}} \Rightarrow$$

$$\Rightarrow V_{SD} = \begin{cases} 1.697mV \\ (5.498V) \end{cases}$$

The same calculation as for transistor M10 gives for M7

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD}) \Rightarrow V_{SG} = \sqrt{\frac{I_D}{(1 + \lambda V_{SD})} \frac{2}{\mu_p C_{ox} \frac{W}{L}}} + |V_{TP}| \Rightarrow$$

$V_{SG} = 0.6466V$  which is also the  $V_{SG}$  for transistor M3.

Transistor M3 is in saturation as long as  $(V_{GS} > |V_{TP}|)$  and  $(V_{SD} < V_{SG} - |V_{TP}|)$

$$V_{SD} = V_{SG} - |V_{TP}| = 0.6466V - 0.55V = 96.6mV$$

The maximum output voltage is then  $V_{dd} - V_{SDM4} - V_{DSM3} = 3.3 - 1.697mV - 96.6mV = 3.202V$

The output range of the charge pump is thus  $69.1mV < V_{out} < 3.202V$ .

2)

Start by deriving an expression for each output voltage,  $V_{out1}$  and  $V_{out2}$ , as a function of the input voltages  $V_{in1}$  and  $V_{in2}$ .

$$V_{out1} = -g_{m1} R_D (V_{in1} - V_P)$$

$$V_{out2} = -g_{m2} R_D (V_{in2} - V_P)$$

The voltage at node P is equal to the voltage drop over  $R_{SS}$  generated by the total drain current of the two transistors.

$$V_P = (I_{D1} + I_{D2}) R_{SS} = g_{m1} (V_{in1} - V_P) R_{SS} + g_{m2} (V_{in2} - V_P) R_{SS} \Rightarrow$$


$$V_P = \frac{g_{m1} V_{in1} + g_{m2} V_{in2}}{(g_{m1} + g_{m2}) R_{SS} + 1} R_{SS}$$

The voltages at outputs,  $V_{out1}$  and  $V_{out2}$ , can then be found by substituting  $V_P$  for the expression above and simplifying:

$$V_{out1} = -g_{m1} R_D (V_{in1} - V_P) = -\frac{g_{m1} R_D}{(g_{m1} + g_{m2}) R_{SS} + 1} (V_{in1} + (V_{in1} - V_{in2}) g_{m2} R_{SS})$$

$$V_{out2} = -g_{m2} R_D (V_{in2} - V_P) = -\frac{g_{m2} R_D}{(g_{m1} + g_{m2}) R_{SS} + 1} (V_{in2} + (V_{in2} - V_{in1}) g_{m1} R_{SS})$$

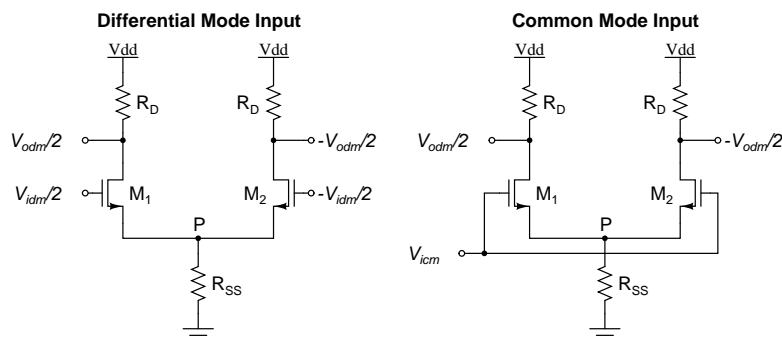Now we need to find the gain for the two different input configurations shown below:



**Differential mode:**  $A_{DM-DM} = \frac{V_{odm}}{V_{idm}} = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}}$

We insert  $V_{in1} = V_{idm}/2$  and  $V_{in2} = -V_{idm}/2$  into the expressions for  $V_{out1}$  and  $V_{out2}$  above to get:

$$V_{out1} = \frac{V_{odm}}{2} = -\frac{g_{m1}R_D}{(g_{m1} + g_{m2})R_{SS} + 1} (1 + 2g_{m2}R_{SS}) \frac{V_{idm}}{2}$$

$$V_{out2} = -\frac{V_{odm}}{2} = \frac{g_{m2}R_D}{(g_{m1} + g_{m2})R_{SS} + 1} (1 + 2g_{m1}R_{SS}) \frac{V_{idm}}{2}$$

Now we find the differential gain as:

$$A_{DM-DM} = \frac{V_{out1} - V_{out2}}{V_{idm}} = -\frac{R_D}{2} \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{(g_{m1} + g_{m2})R_{SS} + 1}$$

**Common mode:**  $A_{CM-DM} = \frac{V_{odm}}{V_{icm}} = \frac{V_{out1} - V_{out2}}{V_{icm}}$

We insert  $V_{in1} = V_{in2} = V_{icm}$  into the expressions for  $V_{out1}$  and  $V_{out2}$  above to get:

$$V_{out1} = -\frac{g_{m1}R_D}{(g_{m1} + g_{m2})R_{SS} + 1} V_{icm}$$

$$V_{out2} = -\frac{g_{m2}R_D}{(g_{m1} + g_{m2})R_{SS} + 1} V_{icm}$$

Now we find the common-mode gain as:


$$A_{CM-DM} = \frac{V_{out1} - V_{out2}}{V_{icm}} = -\frac{(g_{m1} - g_{m2})R_D}{(g_{m1} + g_{m2})R_{SS} + 1} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$

So the common-mode rejection ratio is:

$$CMRR = \left| \frac{A_{DM-DM}}{A_{CM-DM}} \right| = \frac{g_{m1} + g_{m2} + 4g_{m1}g_{m2}R_{SS}}{2\Delta g_m}$$

3)

(a) Small-signal model:

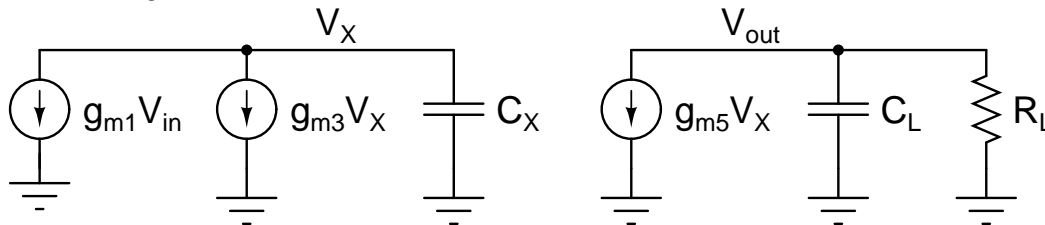

Write the nodal equations for the circuit:

KCL @  $V_X$ :  $g_{m1}V_{in} + g_{m3}V_X + sC_X V_X = 0 \Rightarrow V_X = -\frac{g_{m1}}{g_{m3} + sC_X} V_{in}$

$$\text{KCL @ } V_{out}: \quad g_{m5}V_X + sC_L V_{out} + \frac{V_{out}}{R_L} = 0 \Rightarrow V_{out} = -\frac{g_{m5}R_L}{1 + sC_L R_L} V_X$$

The transfer function is then found to be:

$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{g_{m1}g_{m5}R_L}{g_{m3}} \cdot \frac{1}{1 + sC_L R_L} \cdot \frac{1}{1 + s\frac{C_X}{g_{m3}}}$$

(b) We rewrite the transfer function in terms of the DC gain,  $A_0$ , and the two poles  $\omega_{p1}$  and  $\omega_{p2}$ .

$$H(s) = A_0 \cdot \frac{1}{1 + \frac{s}{\omega_{p1}}} \cdot \frac{1}{1 + \frac{s}{\omega_{p2}}}$$

$$\text{where } A_0 = \frac{g_{m1}g_{m5}R_L}{g_{m3}} = 6000g_{m1} \quad \omega_{p1} = \frac{1}{C_L R_L} = \frac{2}{30} \text{ Grad/s} \quad \omega_{p2} = \frac{g_{m3}}{C_X} = 3.28 \text{ Grad/s}$$

The unity gain frequency,  $\omega_u = 2 \text{ Grad/s}$ , occurs when  $|H(j\omega_u)| = 1$ .

$$|H(j\omega_u)| = A_0 \cdot \frac{1}{\sqrt{1 + \left(\frac{\omega_u}{\omega_{p1}}\right)^2}} \cdot \frac{1}{\sqrt{1 + \left(\frac{\omega_u}{\omega_{p2}}\right)^2}} = 1$$

$$\Rightarrow A_0 = \sqrt{1 + \left(\frac{2 \times 30}{2}\right)^2} \cdot \sqrt{1 + \left(\frac{2}{3.28}\right)^2} \approx 35.1 \Rightarrow g_{m1} = 5.85 \text{ mS}$$

The phase margin is defined as  $PM = 180^\circ + \angle\beta H(j\omega_u) = 180^\circ + \angle H(j\omega_u)$  if  $\beta=1$ .

$$\angle H(j\omega_u) = -\arctan\left(\frac{\omega_u}{\omega_{p1}}\right) - \arctan\left(\frac{\omega_u}{\omega_{p2}}\right) = -\arctan\left(\frac{2 \times 30}{2}\right) - \arctan\left(\frac{2}{3.28}\right) \approx -119.5^\circ$$

So the phase margin is

$$PM = 180^\circ - 119.5^\circ = 60.5^\circ$$

4)

$$\text{The total delay } D = mt_p + m \left[ 0.38 \left(\frac{d}{m}\right)^2 rc \right] = mt_p + 0.38 \frac{d^2}{m} rc$$

$$\text{For optimum delay we should have } \frac{dD}{dm} = t_p - 0.38 \frac{d^2}{m^2} rc = 0$$

$$m_{opt} = \sqrt{\frac{0.38rcd^2}{t_p}}$$

Replacing the values for  $rc$ ,  $d$  and  $t_p$  results in:

$$m_{opt} = \sqrt{\frac{0.38 \times 960 \times 10^{-6} (2 \times 10^{-3})^2}{50 \times 10^{-12}}} = 5.4$$

Since the line is non-inverting then we choose  $m = 6$ .

5)

a) Initially we assume that  $V_{out}=0$  and there is no charge on C.  $M_3$  is off and  $M_2$  is on and  $M_1$  charges the capacitor. Then  $V_{DS1}=3$  and  $V_{GS1}-|V_t|=1.5$  and  $M_1$  is in saturation:

$$I_1 = \frac{1}{2} \times 50 \times 40 \times 10^{-6} \times (2 - 0.5)^2 = 2.25 \text{ mA}$$

$M_1$  will be in saturation region until  $V_{DS1}=V_{GS1}-|V_t|=1.5$  V or the voltage on capacitor is 1.5 V which is the switching threshold for the coming stage. To get this point:

$$\Delta t = \frac{C \cdot \Delta V}{I_1} = \frac{150 \times 10^{-15} \times 1.5}{2.25 \times 10^{-3}} = 100 \text{ ps}$$

From this point on, after  $200+225=425$  ps  $V_{out}$  goes 1. Now we should calculate the time in which the output of the first stage reaches to  $V_{DD}$ . When  $M_1$  enters the linear region, to have a rough estimation about the charging time we can assume that the capacitor is charged with a constant current which is the average of the currents in the beginning and end of the transition. Then:

$$I_1(V_c = 1.5) = 50 \times 40 \times 10^{-6} \times \left(1.5^2 - \frac{1.5^2}{2}\right) = 2.25 \text{ mA}$$

$$I_1(V_c = 3) = 50 \times 40 \times 10^{-6} \times \left(1.5 \times 0 - \frac{0^2}{2}\right) = 0 \text{ mA}$$

$$\Delta t = \frac{C \cdot \Delta V}{I_{avg}} = \frac{150 \times 10^{-15} \times 1.5}{1.125 \times 10^{-3}} = 200 \text{ ps}$$

Since 200 ps is less than the total propagation delay in the second and third stages (425 ps) then the voltage at the output of the first stage reaches  $V_{DD}$  before the next transition.

When  $V_{out}$  goes high,  $M_3$  is on and  $M_2$  is off and C is discharged by  $M_4$ . To reach  $V_{DD}/2$  which is the switching point for the coming stage:

$$I_4 = \frac{1}{2} \times 200 \times 20 \times 10^{-6} \times (2 - 0.5)^2 = 4.5 \text{ mA}$$

$M_4$  will be in saturation region until  $V_{DS4}=V_{GS4}-V_t=1.5$  V or the voltage on capacitor is 1.5 V which is the switching threshold for the coming stage. To get this point:

---

$$\Delta t = \frac{C \cdot \Delta V}{I_4} = \frac{150 \times 10^{-15} \times 1.5}{4.5 \times 10^{-3}} = 50 \text{ ps}$$

From this point on, after 425 ps  $V_{out}$  goes low. Using a similar method we can be sure that the capacitor is completely discharged before the next transition. Then  $V_{out}$  is 425+50=475 ps at high and 425+100= 525 ps at low. The period is 475+525=1000 ps=1 ns and the oscillation frequency is 1 GHz.

6)

