

**EXAMINATION IN**  
**-**  
**TSEK37/TEN1**  
**ANALOG CMOS INTEGRATED**  
**CIRCUITS**

Date: 2012-04-13  
Time: 14-18  
Location: TER2  
Aids: Calculator, Dictionary  
Teachers: Behzad Mesgarzadeh (5719)  
Ali Fazli (2794)  
Daniel Svärd (8946)

8 points are required to pass.

**Please start each new problem at the top of a page!**  
**Only use one side of each paper!**

---

- 1) A current mirror circuit is shown in Fig. 1. If properly sized, this circuit can realize accurate mirroring with a high output impedance while consuming low voltage headroom.

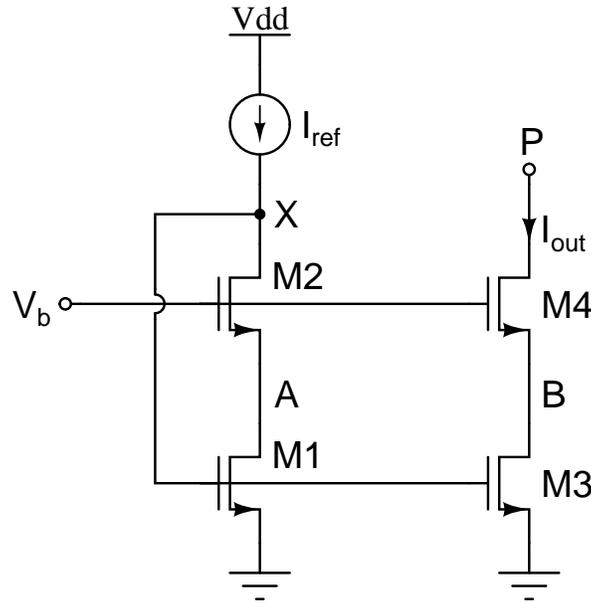


Fig. 1. Current mirror.

- (a) Derive the bounds on  $V_b$  such that  $M_1$  and  $M_2$  are in the saturation region. Determine the restriction on the sizing of  $M_2$  for this to be possible. Give the answers in terms of  $V_{GS1}$ ,  $V_{GS2}$ ,  $V_{TH1}$  and  $V_{TH2}$ . (2 p)
- (b) Using the lowest value of  $V_b$  from (a), determine the minimum allowable voltage at node P to keep  $M_3$  and  $M_4$  in saturation. Assume that  $M_3=M_1$  and that the transistors are sized such that  $V_{GS4}=V_{GS2}$ . Give the answer in terms of  $V_{GS3}$ ,  $V_{GS4}$ ,  $V_{TH3}$  and  $V_{TH4}$ . (1 p)
- 2) An amplifier with a DC gain of  $A_0$  and poles at 1 MHz and 450 MHz is connected in a feedback loop with a gain of 4 (i.e. the feedback factor ( $\beta$ ) is  $1/4$ ). Compute the value of  $A_0$  such that the phase margin is  $60^\circ$ . (2 p)

**Hint:**  $\arctan u + \arctan v = \arctan\left(\frac{u+v}{1-uv}\right) \pmod{\pi}$ ,  $uv \neq 1$

- 3) A fully differential current-mirror amplifier is shown in Fig. 2. The bias current of the device  $M_4$  is mirrored  $B$  times to the output stage, i.e.  $I_{D4} = B \times I_{D2}$ . A local positive feedback composed of transistors  $M_3$  and  $M_{3b}$  is used to enhance the DC gain.

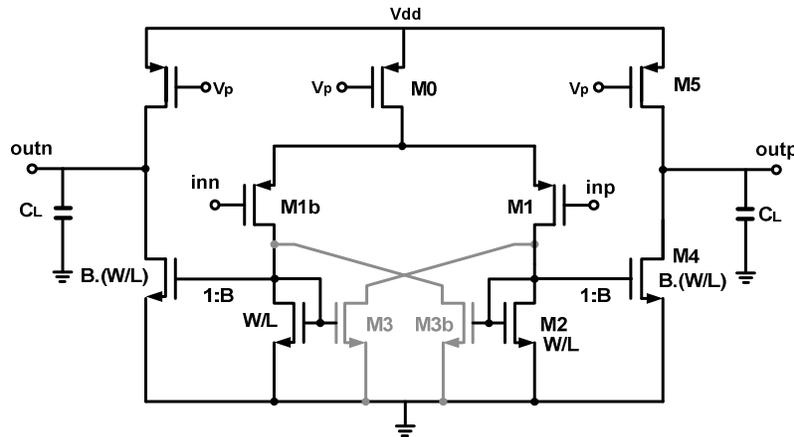


Fig. 2. Current mirror amplifier.

- (a) Disregard the positive feedback containing  $M_3$ - $M_{3b}$  devices and draw the small-signal model. Determine the DC gain in terms of the transconductance  $g_m$ , the conductance  $g_{ds}$ , and the mirroring ratio  $B$ . Assume that  $\gamma = 0$ . (2 p)
- (b) Consider the positive feedback and derive the DC gain expression. How can the DC gain be enhanced by sizing of the transistors  $M_3$  and  $M_{3b}$ ? (2 p)
- (c) Consider the current-mirror amplifier as a two-pole system and that it is frequency compensated by the load capacitor  $C_L$ , rather than miller capacitor. Also, assume that the second pole (non-dominant) occurs in the gate of the transistors  $M_2$ ,  $M_{3b}$ , and  $M_4$ . Derive the approximate expressions for the two poles. (1 p)
- 4) A lossless interconnect is shown in Fig. 3. At time 0, the voltage step of  $V_0$  drives a transmission line that is splitted into different sections, each driving an inverter with a high impedance input. With the impedance given below, calculate the voltage at A, B and C at the time instant 7.5 ns.  $R_0 = 75 \Omega$ ,  $Z_0 = 75 \Omega$ ,  $Z_1 = 150 \Omega$ , and  $Z_2 = 50 \Omega$ . (4 p)

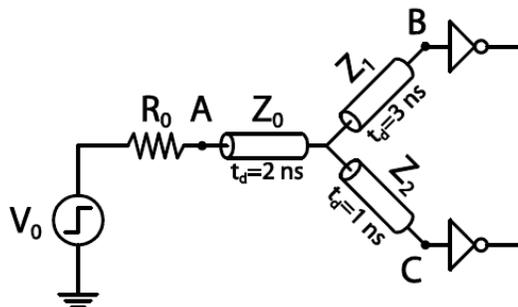


Fig. 3. A transmission-line circuit.

- 5) Assume that the output of a voltage-controlled oscillator (VCO) is a sinusoidal as it is shown in Fig. 4. In this figure,  $\omega_0$  is the output frequency when  $V_{\text{cont}}=0$ ,  $K_{\text{VCO}}$  is the gain of the VCO, and  $V_{\text{cont}}$  is the control voltage of the VCO. Now Assume that we apply a small sinusoidal control voltage to this VCO (i.e.,  $V_{\text{cont}} = V_m \cos(\omega_m t)$ ). If  $V_m$  is small enough to satisfy  $K_{\text{VCO}}V_m \ll \omega_m$  and  $\omega_m < \omega_0$ , draw the output spectrum of the VCO. Motivate your answer by presenting the details of your calculations. We can assume that the VCO characteristic is linear. (4 p)

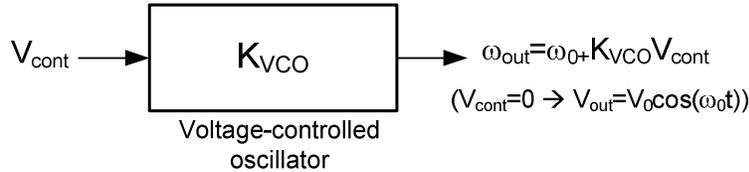


Fig. 4. A voltage-controlled oscillator.

- 6) A PLL type I with  $\zeta = 0.1$  is utilized to generate a 200-MHz carrier frequency. If  $\omega_{LPF} = 2\pi \times 28.6 \text{ KHz}$  and the output is to be changed from 201 MHz to 201.5 MHz, how long does it take in the worst-case for the PLL to settle within 100 Hz of its final value? (2 p)


**Hint:** The step response of a PLL type I with underdamped response is as:

$$\omega_{out}(t) = \left\{ 1 - \frac{1}{\sqrt{1-\zeta^2}} \cdot e^{-\zeta\omega_n t} \sin(\omega_n \sqrt{1-\zeta^2} t + \theta) \right\} \Delta\omega u(t)$$

where

$$2\zeta\omega_n = \omega_{LPF}$$

## TRANSISTOR EQUATIONS

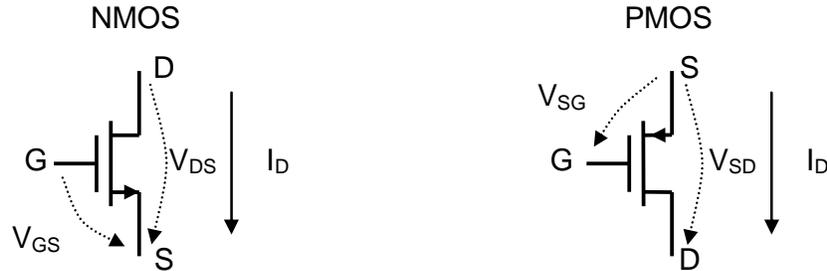

### NMOS

- **Cutoff:**  $I_D = 0$  ( $V_{GS} < V_{TN}$ )
- **Linear mode:**

$$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$
 ( $V_{GS} > V_{TN}$ ) and ( $V_{DS} < V_{GS} - V_{TN}$ )
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$
 ( $V_{GS} > V_{TN}$ ) and ( $V_{DS} > V_{GS} - V_{TN}$ )

### PMOS



- **Cutoff:**  $I_D = 0$  ( $V_{GS} < |V_{TP}|$ )
- **Linear mode:**

$$I_D = \mu_p C_{ox} \frac{W}{L} \left( (V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right)$$
 ( $V_{GS} > |V_{TP}|$ ) and ( $V_{SD} < V_{SG} - |V_{TP}|$ )
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD})$$
 ( $V_{GS} > |V_{TP}|$ ) and ( $V_{SD} > V_{SG} - |V_{TP}|$ )
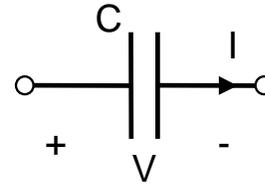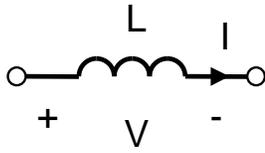
## TRANSMISSION LINE EQUATIONS

- Complex characteristic impedance:
 
$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$
- Inductance voltage-current relation:
 
$$V = L \frac{dI}{dt}$$
- Characteristic impedance for lossless TL:
 
$$Z_0 = \sqrt{\frac{L}{C}}$$
- Capacitance voltage-current relation:
 
$$I = C \frac{dV}{dt}$$



- Mutual inductance:

$$V_{mn} = L_{mn} \frac{dI_n}{dt} \text{ where } m \neq n$$

Telegrapher's Equation				
<b>Reflection Coefficient</b>	$k_r = \frac{V_r}{V_i} = \frac{I_r}{I_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$			
<b>Skin Effect</b>				
<b>Skin Depth</b>	$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$			
<b>Skin Depth Frequency</b>	$f_s = \frac{\rho}{\pi \mu (t/2)^2} \quad f_s = \frac{\rho}{\pi \mu r^2}$			
<b>Skin Depth Resistance</b>	$R(f) = \frac{\sqrt{\pi f \mu \rho}}{2w} = R_{DC} \left(\frac{f}{f_s}\right)^{1/2} \quad R(f) = \frac{\sqrt{f \mu \rho / \pi}}{2r} = \frac{R_{DC}}{2} \left(\frac{f}{f_s}\right)^{1/2}$			
Attenuation in Lossy Line				
<b>Attenuation</b>	$\frac{V_i(L)}{V_i(0)} = \exp[-(\alpha_R + \alpha_D)L] = \exp\left[-\left(\frac{R}{2Z_0} + \frac{GZ_0}{2}\right)L\right]$			
<b>Conductor Loss</b>	$\alpha_R(f) = \frac{R_{DC}}{4Z_0} \left(\frac{f}{f_s}\right)^{1/2} \text{ (Round)} \quad \alpha_R(f) = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s}\right)^{1/2} \text{ (Strip)}$			
<b>Dielectric Loss (Homogeneous)</b>	$\alpha_D(f) = \frac{\pi \sqrt{\epsilon_r} \tan \delta}{c} f \quad \text{Dielectric Loss Tangent } \tan \delta = \frac{G}{\omega C} = \frac{\sigma_{Diel}}{\omega \epsilon_r}$			
R,C,Z0 for Various Geometries (Homogeneous Dielectric, L = εμ/C)				
$R_{DC} = 2 \frac{\rho}{wh}$	$R_{DC} = \frac{\rho}{\pi r_1^2} + \frac{\rho}{\pi (r_2^2 - r_1^2)}$	$R_{DC} = \frac{2\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{wh}$
$C = \frac{\epsilon w}{s}$	$C = \frac{2\pi \epsilon}{\log(r_2/r_1)}$	$C = \frac{\pi \epsilon}{\log(s/r)}$	$C = \frac{\pi \epsilon}{\log(2s/r)}$	$C = \frac{\epsilon w}{s} + \frac{2\pi \epsilon}{\log(s/w)}$
$Z_0 = \sqrt{\frac{\mu s}{\epsilon W}}$	$Z_0 = \sqrt{\frac{\mu \log(r_2/r_1)}{\epsilon 2\pi}}$	$Z_0 = \sqrt{\frac{\mu \log(s/r)}{\epsilon \pi}}$	$Z_0 = \sqrt{\frac{\mu \log(2s/r)}{\epsilon \pi}}$	$Z_0 = \frac{\sqrt{\epsilon \mu}}{C}$