

EXAMINATION IN
-
TSEK37/TEN1
ANALOG CMOS INTEGRATED
CIRCUITS

Date: 2013-03-27
Time: 8-12
Location: U7-U10
Aids: Calculator, Dictionary
Teachers: Behzad Mesgarzadeh (5719)
Daniel Svärd (8946)

8 points are required to pass.

Please start each new problem at the top of a page!
Only use one side of each paper!

3) Transimpedance amplifiers are commonly used in optical receiver circuits. This type of amplifier converts an input current, i_{in} , into a voltage, v_{out} . Figure 3 shows an example circuit implementation of such an amplifier. For all subproblems, neglect all capacitances except C_X and C_L ; and assume $\lambda \neq 0$ and $\gamma \neq 0$.

- (a) Draw the small-signal model of the amplifier. (1 p)
- (b) Derive an expression for the transfer function, $R(s) = v_{out}/i_{in}$, of the amplifier. Identify the DC transimpedance and the two poles. (2 p)
- (c) Calculate the DC transimpedance and the location of the poles given the bias conditions in Fig. 3. (2 p)

$$\begin{aligned} \mu_n C_{ox} &= 160 \mu\text{A}/\text{V}^2 \\ L &= 0.35 \mu\text{m} \\ W_1 = W_2 &= 35 \mu\text{m} \\ \lambda_n &= 0.1 \text{V}^{-1} \\ \gamma_n &= 0.4 \text{V}^{1/2} \\ V_{t0n} &= 0.5 \text{V} \\ 2\Phi_F &= 0.9 \text{V} \\ V_{dd} &= 3.3 \text{V} \\ I_1 &= 500 \mu\text{A} \\ I_2 &= 2 \text{mA} \\ R_{D1} &= 2 \text{k}\Omega \\ R_{D2} &= 500 \Omega \\ R_S &= 2 \text{k}\Omega \\ C_X &= 0.25 \text{pF} \\ C_L &= 2 \text{pF} \end{aligned}$$

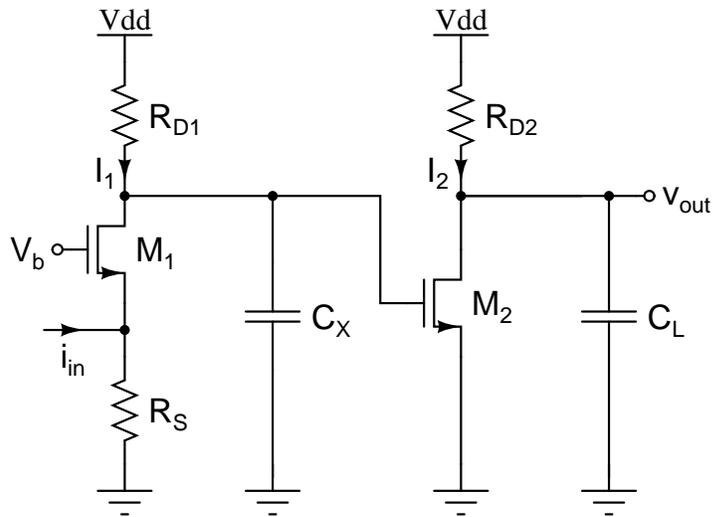


Fig. 3. Transimpedance amplifier.

4) Estimate the propagation delay of a 2-mm wire with a high-frequency characteristic impedance of 50Ω and resistance per length of $r=5 \text{ K}\Omega/\text{m}$ and dielectric constant $\epsilon_r=4$. (3 p)

- 5) A 3-stage ring oscillator is shown in Fig. 4. Assume that all of the transistors are identical and ignore their parasitics. Calculate the phase margin of this circuit. Assume $R = 3.5 \text{ K}\Omega$, $C = 1 \text{ pF}$, $g_m = 1 \text{ mA/V}$, and $r_o = 10 \text{ K}\Omega$. (4 p)


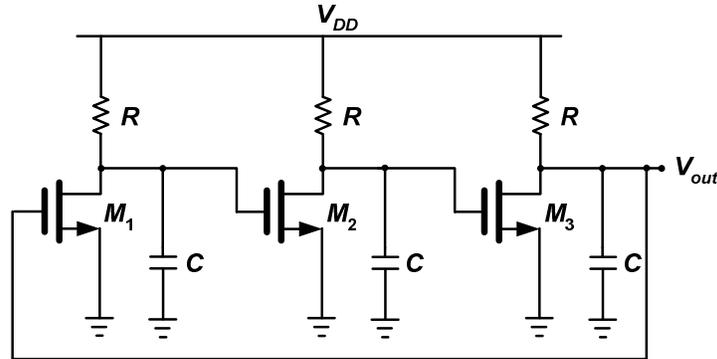


Fig. 4. A three-stage ring oscillator.

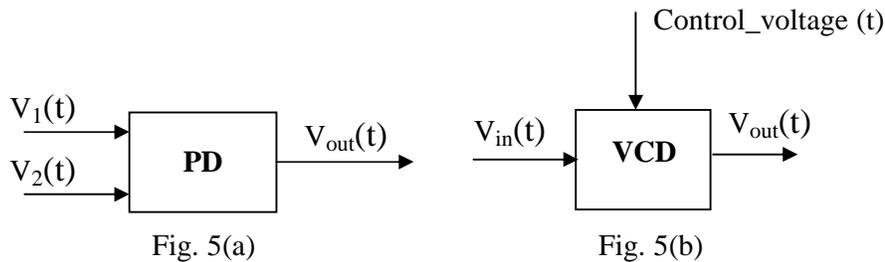- 6) Assume you have access to the following components:
- An *ideal* Phase-Detector (PD), shown in Fig. 5(a).
 - Many *ideal* Voltage-Controlled Delay elements (VCD), such as the one shown in Fig. 5(b).



Use the abovementioned components and design a clock phase generator (Fig. 5(c)) which receives a periodic clock signal (Clk_{in}) with an arbitrary frequency, and generates a clock signal (Clk_{out}) with the same frequency but with 90 degree phase shift.

(2 p)


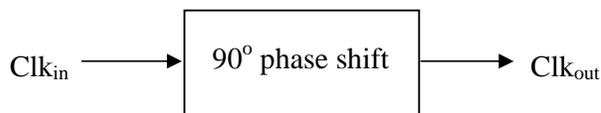


Fig. 5(c)

TRANSISTOR EQUATIONS

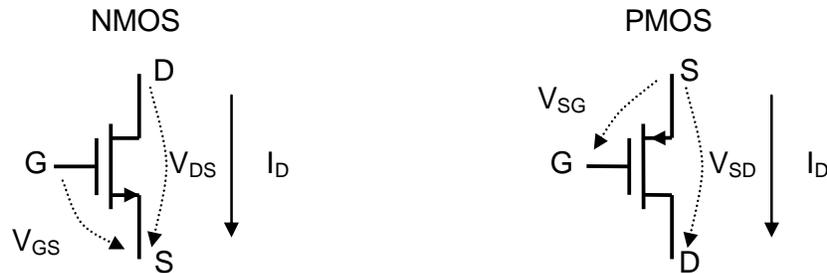

NMOS

- **Cutoff:** $I_D = 0$ ($V_{GS} < V_{TN}$)
- **Linear mode:**

$$I_D = \mu_n C_{ox} \frac{W}{L} \left((V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right)$$
 ($V_{GS} > V_{TN}$) and ($V_{DS} < V_{GS} - V_{TN}$)
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$
 ($V_{GS} > V_{TN}$) and ($V_{DS} > V_{GS} - V_{TN}$)

PMOS

- **Cutoff:** $I_D = 0$ ($V_{GS} < |V_{TP}|$)
- **Linear mode:**

$$I_D = \mu_p C_{ox} \frac{W}{L} \left((V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right)$$
 ($V_{GS} > |V_{TP}|$) and ($V_{SD} < V_{SG} - |V_{TP}|$)
- **Saturation mode:**

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD})$$
 ($V_{GS} > |V_{TP}|$) and ($V_{SD} > V_{SG} - |V_{TP}|$)

TRANSMISSION LINE EQUATIONS



- Complex characteristic impedance

$$Z_c = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$
- Inductance voltage-current relation:

$$V = L \frac{dI}{dt}$$
- Characteristic impedance for lossless TL:

$$Z_0 = \sqrt{\frac{L}{C}}$$
- Capacitance voltage-current relation:

$$I = C \frac{dV}{dt}$$

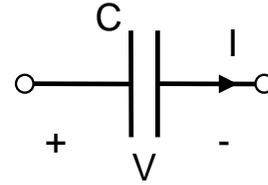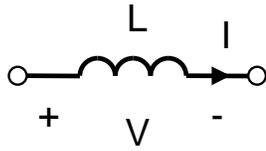

- Mutual inductance:

$$V_{mn} = L_{mn} \frac{dI_n}{dt} \text{ where } m \neq n$$

Telegrapher's Equation			
Reflection Coefficient	$k_r = \frac{V_r}{V_i} = \frac{I_r}{I_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$		
Skin Effect			
Skin Depth	$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$		
Skin Depth Frequency	$f_s = \frac{\rho}{\pi \mu (t/2)^2}$		
Skin Depth Resistance	$R(f) = \frac{\sqrt{\pi f \mu \rho}}{2w} = R_{DC} \left(\frac{f}{f_s}\right)^{1/2}$ $R(f) = \frac{\sqrt{f \mu \rho / \pi}}{2r} = \frac{R_{DC}}{2} \left(\frac{f}{f_s}\right)^{1/2}$		
Attenuation in Lossy Line			
Attenuation	$\frac{V_i(L)}{V_i(0)} = \exp[-(\alpha_R + \alpha_D)L] = \exp\left[-\left(\frac{R}{2Z_0} + \frac{GZ_0}{2}\right)L\right]$		
Conductor Loss	$\alpha_R(f) = \frac{R_{DC}}{4Z_0} \left(\frac{f}{f_s}\right)^{1/2} \text{ (Round)}$ $\alpha_R(f) = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s}\right)^{1/2} \text{ (Strip)}$		
Dielectric Loss (Homogeneous)	$\alpha_D(f) = \frac{\pi \sqrt{\epsilon_r} \tan \delta}{c} f$		
Dielectric Loss Tangent	$\tan \delta = \frac{G}{\omega C} = \frac{\sigma_{Diels}}{\omega \epsilon_r}$		
R, C, Z ₀ for Various Geometries (Homogeneous Dielectric, L = εμ/C)			
$R_{DC} = \frac{2\rho}{wh}$	$R_{DC} = \frac{\rho}{\pi r_1^2} + \frac{\rho}{\pi (r_3^2 - r_2^2)}$	$R_{DC} = \frac{2\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{\pi r^2}$
$C = \frac{\epsilon w}{s}$	$C = \frac{2\pi \epsilon}{\log(r_2/r_1)}$	$C = \frac{\pi \epsilon}{\log(s/r)}$	$C = \frac{\pi \epsilon}{\log(2s/r)}$
$Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{s}{W}$	$Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{\log(r_2/r_1)}{2\pi}$	$Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{\log(s/r)}{\pi}$	$Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{\log(2s/r)}{\pi}$
			$R_{DC} = \frac{\rho}{wh}$
			$C = \frac{\epsilon w}{s} + \frac{2\pi \epsilon}{\log(s/w)}$
			$Z_0 = \frac{\sqrt{\epsilon \mu}}{C}$