

TSEK37

ANALOG CMOS INTEGRATED CIRCUITS

EXAMINATION (TEN1)

Time: 16 January 2016 at 14.00 - 18.00

Place: G32

Responsible teacher: Martin Nielsen-Lönn, ISY, 070-361 52 44 (martin.nielsen.lonn@liu.se)
Will visit exam location at 15 and 17.

Number of tasks: 6

Number of pages: 7

Allowed aids: Calculator, dictionary

Total points: 20

Notes: Remember to indicate the steps taken when solving problems.
Please start each new problem at the top of a page!
Only use one side of each paper!

Exam presentation: 22 Januari 2016 at 12:00-13:00 in 3D:535, B-building

Grade	Points
U	<8
3	8 - <12
4	12 - <16
5	16 - 20

Questions

- 1) Consider the circuit shown in Fig. 1.

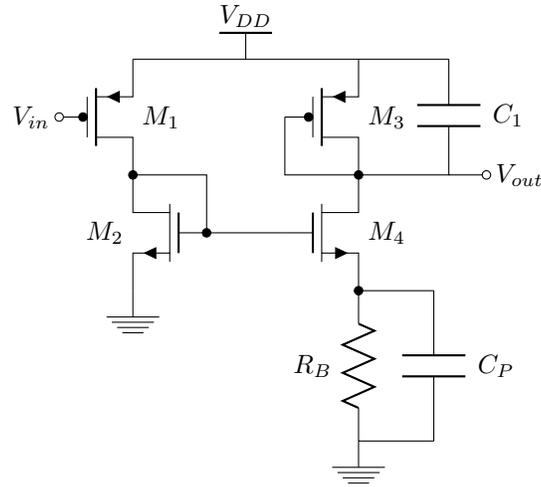


Figure 1: Schematic of a circuit.

- (a) Draw the equivalent small-signal model and derive the expression for the transfer function and from that transfer function identify the DC voltage gain, pole(s) and zero(s). Neglect channel-length modulation and body effect ($\lambda = 0$, $\gamma = 0$). Ignore all parasitic capacitances except C_p and C_1 . (3)
- (b) For the circuit in Fig. 1, let the unity-gain frequency $\omega_{ug} = 20$ krad/s, the dominant pole $\omega_{p1} = 1$ krad/s and the phase margin $PM = 55^\circ$. Determine the value of the non-dominant pole ω_{p2} . Ignore the effect of the zero(s) on the PM. (1)
-
- 2) Consider the fully differential amplifier shown in Fig. 2. The amplifier is completely symmetric. Neglect body effect ($\gamma = 0$). However, channel-length modulation must be considered ($\lambda \neq 0$). The parasitic capacitance C_{gs} of the MOSFETs at nodes X, Y and the load capacitance C_L must be considered. Ignore other parasitic capacitances. Assume that C_{gs} of $M_{4a,4b} = B \times C_{gs}$ of $M_{2a,2b}$, $g_{m4a,4b} = B \times g_{m2a,2b}$ and $g_m \gg g_{ds}$. B is an adjustable parameter.
- (a) Draw the small-signal model of the amplifier shown in Fig. 2 and derive the transfer function. (2 $\frac{1}{2}$)
- (b) Derive the expressions for the DC gain, the two pole frequencies and the unity-gain frequency. It is assumed that the dominant pole is formed by the load capacitor C_L . (1)
- (c) If the factor B is increased, how will the non-dominant pole and unity-gain frequency change? It is assumed that the dominant pole is formed by the load capacitor C_L . (1 $\frac{1}{2}$)

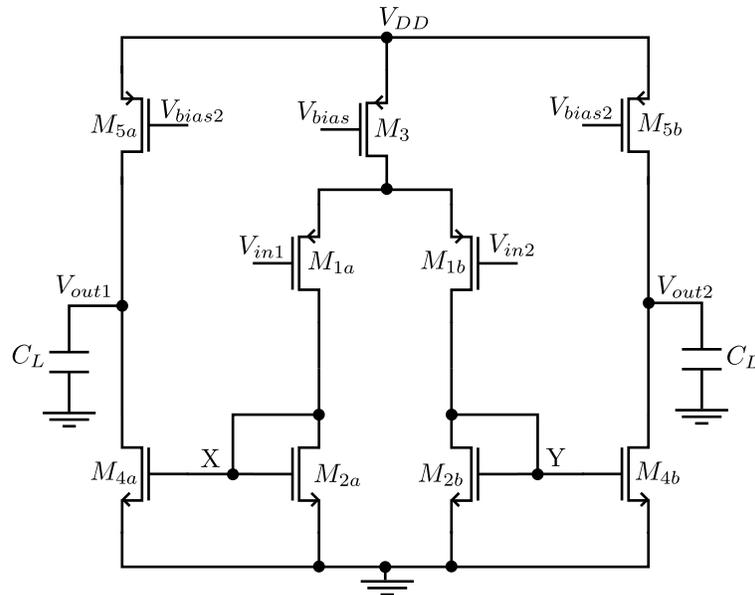


Figure 2: A fully differential amplifier.

- 3) In Fig. 3 a wide-swing cascode current mirror is shown. The aim here is to copy the reference current I_1 to I_2 . Assume that all transistors are in saturation and have the same threshold voltage. Neglect body effect and channel-length modulation. The transistor M_2 is designed to be at the edge of the saturation region to have the maximum voltage swing at the output node. What should be the value of n such that $I_1 = I_2$?

(3)

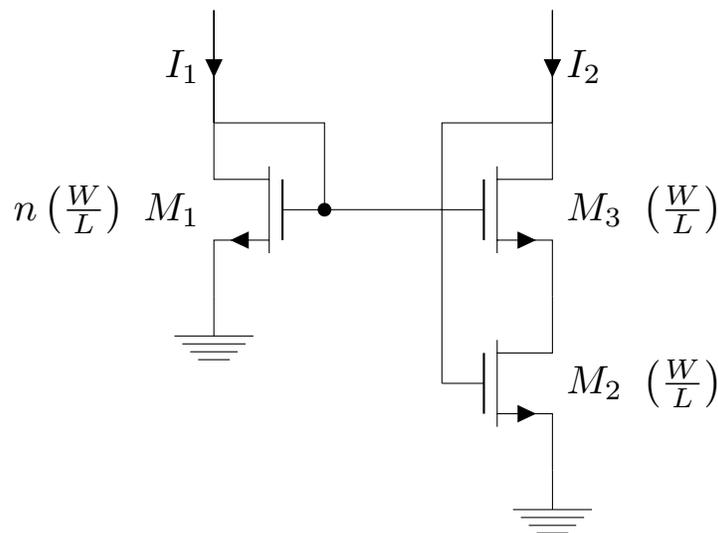


Figure 3: A wide-swing cascode current mirror.

- 4) Figure 4 shows a lossless interconnect circuit. At $t = 0$ the voltage step V_0 goes high and propagates a pulse through the circuit. Given the values below, calculate the voltage at nodes A, B and C at $t = 7$ ns. t_{d,Z_x} is the delay through transmission line Z_x . Assume that the inverters have a infinite (high) input impedance. (3)

$R_0 = 150 \Omega$, $Z_0 = 150 \Omega$, $Z_1 = 75 \Omega$, $Z_2 = 50 \Omega$, $t_{d,Z_0} = 2$ ns, $t_{d,Z_1} = 3$ ns and $t_{d,Z_2} = 4$ ns.

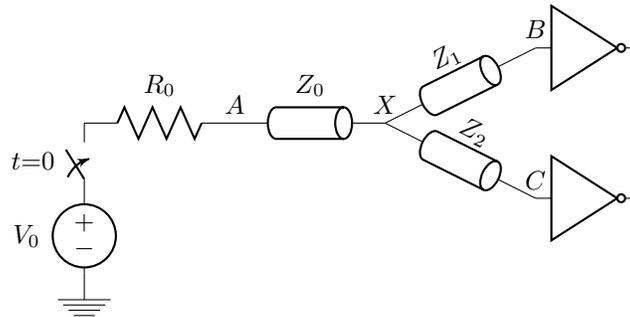


Figure 4: Transmission line circuit.

- 5) Assume that an inverter stage can be approximated as a first order circuit with a single pole at ω_0 and a stage DC-gain of $-A$. (1)
- (a) What are the possible number of stages required to construct a ring oscillator and what is the minimum number assuming each stage is made using a single-ended inverter? How would this change if differential inverters are used instead and why? (1)
- (b) Draw such a ring oscillator with a minimum amount of stages. Derive the open-loop transfer function for this ring oscillator. (1)
- (c) Calculate the minimum required voltage gain per stage in order to have oscillation and how this gain requirement changes with the number of stage, N . ($1\frac{1}{2}$)
- (d) Assume that the ring oscillator has settled into its steady state which occurs when the output signals starts to swing from roughly 0 to roughly V_{DD} . At this point the propagation delay of each stage is $t_{p,s}$. What is the output frequency if we have N number of stages? ($\frac{1}{2}$)

6) A PLL type I contains a low-pass filter, phase detector and VCO.

- (a) Draw the block diagram of the PLL, derive the total transfer function as $H(s) = \frac{\theta_{out}(s)}{\theta_{in}(s)}$ and show that θ_{out} is equal to θ_{in} when θ_{in} is constant. (1½)


$$H_{PD}(s) = K_{PD}[\theta_{in}(s) - \theta_{out}(s)]$$

$$H_{LP}(s) = \frac{1}{1 + \frac{s}{\omega_{p1}}}$$


$$H_{VCO}(s) = \frac{K_{VCO}}{s}$$

- (b) A PLL can be used to multiply a frequency. Assume that the PLL is supposed to generate a frequency of 1 GHz from a 250 MHz clock. Modify and insert additional needed blocks in the block diagram to implement this behaviour. (½)
-

Transistor equations

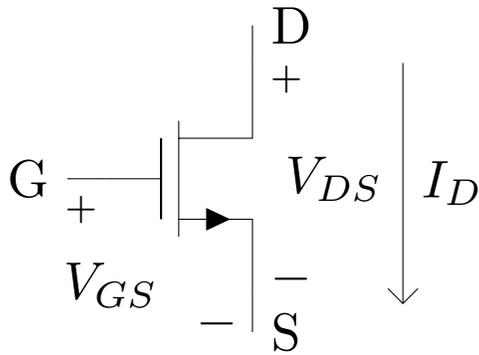

(a) NMOS

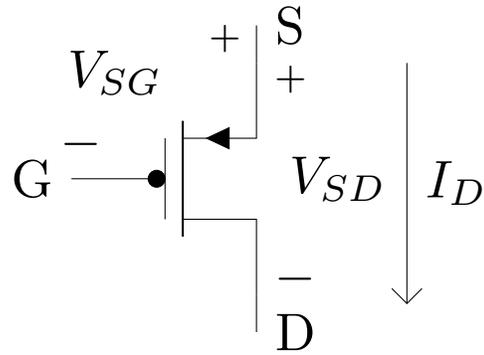

(b) PMOS

NMOS

Cutoff $I_D = 0$ ($V_{GS} < V_{TN}$)

Linear mode

$$I_D = \mu_n C_{ox} \frac{W}{L} \left((V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} < V_{GS} - V_{TN})$$

Saturation mode

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} > V_{GS} - V_{TN})$$

PMOS

Cutoff $I_D = 0$ ($V_{SG} < |V_{TP}|$)


Linear mode

$$I_D = \mu_p C_{ox} \frac{W}{L} \left((V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right) \quad (V_{SG} > |V_{TP}|) \text{ and } (V_{SD} < V_{SG} - |V_{TP}|)$$


Saturation mode

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD}) \quad (V_{SG} > |V_{TP}|) \text{ and } (V_{SD} > V_{SG} - |V_{TP}|)$$

Transmission line equations

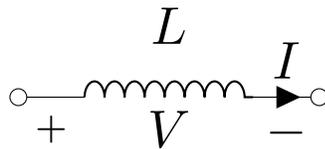

(a) Inductor

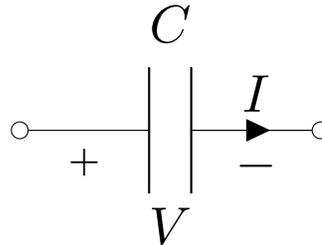

(b) Capacitor

Complex characteristic impedance

$$Z_c = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Characteristic impedance for lossless TL

$$Z_0 = \sqrt{\frac{L}{C}}$$

Inductance voltage-current relation








$$V = L \frac{dI}{dt}$$

Capacitance voltage-current relation

$$I = C \frac{dV}{dt}$$

Mutual inductance

$$V_{mn} = L_{mn} \frac{dI_n}{dt} \text{ where } m \neq n$$

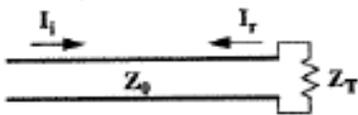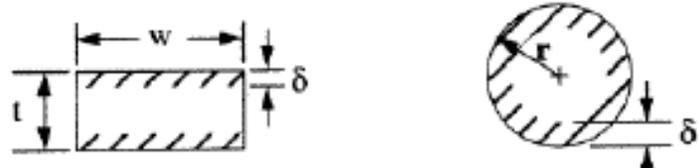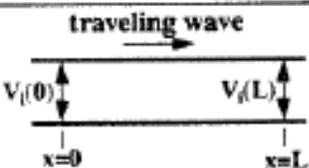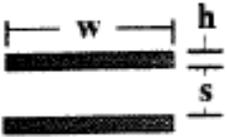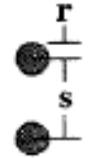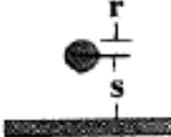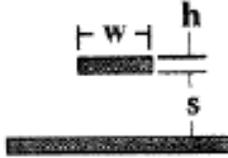Telegrapher's Equation				
Reflection Coefficient	$k_r = \frac{V_r}{V_i} = \frac{I_r}{I_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$			
Skin Effect				
Skin Depth	$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$			
Skin Depth Frequency	$f_s = \frac{\rho}{\pi \mu (t/2)^2}$	$f_s = \frac{\rho}{\pi \mu r^2}$		
Skin Depth Resistance	$R(f) = \frac{\sqrt{\pi f \mu \rho}}{2w} = R_{DC} \left(\frac{f}{f_s}\right)^{1/2}$	$R(f) = \frac{\sqrt{f \mu \rho / \pi}}{2r} = \frac{R_{DC}}{2} \left(\frac{f}{f_s}\right)^{1/2}$		
Attenuation in Lossy Line				
Attenuation	$\frac{V_i(L)}{V_i(0)} = \exp[-(\alpha_R + \alpha_D)L] = \exp\left[-\left(\frac{R}{2Z_0} + \frac{GZ_0}{2}\right)L\right]$			
Conductor Loss	$\alpha_R(f) = \frac{R_{DC}}{4Z_0} \left(\frac{f}{f_s}\right)^{1/2}$ (Round) $\alpha_R(f) = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s}\right)^{1/2}$ (Strip)			
Dielectric Loss (Homogeneous)	$\alpha_D(f) = \frac{\pi \sqrt{\epsilon_r} \tan \delta}{c} f$	Dielectric Loss Tangent $\tan \delta = \frac{G}{\omega C} = \frac{\sigma_{Diel}}{\omega \epsilon_r}$		
R,C,Z0 for Various Geometries (Homogeneous Dielectric, L = εμ/C)				
				
$R_{DC} = \frac{2\rho}{wh}$	$R_{DC} = \frac{\rho}{\pi r_1^2} + \frac{\rho}{\pi(r_2^2 - r_1^2)}$	$R_{DC} = \frac{2\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{wh}$
$C = \frac{\epsilon w}{s}$	$C = \frac{2\pi \epsilon}{\log(r_2/r_1)}$	$C = \frac{\pi \epsilon}{\log(s/r)}$	$C = \frac{\pi \epsilon}{\log(2s/r)}$	$C = \frac{\epsilon w}{s} + \frac{2\pi \epsilon}{\log(s/w)}$
$Z_0 = \sqrt{\frac{\mu s}{\epsilon W}}$	$Z_0 = \sqrt{\frac{\mu \log(r_2/r_1)}{\epsilon 2\pi}}$	$Z_0 = \sqrt{\frac{\mu \log(s/r)}{\epsilon \pi}}$	$Z_0 = \sqrt{\frac{\mu \log(2s/r)}{\epsilon \pi}}$	$Z_0 = \frac{\sqrt{\epsilon \mu}}{C}$