

TSEK37

ANALOG CMOS INTEGRATED CIRCUITS

EXAMINATION (TEN1)

Time: 1 April 2016 at 8.00 - 12.00

Place: G32

Responsible teacher: Martin Nielsen-Lönn, ISY, 070-361 52 44 (martin.nielsen.lonn@liu.se)

Will visit exam location at 9 and 11.

Number of tasks: 6

Number of pages: 6

Allowed aids: Calculator, dictionary

Total points: 20

Notes: Remember to indicate the steps taken when solving problems.

Please start each new problem at the top of a page!

Only use one side of each paper!

Exam presentation: 8 April 2016 at 12:00-13:00 in 3D:535, B-building

Grade	Points
U	<8
3	8 - <12
4	12 - <16
5	16 - 20

Questions

- 1) Consider the circuit shown in Fig. 1.

 


Figure 1: Schematic of a single-ended amplifier.

- (a) Draw the equivalent small-signal model and derive the expression for the transfer function and from that transfer function identify the DC voltage gain and pole(s). Neglect channel-length modulation and body effect ($\lambda = 0$, $\gamma = 0$). Ignore all parasitic capacitances. (3)
- (b) Assume that a parasitic pole ω_{p2} appears in the circuit shown in Fig. 1 and the unity-gain frequency $\omega_{ug} = 20$ krad/s, the dominant pole $\omega_{p1} = 2$ krad/s and the phase margin $PM = 60^\circ$. Determine the value of this non-dominant pole ω_{p2} caused by parasitics. Assume that the poles are well separated. (1)

- 2) Consider the fully differential amplifier shown in Fig. 2. The amplifier is completely symmetric. Neglect body effect ($\gamma = 0$). However, channel-length modulation must be considered ($\lambda \neq 0$). The parasitic capacitance C_{gs} of the MOSFETs at nodes X, Y and the load capacitance C_L must be considered. Ignore other parasitic capacitances. Assume that $g_m \gg g_{ds}$.

 


Figure 2: A fully differential amplifier.

- (a) Draw the small-signal model of the amplifier shown in Fig. 2 and derive the transfer function. (2 $\frac{1}{2}$)
- (b) Derive the expressions for the DC gain, the two pole frequencies and the unity-gain frequency. It is assumed that the dominant pole is formed by the load capacitor C_L . (1)
- (c) If the width of M_4 increases, how will this change the non-dominant pole and the unity-gain frequency? It is assumed that the dominant pole is formed by the load capacitor C_L . (1 $\frac{1}{2}$)

- 3) In Fig. 3 a current mirror circuit is shown. The aim is to copy the reference current I_{ref} to I_{out} . This requires a high output impedance and preferably a low voltage headroom.

 


Figure 3: A wide-swing cascode current mirror.

- (a) Derive the bounds for V_{bias} such that both M_1 and M_2 are in the saturation region. Give the answers in terms of V_{gs1} , V_{gs2} , V_{th1} and V_{th2} . (2)
- (b) Using the lowest value for V_{bias} derived in part 1, determine the minimum allowable voltage at the output node to keep both M_3 and M_4 in the saturation region. Assume that $M_3 = M_1$ and $V_{gs4} = V_{gs2}$. Give the answer in terms of V_{gs3} , V_{gs4} , V_{th3} and V_{th4} . (1)
-
- 4) Figure 4 shows a lossless interconnect circuit. At $t = 0$ the voltage step V_0 goes high and propagates a pulse through the circuit. Given the values below, calculate the voltage at nodes A, B and C at $t = 7$ ns. t_{d,Z_x} is the delay through transmission line Z_x . Assume that the inverters have a infinite (high) input impedance. (3)

$R_0 = 150 \Omega$, $Z_0 = 150 \Omega$, $Z_1 = 75 \Omega$, $Z_2 = 50 \Omega$, $t_{d,Z_0} = 2$ ns, $t_{d,Z_1} = 3$ ns and $t_{d,Z_2} = 4$ ns.

 


Figure 4: Transmission line circuit.

 


Figure 5: 3-stage ring oscillator

- 5) (a) In Fig. 5 a 3-stage ring oscillator is shown. What is the *maximum* phase of V_{out} this circuit can have when $\omega \rightarrow \infty$? Divide the phase shift into DC phase shift and frequency dependent phase shift. (1)
- (b) Given the Barkhausen criteria, (2)

$$|H(j\omega_0)| \geq 1$$


$$\angle H(j\omega_0) = 180^\circ$$

and the pole frequency ω_p and DC-gain A_0 for each stage. At what frequency will the circuit oscillate? And what gain is required for each stage? Assume that all stages are equal.

Hint: $\tan(60^\circ) = \sqrt{3}$.

- (c) Derive the total transfer function for the system first in terms of DC-gain, A_0 , and poles, ω_{p1} and then with the circuit components R_D , C_L , g_m and g_{ds} . Identify the DC-gain and pole location in the second transfer function. Assume that all stages are equal, that parasitic capacitances can be neglected and $1/g_{ds} \gg R_D$. (1)
-
- 6) (a) An XOR gate is used as a phase detector in a DLL. Assume that the phase difference between the input and output of the DLL is 225° . Draw the input and output waveforms of the XOR ($DLL In$, $DLL Out$ and $XOR Out$). Also calculate the average output voltage of the phase detector. Assume that the waveforms are ideal square waves with a swing between 0 V and 1 V. (1)
- (b) A PLL type I can be used to multiply a frequency. Assume that the PLL is supposed to generate a frequency of 1 GHz from a 250 MHz clock. Draw the block diagram for this kind of PLL. (1)
-

Transistor equations

 

NMOS

Cutoff $I_D = 0$ ($V_{GS} < V_{TN}$)

Linear mode

$$I_D = \mu_n C_{ox} \frac{W}{L} \left((V_{GS} - V_{TN}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} < V_{GS} - V_{TN})$$

Saturation mode

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS}) \quad (V_{GS} > V_{TN}) \text{ and } (V_{DS} > V_{GS} - V_{TN})$$

PMOS

Cutoff $I_D = 0$ ($V_{SG} < |V_{TP}|$)


Linear mode

$$I_D = \mu_p C_{ox} \frac{W}{L} \left((V_{SG} - |V_{TP}|) V_{SD} - \frac{V_{SD}^2}{2} \right) \quad (V_{SG} > |V_{TP}|) \text{ and } (V_{SD} < V_{SG} - |V_{TP}|)$$


Saturation mode

$$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TP}|)^2 (1 + \lambda V_{SD}) \quad (V_{SG} > |V_{TP}|) \text{ and } (V_{SD} > V_{SG} - |V_{TP}|)$$

Transmission line equations

 

(a) Inductor

 

(b) Capacitor

Complex characteristic impedance

$$Z_c = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

Characteristic impedance for lossless TL

$$Z_0 = \sqrt{\frac{L}{C}}$$

Inductance voltage-current relation







$$V = L \frac{dI}{dt}$$

Capacitance voltage-current relation

$$I = C \frac{dV}{dt}$$

Mutual inductance

$$V_{mn} = L_{mn} \frac{dI_n}{dt} \text{ where } m \neq n$$

      Telegrapher's Equation			
Reflection Coefficient	$k_r = \frac{V_r}{V_i} = \frac{I_r}{I_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$		
Skin Effect			
Skin Depth	$\delta = \frac{1}{\sqrt{\pi f \mu \sigma}}$		
Skin Depth Frequency	$f_s = \frac{\rho}{\pi \mu (t/2)^2}$	$f_s = \frac{\rho}{\pi \mu r^2}$	
Skin Depth Resistance	$R(f) = \frac{\sqrt{\pi f \mu \rho}}{2w} = R_{DC} \left(\frac{f}{f_s}\right)^{1/2}$ $R(f) = \frac{\sqrt{f \mu \rho / \pi}}{2r} = \frac{R_{DC}}{2} \left(\frac{f}{f_s}\right)^{1/2}$		
Attenuation in Lossy Line			
Attenuation	$\frac{V_i(L)}{V_i(0)} = \exp[-(\alpha_R + \alpha_D)L] = \exp\left[-\left(\frac{R}{2Z_0} + \frac{GZ_0}{2}\right)L\right]$		
Conductor Loss	$\alpha_R(f) = \frac{R_{DC}}{4Z_0} \left(\frac{f}{f_s}\right)^{1/2}$ (Round)	$\alpha_R(f) = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s}\right)^{1/2}$ (Strip)	
Dielectric Loss (Homogeneous)	$\alpha_D(f) = \frac{\pi \sqrt{\epsilon_r} \tan \delta}{c} f$	Dielectric Loss Tangent	$\tan \delta = \frac{G}{\omega C} = \frac{\sigma_{Diel}}{\omega \epsilon_r}$
R,C,Z0 for Various Geometries (Homogeneous Dielectric, L = εμ/C)			
			
$R_{DC} = \frac{2\rho}{wh}$	$R_{DC} = \frac{\rho}{\pi r_1^2} + \frac{\rho}{\pi(r_2^2 - r_1^2)}$	$R_{DC} = \frac{2\rho}{\pi r^2}$	$R_{DC} = \frac{\rho}{wh}$
$C = \frac{\epsilon w}{s}$	$C = \frac{2\pi \epsilon}{\log(r_2/r_1)}$	$C = \frac{\pi \epsilon}{\log(s/r)}$	$C = \frac{\epsilon w}{s} + \frac{2\pi \epsilon}{\log(s/w)}$
$Z_0 = \sqrt{\frac{\mu s}{\epsilon w}}$	$Z_0 = \sqrt{\frac{\mu \log(r_2/r_1)}{\epsilon 2\pi}}$	$Z_0 = \sqrt{\frac{\mu \log(s/r)}{\epsilon \pi}}$	$Z_0 = \frac{\sqrt{\epsilon \mu}}{C}$