

DAC input/output

The digital input to a DAC is given in a binary representation

$$B = \langle b_1, b_2, b_3 \rangle = b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}$$

Minimum input change is 1 LSB = 2^{-N}

The converter translates this to an analog output as

$$V_{out} = B \cdot V_{ref}$$

where V_{ref} often is a constant voltage, but could be current or charge

Minimum output change is $V_{LSB} = 2^{-N} \cdot V_{ref}$

Ex: Converter with $N = 3$ bit, $V_{ref} = 1.0 \text{ V} \Rightarrow$

$$V_{out} = \left(b_1 \frac{1}{2} + b_2 \frac{1}{4} + b_3 \frac{1}{8} \right) \cdot 1.0 \text{ V}$$


Min value is given by $B = \langle 0, 0, 0 \rangle = 0 \text{ V}$

Max value is given by $B = \langle 1, 1, 1 \rangle = 7/8 \text{ V}$

V_{LSB} is $1/8 \cdot V_{ref}$


DAC transfer curve

Ideal 2-bit DAC

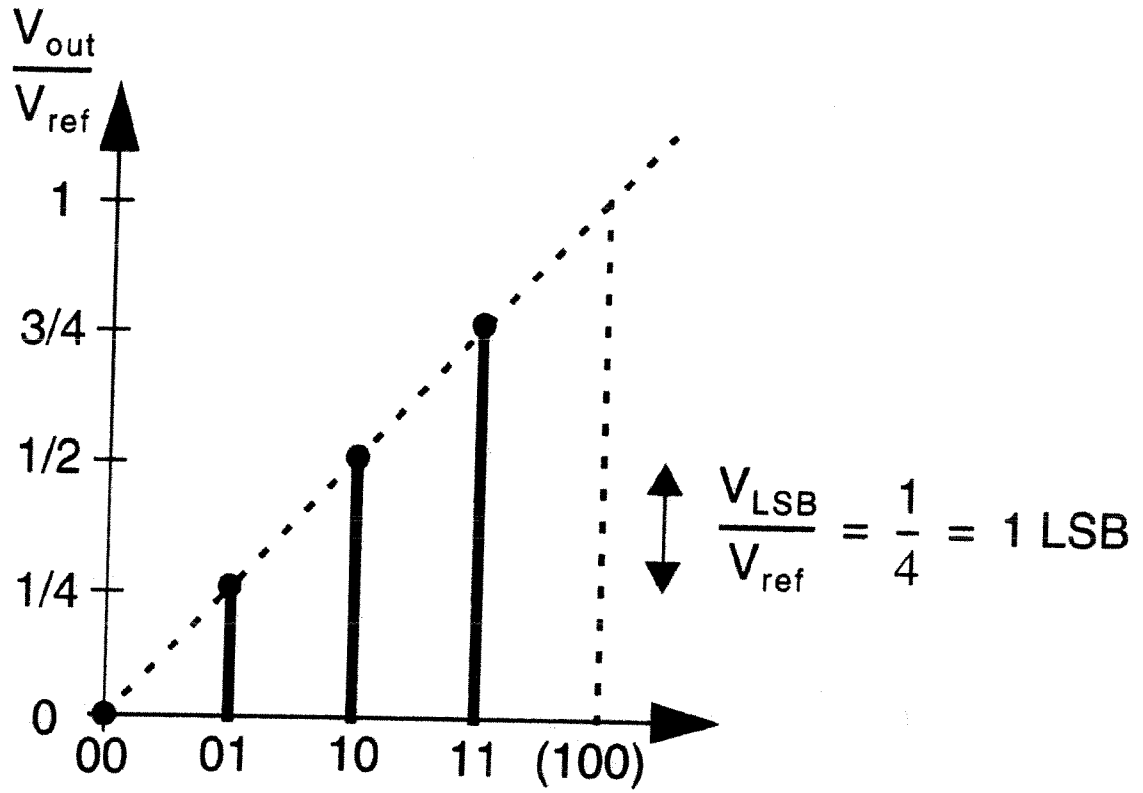

DAC performance

Offset and gain error

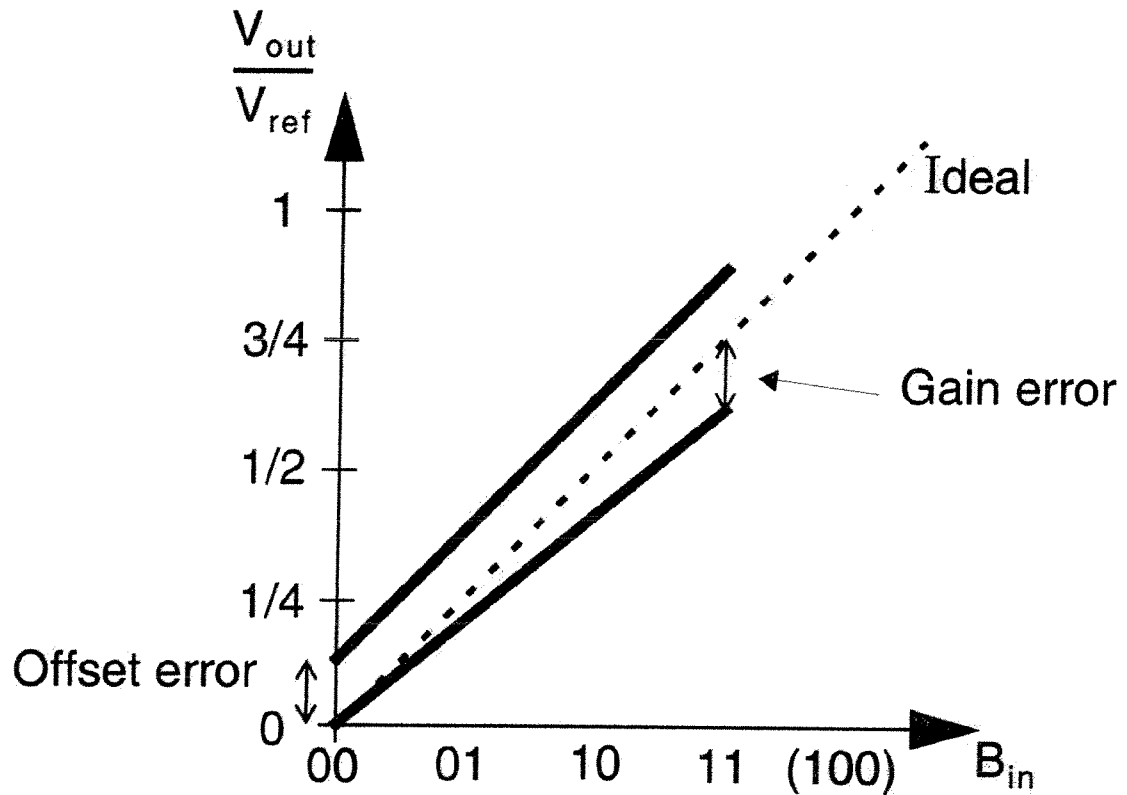


Resolution is the number of input bits

Accuracy is the effective number of bits


Ex: N-bit resolution corresponds to 2^N analog output levels

M-bit accuracy corresponds to $\text{Error} < V_{ref} \cdot 2^{-M}$

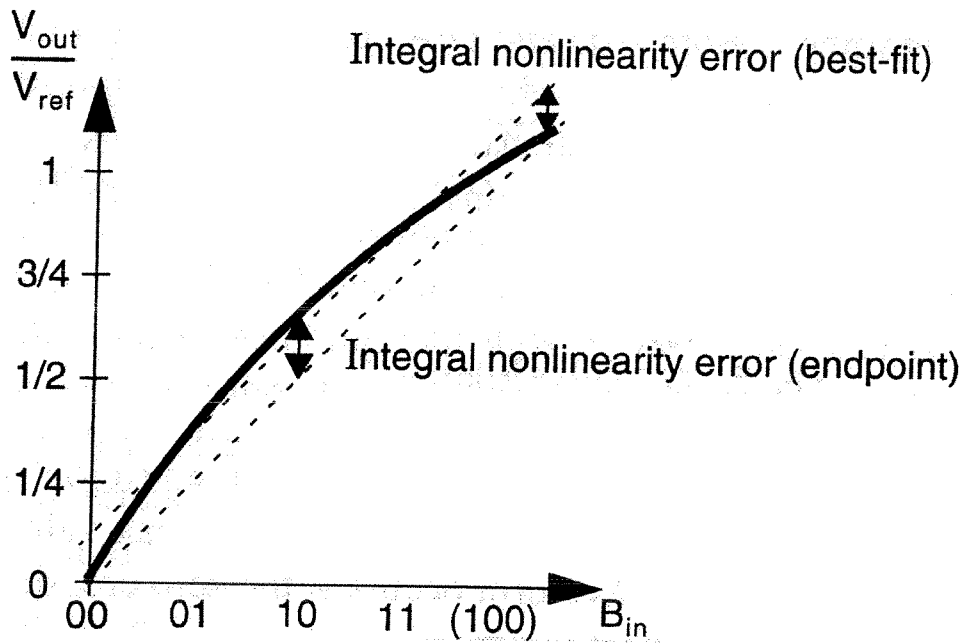Integral nonlinearity (INL) is the transfer function's deviation from a straight line




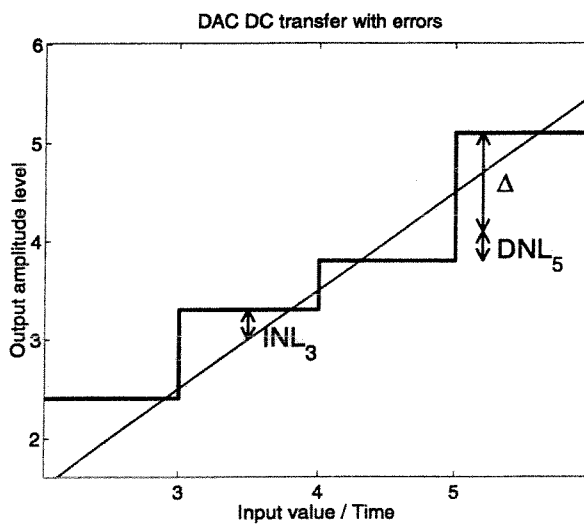Differential nonlinearity (DNL) is the deviation of a transfer function step from an ideal 1 LSB step



(Monotonicity of a DAC is when the output always increases for increasing input)

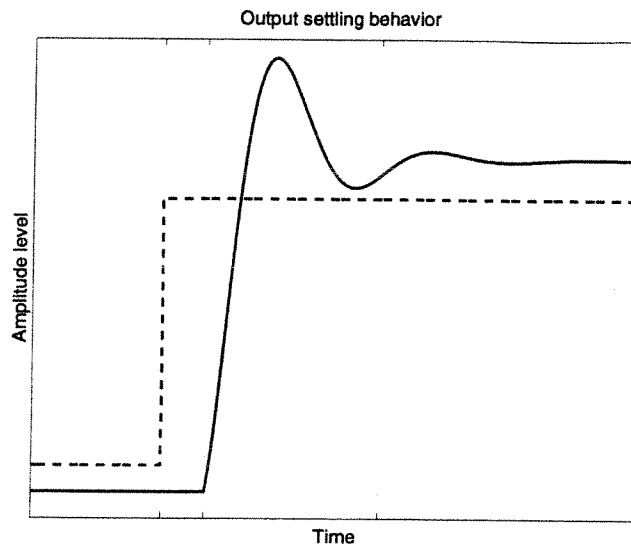
Settling time τ is the time it takes for a DAC output to settle within a $\frac{1}{2}$ LSB



Sampling rate $f_{sample} = 1/\tau$

R-2R-based converters

R-2R ladder

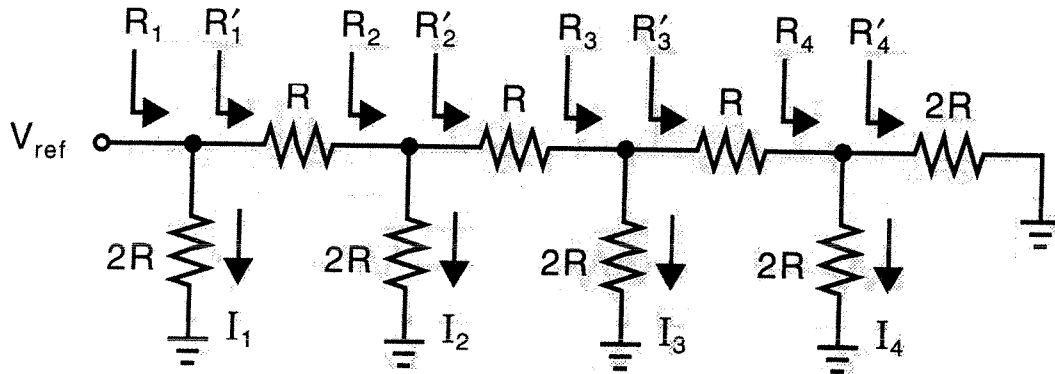

Resistance in nodes

$$R'_4 = 2R$$

$$R_4 = 2R \parallel 2R = R$$

$$R'_3 = R + R_4 = 2R$$

$$R_3 = 2R \parallel R'_3 = R$$

...

i.e., $R'_i = 2R$ for all i

Currents

$$I_1 = V_{ref} / 2R$$

$$I_2 = V_{ref} / 4R = I_1 / 2$$

$$I_3 = V_{ref} / 8R = I_2 / 2$$

...

i.e., $I_i = I_{i-1} / 2$