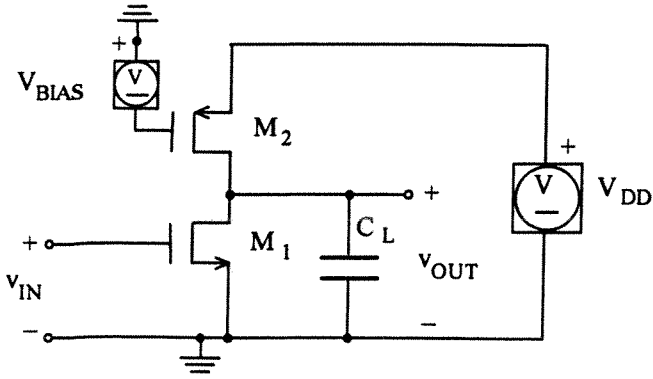


PROPERTIES BASIC AMPLIFIERS



	COMMON SOURCE (CS)	COMMON DRAIN (CD)	COMMON GATE (CG)	CMOS INVERTER (CI)
Voltage-gain	high (inv.)	low (<1) (non-inv.)	high (non- inv.)	high (inv.)
Output resistance	high	low	high	high
Input resistance	high	high	low	high
Application areas	inp.stage OP	outp.stage OP	low-resistance inp.stage (signal from transmission line)	uncommon sensitive hard to design

	CS	CD	CG	CI
A_o	$-\frac{g_{m1}}{g_{out}}$	$\frac{g_m}{g_{out}} \approx 1$	$\frac{g_{m1} + g_{b1}}{g_{out}} \approx \frac{g_{m1}}{g_{out}}$	$-\frac{g_{m1} + g_{m2}}{g_{out}}$
p_1	$-\frac{g_{out}}{C'_L}$	$-\frac{g_{out}}{C'_L}$	$-\frac{g_{out}}{C'_L}$	$-\frac{g_{out}}{C'_L}$
ω_u	$\frac{g_{m1}}{C'_L}$	$\frac{g_{m1}}{C'_L}$	$\approx \frac{g_{m1}}{C'_L}$	$\frac{g_{m1} + g_{m2}}{C'_L}$
g_{out}	$g_{ds1} + g_{ds2}$	$g_{m1} + g_{b1} + g_{ds1} + g_{ds2}$	$g_{ds1} + g_{ds2}$	$g_{ds1} + g_{ds2}$
g_{in}	0	0	$g_{m1} \cdot \frac{1}{1 + \frac{g_{ds1}}{g_{ds2}}}$	0


COMMON SOURCE AMPLIFIER





SMALL-SIGNAL EQUIVALENT CIRCUIT (SSEC)

  


COMMON DRAIN AMPLIFIER

 



SMALL-SIGNAL EQUIVALENT CIRCUIT (SSEC)

  


COMMON GATE AMPLIFIER

 


SMALL-SIGNAL EQUIVALENT CIRCUIT (SSEC)

  


CMOS-INVERTER

 


SMALL-SIGNAL EQUIVALENT CIRCUIT (SSEC)

 


**COMMON SOURCE AMPLIFIER
WITH CASCODE**

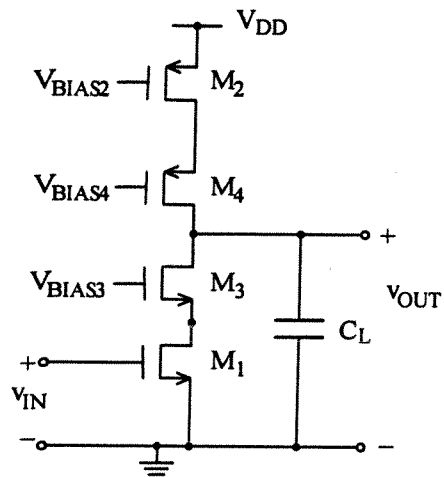

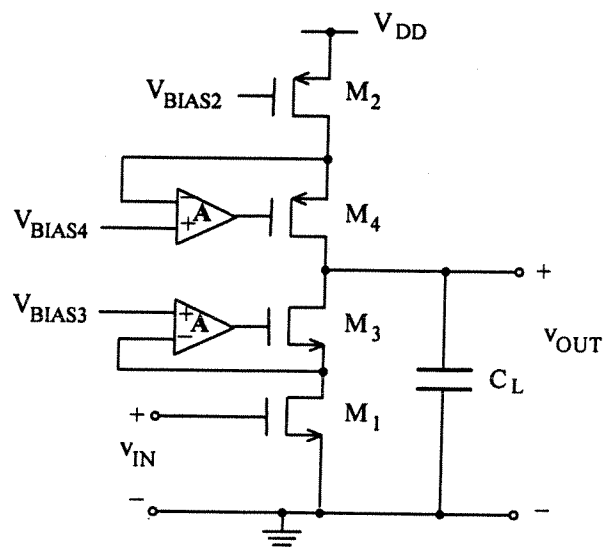
**COMMON SOURCE AMPLIFIER
WITH CASCODE. EXTRA BIAS**



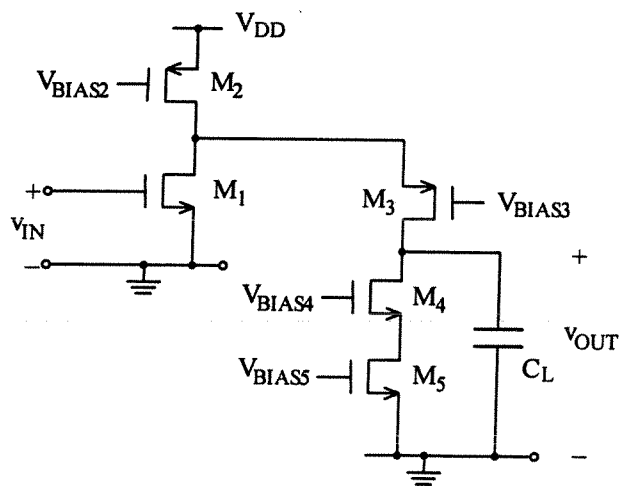**COMMON SOURCE AMPLIFIER
WITH FOLDED CASCODE**




COMMON SOURCE AMPLIFIER
WITH CASCODE

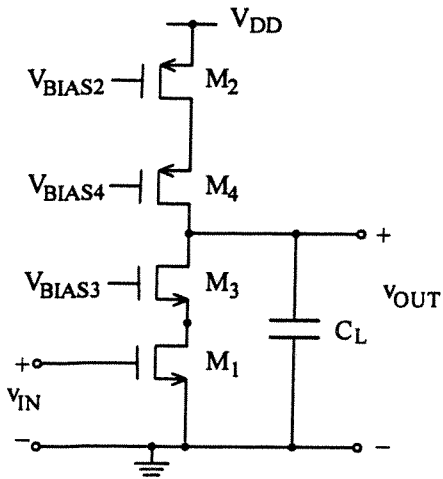


SSEC

NMOS-part

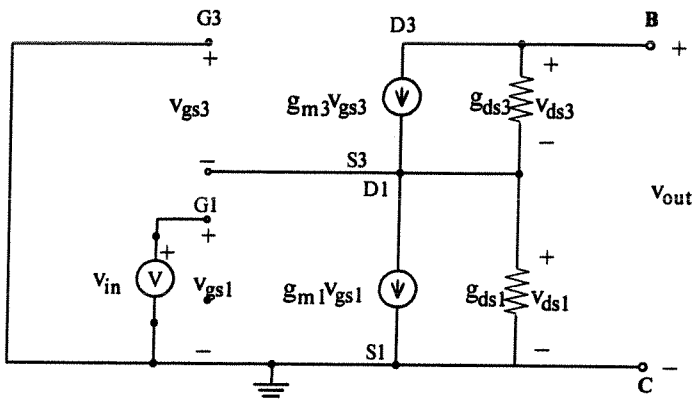


SSEC

PMOS-part

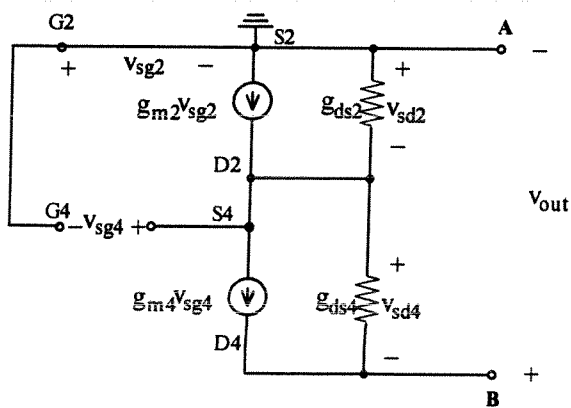


COMMON SOURCE AMPLIFIER
WITH CASCODE

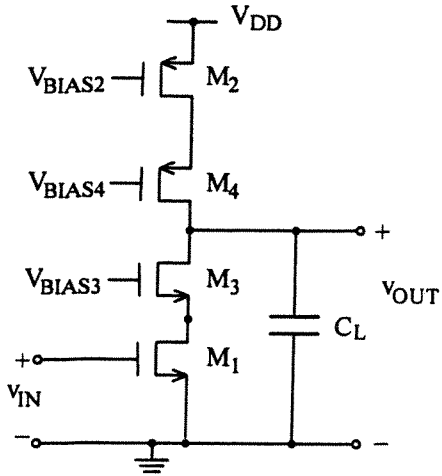

Determine r_{out}


SSEC

NMOS-part

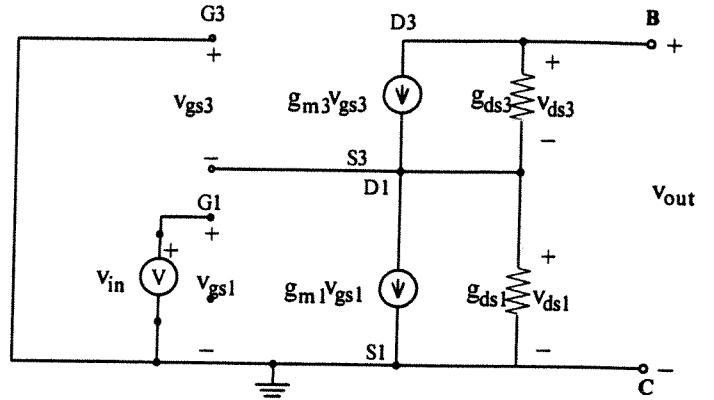


SSEC

NMOS-part

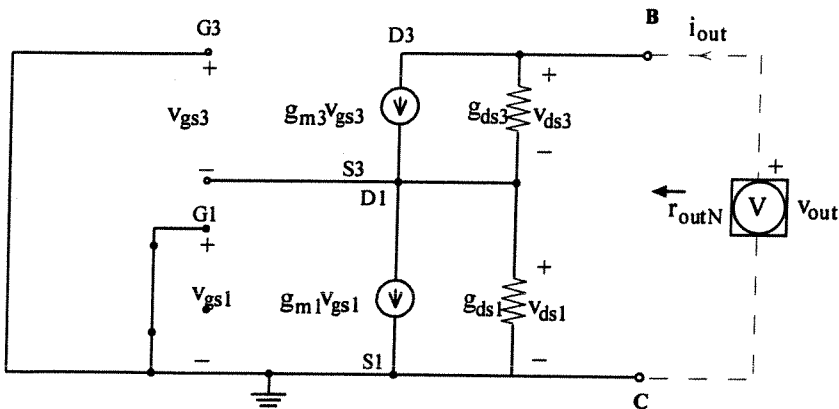


SSEC

PMOS-part

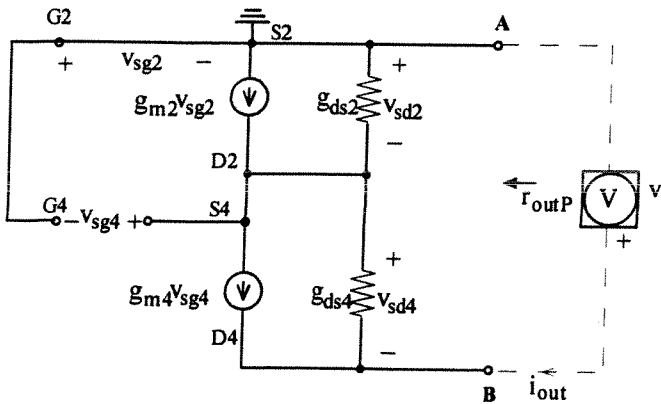

 
COMMON SOURCE AMPLIFIER
WITH CASCODE. EXTRA BIAS



Determine r_{out}


SSEC





NMOS-part

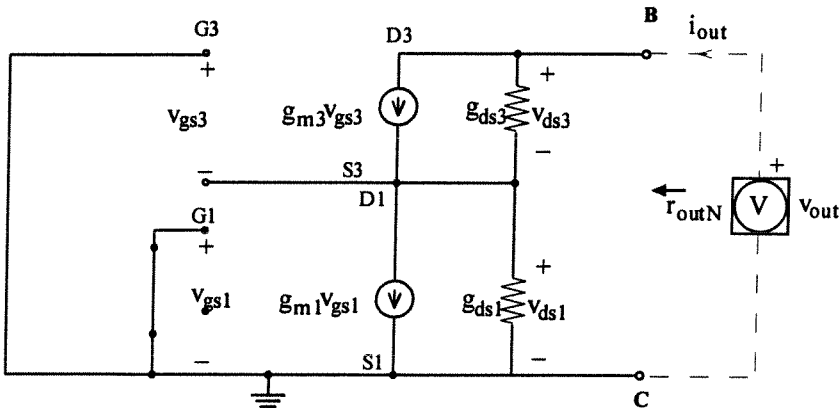


SSEC


PMOS-part

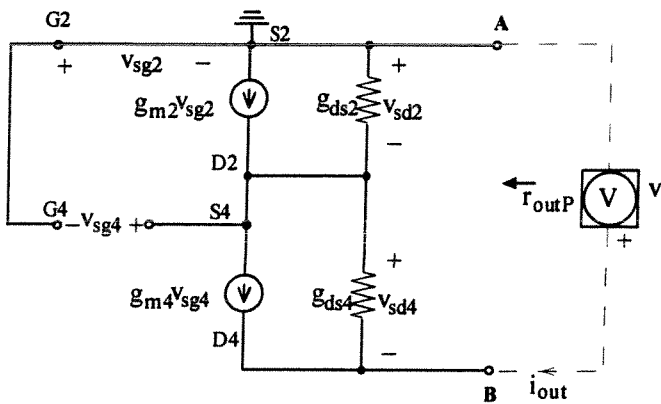

    
 
CURRENT MIRROR**SMALL SIGNAL EQUIVALENT CIRCUIT (SSEC)****CASCODE CURRENT MIRROR****WIDE-SWING CURRENT MIRROR**



SSEC

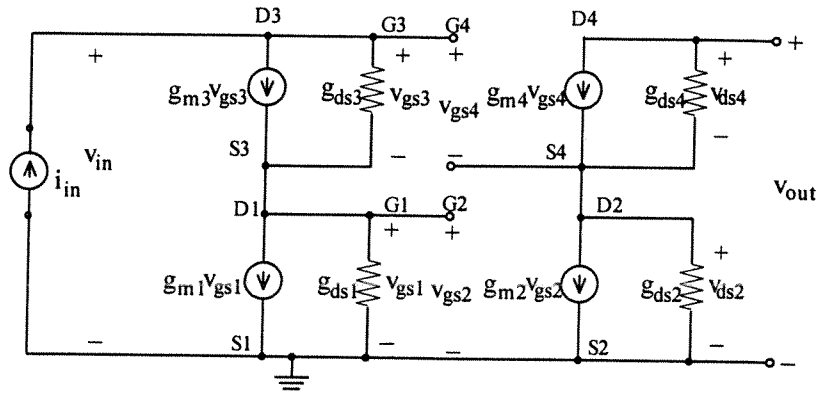


Determine r_{out}

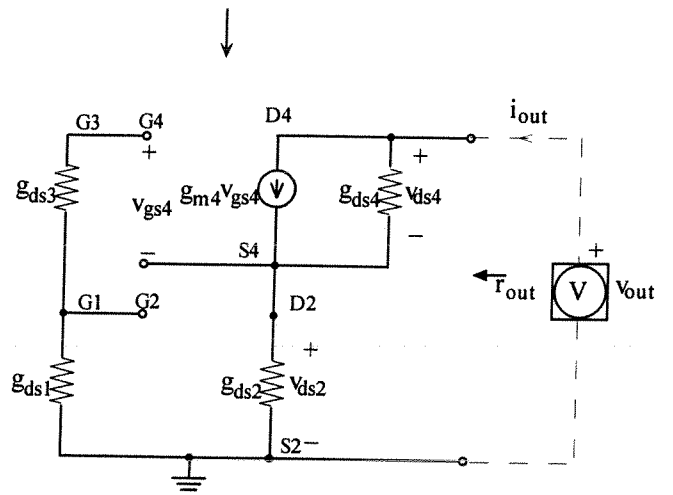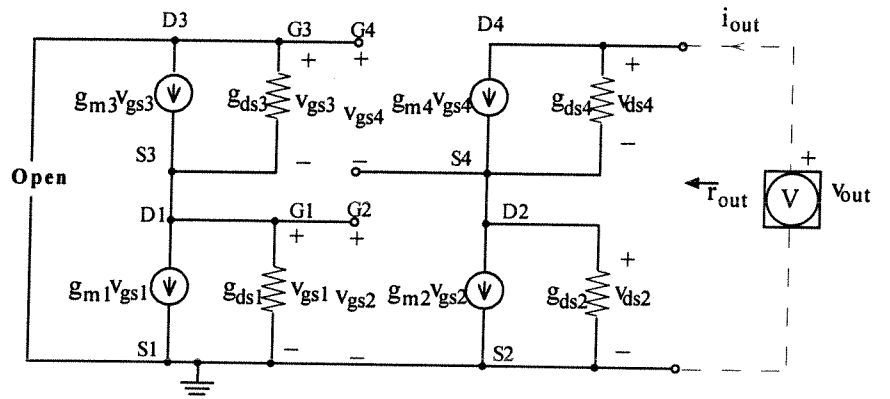

DIFFERENTIAL GAINSTAGE

(Large signal analysis)

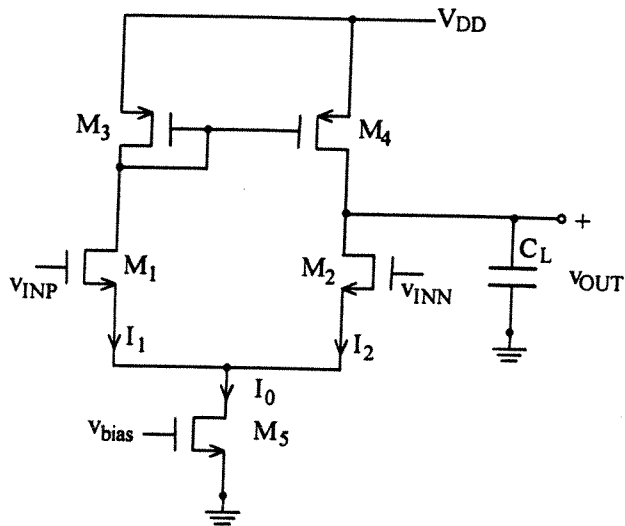

- Assumptions:**
- 1) All transistors saturated
 - 2) $V_{INP} = V_{INN} = V_{IN}$ (COMMON MODE)

$$\text{CMR (Common Mode Range)} = [V_{IN \min}, V_{IN \max}]$$

$$\text{OR (Output Range)} = [V_{OUT \min}, V_{OUT \max}]$$


$$V_{IN \min} = V_{DS5} + V_{GS1} = V_{eff5} + V_{eff1} + V_{t1} = \sqrt{\frac{I_0}{\alpha_5}} + \sqrt{\frac{I_0/2}{\alpha_1}} + V_{t1}$$

$$\begin{aligned} V_{IN \max} &= V_{DD} - V_{SG3} - V_{DS1} + V_{GS1} = V_{DD} - V_{eff3} - V_{t3} - V_{eff1} + V_{eff1} + V_{t1} = \\ &= V_{DD} - \sqrt{\frac{I_0/2}{\alpha_3}} - V_{t3} + V_{t1} \end{aligned}$$


$$V_{OUT \min} = V_{DS5} + V_{DS2} = V_{eff5} + V_{eff1} = \sqrt{\frac{I_0}{\alpha_5}} + \sqrt{\frac{I_0/2}{\alpha_2}}$$

$$V_{OUT \max} = V_{DD} - V_{SD4} = V_{DD} - V_{eff4} = V_{DD} - \sqrt{\frac{I_0/2}{\alpha_4}}$$

DIFFERENTIAL GAINSTAGE

 

SSEC

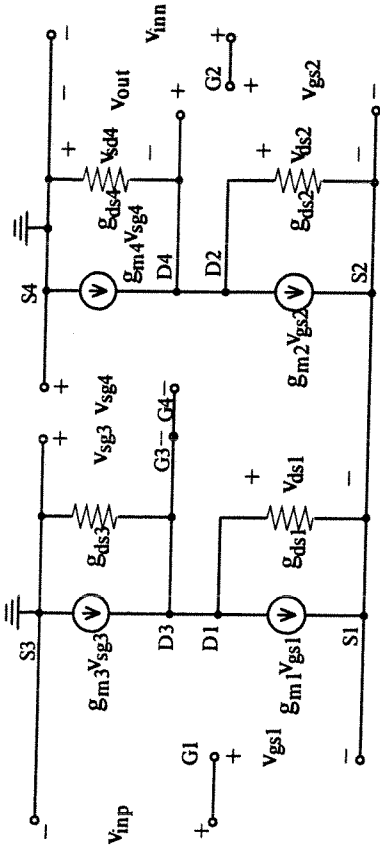

Determine $\frac{v_{out}}{v_{inp} - v_{inn}}$ for differential gain stage.

1) Introduce variables v_x (at node x, i.e. node D1,D3) and v_y (at node y, i.e. node S1,S2).

2) Express $v_{gs1}, v_{gs2}, v_{sg3} (=v_{sd3}), v_{sg4}, v_{ds1}, v_{ds2}, v_{sd4}$ in $v_{inp}, v_{inn}, v_x, v_y$ and v_{out} .

$$\begin{aligned} v_{gs1} &= v_{g1} - v_{s1} = v_{inp} - v_y & v_{ds1} &= v_x - v_y \\ v_{gs2} &= v_{g2} - v_{s2} = v_{inn} - v_y & v_{ds2} &= v_{out} - v_y \\ v_{sg3} &= -v_x & v_{sd3} &= v_{sg3} = -v_x \\ v_{sg4} &= v_{sg3} = -v_x & v_{sd4} &= -v_{out} \end{aligned}$$

3) Nodal analysis on node x, node out and gnd.

$$\text{Node x: } g_{m3}(-v_x) - g_{ds3}v_x - g_{m1}(v_{inp} - v_y) - g_{ds1}(v_x - v_y) = 0 \quad (1)$$

$$\text{Node out: } g_{m4}(-v_x) - g_{ds4}v_{out} - g_{m2}(v_{inn} - v_y) - g_{ds2}(v_{out} - v_y) = 0 \quad (2)$$

$$\text{gnd.: } -g_{m3}(-v_x) + g_{ds3}v_x - g_{m4}(-v_x) + g_{ds4}v_{out} = 0 \quad (3)$$

$$(3) \Rightarrow v_x = \frac{-g_{ds4}v_{out}}{g_{m3} + g_{m4} + g_{ds3}} \quad (4)$$

$$(1),(2) \Rightarrow v_x(g_{m3} - g_{m4} + g_{ds3}) - g_{ds4}v_{out} + g_{m1}v_{inp} - g_{m2}v_{inn} - v_y(g_{m1} - g_{m2}) + g_{ds1}v_x - g_{ds2}v_{out} - v_y(g_{ds1} - g_{ds2}) = 0 \quad (5)$$

4) Assume $g_{ds1} = g_{ds2}, g_{ds3} = g_{ds4}, g_{m1} = g_{m2}$ and $g_{m3} = g_{m4}$

$$(5) \Rightarrow v_x g_{ds4} - g_{ds4}v_{out} + g_{m1}(v_{inp} - v_{inn}) + g_{ds2}(v_x - v_{out}) = 0 \quad (6)$$

$$(4),(6) \Rightarrow g_{m1}(v_{inp} - v_{inn}) = v_{out} \left(g_{ds2} + \frac{g_{ds2}g_{ds4}}{g_{m3} + g_{m4} + g_{ds3}} + g_{ds4} + \frac{g_{ds4}^2}{g_{m3} + g_{m4} + g_{ds3}} \right) \quad (7)$$

But $g_{ds3} = g_{ds4}$ and $g_{m3} = g_{m4}$ which gives:

$$(7) \Rightarrow g_{m1}(v_{inp} - v_{inn}) = v_{out} \left(g_{ds2} + \frac{g_{ds2}g_{ds4}}{2g_{m4} + g_{ds4}} + g_{ds4} + \frac{g_{ds4}^2}{2g_{m4} + g_{ds4}} \right) \quad (8)$$

$$(8) \Rightarrow g_{m1}(v_{inp} - v_{inn}) = v_{out} g_{ds2} \left(1 + \frac{g_{ds4}}{2g_{m4} + g_{ds4}} \right) + v_{out} g_{ds4} \left(1 + \frac{g_{ds4}}{2g_{m4} + g_{ds4}} \right) \quad (9)$$

$$(9) \Rightarrow g_{m1}(v_{inp} - v_{inn}) = v_{out} \left(1 + \frac{g_{ds4}}{2g_{m4} + g_{ds4}} \right) (g_{ds2} + g_{ds4}) \quad (10)$$

$$(10) \Rightarrow g_{m1}(v_{inp} - v_{inn}) = v_{out} \left(\frac{2g_{m4} + 2g_{ds4}}{2g_{m4} + g_{ds4}} \right) (g_{ds2} + g_{ds4}) \quad (11)$$

$$(11) \Rightarrow \frac{v_{out}}{v_{inp} - v_{inn}} = \frac{g_{m1}(2g_{m4} + g_{ds4})}{2(g_{ds2} + g_{ds4})(g_{m4} + g_{ds4})} \approx \frac{g_{m1}}{g_{ds2} + g_{ds4}}$$

PERFORMANCE MEASURES FOR DIFFERENTIAL GAIN STAGE

LARGE SIGNAL ANALYSIS:

- Common Mode Range, $CMR = [V_{inmin}, V_{inmax}]$
- Output range, $OR = [V_{outmin}, V_{outmax}]$
- Slew Rate, $SR = \max \left\{ \frac{dv_{out}}{dt} \right\}$

SMALL SIGNAL ANALYSIS:


- Common Mode Rejection Ratio, $CMRR = 20 \cdot 10 \log \frac{A_d}{A_{cm}}$
- Power Supply Rejection Ratio +, $PSRR_+ = 20 \cdot 10 \log \frac{A_d}{A_{V_{dd} \rightarrow V_{out}}}$
- Power Supply Rejection Ratio -, $PSRR_- = 20 \cdot 10 \log \frac{A_d}{A_{gnd \rightarrow V_{out}}}$

- A_d = Amplification for differential input signals
- A_{cm} = Amplification for common-mode input signals
- $A_{V_{dd} \rightarrow V_{out}}$ = Amplification for variations in $+V_{dd}$ from V_{dd} to V_{out}
- $A_{gnd \rightarrow V_{out}}$ = Amplification for variations in ground from ground to V_{out}

To determine $A_{V_{dd} \rightarrow V_{out}}$ set the AC-input signal to zero and introduce an AC-source at V_{dd+} . $A_{gnd \rightarrow V_{out}}$ determines in the same way by setting the AC-input signal to zero and introduce an AC-source at V_{dd-} (ground).

DETERMINATION OF SLEW-RATE

To determine Slew-Rate (SR) for the differential gain-stage below, apply a square-pulse on V_{INP} and an inverted square-pulse on V_{INN} . Figure a) gives phase 1, when V_{INP} grows instantaneously from 0 to E and V_{INN} at the same time instantaneously goes from E to 0. Figure b) shows phase II that starts with V_{INP} instantaneously decreasing from E to 0 and V_{INN} instantaneously increasing from 0 to E . E is larger than V_{tn} ($E > V_{tn}$). Transistors M1 and M3 are identical as well as M2 and M4.

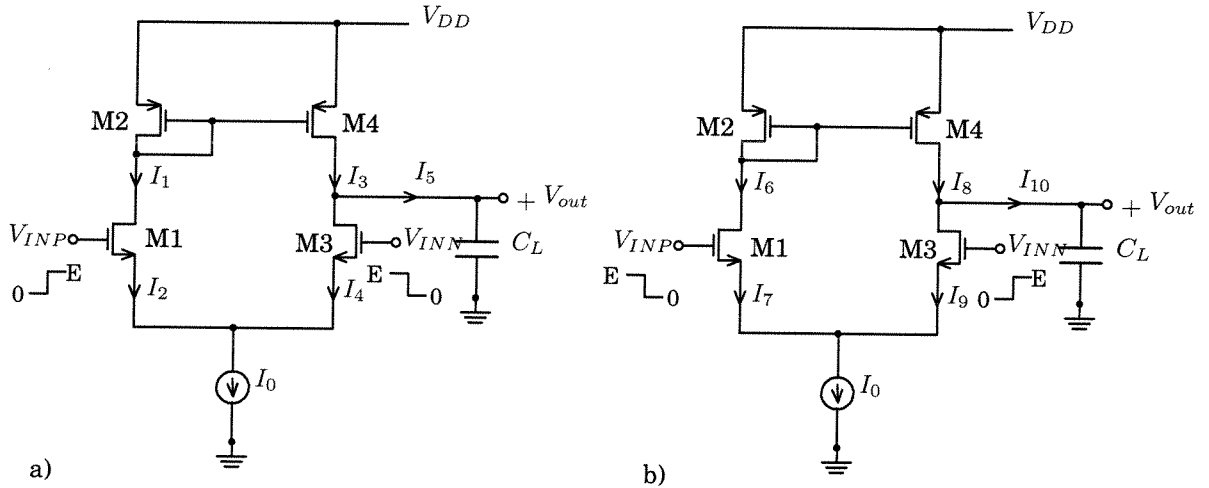

- Phase I:
- $V_{INP} = +E, V_{INN} = 0 \Rightarrow$ M1 conducts and M3 blocks.
 - M3 blocks $\Rightarrow I_4 = 0$
M1 conducts $\Rightarrow I_1 = I_2 = I_0$
 - M2 and M4 is a current mirror and as M2 and M4 are identical $I_3 = I_1 = I_0$
 - M3 blocks ($I_4 = 0$) $\Rightarrow I_5 = I_3 = I_0$
- Phase II:
- $V_{INP} = 0, V_{INN} = +E \Rightarrow$ M1 blocks and M3 conducts.
 - M1 blocks $\Rightarrow I_6 = I_7 = 0$
 - M2 and M4 is a current mirror $\Rightarrow I_8 = I_6 = 0$
 - M3 conducts $\Rightarrow I_9 = I_0$
 - $I_8 = 0$ and $I_9 = I_0 \Rightarrow I_{10} = -I_9 = -I_0$

$$\text{Definition: Slew-Rate (SR)} = \max \frac{dv_{out}(t)}{dt}$$

For capacitor C_L :

$$i_{CL}(t) = C_L \frac{dv_{CL}(t)}{dt} = C_L \frac{dv_{out}(t)}{dt} \Rightarrow \frac{dv_{out}}{dt} = \frac{i_{CL}(t)}{C_L}$$

Thus, maximum value of $\frac{dv_{out}(t)}{dt}$ obtains for maximum value of $i_{CL}(t)$, which has been shown above to be I_0 .

$$\text{I.e. Slew-Rate} = \underline{\underline{\frac{I_0}{C_L}}}$$