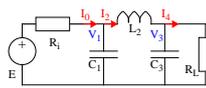


### Lektion 7 – Extra

Uppgift 1.22



Sambanden:

$$I_0 = \frac{E - V_1}{R_1}$$

$$V_1 = \frac{1}{sC_1}(I_0 - I_2)$$

$$I_2 = \frac{V_1 - V_3}{sL_2}$$

$$V_3 = \frac{1}{sC_3}(I_2 - I_4)$$

$$I_4 = \frac{V_3}{R_L}$$

Normerade med ett R :

$$RI_0 = \frac{R}{R_1}(E - V_1)$$


$$V_1 = \frac{1}{sC_1 R}(RI_0 - RI_2)$$

$$RI_2 = \frac{R}{sL_2}(V_1 - V_3)$$



$$V_3 = \frac{1}{sC_3 R}(RI_2 - RI_4)$$

$$RI_4 = \frac{R}{R_L} V_3$$

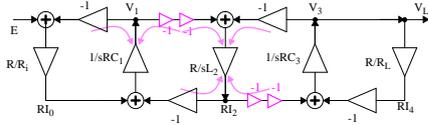Ur dessa ekvationer skisseras ett signalflödesschema:



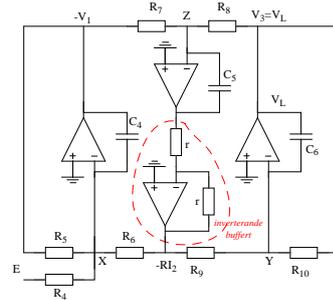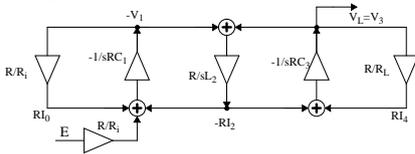Nätet modifieras genom att dra inverterare (-1) genom nätet:



Leapfrog SignalflödesschemaResultat

$$[-V_1]_E = \frac{1}{sC_4} \cdot \frac{E}{R_4} [-V_1]_E = \frac{R}{R_4} \cdot \frac{E}{sRC_1} = -\frac{E}{sRC_1} C_4 R_4 = C_1 R_4$$

$$[-V_1]_{-V_1} = \frac{1}{sC_4} \cdot \frac{V_1}{R_5} [-V_1]_{-V_1} = \frac{R}{R_5} \cdot \frac{-V_1}{sRC_1} = -\frac{V_1}{sRC_1} C_4 R_5 = C_1 R_5$$

$$[-V_1]_{-RI_2} = -\frac{1}{sC_4} \cdot \frac{-RI_2}{R_6} [-V_1]_{-RI_2} = -\frac{1}{sRC_1} (-RI_2) C_4 R_6 = C_1 R_6$$


$$[-RI_2]_{-V_1} = \frac{(-1)}{sC_5} \cdot \frac{-V_1}{R_7} [-RI_2]_{-V_1} = \frac{R}{sL_2} \cdot \frac{(-V_1)}{C_5 R_7} = L_2 / R$$

$$[-RI_2]_{V_3} = \frac{(-1)}{sC_5} \cdot \frac{V_3}{R_8} [-RI_2]_{V_3} = \frac{R}{sL_2} V_3 C_5 R_8 = L_2 / R$$

$$[V_3]_{-RI_2} = -\frac{1}{sC_6} \cdot \frac{-RI_2}{R_9} [V_3]_{-RI_2} = -\frac{1}{sRC_3} (-RI_2) C_6 R_9 = C_3 R_9$$

$$[V_3]_{V_3} = -\frac{1}{sC_6 R_{10}} \cdot \frac{V_3}{R_{10}} [V_3]_{V_3} = -\frac{1}{sRC_3 R_L} V_3 = -\frac{V_3}{sC_3 R_L} C_6 R_{10} = C_3 R_{10}$$

Uppgift 1.26

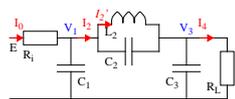

Samband:

$$I_0 = \frac{E - V_1}{R_1}$$

$$V_1 = \frac{1}{sC_1}(I_0 - I_2)$$

$$I_2 = \frac{1}{L_2} \parallel \frac{1}{C_2}(V_1 - V_3)$$

$$V_3 = \frac{1}{sC_3}(I_2 - I_4)$$

$$I_4 = \frac{V_3}{R_L}$$

Normerade med R :

$$RI_0 = \frac{R}{R_1}(E - V_1)$$

$$V_1 = \frac{1}{sRC_1}(RI_0 - RI_2)$$

$$RI_2 = \frac{R}{sL_2 / (1 + s^2 L_2 C_2)}(V_1 - V_3)$$

$$V_3 = \frac{1}{sRC_3}(RI_2 - RI_4)$$

$$RI_4 = \frac{R}{R_L} V_3$$





Formlerna för I2 modifieras till:

$$RI_2 = RI_2' + sRC_2(V_1 - V_3) \text{ och } RI_2' = \frac{R}{sL_2}(V_1 - V_3)$$

På detta sätt kan uttrycket för RI2 elimineras i ekvationerna för V1 och V3:

$$V_1 = \frac{1}{sR(C_1 + C_2)}(RI_2' - RI_2) + \frac{C_2}{C_1 + C_2} V_3$$
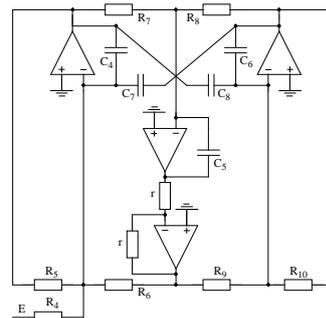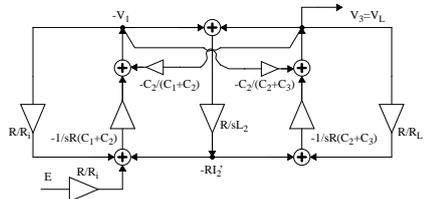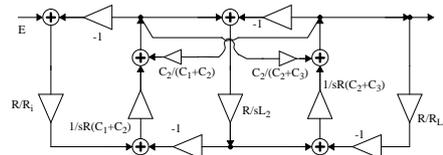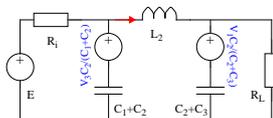
$$V_3 = \frac{1}{sR(C_2 + C_3)}(RI_2' - RI_4) + \frac{C_2}{C_2 + C_3} V_1$$



Aktivt leapfrogfilter	Signalflödesschema	Resultat
$[-V_1]_E = -\frac{1}{sC_4} \cdot \frac{E}{R_4}$	$[-V_1]_E = \frac{R}{R_i} \cdot \frac{E}{sR\alpha_1} = -\frac{E}{sR_i\alpha_1}$	$C_4R_4 = \alpha_1R_i$
$[-V_1]_{-V_1} = -\frac{1}{sC_4} \cdot \frac{V_1}{R_5}$	$[-V_1]_{-V_1} = \frac{R}{R_i} \cdot \frac{-V_1}{sR\alpha_1} = -\frac{V_1}{sR_i\alpha_1}$	$C_4R_5 = \alpha_1R_i$
$[-V_1]_{-RI_2} = -\frac{1}{sC_4} \cdot \frac{-RI_2}{R_6}$	$[-V_1]_{-RI_2} = -\frac{1}{sR\alpha_1} (-RI_2)$	$C_4R_6 = \alpha_1R$
$[-V_1]_{-V_3} = -\frac{C_7}{C_4} V_3$	$[-V_1]_{-V_3} = -\frac{C_2}{\alpha_1} V_3$	$C_4C_2 = C_7\alpha_1$
$[-RI_2]_{-V_1} = -\frac{(-1)}{sC_5} \cdot \frac{-V_1}{R_7}$	$[-RI_2]_{-V_1} = \frac{R}{sL_2} (-V_1)$	$C_5R_7 = L_2/R$
$[-RI_2]_{V_3} = -\frac{(-1)}{sC_5} \cdot \frac{V_3}{R_8}$	$[-RI_2]_{V_3} = \frac{R}{sL_2} V_3$	$C_5R_8 = L_2/R$
$[V_3]_{-RI_2} = \frac{1}{sC_6} \cdot \frac{-RI_2}{R_9}$	$[V_3]_{-RI_2} = -\frac{1}{sR\alpha_2} (-RI_2)$	$C_6R_9 = \alpha_2R$
$[V_3]_{V_3} = -\frac{1}{sC_6R_{10}} V_3$	$[V_3]_{V_3} = \frac{1}{sR\alpha_2R_L} R V_3 = -\frac{V_3}{s\alpha_2R_L}$	$C_6R_{10} = \alpha_2R_L$
$[V_3]_{-V_1} = -\frac{C_8}{C_6} (-V_1)$	$[V_3]_{-V_1} = -\frac{C_2}{\alpha_2} (-V_1)$	$C_2C_6 = C_8\alpha_2$

Där  $\alpha_1 = C_1 + C_2$  och  $\alpha_2 = C_2 + C_3$ .