
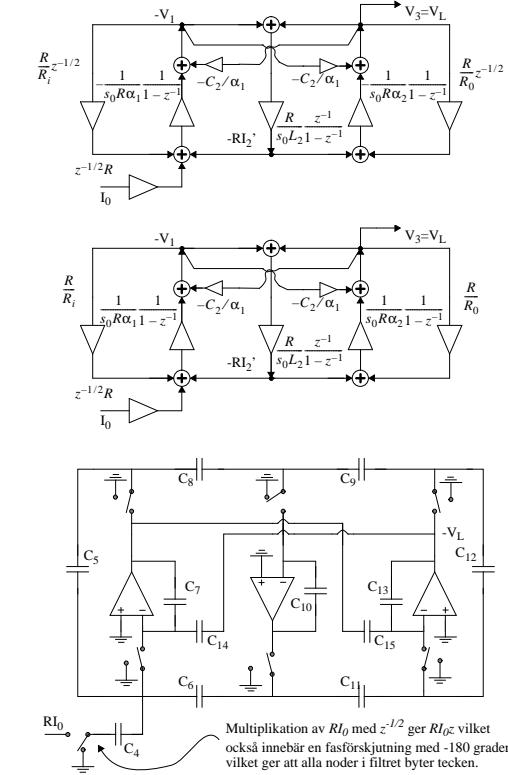


## Lektion 9 – OH

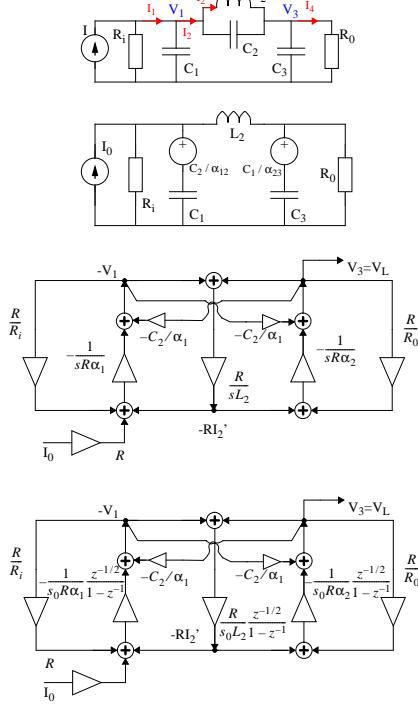

SC-filter	Signalflödesschema	Resultat
$[-V_1]_E = \frac{C_4}{C_7} \frac{z^{-1/2}}{1-z^{-1}}$	$[-V_1]_E = \frac{1}{s_0 R \alpha_1} \frac{z^{-1/2}}{1-z^{-1}}$	$\frac{C_4}{C_7} = \frac{1}{s_0 R \alpha_1}$
$[-V_1]_{-RI_0'} = \frac{C_6}{C_7} \frac{1}{1-z^{-1}}$	$[-V_1]_{-RI_0'} = \frac{1}{s_0 R \alpha_1}$	$\frac{C_6}{C_7} = \frac{1}{s_0 R \alpha_1}$
$[-V_1]_{-V_1} = \frac{C_5}{C_7} \frac{1}{1-z^{-1}}$	$[-V_1]_{-V_1} = \frac{-1}{s_0 R \alpha_1} \frac{R}{R_i} = \frac{-1}{s_0 R \alpha_1}$	$\frac{C_5}{C_7} = \frac{1}{s_0 R \alpha_1}$
$[-RI_2']_{-V_1} = \frac{C_8}{C_{10}} \frac{z^{-1}}{1-z^{-1}}$	$[-RI_2']_{-V_1} = \frac{R}{s_0 L_2} \frac{z^{-1}}{1-z^{-1}}$	$\frac{C_8}{C_{10}} = \frac{R}{s_0 L_2}$
$[-RI_2']_{V_1} = \frac{C_9}{C_{10}} \frac{z^{-1}}{1-z^{-1}}$	$[-RI_2']_{V_1} = \frac{R}{s_0 L_2} \frac{z^{-1}}{1-z^{-1}}$	$\frac{C_9}{C_{10}} = \frac{R}{s_0 L_2}$
$[V_3]_{-RI_0'} = \frac{C_{11}}{C_{13}} \frac{1}{1-z^{-1}}$	$[V_3]_{-RI_0'} = \frac{R}{R_L} \cdot \frac{1}{s_0 R C_3} \cdot \frac{1}{1-z^{-1}}$	$\frac{C_{11}}{C_{13}} = \frac{1}{s_0 R_L \alpha_3}$
$[V_3]_{V_1} = \frac{C_{12}}{C_{13}} \frac{1}{1-z^{-1}}$	$[V_3]_{V_1} = \frac{R}{R_L} \cdot \frac{1}{s_0 R C_3} \cdot \frac{1}{1-z^{-1}}$	$\frac{C_{12}}{C_{13}} = \frac{1}{s_0 R_L \alpha_3}$

För återkopplingarna gäller att:

$$\begin{aligned} [-V_1]_{V_3} &= \frac{C_{14}}{C_7} & [-V_1]_{V_3} &= \frac{C_2}{\alpha_1} & \frac{C_{14}}{C_7} &= \frac{C_2}{\alpha_1} \\ [V_3]_{-V_1} &= -\frac{C_{15}}{C_{13}} & [V_3]_{-V_1} &= -\frac{C_2}{\alpha_3} & \frac{C_{15}}{C_{13}} &= \frac{C_2}{\alpha_3} \end{aligned}$$

Dessutom kan antas att  $R_i = R_L = R$

Skalning:

