



# Lecture 10, ANIK

## Data converters 2

# What did we do last time?

## Data converter fundamentals

Quantization noise

Signal-to-noise ratio

## ADC and DAC architectures

Overview, since literature is more useful explaining many, many different architectures

# What will we do today?

A quick glance at the pipelined ADC again

Sigma-delta modulators

- Oversampling as such

- Noise-shaping

- Modulator structures


Wrap-up

- Some comments on the course
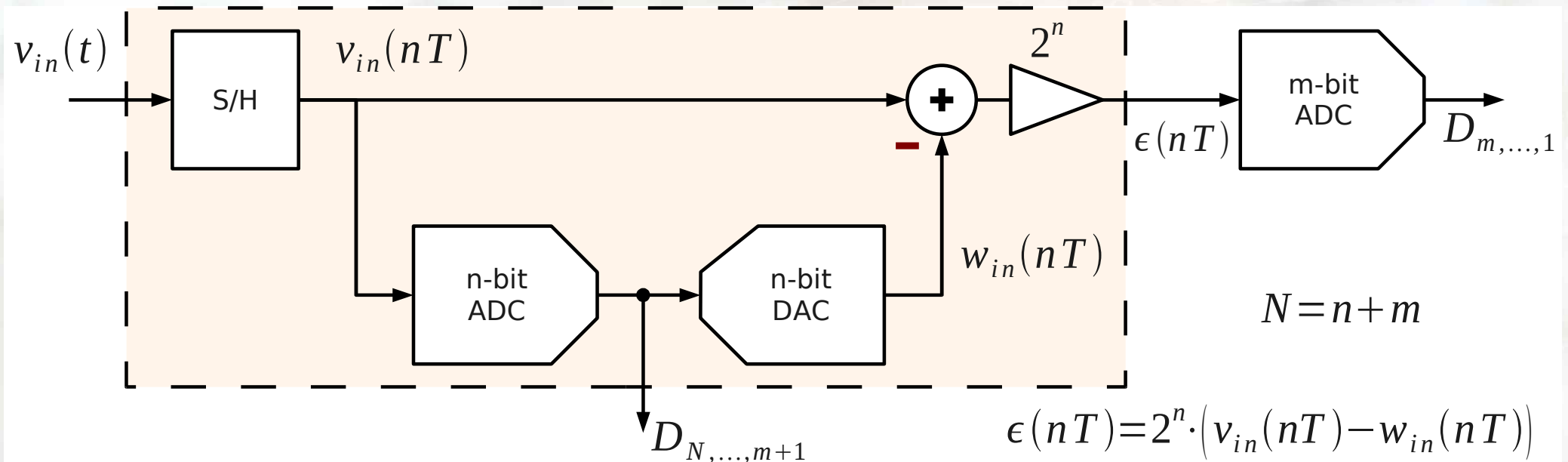
# First - the subranging ADC - Basic operation

The converter "zooms" a range and converts the residue.

If flash is used as subconverter, there is only  $2^n + 2^m$  comparators




Another analog adder is required as well as a gain circuit, which limits the speed.

# Pipelined ADC in one picture

Multiple subranging ADC in series

A series of refinements, zoom-ins, of the convertible range


Assume same range in each stage

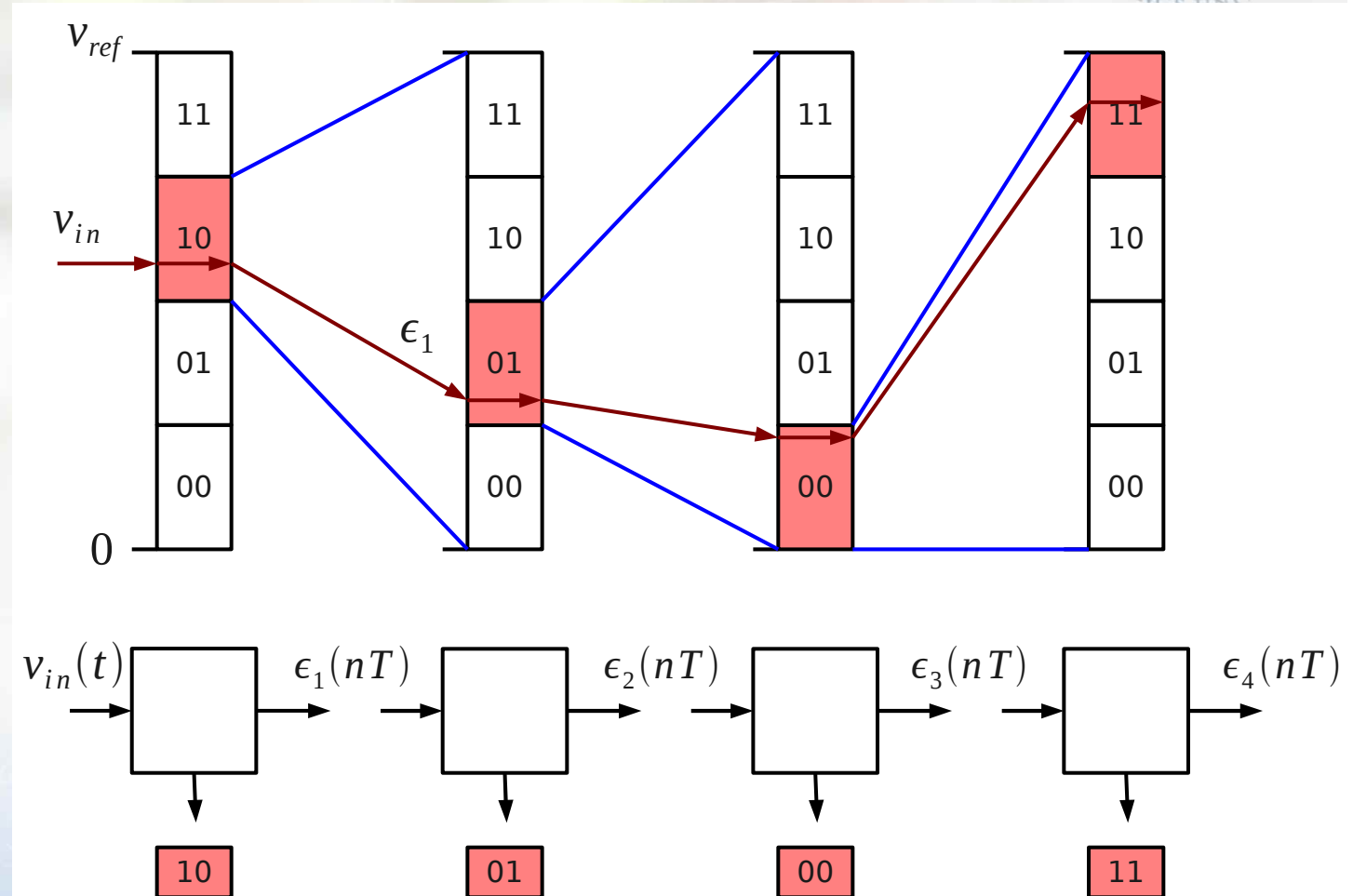


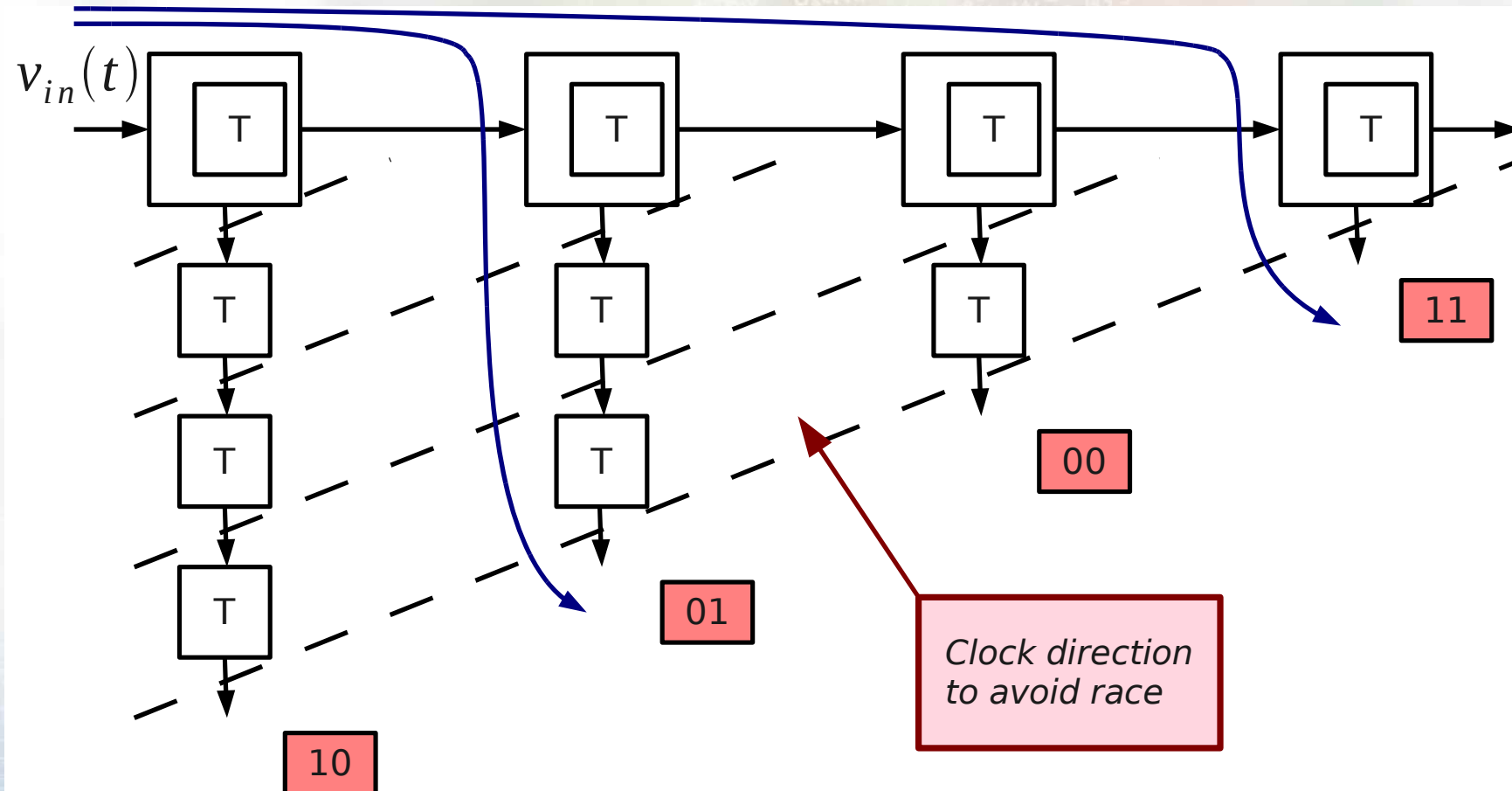
# Pipelined ADC - delays


Balance the delays and "cleverly" distribute the clock to avoid race



A pipelined ADC will have longer latency
 
# Pipelined ADC - sensitive towards errors


Any misinterpreted level quickly diverges and never recovers!



Overlap can be digitally corrected (without training!)
 
# Pipelined ADC - error correction

Increase the number of stages and reduce overlap, i.e., decrease the scaling factor,  $2^n$ . Now, less likely to diverge and is able to recover.




More stages are required, but typically worth it


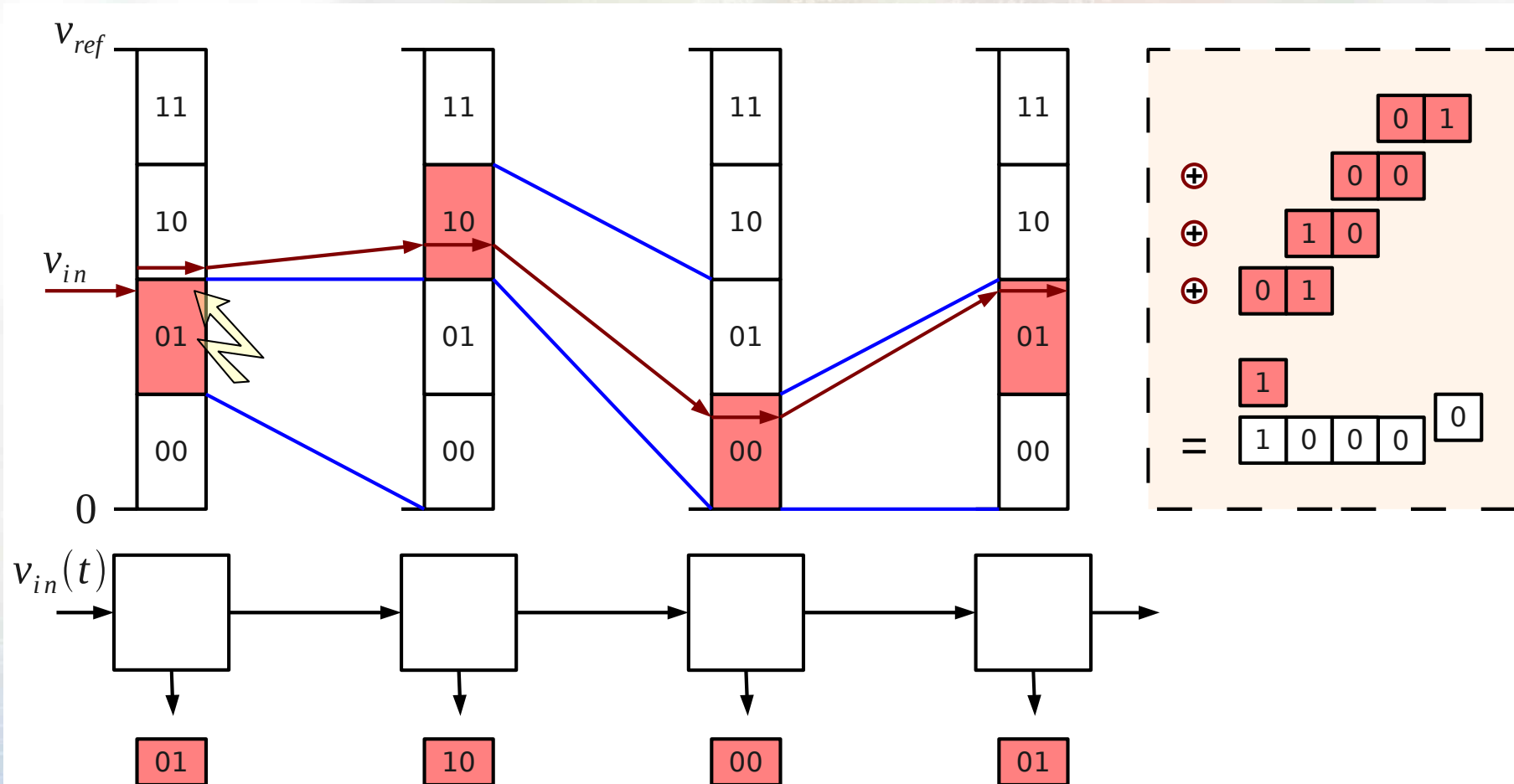
# Pipelined ADC - error correction cont'd



Trivial circuitry to retrieve the most likely code!




# Quantization noise revisited 1

Assume signal-independent (not true for a low number of bits)

Assume white noise, uniformly distributed in  $\left[-\frac{\Delta}{2}, \frac{\Delta}{2}\right]$ , with  $\Delta = \frac{V_{ref}}{2^N}$

Noise power spectral density (PSD)

 

## Quantization noise revisited 2 (quiz ...)

Noise power given by the sigma:  $P_{q, tot} = \sigma^2 = \frac{\Delta^2}{12}$

Signal-to-quantization-noise ratio:  $SQNR = \frac{P_{avg}}{P_{q, tot}} = \frac{P_{pk}}{P_{q, tot} \cdot PAR}$

With values inserted

$$SQNR = \frac{\frac{1}{4} \cdot V_{ref}^2}{\frac{1}{12} \cdot \left(\frac{V_{ref}}{2^N}\right)^2 \cdot PAR} = \frac{3 \cdot 2^{2N}}{PAR}$$

In logarithmic scale


$SQNR \approx 6.02 \cdot N + 4.77 - PAR = 6.02 \cdot N + 1.76$  for our sinusoid.

# Oversampling 1

Assume we have headroom to increase the sample frequency

Apply filtering to remove the excessive noise

 We can effectively increase the performance! Or ... ?



# Oversampling converters

Noise power over the entire Nyquist range

$$\text{SQNR} = 6.02 \cdot N + 1.76 \text{ [dB]}$$


Assume we oversample, or put it this way, we have a anti-aliasing/reconstruction filter there anyway. We get

$$\text{SQNR} = 6.02 \cdot N + 1.76 + 10 \cdot \log_{10} \frac{f_s}{2 \cdot f_{bw}}$$

where the oversampling ratio is

$$\text{OSR} = \frac{f_s}{2 \cdot f_{bw}}$$

 "For each doubling of the sample frequency, we gain 3 dB"





# Oversampling converters

Assume we take a lower order converter to start with

$$\text{ENOB} = \frac{\text{SQNR} - 1.76}{6.02} = N + \frac{10 \cdot \log_{10} \text{OSR}}{6.02}$$

A 16-bit resolution can be obtained using a 12-bit converter if we oversample 256 times.

For some applications not an impossible scenario

A 16-bit resolution can be obtained using a 1-bit converter if we oversample 1073741824 times.

1 Hz would require 1 GHz of sampling frequency.

Luckily, there are more effective ways ...

# Attacking the filtering problem



Ideal reconstruction and ideal sampling requires ideal filters

Increase your frequency range

DAC: Interpolation and upsampling


ADC: Decimation and downsampling

Drawbacks

Higher power consumption

More difficult to design

FOM limit

 

# Digital implementation




Interpolation

Example

Decimation

Example

 

SCIENCEPHOTOLIBRARY

# Oversampling converters, cont'd



Since we are introducing another converter, and increasing the frequency - why not spice it a bit?


Create a converter that can also shape the new added noise

This can be done through sigma-delta modulation

High-pass filters the added noise

All-pass filters the signal

 Designing a sigma-delta modulator is very much a filtering problem



Notice that a DAC can never increase the number of bits!



# Sigma-delta converters, cont'd

Consider the transfer function

$$Y = Q + A \cdot \underbrace{(X - B \cdot Y)}_{\epsilon} \Rightarrow Y = \frac{Q + A \cdot X}{1 + A \cdot B}$$

Noise and signal transfer functions

$$\text{NTF} = \frac{1}{1 + A \cdot B}, \quad \text{STF} = \frac{A}{1 + A \cdot B}$$

For example, A is an integrator and B is unity:

$$\text{NTF} = 1 - z^{-1}, \quad \text{STF} = z^{-1}$$

Order of the filters and oversampling determines the SQNR. Ideally, we get:

$$\text{SQNR} = 6.02 \cdot N + 1.76 + 10 \cdot (2 \cdot L + 1) \cdot \log_{10} \text{OSR} - 10 \cdot \log_{10} \frac{\pi^{2L}}{2L + 1}$$



# Sigma-delta converters, cont'd

**First-order modulator.** 16-bit resolution can be obtained using a:

12-bit converter if we oversample 16 times

1-bit converter if we oversample 1522 times (c.f. 1G-times before)

**Second-order modulator.** 16-bit resolution ...

12-bit converter if we oversample 6 times.

1-bit converter if we oversample 116 times.

**Third-order modulator.** 16-bit resolution ...

12-bit converter if we oversample 5 times.

1-bit converter if we oversample 40 times.

**Momentum slightly lost and filtering problem recreated!**

# Sigma-delta, the audio example



HIFI

16 bits, i.e., 100 dB


Signal bandwidth

22 kHz

Choose as few bits in coarse quantizer as possible

Choose minimum possible order

Choose minimum possible sample frequency

 

What configurations are possible?

# Sigma-delta, the audio example

Plugging the formula into MATLAB

$$\text{SQNR} = 6.02 \cdot N + 1.76 + 10 \cdot (2 \cdot L + 1) \cdot \log_{10} \text{OSR} - 10 \cdot \log_{10} \frac{\pi^{2L}}{2L + 1}$$

gives us

```
>> antikAudioSigmaDelta
```

```
SNR = 100.2442 dB, L = 2, M = 1, OSR = 128 fs = 5.632 MHz.      *****  
SNR = 115.2957 dB, L = 2, M = 1, OSR = 256 fs = 11.264 MHz.  
  
SNR = 106.2642 dB, L = 2, M = 2, OSR = 128 fs = 5.632 MHz.  
SNR = 112.2842 dB, L = 2, M = 3, OSR = 128 fs = 5.632 MHz.  
SNR = 103.2527 dB, L = 2, M = 4, OSR = 64 fs = 2.816 MHz.  
  
SNR = 112.8346 dB, L = 3, M = 1, OSR = 64 fs = 2.816 MHz.  
SNR = 103.8025 dB, L = 3, M = 3, OSR = 32 fs = 1.408 MHz.  
SNR = 109.8225 dB, L = 3, M = 4, OSR = 32 fs = 1.408 MHz.
```

# What did we do today?

Sigma-delta modulators

Oversampling as such

Noise-shaping

Modulator structures

Wrap-up

Some comments on the course

# What will we do next time?



Exam ...