



# Lecture 2, ANIK

CMOS, Analog building blocks  
Monday, January 23, 2012 in P26



# What did we do last time?

Introduction to the course

Labs, quizzes, exam, etc.

The transistor

Operating regions (cut-off, linear, saturation)

Functionality (output current as a function of the width and length)

First amplifier and parameters





# What will we do today?


Small-signal schematics

Linearization


Further work on the analog building blocks

Common-source, common-drain, common-gate, etc.

# The transistor revisited 1

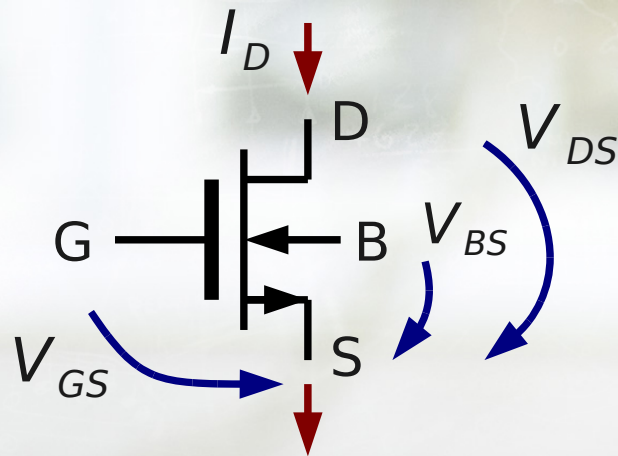


(a) NMOS

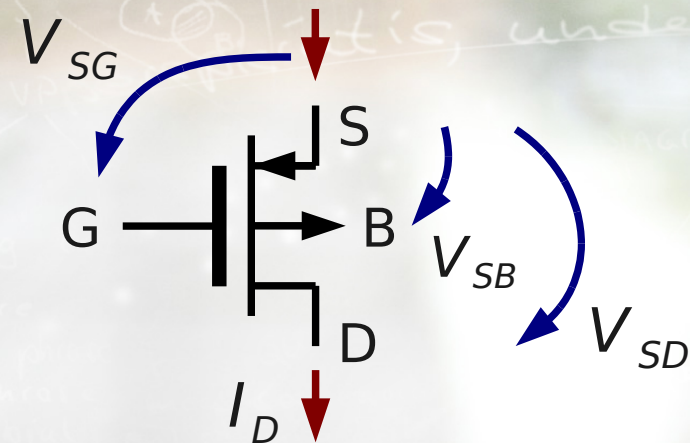

(b) PMOS



# The transistor revisited 2

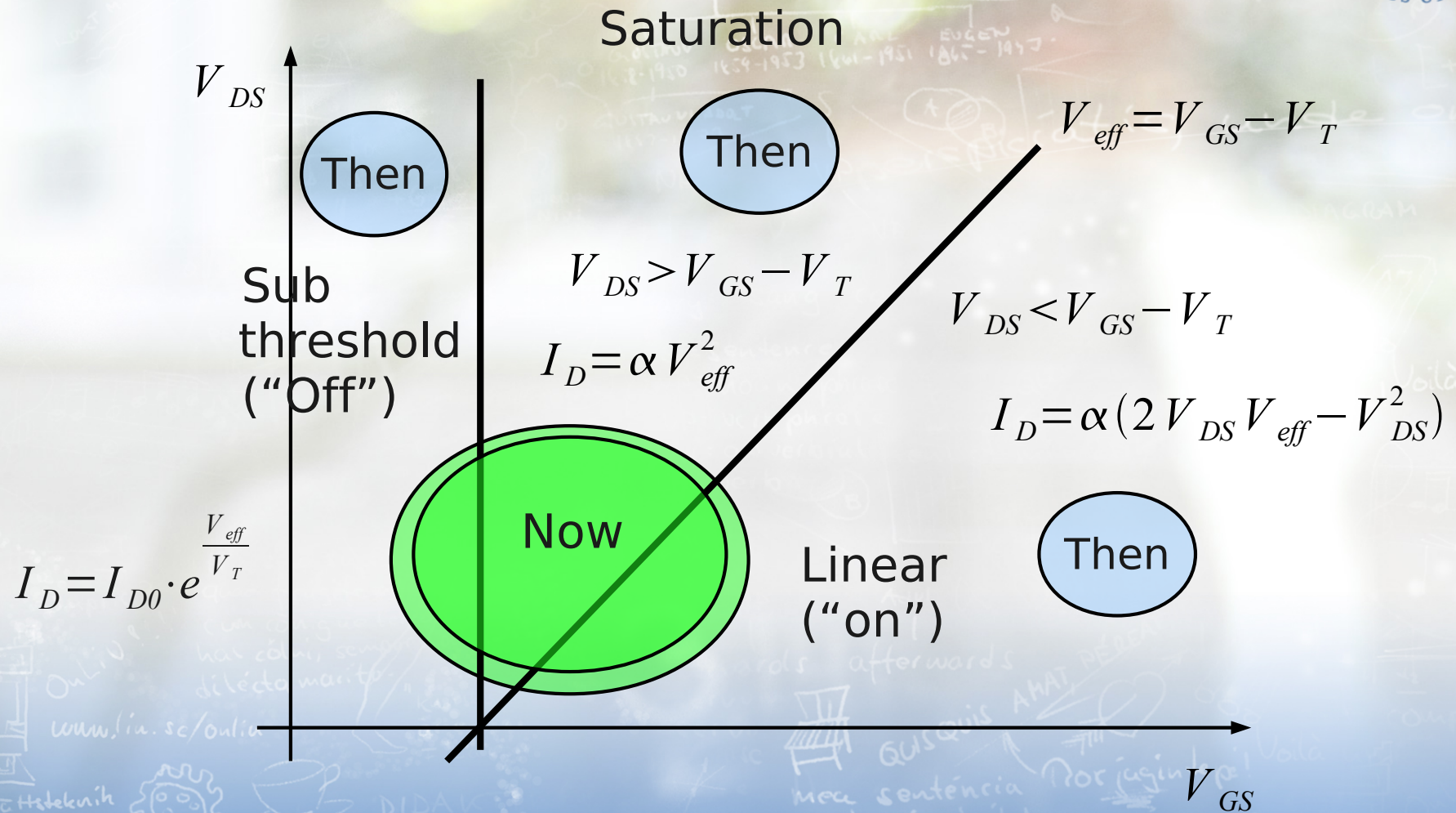

# The first amplifier revisited

A common-source amplifier


$$v_{out} = V_{DD} - R_L \cdot I_D$$

Saturation region

$$v_{out} = V_{DD} - R_L \cdot \alpha \cdot v_{eff}^2$$

Linear region
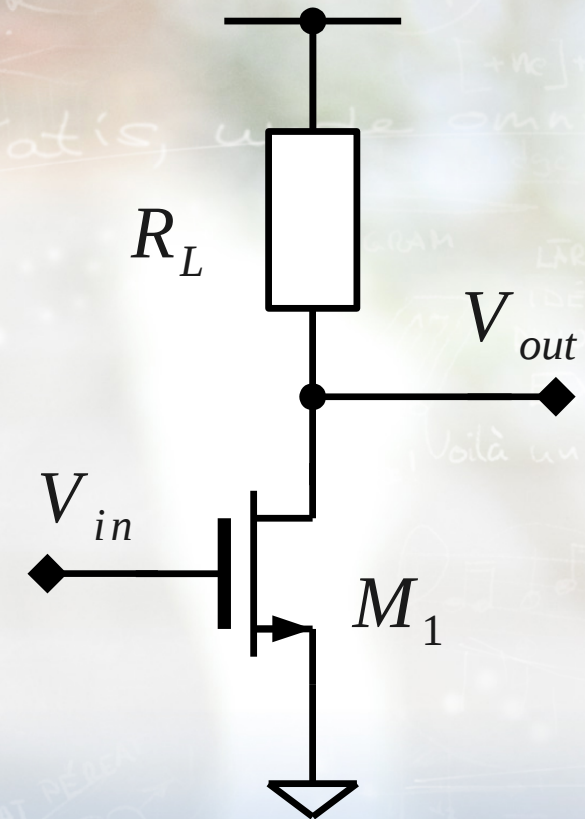
$$v_{out} = V_{DD} - R_L \cdot \alpha \cdot (2v_{out}v_{eff} - v_{out}^2)$$






# The first amplifier revisited



Large-signal transfer characteristics

Position of DC point

Other design requirements

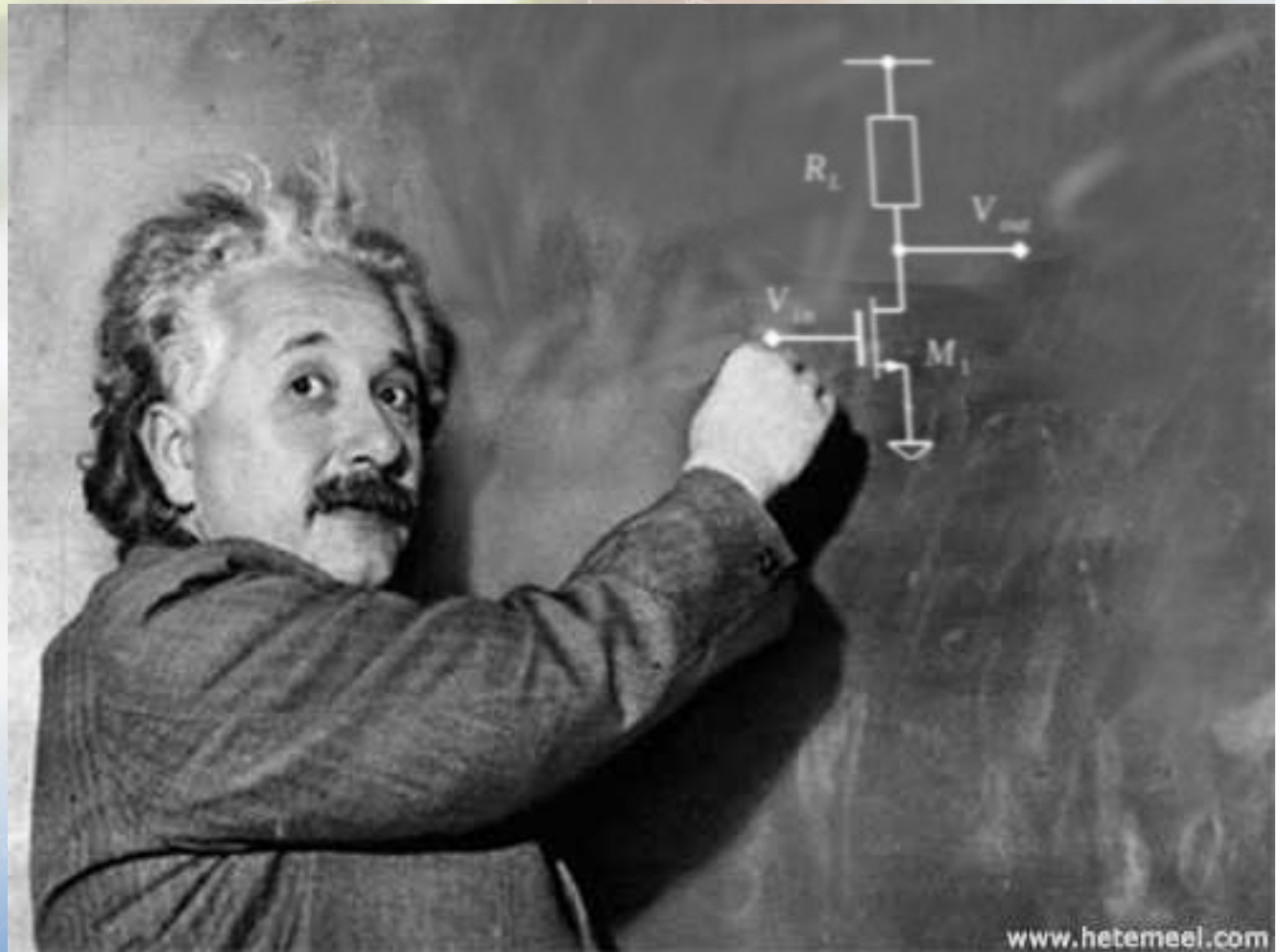

[www.hetemeel.com](http://www.hetemeel.com)

LiU EXPANDING REALITY

# Small-signal schematics

Linearization around a DC point

Small variations around the DC point are assumed

We will sum (superposition) the contributions from all different sources to the output

(Linearization implies no distortion)

Notice that there might be a trade-off between swing and max gain

The choice of DC point is non-trivial...



# Linearization example

Original

$$I_D = \frac{\mu C_{ox}}{2} \cdot \frac{W}{L} \cdot (V_{gs} - V_T)^2 \cdot \left( 1 + \frac{V_{ds}}{V_\theta} \right)$$

Apply partial derivation, i.e., linearize

$$\begin{aligned} \Delta I_D = & \frac{d I_D}{d \mu} \cdot \Delta \mu + \frac{d I_D}{d C_{ox}} \cdot \Delta C_{ox} + \frac{d I_D}{d W} \cdot \Delta W + \frac{d I_D}{d L} \cdot \Delta L + \\ & + \frac{d I_D}{d V_{GS}} \cdot \Delta V_{GS} + \frac{d I_D}{d V_T} \cdot \Delta V_T + \frac{d I_D}{d V_{DS}} \cdot \Delta V_{DS} + \frac{d I_D}{d V_\theta} \cdot \Delta V_\theta \end{aligned}$$

## Linearization example, cont'd

We assume the physical parameters to be constant

$$\Delta I_D = \frac{d I_D}{d V_{GS}} \cdot \Delta V_{GS} + \frac{d I_D}{d V_{DS}} \cdot \Delta V_{DS} + \frac{d I_D}{d V_T} \cdot \Delta V_T$$

Apply the chain rule

$$\frac{d I_D}{d V_T} \cdot \Delta V_T = \frac{d I_D}{d V_T} \cdot \frac{d V_T}{d V_{BS}} \cdot \Delta V_{BS}$$



# Linearization example, cont'd

Introduce some nomenclature

$$\Delta I_D = \underbrace{\frac{d I_D}{d V_{GS}}}_{g_m} \cdot \Delta V_{GS} + \underbrace{\frac{d I_D}{d V_{DS}}}_{g_{ds}} \cdot \Delta V_{DS} + \underbrace{\frac{d I_D}{d V_T} \cdot \frac{d V_T}{d V_{BS}}}_{g_{mbs}} \cdot \Delta V_{BS}$$

and skip the deltas

$$i_d = g_m \cdot v_{gs} + g_{ds} \cdot v_{ds} + g_{mbs} \cdot v_{bs}$$

Which gives us a transistor "consisting" of three current sources


# The small signal model and its impact



Illustration of the small signal model

Some calculations

(More practice in the lessons)

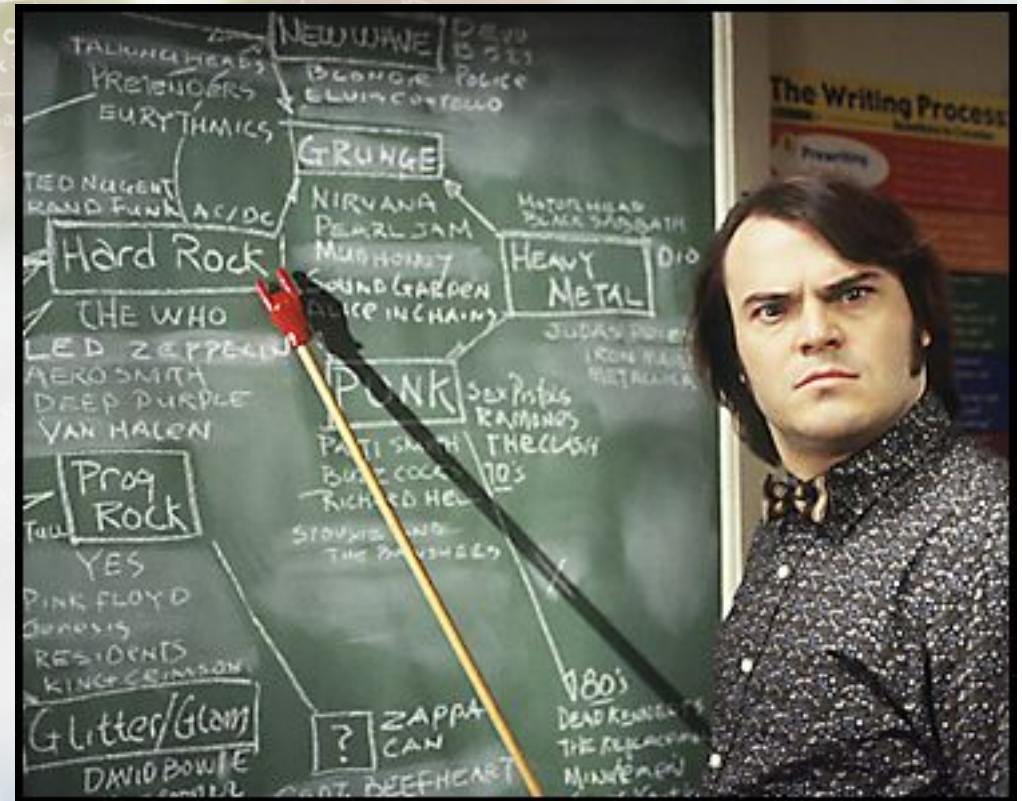



# Transistors compiled

Expression

Cut-off

Linear

Saturation

$$g_m$$

$$\frac{\kappa I_D}{kT/q}$$

$$2\alpha v_{ds}$$

$$\frac{2I_D}{v_{eff}}$$

$$2\sqrt{\alpha I_D}$$

$$g_{mbs}$$

$$g_m \cdot \frac{1-\kappa}{\kappa}$$

$$g_m \cdot \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}}$$

$$g_m \cdot \frac{\gamma}{2\sqrt{V_{SB} + 2\phi_F}}$$

$$g_{ds}$$

$$\lambda I_D$$

$$2\alpha(v_{eff} - v_{ds})$$

$$\lambda I_D$$

**How large are these values?**

# Transistor gain vs region

Expression

$$A = \frac{g_m}{g_{ds}}$$

Cut-off

$$\frac{\kappa \cdot q}{\lambda \cdot kT}$$

Linear

$$\frac{v_{ds}}{v_{eff} - v_{ds}}$$

Saturation


$$\frac{2}{\lambda \cdot v_{eff}} \quad \frac{2\sqrt{\alpha}}{\lambda \sqrt{I_D}}$$

**? What can you spot (where is the gain highest)  $\kappa \approx 0.75$  and  $kT/q \approx 26$  mV.**




# The three amplifier stages


With passive load

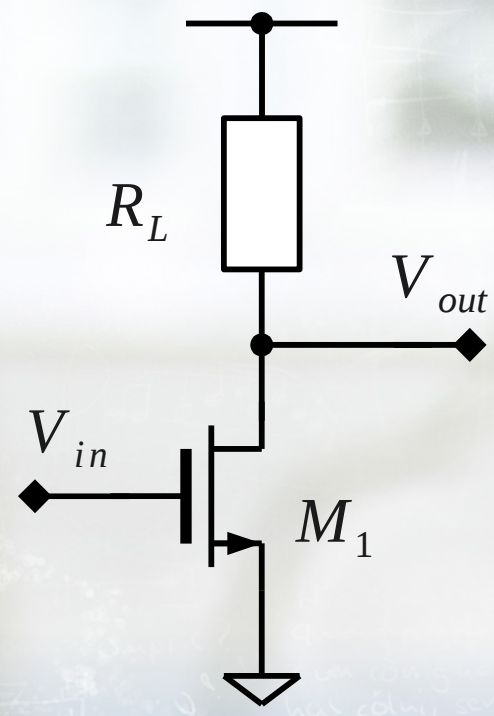

(a) NMOS CS

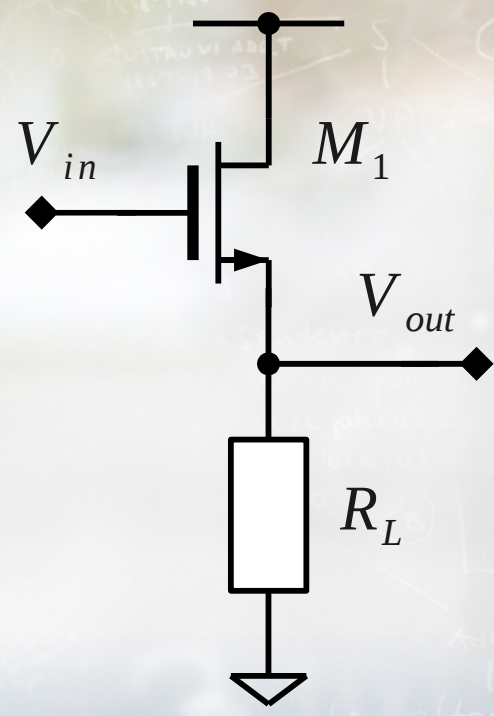




(b) NMOS CD

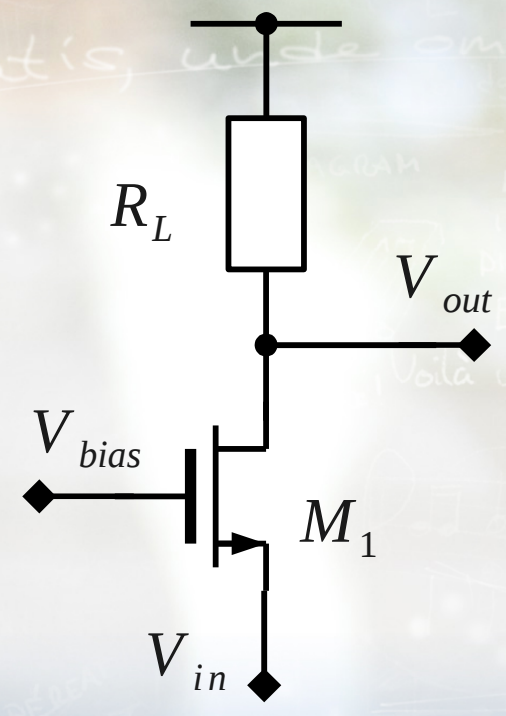

(c) NMOS CG

# The three amplifier stages

With active load

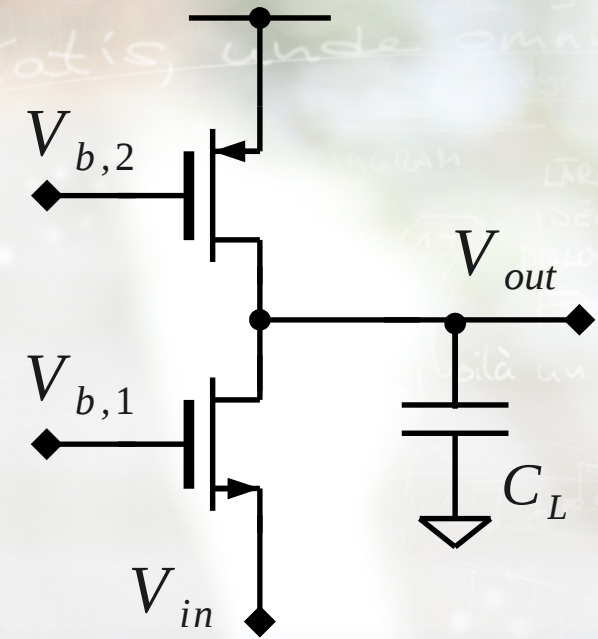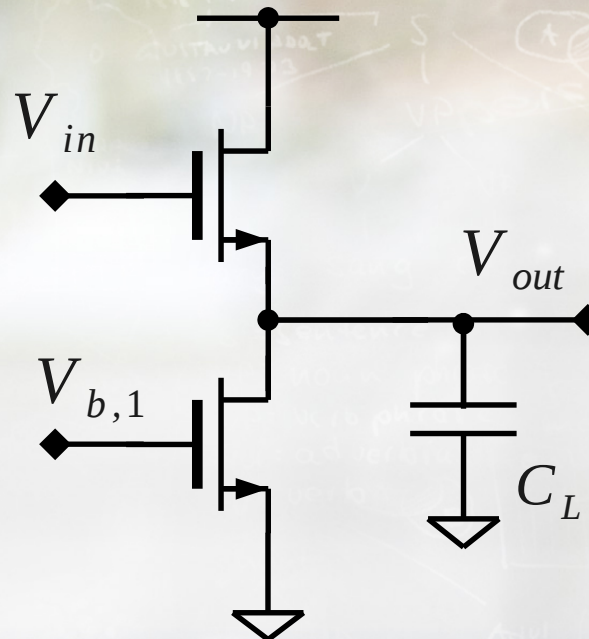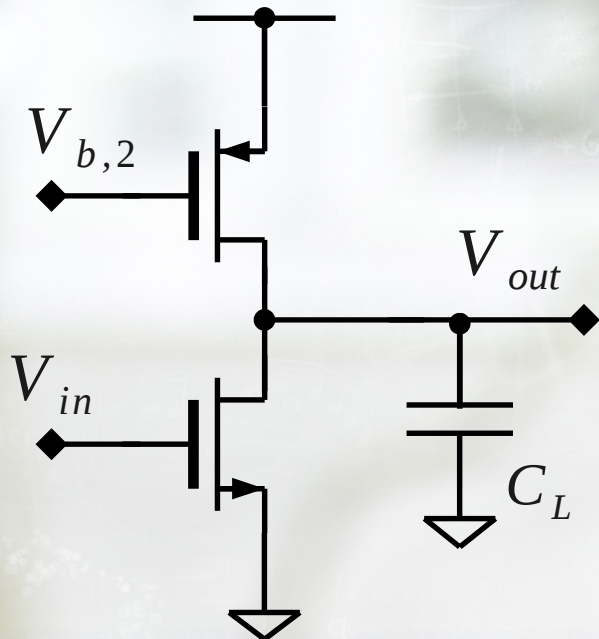


**Why active load?**


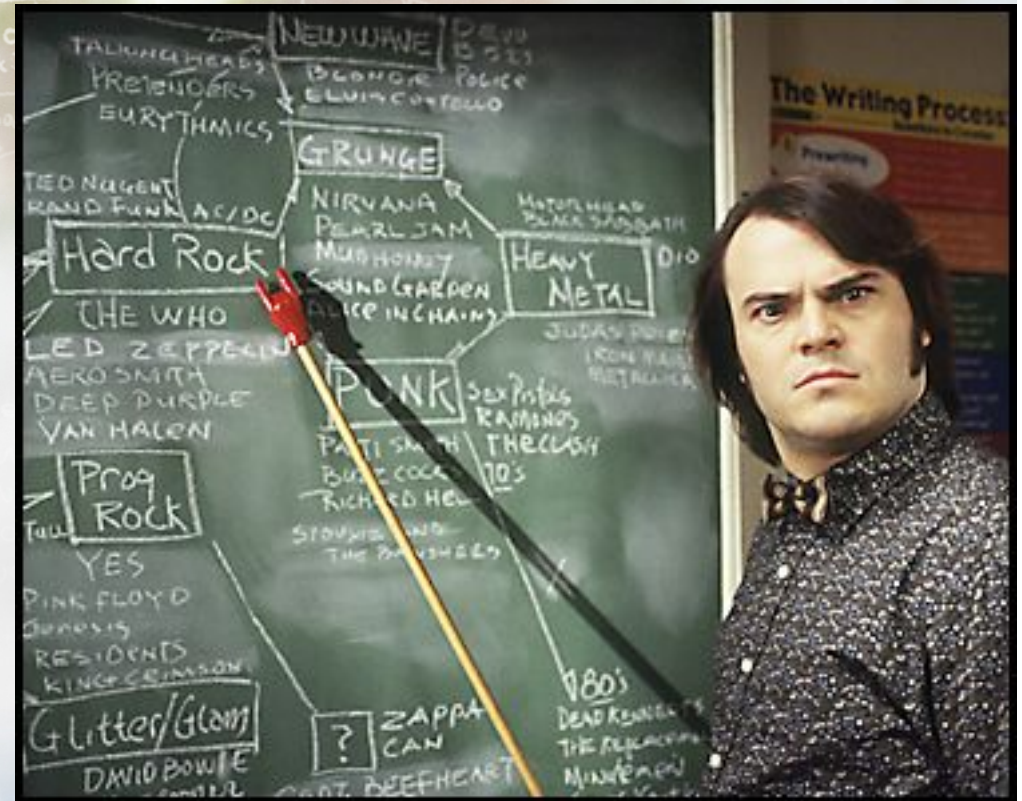
# The small signal exercises



Using the small signal approach to derive the gain



# Amplifier stages, compiled 1

	Expression	CS	CD	CG
DC gain,	$A_0 \approx \frac{g_m}{g_{out}}$	$\approx \frac{g_m}{g_P + g_N}$	$\approx \frac{g_m}{g_m + g_P + g_N} \approx 1$	$\approx \frac{g_m}{g_P + g_N}$
Output impedance,	$\approx g_{out}$	$\approx g_P + g_N$	$\approx g_m$	$\approx g_P + g_N$
Input impedance,	$\approx g_{in}$	$\infty$	$\infty$	$\approx g_m$
Bandwidth,	$p_1 \approx \frac{g_{out}}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$	$\approx \frac{g_m}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$
Unity gain,	$\approx A_0 \cdot p_1$	$\approx \frac{g_m}{C_L}$	N/A (why?)	$\approx \frac{g_m}{C_L}$



# Amplifier stages, compiled 2



Expression	CS	CD	CG*)
DC gain, $A_0 \approx g_m / g_{out}$	$\approx 1 / \lambda \cdot v_{eff}$	$\approx 1$	$\approx 1 / \lambda \cdot v_{eff}$
Output impedance, $\approx g_{out}$	$\approx \lambda I_D$	$\approx 2 I_D / v_{eff}$	$\approx \lambda I_D$
Input impedance, $\approx g_{in}$	$\infty$	$\infty$	$\approx 2 I_D / v_{eff}$
Bandwidth, $p_1 \approx g_{out} / C_L$	$\approx \lambda I_D / C_L$	$\approx 2 I_D / C_L \cdot v_{eff}$	$\approx \lambda I_D / C_L \cdot v_{eff}$
Unity gain, $\approx A_0 \cdot p_1$	$\approx I_D / C_L \cdot v_{eff}$	N/A (why?)	$\approx I_D / C_L \cdot v_{eff}$

# Amplifier stages, compiled 3

## Amplifier stage

## When and what to use?

Common-source

High-gain amplifier with high output impedance and high input impedance. Drive capacitive loads, typically in feedback.

Common-gate

High-gain amplifier with high output impedance and "low" input impedance. Drive capacitive loads, typically in feedback.

Common-drain

Low-gain amplifier with "low" output impedance and high input impedance. Drive resistive loads, can be in open-loop.





# What did we do today?

"Simple" amplifier stages

A single transistor can be troublesome enough ...

Small-signal schematics practice

Practice, practice, practice

How do we increase gain?

What are our handles?



# What will we do next time?

Swing

How many transistors can we stack?

Improving the gain

We need high gain - how do we do it?

Current mirrors