



Lecture 3, ANIK

Current mirrors, Improved gain stages

What did we do last time?

"Simple" amplifier stages

A single transistor can be troublesome enough ...

Small-signal schematics practice

Practice, practice, practice

How do we increase gain?

What are our handles?



What will we do today?

Swing

How many transistors can we stack?

Improving the gain

What are our handles? (again)

We need high gain - how do we do it?

Voltage swing

Walk around the circuit

Check for all the required voltage levels to maintain transistors in their saturation region

Use the following relations

$$V_{GS} = V_{EFF} + V_T$$

$$V_{DS} > V_{EFF} \Rightarrow V_{DS} = V_{EFF}$$

$$V_{EFF} = \sqrt{\frac{I_D}{\alpha}}$$

The lower v_{eff} ...

the higher swing

the higher gain

Examples on the board



Consider the three amplifiers

CG, CD, CS

Check the potentials

When are the transistors saturated?

What does this imply?

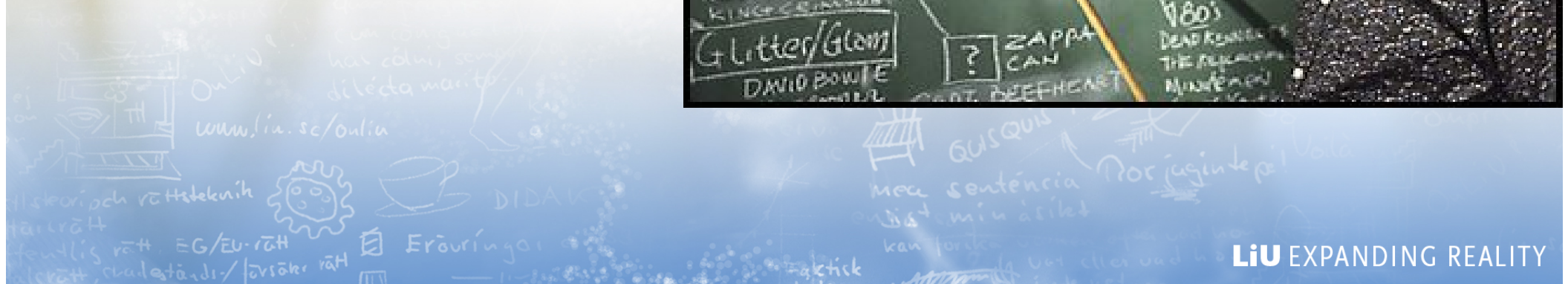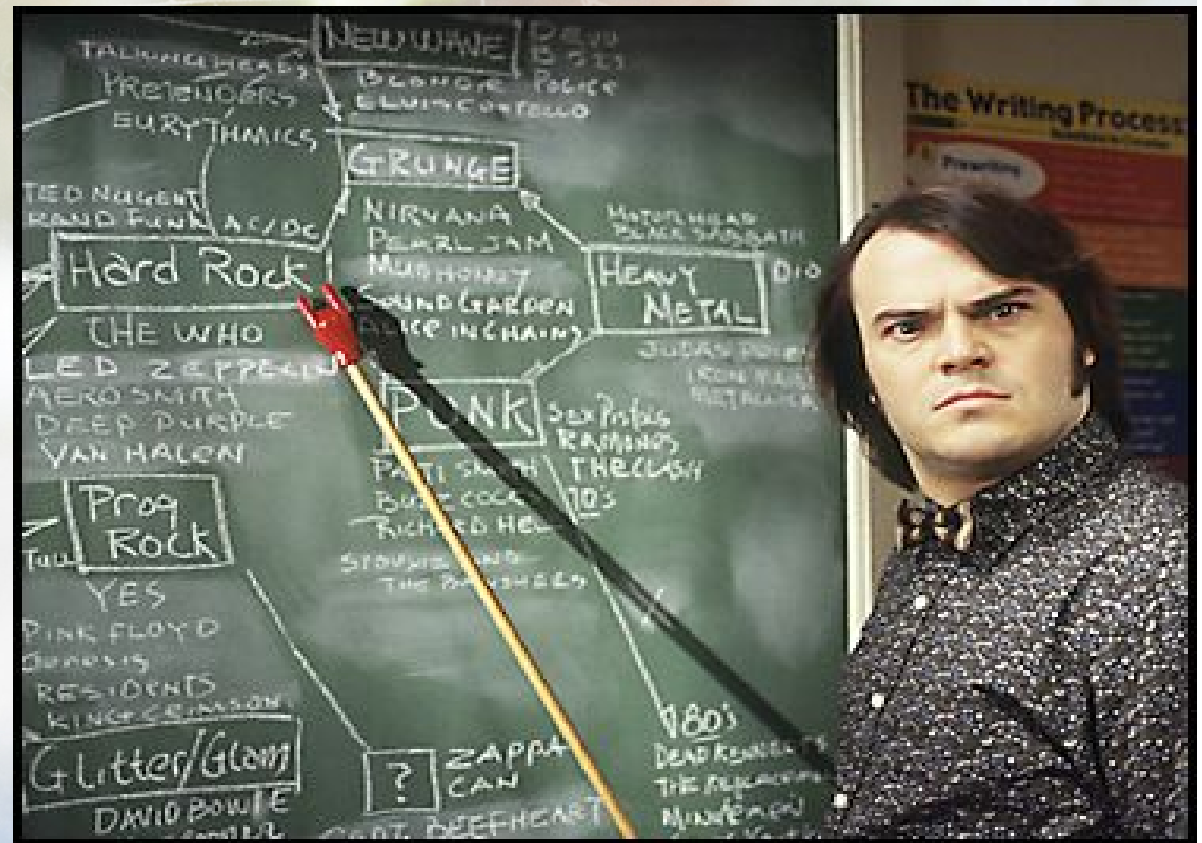

How do I increase my gain?

Assuming a simple common-source stage:

$$A = \frac{g_m}{g_{out}} = \frac{1}{\lambda \cdot v_{eff}} = \frac{2\sqrt{\alpha}}{\lambda \sqrt{I_D}}$$

The answer depends on the biasing conditions

Decrease v_{eff}


Decrease $\lambda \sim 1/L$, i.e., increase the channel length.

Decrease (!) the current I_D

Increase the transistor sizes, $\alpha \sim S \sim W$

Another observation

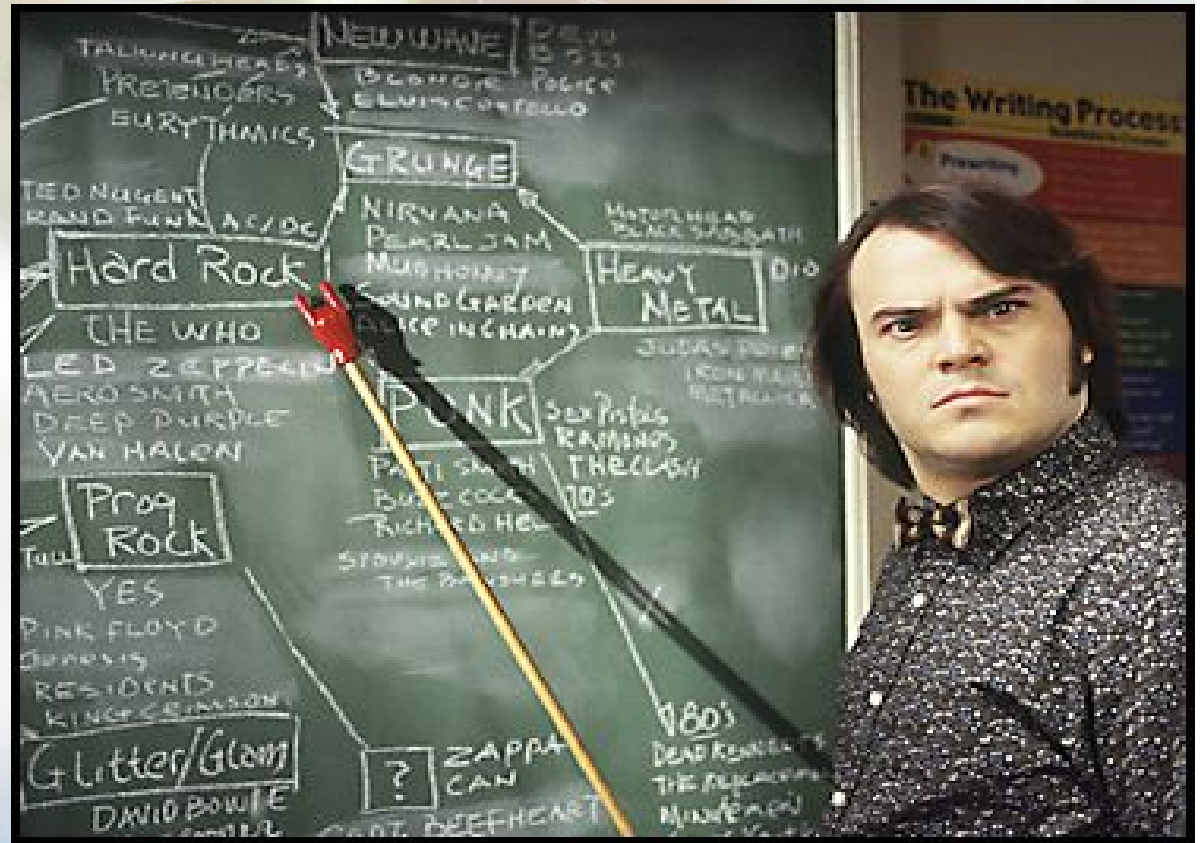
DC gain vs the effective voltage and currents



Historisk och rättsteknisk
färdighet
EG/EU-rätt
Erövringar

Improving the gain, the obvious option

We can put several stages in series

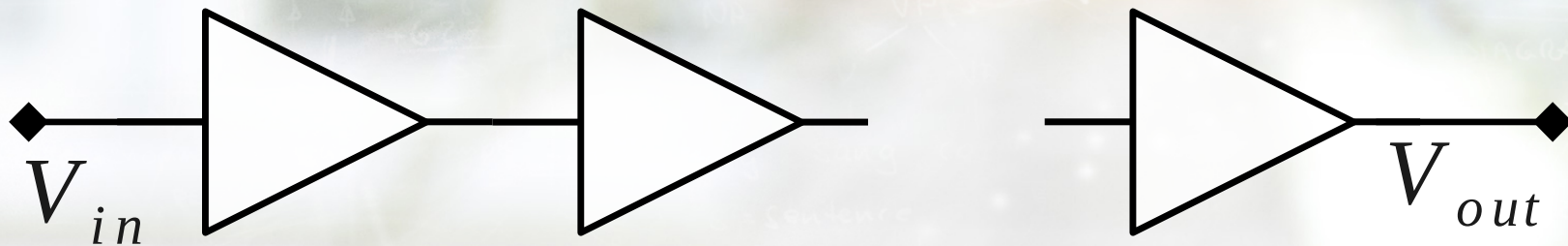

Gain is formed by simply taking the product of all gains

Offers high swing

Might cost us more power consumption (each stage needs a current).

Improving the gain, the electrical option

Revisit the expression on gain!

$$A = \frac{g_m}{g_{out}}$$

Increase the transconductance

Decrease the output conductance (i.e., increase output impedance)

We've done that kind of, c.f., lowering the v_{eff} , etc.

Cascodes, the hardware option

Introduce more hardware to increase impedance


Cascodes increase the gain

How? - a small-signal exercise

We must balance the load

both in PMOS and NMOS "direction"

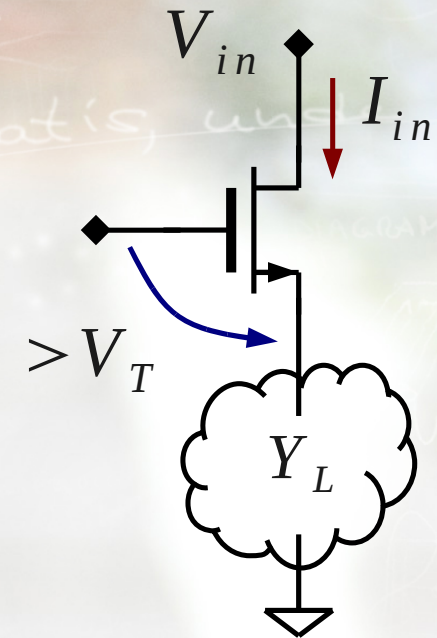(Traditional way to maximize power efficiency)



$$Y_{out} = \frac{I_{in}}{V_{in}} \approx \frac{Y_L}{A} \approx \frac{Y_L \cdot g}{g_m}$$

So ... it's all about impedance levels


Cascodes

(Quickly) eats up the voltage headroom

For every diode-connected transistor, we lose one V_T of swing

We can save current since only one stage

Complexing biasing schemes

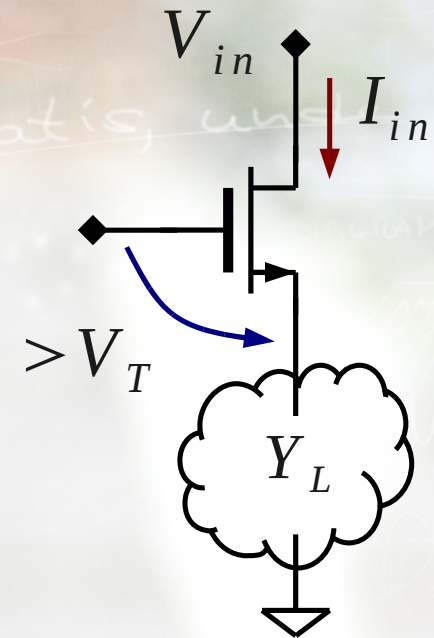

$$Y_{out} = \frac{I_{in}}{V_{in}} \approx \frac{Y_L}{A} \approx \frac{Y_L \cdot g}{g_m}$$


"The output impedance is multiplied"

Cascodes, common-source example



Voltage swing

Calculating the gain

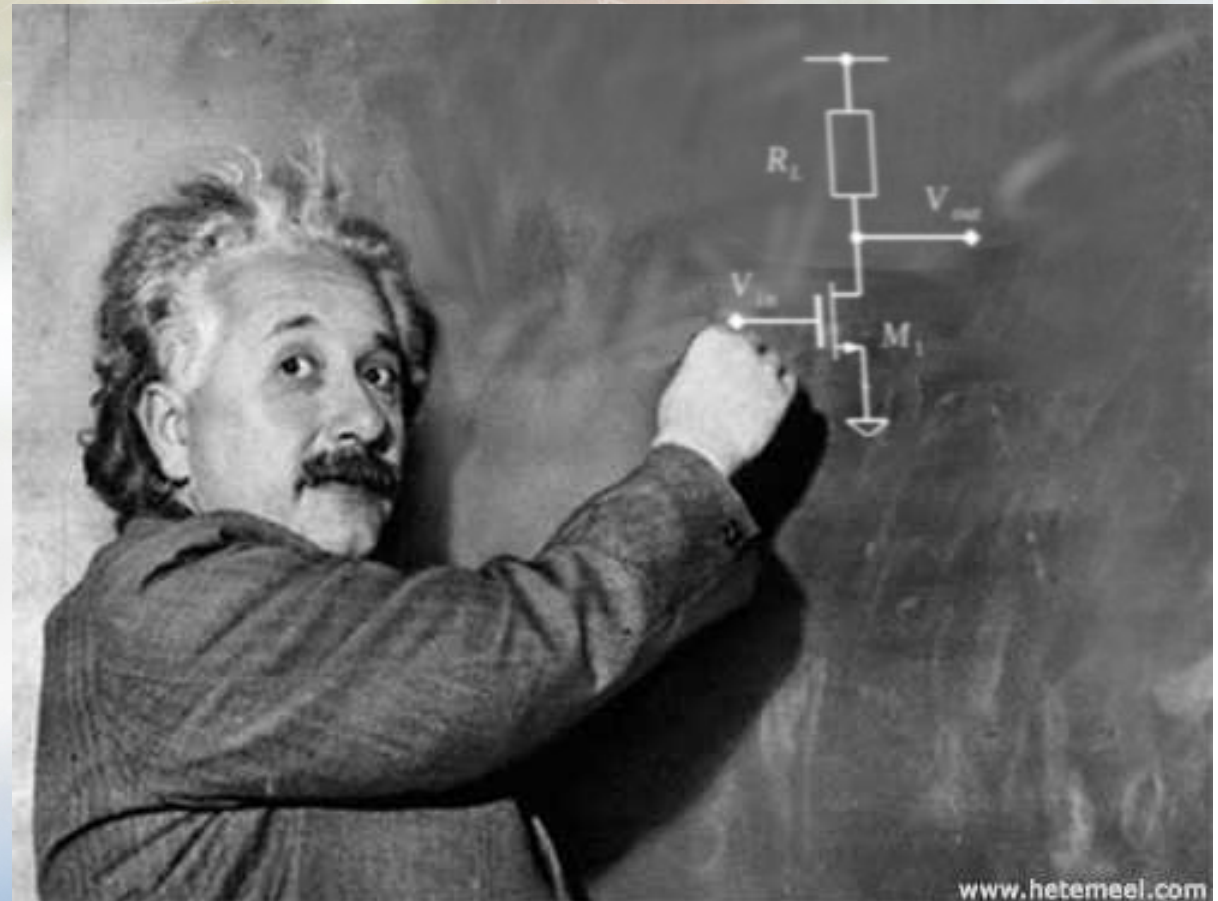

Cascodes, common-source example

This formula still holds $A = g_m / g_{out}$ and the output conductance is

$$A = \frac{g_{m1}}{\frac{g_{n1} \cdot g_{n2}}{g_{m2}} + \frac{g_{p3} \cdot g_{p4}}{g_{m3}}} \approx \frac{g_{m1} \cdot g_{m2}}{2 \cdot g_{n1} \cdot g_{n2}}$$


Now, we have some more handles to increase (set) the gain.

Effective voltage of input can be decoupled.

Classical analog trade-offs to distribute the gain).

But ... what happens to the gain if the impedance levels are not balanced?

Cascodes are also multiple stages ...

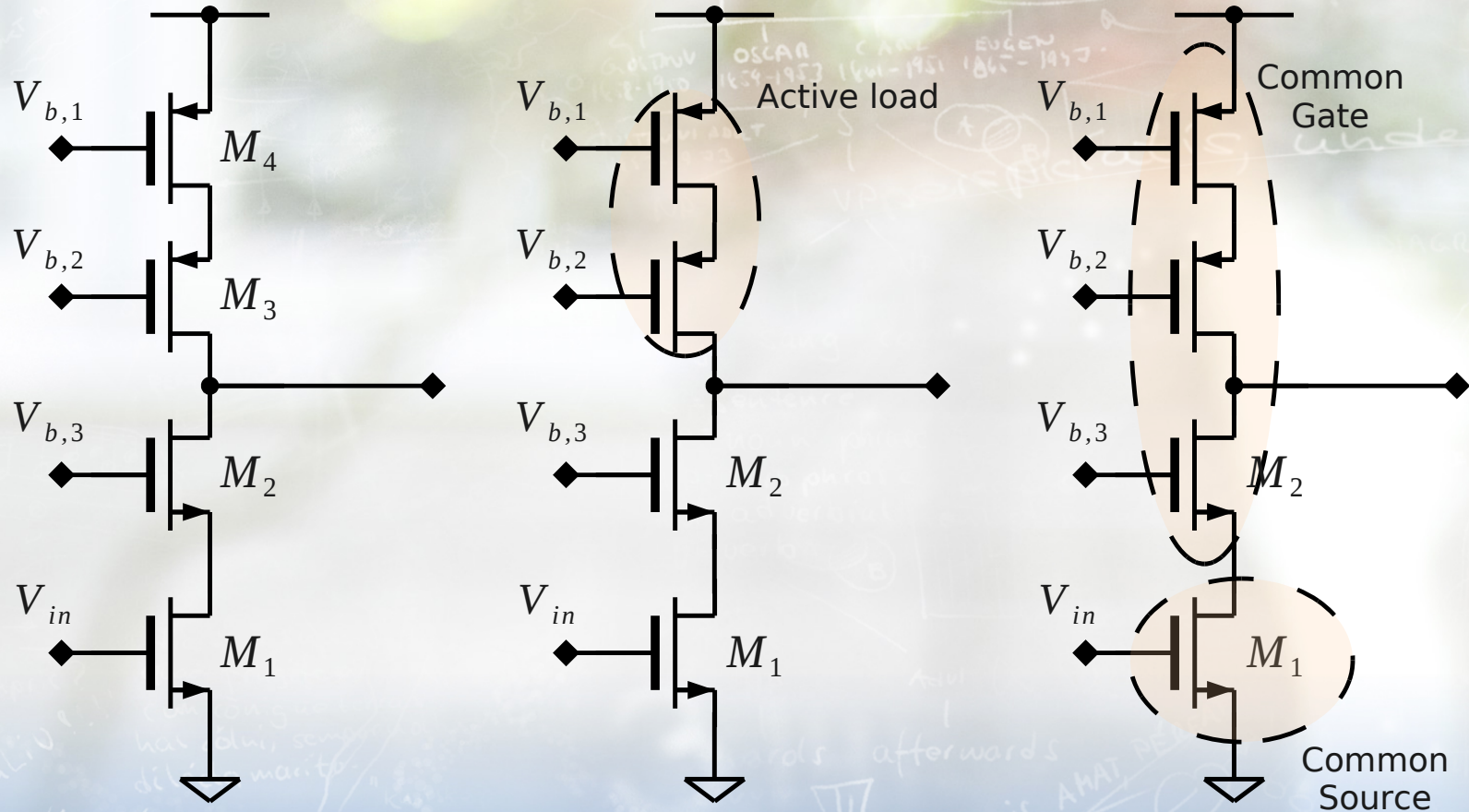

Some conclusions on one slide

Cascodes eat up the swing

Cascodes save current compared to multi-stage

Cascodes and multi-stage have comparatively same area

Cascodes have more complex biasing schemes compared to multi-stage

Cascodes might not be feasible in future (analog) designs

What did we do today?



Voltage swing

Cascodes to increase gain



What will we do next time?

Current mirrors

Simple, Wilson, Wide-Swing, Cascoded

Improved amplifier stages

Folded-cascode gain stage

Decoupling design parameters

Using for example current mirrors