



Lecture 4, ANIK

Current mirrors
More on amplifiers (frequency domain)

What did we do last time?



Voltage swing

How far can we push the transistors?

Target: Force all operate in saturation region

Ways to increase the gain?

0) Physical sizing

1) Electrical handles

2) Cascodes

3) Multiple stages

What will we do today?



Current mirrors

Simple, Wilson, Wide-Swing, Cascoded

Decoupling design parameters using current mirrors

Improved amplifier stages

Folded-cascoded gain stage

Gain-boosting

The frequency domain

Dominant-pole, DC gain, unity-gain frequency

Some kind of wrap-up session


Current mirrors

Use currents to distribute references (low speed) over a chip

Receiver determines voltage across resistor

Resistance in wire does not matter

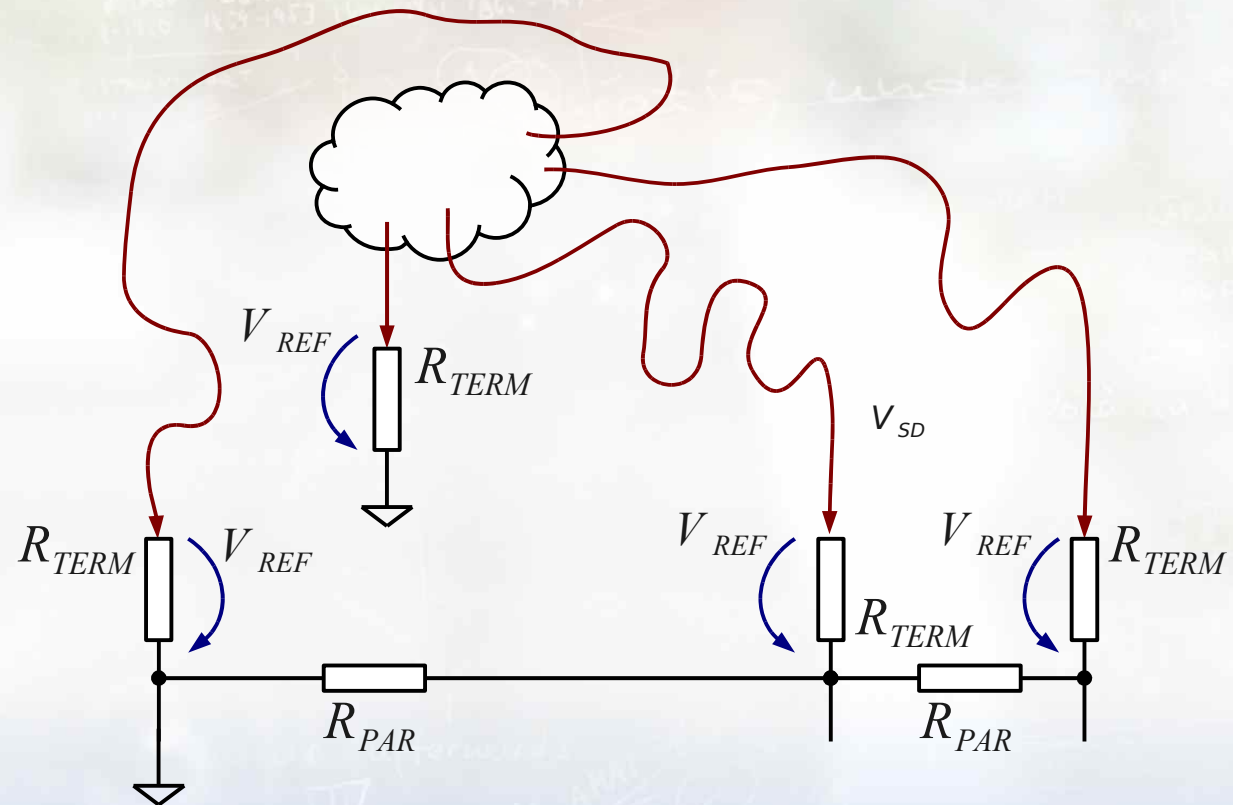Local "ground" does not influence the result




Current mirrors, cont'd

Use currents to bias amplifier stages

Decouples the design parameters!

We can "ignore" the size and v_{eff} of the bias transistor (active load)

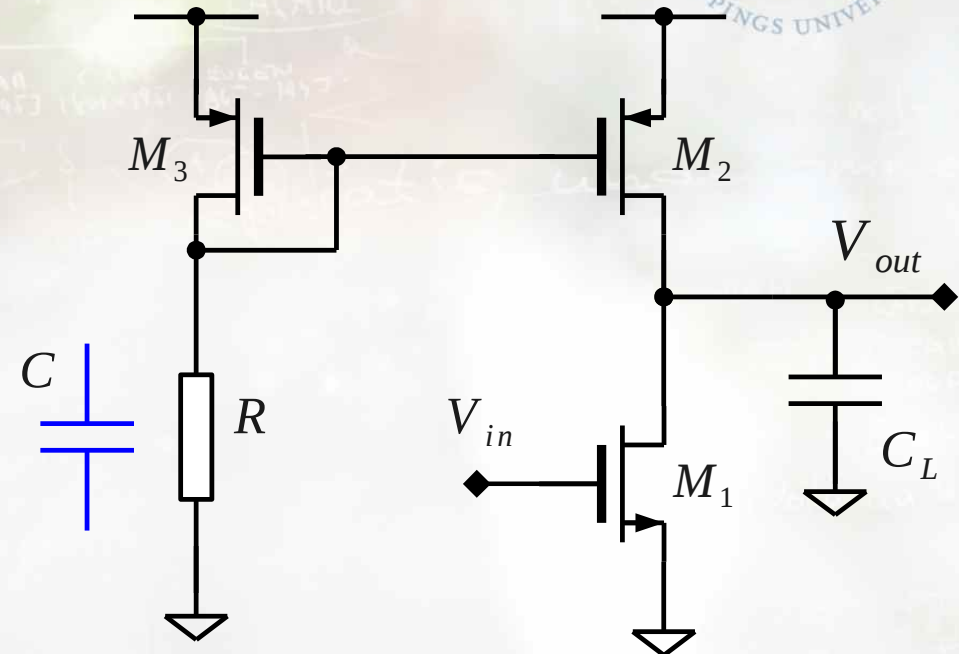Set the current through a reference of some kind



Current mirrors, cont'd




Input (primary) should behave as a current sink, i.e., have


$$Z_{in} = 0$$

Output (secondary) should behave as a current source, i.e., have


$$Z_{out} = 0$$

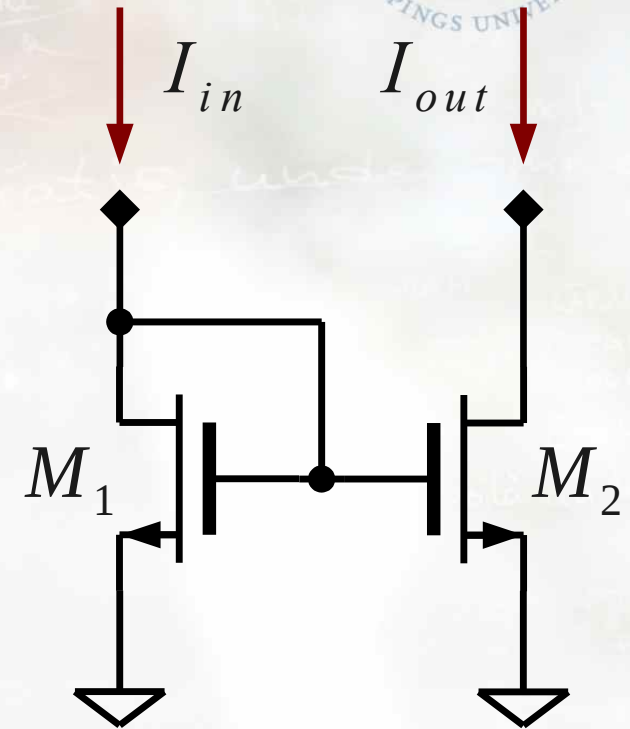


Current mirrors

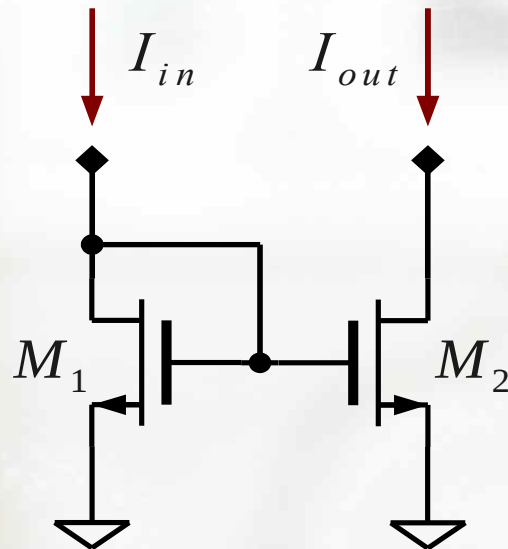

(a) Simple

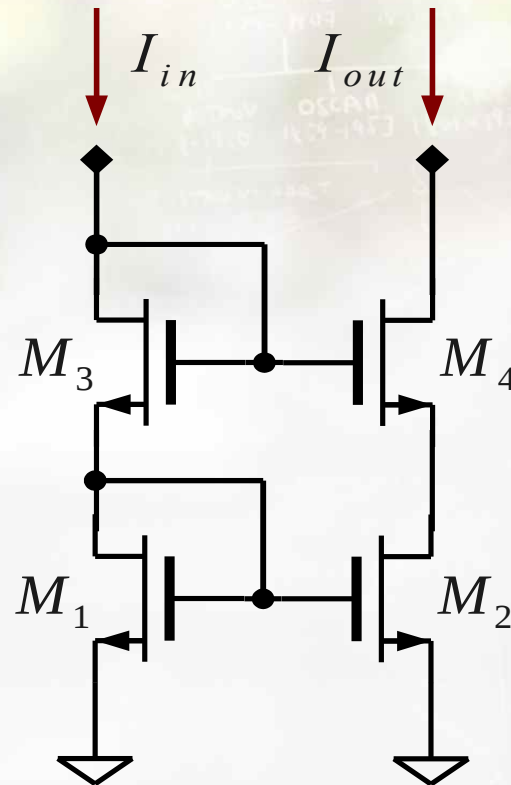

(b) Cascode

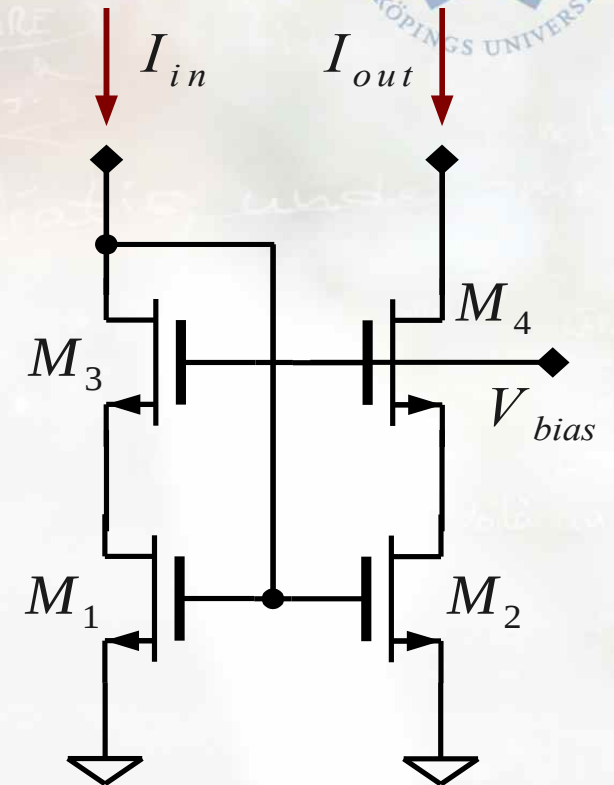

(c) Wideswing

Current mirrors, operation

The current relationship is given by the transistor sizes.

Notice that the v_{eff} is constant on the lower transistors.

$$I_{out} = \frac{\alpha_{out}}{\alpha_{in}} \cdot I_{in}$$

Compare with second-order model

$$\frac{I_{out}}{I_{in}} = \frac{\alpha_{out}}{\alpha_{in}} \cdot \frac{1 + \lambda v_{out}}{1 + \lambda v_{in}}$$

which will be too big of variations.

Current mirrors, nonidealities




Voltage swing

Potential drops back and forth

Calculating the impedances

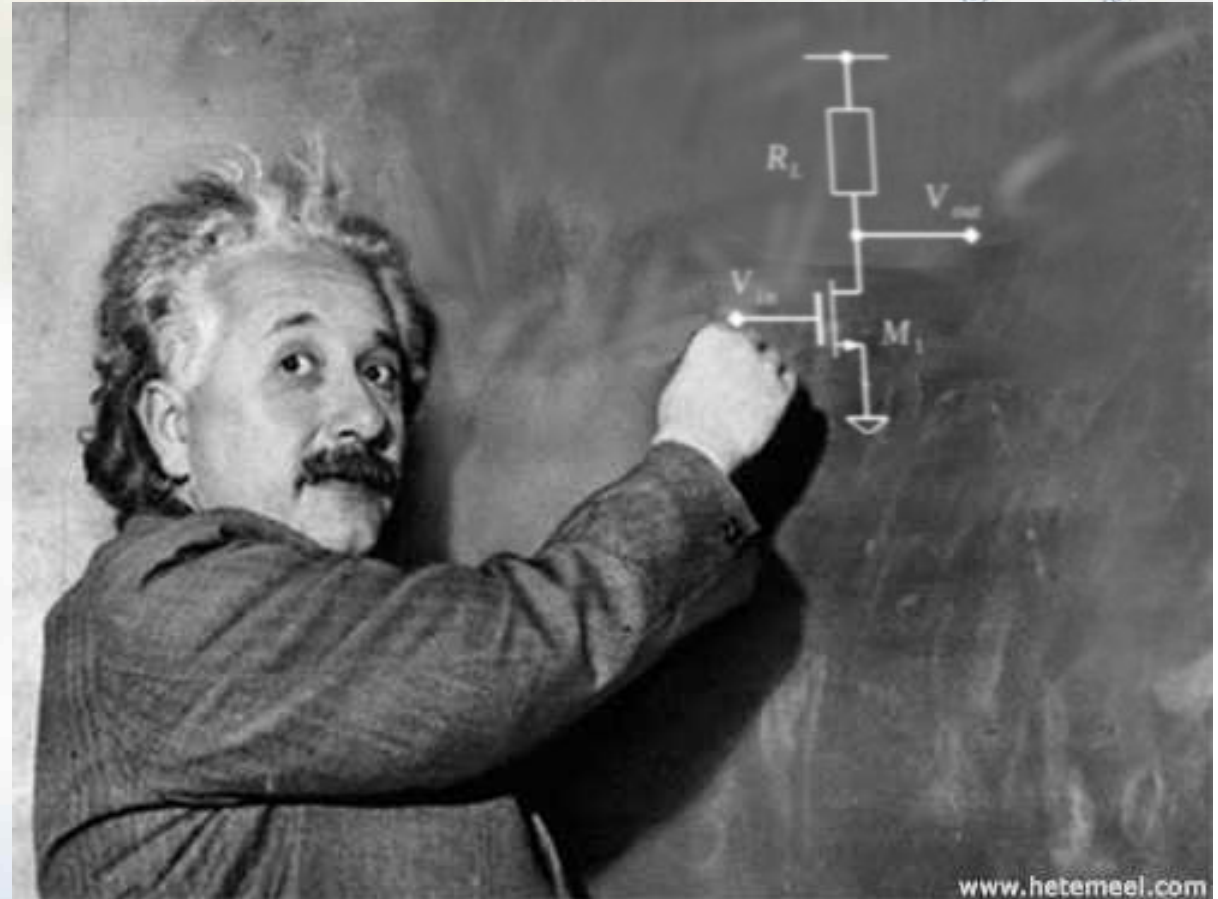Use the quick-trick from cascodes for cascodes



Improved amplifier stages


Folded cascode

Common-source + common-gate

Same type of gain as in cascoded gain stage

Range increases (feedback configuration)

Why do we need the lower NMOS?

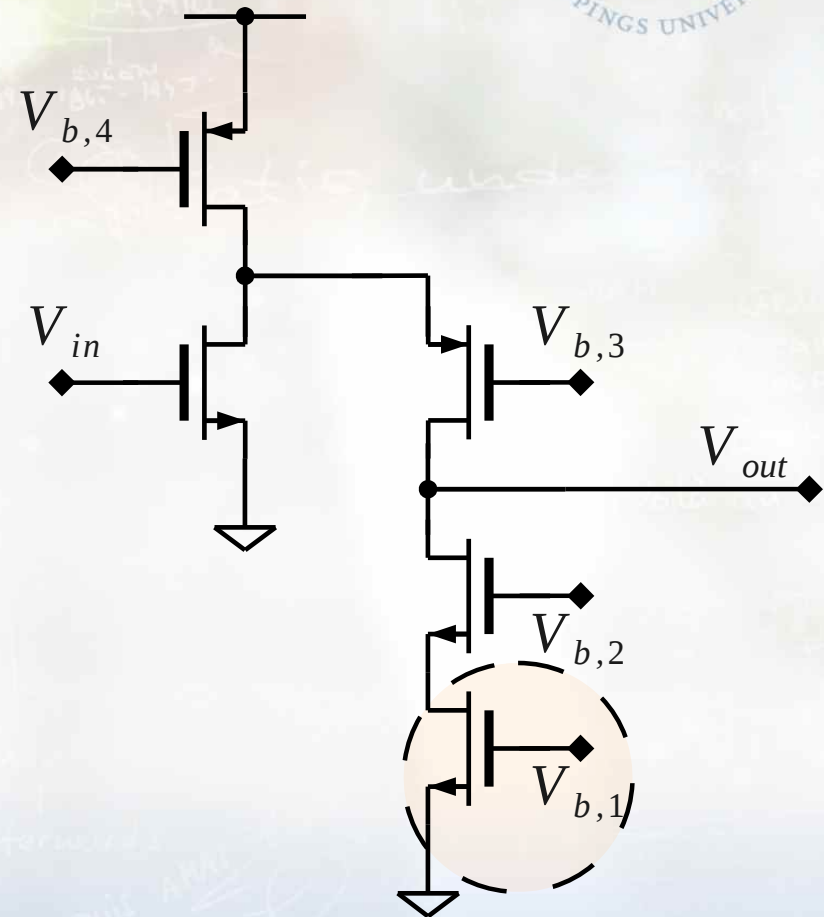


Improved amplifier stages

Gain-boosting

Additional amplifier sets the gain of the cascode

"Output impedance is multiplied by cascode"

What about the swing now?

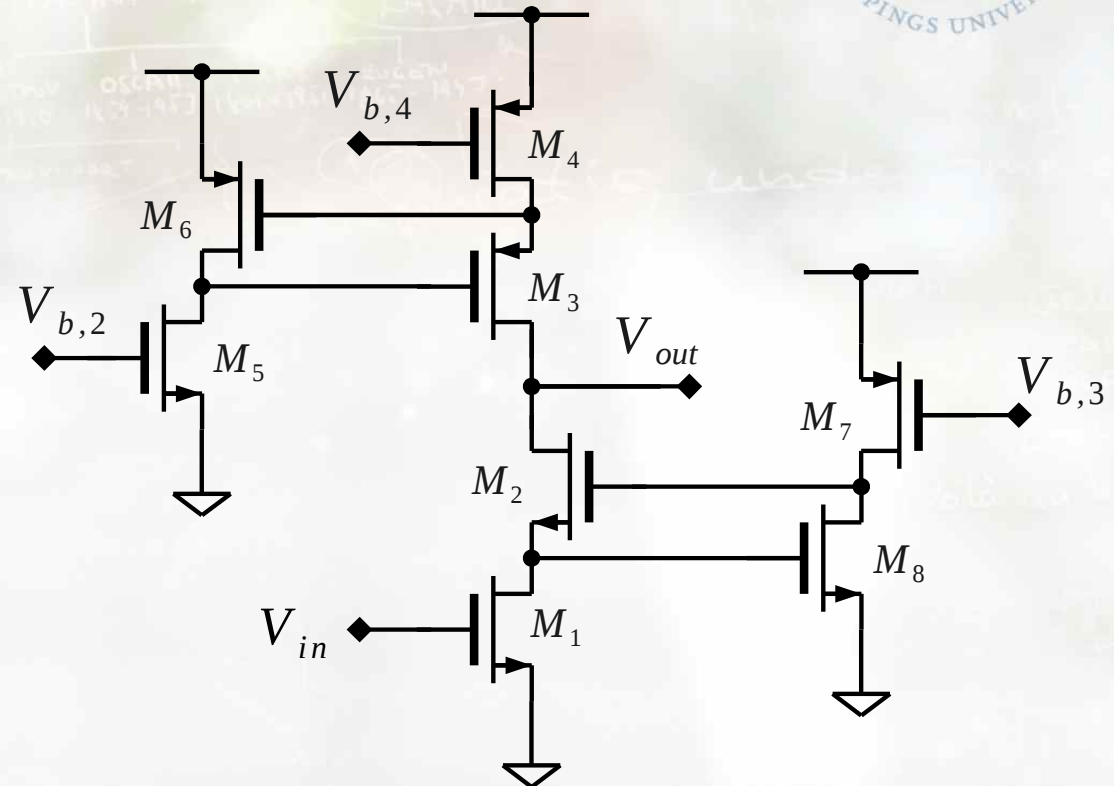

Improved amplifier stages, cont'd




Folded cascode and gain boosting

Operation

Calculating the impedances



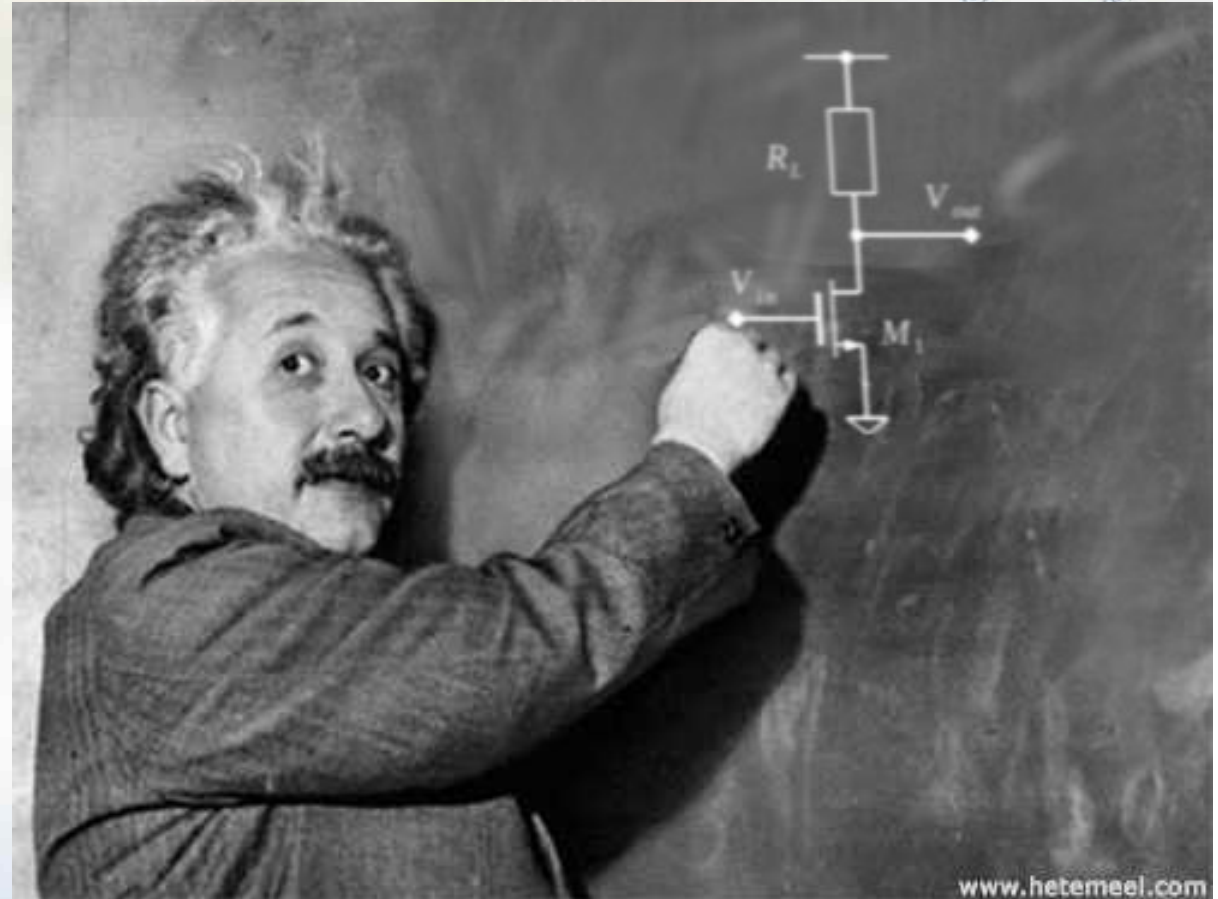
Use the quick-tricks from cascodes for cascodes



The frequency domain



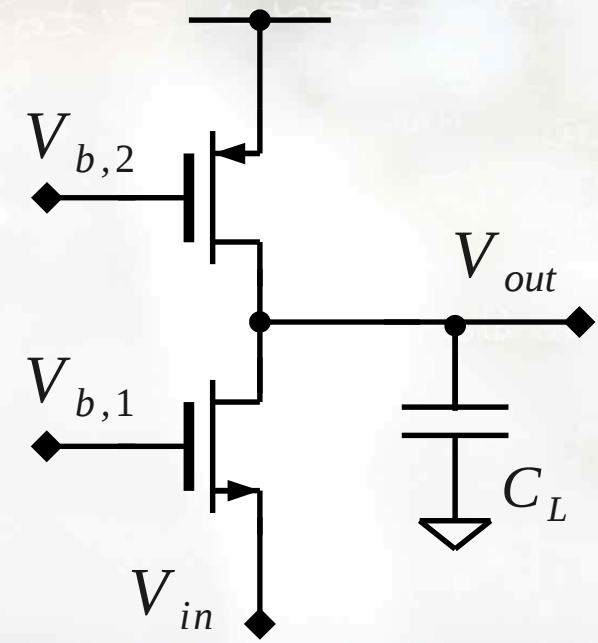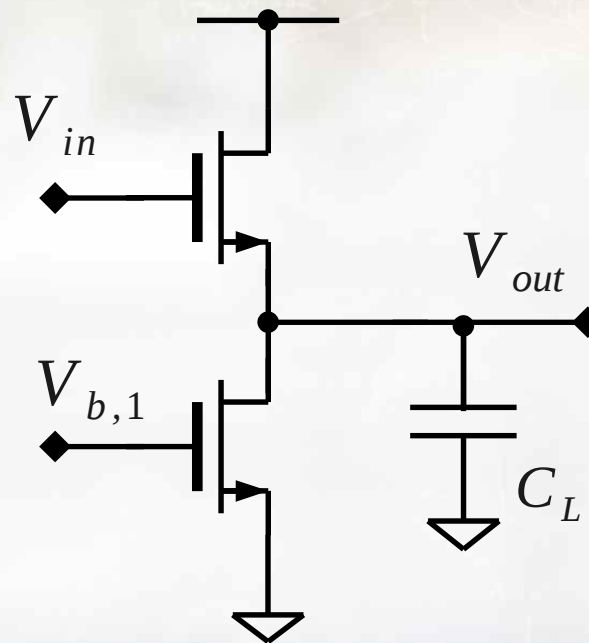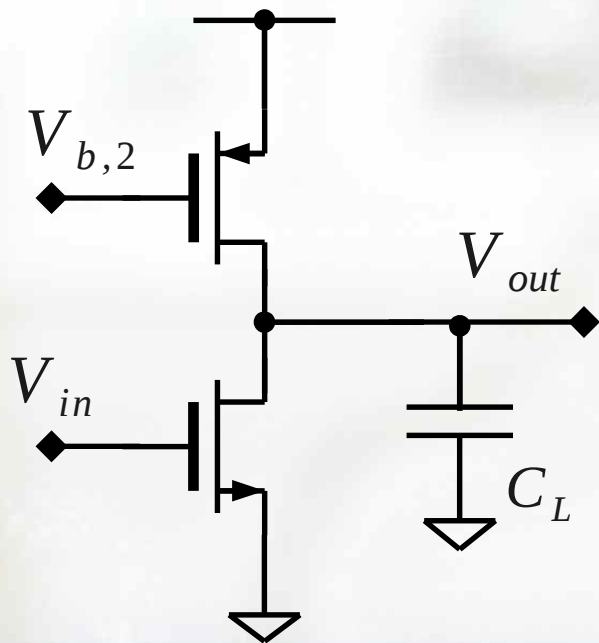Include the capacitor in your calculations



The frequency domain



Small-signal exercise


Impact of capacitor on
common-source stage

Bode plot

Pole

DC gain

Unity-gain frequency

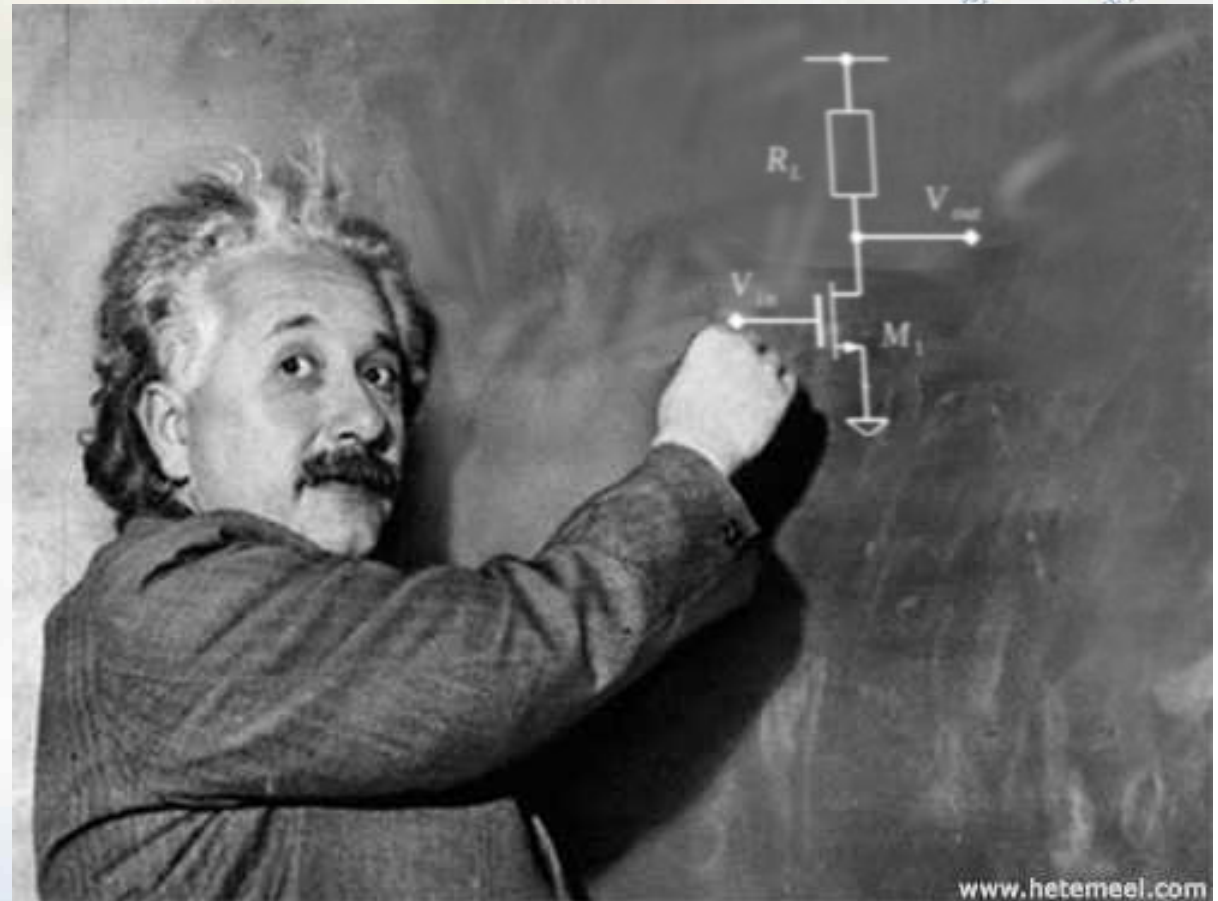

www.hetemeel.com

Compilation



The overall transfer function

$$A(s) = \frac{A_0}{1 + \frac{s}{p_1}} = \frac{\frac{g_m}{g_{out}}}{1 + \frac{s}{\frac{g_{out}}{C_L}}}$$

Notice the trade-off between bandwidth and gain!

$$A_0 \cdot p_1 \approx \omega_{ug}$$

Very crucial in your OP amp design

Amplifier stages, compiled 1



	Expression	CS	CD	CG*)
DC gain,	$A_0 \approx \frac{g_m}{g_{out}}$	$\approx \frac{g_m}{g_P + g_N}$	$\approx \frac{g_m}{g_m + g_P + g_N} \approx 1$	$\approx \frac{g_m}{g_P + g_N}$
Output impedance,	$\approx g_{out}$	$\approx g_P + g_N$	$\approx g_m$	$\approx g_P + g_N$
Bandwidth,	$p_1 \approx \frac{g_{out}}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$	$\approx \frac{g_m}{C_L}$	$\approx \frac{g_P + g_N}{C_L}$
Unity gain,	$\approx A_0 \cdot p_1$	$\approx \frac{g_m}{C_L}$	N/A (why?)	$\approx \frac{g_m}{C_L}$

*) Source impedance not mentioned, see the exercise manual.

Amplifier stages, compiled 2



	Expression	CS	CD	CG*)
DC gain,	$A_0 \approx \frac{g_m}{g_{out}}$	$\approx \frac{1}{\lambda \cdot v_{eff}}$	≈ 1	$\approx \frac{1}{\lambda \cdot v_{eff}}$
Output impedance,	$\approx g_{out}$	$\approx \lambda I_D$	$\approx \frac{2I_D}{v_{eff}}$	$\approx \lambda I_D$
Bandwidth,	$p_1 \approx \frac{g_{out}}{C_L}$	$\approx \frac{\lambda I_D}{C_L}$	$\approx \frac{2I_D}{C_L \cdot v_{eff}}$	$\approx \frac{\lambda I_D}{C_L \cdot v_{eff}}$
Unity gain,	$\approx A_0 \cdot p_1$	$\approx \frac{I_D}{C_L \cdot v_{eff}}$	N/A (why?)	$\approx \frac{I_D}{C_L \cdot v_{eff}}$

Other tips-and-tricks



Common-drain

If the voltage levels are not good enough, you can shift up/down

Isolation of sensitive nodes (buffering)

"Current-stealing"

Consider the folded cascode amplifier. Notice that the two branches steal current from a common current source. Also remember that gain is inversely proportional to current. By stealing current, we can lower current, and thus increase gain.

The transistor as a switch/resistor




The last operation

$$I_{PN} = \alpha \cdot (2V_{eff} V_{ds} - V_{ds}^2)$$

or
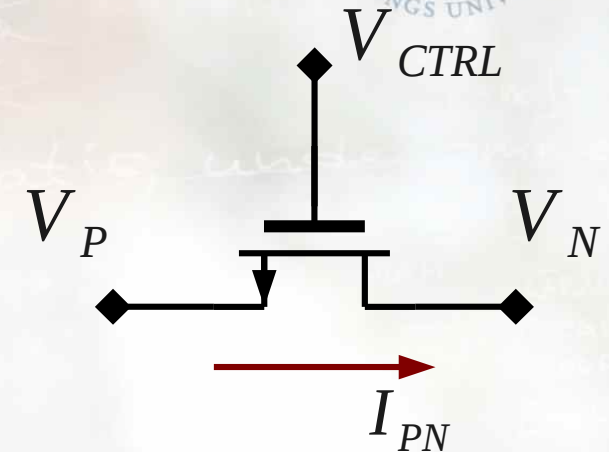
$$I_{PN} = 2\alpha V_{ds} \cdot \left(V_G - V_T - \frac{V_D + V_S}{2} \right)$$



Voltage dependent resistor, with conductance:

$$G_{PN} = \frac{I_{PN}}{V_{ds}} = 2\alpha \cdot \left(V_G - V_T - \frac{V_D + V_S}{2} \right)$$

The transistor as a switch/resistor




The linearized model

$$G_{PN} = 2\alpha \cdot (V_G - V_D - V_T)$$

What to think about

How to use it

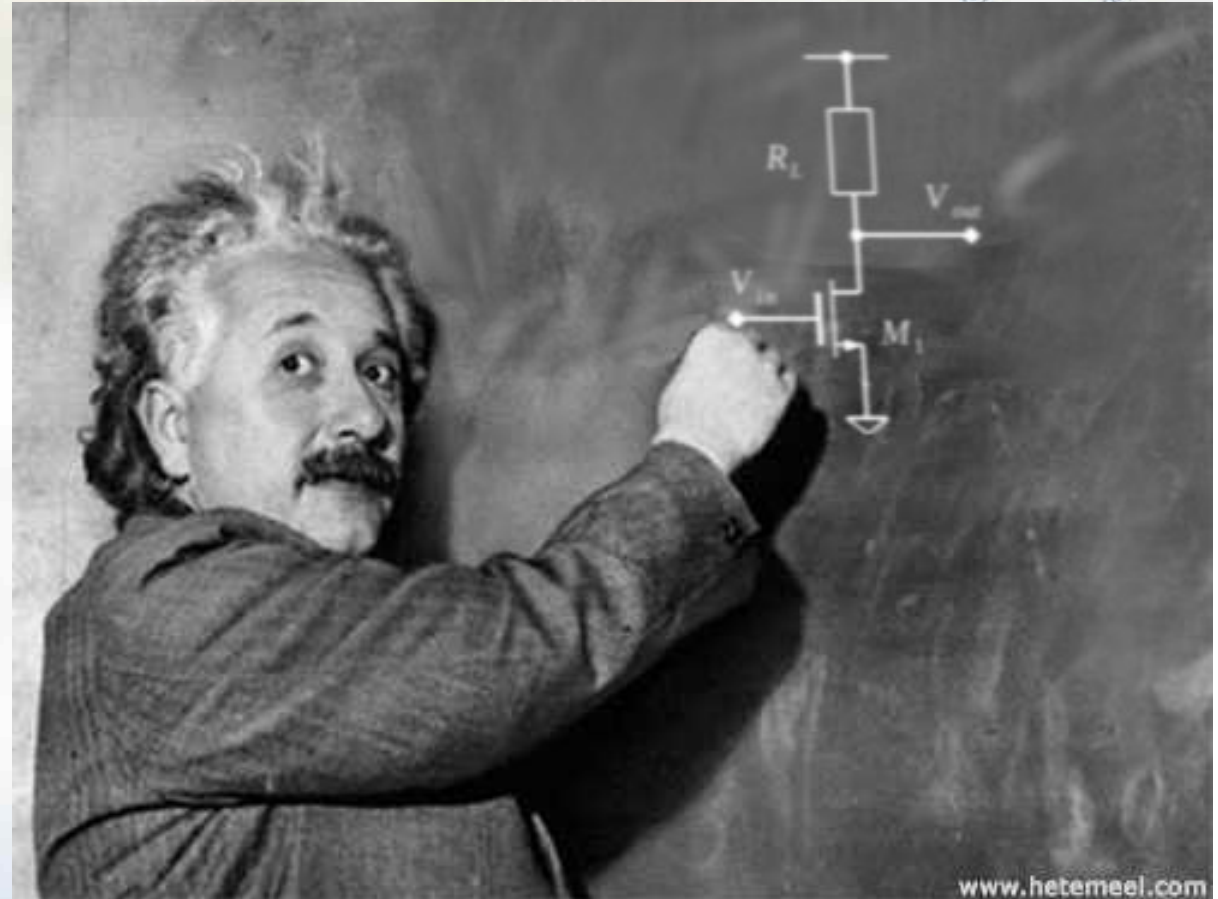

What did we do today?



Current mirrors

Simple, Cascoded, and Wide-Swing

Decoupling design parameters using current mirrors

Improved amplifier stages

Folded-cascode gain stage

Gain-boosting

The switch

The frequency domain

Dominant-pole, DC gain, unity-gain frequency

What will we do next time?



Differential signals

Why differential?

Common-mode definitions

Differential pair

Analysis

Operation

Mismatch

Impact of mismatch on design/performance/behavior