



Lecture 5, ANIK

Differential signals and circuits
Mismatch

What did we do last time?



Current mirrors

Simple, Cascoded, and Wide-Swing

Decoupling design parameters using current mirrors

Improved amplifier stages

Folded-cascode gain stage

Gain-boosting

The switch

The frequency domain

Dominant-pole, DC gain, unity-gain frequency

Revisit frequency domain

Bode plot


Pole

Zero

Phase margin

Gain vs frequency trade-off

$$A_0 \cdot p_1 \approx \omega_{ug}$$

 

What will we do today?



Differential signals

Why differential?

Common-mode definitions

Differential pair

Analysis

Operation

Mismatch

Impact of mismatch on design/performance/behavior

Differential signals

Differential signals

$$\Delta V = V_p - V_n$$


Common-mode signal

$$\nabla V = \frac{V_p + V_n}{2}$$

Common-mode suppression

Should cancel common-mode (why?)

The matrix

 

Differential signals, the matrix compiled



Compile the transfer functions into a handy matrix

$$\begin{bmatrix} \Delta V_{out} \\ \nabla V_{out} \end{bmatrix} = \begin{bmatrix} A_{df} & A_{df,cm} \\ A_{cm,df} & A_{cm} \end{bmatrix} \begin{bmatrix} \Delta V_{in} \\ \nabla V_{in} \end{bmatrix}$$

Which terms should be 0?

Differential signals, metrics



Common-mode rejection ratio

$$\text{CMRR} = \frac{A_{df}}{A_{cm}}$$

Design targets

Maximize the differential gain

Minimize the common-mode gain


Differential signals, two CS stages



Common-mode range (CMR)

Common-mode levels for which the transistors operate in saturation

 The common-mode rejection is 0 dB - effectively there is no rejection!



Differential signals


Two common-source stages
in parallel

$$\text{CMRR} = \frac{A_{df}}{A_{cm}}$$

The differential pair

Tail source

$$\text{CMRR} = \infty$$

 

Differential signals, differential pair

Improved (infinite) CMRR to the cost of CMR

$$\Delta I = 4\alpha \cdot V_{eff} \cdot \Delta V \text{ and } \nabla I = I_0/2 \text{ (!)}$$

Further on


$$I_0 = 2\alpha \cdot (V_{eff}^2 + \Delta V^2)$$

combines into

$$\Delta I = 4\alpha \cdot \Delta V \cdot \sqrt{\frac{I_0}{2\alpha} - \Delta V^2} \text{ (!)}$$

such that
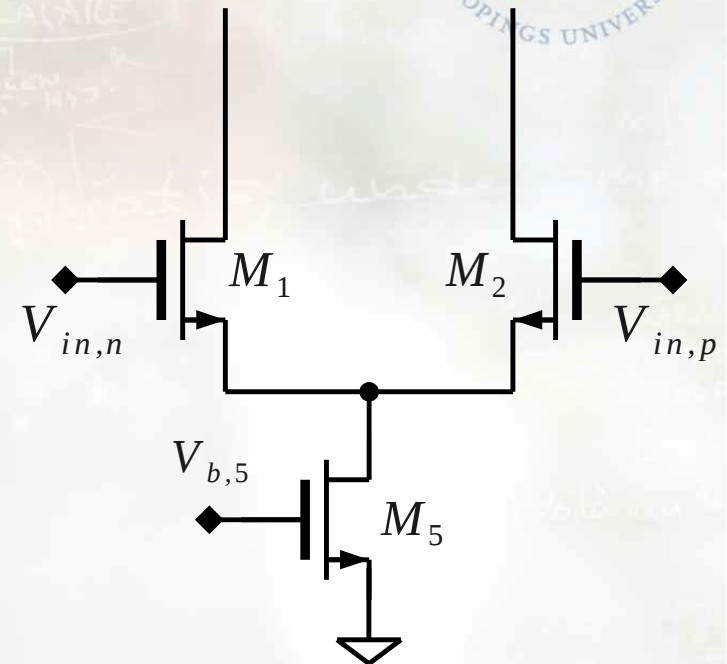
$$\frac{d\Delta I}{d\Delta V} = 4\alpha \cdot \sqrt{\frac{I_0}{2\alpha}} = 4\alpha V_{eff} = \frac{2I_0}{V_{eff}} \text{ and } \frac{d\nabla I}{d\nabla V} = 0$$



Differential pair with active load



Current-to-voltage conversion


Resistors

Current mirror active load

Current-source active load

Common-mode can be further suppressed using a common-mode feedback circuit (CMFB)

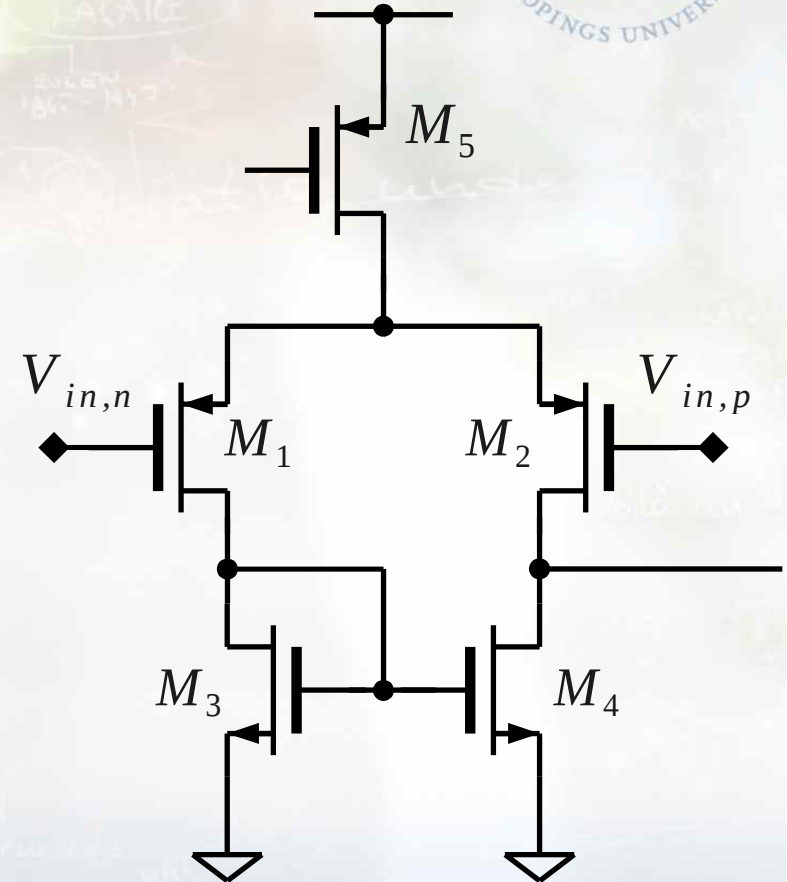Additional feedback amplifier sensing the common-mode level at the output



And that were all basic building blocks!



The basic stages

Common-source, Common-gate, Common-drain

Current-mirror

Enhanced gain

Gain boosting, (Telescopic) cascodes, folded cascode

Multiple-stages

The differential pair

Mismatch, or "In reality, nothing is perfect ..."

Differences in

Fabs (wafer-to-wafer, fabrication, date)

Wafer locations (chip-to-chip, doping)

Transistor (block-by-block, orientation and side effects, doping)

Temperatures, Voltages, Currents

You cannot assume that one transistor is identical to another

Especially not for high-speed, high-accuracy applications

Mismatch, cont'd



The drain current in the saturation region:

$$\Delta I_D = \underbrace{\frac{dI_D}{d\beta} \cdot \Delta\beta + \frac{dI_D}{dS} \cdot \Delta S}_{\Delta\alpha} + \frac{dI_D}{dV_{eff}} \cdot \Delta V_{eff} + \frac{dI_D}{dV_{ds}} \cdot \Delta V_{ds} =$$

$$= \underbrace{\frac{I_D}{\beta} \cdot \Delta\beta + \frac{I_D}{S} \cdot \Delta S}_{\Delta\alpha} + \frac{2I_d}{V_{eff}} \cdot \Delta V_{eff} + \frac{\lambda I_d}{1 + \lambda(V_{ds} - V_{eff})} \cdot \Delta V_{ds} \Rightarrow$$

$$\frac{\Delta I_D}{I_D} = \underbrace{\frac{\Delta\beta}{\beta} + \frac{\Delta S}{S}}_{\Delta\alpha} + \frac{2\Delta V_{eff}}{V_{eff}} + \frac{\lambda \Delta V_{ds}}{1 + \lambda(V_{ds} - V_{eff})} \Rightarrow$$

$$\frac{\Delta I_D}{I_D} \approx \frac{\Delta\alpha}{\alpha} + \frac{2\Delta V_{eff}}{V_{eff}}$$

Mismatch, cont'd

Ignoring the low-impact ones, and assuming that they are decoupled, gives us, with the help of stochastic variables:

$$\sigma^2 \left(\frac{\Delta I_D}{I_D} \right) = \sigma^2 \left(\frac{\Delta \alpha}{\alpha} \right) + \frac{\sigma^2 (\Delta V_{eff})}{V_{eff}^2}$$

First-order assumptions

$$\sigma^2 \left(\frac{\Delta \alpha}{\alpha} \right) \approx \frac{A_S^2}{W \cdot L} \quad \text{and} \quad \sigma^2 (\Delta V_{eff}) \approx \frac{A_{VT}^2}{W \cdot L}$$

Second-order assumptions

Distance-related, correlations, etc.

Mismatch, what does this mean?




Unmatched references

Current mirrors will have different output currents

Offset

 A skewed differential pair can be modeled as an input offset



Mismatch, conclusions


Effective voltage cannot be too low

$$V_{eff} > 100 \text{ mV}$$

Transistors need to be very large for high accuracy

Large transistors mean larger capacitors
mean slower systems

 Mismatch errors will give an offset at input,
unbalanced branches and thus poor CMRR and
PSRR (power supply rejection).



What did we do today?



Differential signals

Why differential?

Common-mode definitions

Differential pair

Analysis

Operation

Mismatch

Impact of mismatch on design/performance/behavior

What will we do next time?



Operational amplifiers

Stability

Frequency analysis

Compensation