

EXERCISE SECTION 13: TRANSMISSION LINES

13.1. Transmission line basics

A transmission line of length L connects a load to a sinusoidal voltage source with an oscillation frequency f . Assuming that the velocity of wave propagation on the line is c .

For which of the following situations is it reasonable to ignore the presence of the transmission line in the solution of the circuit (and why? Figure 13.1.1 might help you.).

- a) $L=20$ cm, $f=20$ kHz
- b) $L=50$ km, $f=60$ Hz
- c) $L=20$ cm, $f=600$ MHz
- d) $L=1$ mm, $f=100$ GHz

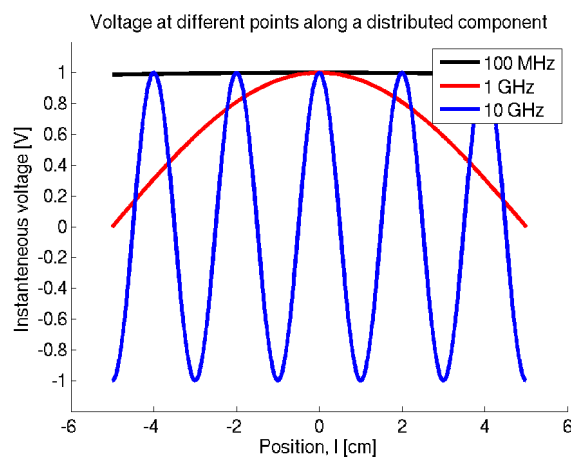


Figure 13.1.1: Example of a (normalized) wave through a physical distance.

13.2. Reflections

Assume a transmission line with characteristic impedance of

$$Z_0=50 \text{ } \Omega \text{ and source resistance of } R_S=1 \text{ } \Omega.$$

The load resistance is $R_L=1000$ Ω and the input voltage describes a step function from 0 to 5 Volts at $t=0$.



The speed-of-propagation is $u = 20$ cm/ns. The transmission line is 20 cm long.

- What are the reflection coefficients at both ends?
- Find the voltage across the load resistor as a function of time.
- What is the final voltage at the load resistor.

x This exercise also exists in the andaLectureTest lab library.

13.3. Matched loads

Assume a transmission line with characteristic impedance of

$Z_0 = 50 \Omega$, and source resistance of $R_S = 25 \Omega$.

The load resistance is $R_L = 50 \Omega$ and the input voltage describes a step function from 0 to 5 Volts at $t = 0$.

The speed-of-propagation is $u = 20$ cm/ns. The transmission line is 20 cm long.

- What are the reflection coefficients at both ends?
- Find the voltage across the load resistor as a function of time.
- What is the final voltage at the load resistor.

x This exercise also exists in the andaLectureTest lab library.

13.4. DC Termination

Assume you have a transmission line with a characteristic impedance of

$Z_0 = 50 \Omega$, and source resistance of $R_S = 67 \Omega$

The termination load consists of two resistors, one from supply to the end point and one to ground from the end point. Call them R_1 and R_2 , respectively. The input describes a step from 0 to 3.3 Volts at $t = 0$.

- Dimension R_1 and R_2 to provide matched load and a DC voltage of 0.75 V.
- Calculate the current through the driver for the high and low states.
- With the "traditional" termination (only resistor R_2), what would be the current through the driver for high and low states?
- Which configuration, b or c, consumes most power?