

## **Written Test TSTE80, Analog and Discrete-time Integrated Circuits**

---

Date:	May 29, 2006
Time:	8-12
Place:	TER1
Max.no. of points:	25
Grades:	10p for 3, 15p for 4, and 20p for 5.
Allowed material:	All types of calculators except laptops. All types of official tables and handbooks. Textbooks: Johns & Martin: Analog Integrated Circuit Design. Razavi: Design of Analog CMOS Integrated Circuits. Sedra&Smith: Microelectronic Circuits. Dictionaries.
Examiner:	Sune Söderkvist
Responsible teacher:	Sune Söderkvist. Tel.: 281355.
Correct (?) solutions:	Solutions and results will be displayed in House B, entrance 25-27, ground floor.

<b>Graded exams are returned on examiner's office times, tuesdays and fridays at 11.00-13.00, during week no.23 and 24.</b>
---

### **Students instructions**

- The CMOS transistor operation regions, small-signal parameters, and noise characteristics are found on the last page of this exam.
- Generally, do not just answer yes or no to a short question. You always have to answer with figures, formulas etc., otherwise no or fewer points will be given.
- You may write down your answers in Swedish or English.

### **For students who has studied earlier variants of the course :**


The conditions for the test is the same as before, i.e. every problem gives max. 8 points and you get credits for project and assignments as before. Mark 3 require 30 p totalt, mark 4 require 42 p and mark 5 require 56 p. Please, tell me on the wrapper if this is of interest.

**Good Luck!**

### Exercise 1.

The circuit in **Figure 1** is a commonly used structure when designing analog circuits. Transistor M1 is assumed to be biased in saturation. Also assume that the  $W/L$  ratio of transistor M2 is  $K$  times larger than that of transistor M1. The channel-length modulation can be neglected.

- Derive the output voltage  $V_{out}$  as a function of the factor  $K$ , i.e.  $V_{out} = f(K)$  when M2 is saturated. Express  $V_{out}$  in terms of the current  $I_0$  and transistor design parameters, but not voltages. (1p)
- Derive the output voltage  $V_{out}$  as a function of the factor  $K$ , i.e.  $V_{out} = f(K)$  when M2 is operating in the linear region. Express  $V_{out}$  in terms of the current  $I_0$  and transistor design parameters, but not voltages. (2p)
- Determine for which values of  $K$  transistor M2 switches from operating in the saturation region to the linear region. (2p)

 


**Figure 1:** A commonly used analog circuit.

## Exercise 2.

**Figure 2** shows an gain-boostered folded-cascode amplifier. All transistors are biased to operate in the saturation region. Assume that the transistors small-signal parameters are  $g_{m1}$ ,  $g_{mbs1}$ ,  $g_{ds1}$ ,  $g_{m2}$ ,  $g_{mbs2}$ ,  $g_{ds2}$  and  $g_{m3}$ ,  $g_{mbs3}$ ,  $g_{ds3}$  respectively.

- Sketch a small-signal equivalent circuit and determine an exact expression for the transfer function  $H(s) = V_{out}(s)/V_{in}(s)$ . The bulk effect can **not** be neglected. However, all capacitors but  $C_L$  can be neglected. (3p)
- Now, neglect the bulk effect and assume that  $g_m \gg g_{ds}$  to get an approximation of  $H(s) = V_{out}(s)/V_{in}(s)$ . From this approximative expression, determine the DC gain, the first pole, and the unity-gain frequency. (1p)
- Express the DC gain in terms of the design parameters  $W_i$ , and  $L_i$  for the transistors  $M_i$ ,  $i = 1, 2, 3$ , and answer (motivate) following questions. (1p)

How is the DC gain changed: If the current  $I_0$  is increased? If the channel-length of transistor  $M3$  is increased? If the channel-width of transistor  $M3$  is increased? Assume that all transistors remain saturated. (1p)

 


**Figure 2:** A gain-boostered folded-cascode amplifier.

### Exercise 3.

A switched capacitor circuit in clock phase 1 is shown in **figure 3**. The value of  $V_{in}$  changes only at time  $t, t + 2\tau, t + 4\tau$ , and so on, i.e.,  $V_{in}(t) = V_{in}(t + \tau)$ .

- Express the output voltage,  $V_{out}(z)$ , as a function of the input voltage,  $V_{in}(z)$ , for clock phase 1. Assume that the operational amplifier is ideal. (4p)
- Is the circuit insensitive to capacitive parasitics? Motivate your answer carefully. (1p)

 


**Figure 3:** A switched-capacitor circuit in clock phase 1.

### Exercise 4.

**Figure 4a** shows a differential gain-stage with single-ended output, and **Figure 4b** shows a differential gain-stage with fully differential output, where  $V_{out} = V_{outp} - V_{outn}$ . In the following you can neglect the parasitics and the current source,  $I_0$ , is assumed to be ideal. Furthermore, the transistors in the gain-stages are matched, i.e. M2 and M4 are identical, as well as M1 and M3. Also the transistors M01 and M02 in the current mirror are identical.


- For the gain-stage in **figure 4a**, derive an expression for the transfer function from GND to the output  $V_{out}$  and use this expression to determine an expression for Power Supply Rejection Ratio (PSRR). Assume that the gain-stage has the gain  $A_{single}$ . (2p)
- Assume that  $A_{single}$  can be approximated with  $A_{single} \approx \frac{g_{m3}}{g_{ds3} + g_{ds4}}$ . Enter that expression in the expression you derived in a) and use this new expression to explain how to change the design of the current mirror to increase PSRR. (1p)
- Now, regard the gain-stage in **figure 4b** and derive an expression for the transfer function from GND to the differentiell output signal, and use this expression to determine an expression for PSRR if the gain-stage has the gain  $A_{diff}$ . (1p)
- Explain what happens to PSRR in c) if you have mismatch between transistors M2 and M4 as well as between M1 and M3. (1p)

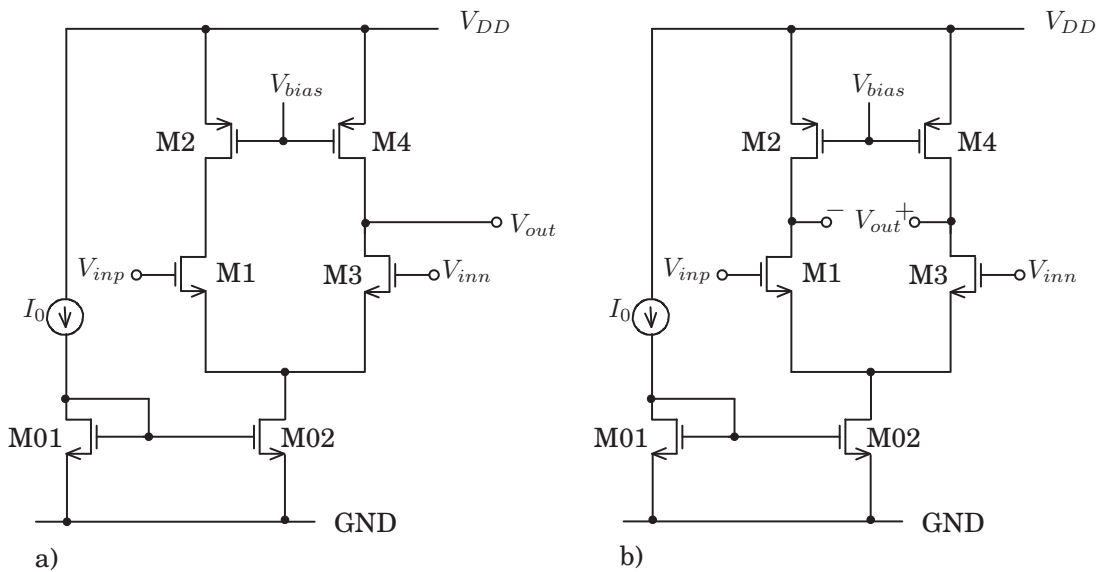

**Figure 4:** Differentialförstärkare.

### Exercise 5.

The inverting amplifier in **Figure 5a** is used in an application where low noise is of major importance. Hence, a low noise design of the amplifier is required. In this exercise, only the thermal noise in the op.amp. is considered. The gain of the op.amp.  $A = g_{m1}/g_{out} = g_{m1}/(g_{ds2} + g_{ds4})$ . Further, the ratio between  $R_2$  and  $R_1$  is  $R_2/R_1 = a$ .

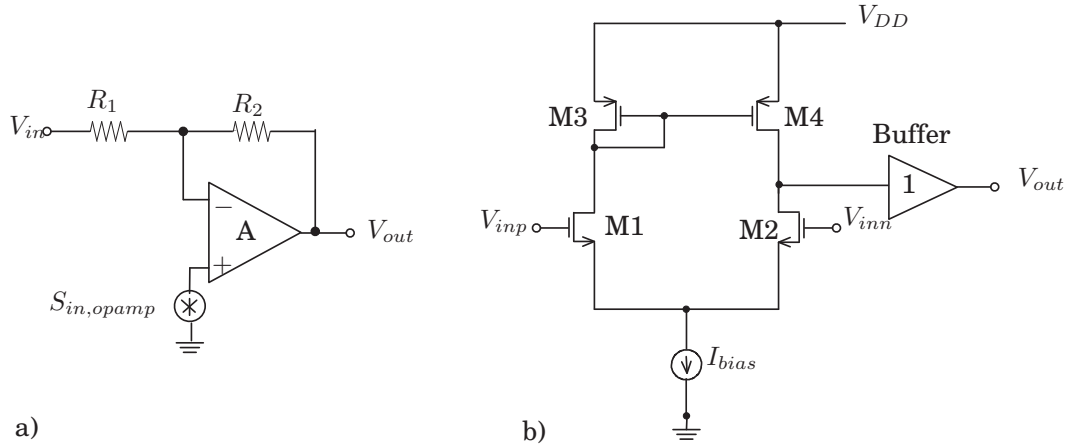

**Figure 5:** a) A noisy inverting op.amp. b) The principal schematic of the op.amp.

- a) Assume that the resistors do not generate any thermal noise while the op.amp. has an equivalent voltage input noise spectral density of

$$S_{in,opamp} = \frac{16kT}{3} \frac{1}{g_{m1}} \left[ 1 + \frac{g_{m4}}{g_{m1}} \right]$$

where the number in the index refers to the op.amp. implementation in **Figure 5b**. Compute the equivalent output noise spectral density for the circuit in **Figure 5a** caused by the noisy amplifier. (4p)

- b) State one approach to decrease the equivalent output noise spectral density of the circuit in **Figure 5a** caused by the operational amplifier. How does this impact the DC gain of the open loop amplifier? (1p)

# Transistor formulas and noise

## 1 CMOS transistors

**Current and threshold voltage formulas and operating regions for an NMOS transistor**

Cut-off:  $V_{GS} < V_T$   $I_D \approx 0$

Linear:  $V_{GS} - V_T > V_{DS} > 0$   $I_D \approx \alpha(2(V_{GS} - V_T) - V_{DS})V_{DS}$

Saturation:  $0 < V_{GS} - V_T < V_{DS}$   $I_D \approx \alpha(V_{GS} - V_T)^2(1 + \lambda V_{DS})$

All regions:  $V_T = V_{T,0} + \gamma(\sqrt{2\phi_F - V_{BS}} - \sqrt{2\phi_F})$

**Small-signal parameters**

Linear:  $g_m \approx 2\alpha V_{DS}$   $g_{ds} \approx 2\alpha(V_{GS} - V_T - V_{DS})$

Saturation:  $g_m \approx 2\sqrt{\alpha I_D}$   $g_{ds} \approx \lambda I_D$

**Constants:**  $\alpha = \frac{1}{2}\mu_0 C_{ox} \frac{W}{L}$   $\lambda = \sqrt{\frac{2K_s \epsilon_0}{q N_A \phi_0}} \cdot \frac{1}{L}$   $\gamma = \frac{\sqrt{2q N_A K_s \epsilon_0}}{C_{ox}}$

## 2 Circuit noise

**Thermal noise in CMOS transistors**

The thermal noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{8kT}{3} \frac{1}{g_m}$$

**Thermal noise in resistors**

The thermal noise spectral density of a resistor is modeled as a parallel noise current source

$$\frac{\bar{i}^2}{\Delta f} = \frac{4kT}{R}$$

**Flicker noise in CMOS transistors**

The flicker noise spectral density at the gate of a CMOS transistor is

$$\frac{\bar{v}^2}{\Delta f} = \frac{K}{WLC_{ox}f}$$