

TSTE12 Design of Digital Systems Lecture 7

Kent Palmkvist

Agenda

- Practical issues
- Algorithm level design
 - Larger models
 - Time multiplexing
- RTL level models
 - Control units
- Gate level models

TSTE12 Deadlines Y,D,ED

- Initial version design sketch and project plan tuesday 12 September
- Weekly meetings should start
 - Internal weekly meeting with transcript sent to supervisor
- Lab 2 soft deadline Wednesday 13 September at 21.00
 - Lab 2 results will be checked after project end

TSTE12 Deadlines MELE, erasmus

- First project meeting no later than today Monday 11 September
- Tuesday 12 September: First version of requirement specification
- Wednesday 13 September 21.00: Lab 1 deadline
 - Pass required to be allowed continued project participation

Handin (homework), Individual!


- 1st handin published today Monday 11 September
 - Deadline Monday 18 September 23:30
 - Use only plan text editor (emacs, vi, modelsim or similar) for code entry.
 - Solve tasks INDIVIDUALLY
 - Submit answers using Lisam assignment function
 - 4 different submissions for code, one for each code task
 - 1 submission for all theory question answers
 - Use a special terminal window when working with handins
- module load TSTE12 ; TSTE12handin

Algorithm level design

- Focus on functions at high abstraction level
 - Subsystems
 - Algorithms to use
- Ignore timing, datapaths etc.

Bigger system example

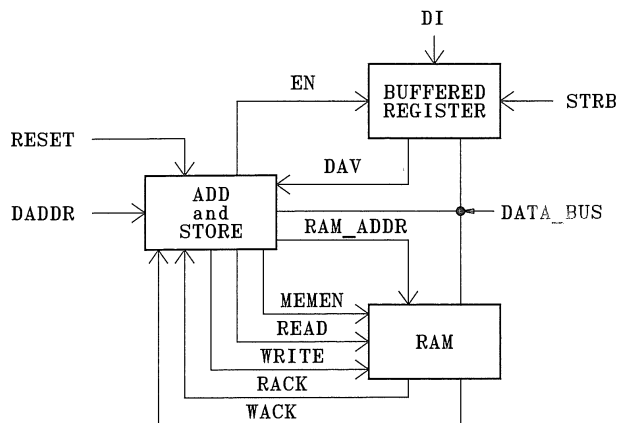- 3 units, Add and Store, Buffered Register, RAM
- Predefined sequence
 - Store value in buffer
 - move buffer value to add and store unit
 - Read memory content and add to input value
 - Write back result to memory



Bigger system example, cont.

- DATA_BUS driven by all modules
 - Requires a resolution function
 - Preset to ZZZ to get a useful value (X will always give X)
 - Note this is done in the entity! Reason: inout => Driver on the entity

```
entity RAM is
  generic(RDEL, DISDEL, ACK_DEL, ACK_PW: TIME);
  port(DATA: inout BUS1(7 downto 0):="ZZZZZZZZ";
        ADDR: in MVL4_VECTOR(4 downto 0);
        RD, WRITE, CS: in MVL4;
        RACK, WACK: out MVL4);
end RAM;
```

Simple RAM model

- Use of MVL4
=> use drive
and sense
functions

```
architecture SIMPLE of RAM is
begin
  MEM: process (CS,RD,WRITE)
    type MEMORY is array(0 to 31) of MVL4_VECTOR(7 downto 0);
    variable MEM: MEMORY:= (others => (others => '0'));
  begin
    if CS = '1' then
      if RD = '1' then
        DATA <= DRIVE(MEM(INTVAL(ADDR))) after RDEL;
        RACK <= '1' after ACK_DEL,
              '0' after ACK_DEL + ACK_PW;
      elsif WRITE = '1' then
        MEM (INTVAL(ADDR)):= SENSE(DATA,'1');
        WACK <= '1' after ACK_DEL, '0' after ACK_DEL+ACK_PW;
      end if;
    else
      DATA <= "ZZZZZZZ" after DISDEL;
    end if;
  end process MEM;
end SIMPLE;
```

Bigger example, cont.

- The RAM-model uses an aggregate to initialize all elements to zero
- ADD and Store is a form of a state machine
 - Go through a sequence step by step
 - Execute some function in each step
 - Each step ends in a wait
- Divide system into datapath and control
- Clock generation as earlier (loop with run)

Bigger example, cont.

```


CON: process
  variable DATA_REG:
    MVL4_VECTOR(7 downto 0);
  begin
    if RESET = '1' then          --CS0
      DATA <= "ZZZZZZZ"after DIS_DEL;
    end if;
    wait on DAV until DAV = '1';
  -----
  EN <= '1' after CON_DEL;      --CS1
  wait for CLK_PER;
  -----
  EN <= '0' after CON_DEL;
  DATA_REG := SENSE(DATA, '1'); --CS2
  wait for CLK_PER;
  -----
  MADDR <= DADDR after MA_DEL;
  MEMEN <= '1' after CON_DEL;   --CS3
  READ <= '1' after CON_DEL;
  wait on RACK until RACK = '1';
  -----
  DATA_REG :=
    ADD8(SENSE(DATA, '1'), DATA_REG);
  READ <= '0'after CON_DEL;
  MEMEN <= '0'after CON_DEL;   --CS4
  wait for CLK_PER;
  -----
  DATA <= DRIVE(DATA_REG) after D0_DEL;
  WRITE <= '1'after CON_DEL;
  MEMEN <= '1'after CON_DEL;   --CS5
  wait on WACK until WACK = '1';
  -----
  WRITE <= '0'after CON_DEL;
  MEMEN <= '0'after CON_DEL;   --CS6
  DATA <= "ZZZZZZZ" after DIS_DEL;
  wait for CLK_PER;
end process CON;

```

Control state machine

- Hardware aspects on the control machine
 - Wait can not be used in synthesis
 - Use a manual direct translation technique
- One-hot encoding
 - Simple and straight forward
 - Suitable for FPGA implementation
 - Low complexity decoding of state

One-hot encoded controller

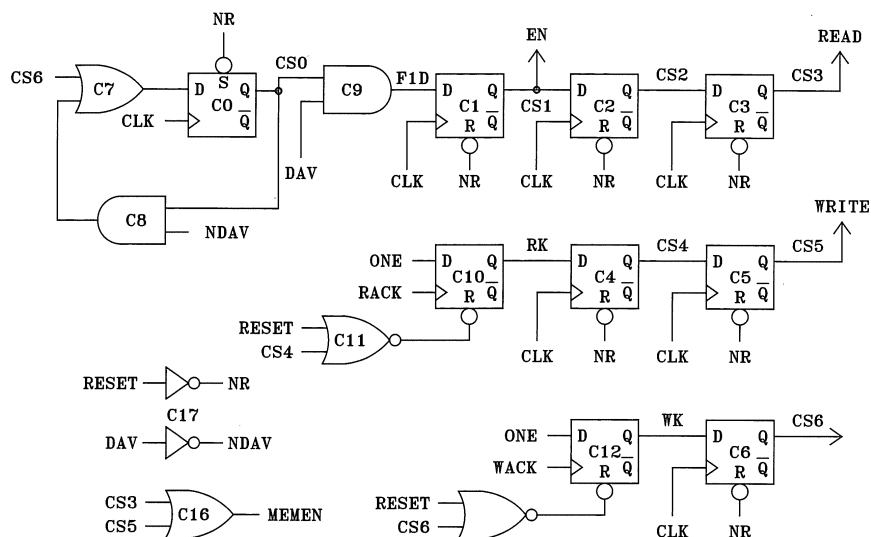

Control step classes

- Automatic increase
 - From step c_i to c_{i+1} after some time
- Handshake
 - Wait for DAV, CS1 \Rightarrow EN = 1, Buffer resets DAV when EN = 1
- Asynchronous stepping
 - CS3 to CS4: Wait for external RACK edge, RACK may be shorter than 1 clock period!

Hardware vs Behavioral model


- Important to have same behavior of hardware and VHDL model
- Reset behavior is different
 - The model only checks for reset in CS0
 - Hardware checked reset everywhere
 - Different behavior between model and HW! Bad.
 - Add reset check in every control step

Why single clock domain

- Reset problems
 - Even single clock domain should synchronize asynchronous reset inputs
 - Must guarantee that whole circuit releases from reset at the same time
- Communication problems
 - Possible race between data and clock
 - Metastability

Control branching

- Want a control machine able to handle conditional execution of sequences
 - Similar to hierarchical finite state machine (FSM)
 - VHDL cannot do jumps, only breaking loops
- Working implementation approach
 - Sequences in individual processes
 - Check at end of process which process to start next
- Output signals from state machine
 - Require Resolution function as assignment done in multiple processes (need to turn off non-active processes)

 

Control branching using multiple processes

architecture TWO of WAIT_STEPS is

```
signal TRIGGERB, TRIGGERBA,
       TRIGGERC, TRIGGERCA: DOT1 := '0';
signal SINT: RINTEGER register;
```

begin

A: process

```
begin
  SINT <= null;
  wait on RUN, TRIGGERBA, TRIGGERCA until RUN = '1';
  SINT <= 0; ---Step 0
  wait for CLK_DEL;
  SINT <= 1; ---Step 1
  wait for CLK_DEL;
  SINT <= null;
  if X = '1' then
    TRIGGERB <= not(TRIGGERB);
  else
    TRIGGERC <= not(TRIGGERC);
  end if;
end process A;
```

B: process

```
begin
  SINT <= null;
  wait on TRIGGERB;
  SINT <= 2; ---Step 2
  wait for CLK_DEL;
  SINT <= 3; ---Step 3
  wait for CLK_DEL;
  SINT <= null;
  TRIGGERBA <= not(TRIGGERBA);
end process B;
```

C: process

```
begin
  SINT <= null;
  wait on TRIGGERC;
  SINT <= 4; ---Step 4
  wait for CLK_DEL;
  SINT <= 5; ---Step 5
  wait for CLK_DEL;
  SINT <= null;
  TRIGGERCA <= not(TRIGGERCA);
end process C;
```

S <= SINT;

end TWO;

Time multiplexing

- Problem: Multiple processes driving one signal
 - Multiple drivers (one for each process)
 - Want to enable separate drivers at non-overlapping intervals
 - Assigned signal value should keep the value even after driver enable removed (memory function)
 - Use signal type containing a resolution function
- Remember: This is NOT for synthesis

Time Multiplexing, non-working

- Two-phase clock
 - One pulse each alternating
- Resolved output signal Z
 - Allows multiple assignment
- Problem
 - Z = 'X' when PH_TWO assign '1'
 - Assignment from PH_ONE will not turn off
 - Each driver always outputs last assigned value

```
entity TIME_MUX is
  generic(DEL1,DEL2: TIME);
  port(PHASE_ONE,PHASE_TWO: in MVL4;
        Z: out DOTX := '0');
end TIME_MUX;

architecture PROCESS_IF_0 of TIME_MUX is
begin
  PH_ONE:process(PHASE_ONE)
  begin
    if PHASE_ONE = '1' then
      Z <= '0' after DEL1;
    end if;
  end process;

  PH_TWO:process(PHASE_TWO)='1')
  begin
    if PHASE_TWO = '1' then
      Z <= '1' after DEL2;
    end if;
  end PH_TWO;
end PROCESS_IF_0;
```

Time multiplexing, cont.

- Ordinary processes

- Assignment of null disables driver
- Keyword register in signal declaration
 - defines what happen when all driver are null


architecture PROC_NULL of TIME_MUX is
signal ZINT: DOTX register;
begin

```
PH_ONE: process(PHASE_ONE)
begin
  if PHASE_ONE = '1' then
    ZINT <= '0' after DEL1;
  else
    ZINT <= null;
  end if;
end process PH_ONE;
```

```
PH_TWO: process(PHASE_TWO)
begin
  if PHASE_TWO = '1' then
    ZINT <= '1' after DEL2;
  else
    ZINT <= null;
  end if;
end process PH_TWO;
```

Z <= ZINT;

end PROC_NULL;

 

Time multiplexing, cont.

- Use bus instead of register

- Default resolution function used if not driven
 - Resolution function receives an empty input
- MVL4 resolution function start with 'Z' value!


architecture PROC_NULL of TIME_MUX is
signal ZINT: DOTX bus;
begin

```
PH_ONE: process(PHASE_ONE)
begin
  if PHASE_ONE = '1' then
    ZINT <= '0' after DEL1;
  else
    ZINT <= null;
  end if;
end process PH_ONE;
```

```
PH_TWO: process(PHASE_TWO)
begin
  if PHASE_TWO = '1' then
    ZINT <= '1' after DEL2;
  else
    ZINT <= null;
  end if;
end process PH_TWO;
```

Z <= ZINT;

end PROC_NULL;

 

Time multiplexing, cont.

- Without the use of Register/Bus.
- Separate signals, check 'QUIET' to find active assignment

```
entity TIME_MUX is
  generic(DEL1,DEL2: TIME);
  port(PHASE_ONE,PHASE_TWO: in
  MVL4;
    Z: buffer MVL4);
end TIME_MUX;

architecture QUIET_MUX of TIME_MUX is
  signal PH1,PH2,Z1,Z2: MVL4;
begin

  PH_ONE: process(PHASE_ONE)
  begin
    if PHASE_ONE = '1' then
      Z1 <= '0' after DEL1;
    end if;
  end process PH_ONE;
```

```
PH_TWO: process(PHASE_TWO)
  begin
    if PHASE_TWO = '1' then
      Z2 <= '1' after DEL2;
    end if;
  end process PH_TWO;

  Z <= Z1 when not Z1'quiet else
    Z2 when not Z2'quiet else
    Z;
end QUIET_MUX;
```

Register transfer level (RTL)

- At this level can the following aspects be analysed
 - Compare timing between different units at register level
 - Delay in subfunctions, etc.
 - Resource allocation
 - Number of buses, registers, processing elements etc.
 - Scheduling (when to perform an operation)
 - Control structure (e.g., microcoded control units)
 - Bus design

Difference between behavior and dataflow descriptions

- Behavioral model
 - System with two registers and an adder
 - Behavior description does not indicate how operations are performed
 - Command selects operation
 - Only signals that corresponds to saved data

```
entity REG_SYS is
  port(C: in BIT;
        COM: in BIT_VECTOR(0 to 1);
        INP: in BIT_VECTOR(0 to 7));
end REG_SYS;

architecture ALG of REG_SYS is
  signal R1,R2: BIT_VECTOR(0 to 7);
begin

  process(C)
  begin
    if C='1' then
      case COM is
        when "00" => R1 <= INP;
        when "01" => R2 <= INP;
        when "10" => R1 <= ADD8(R1,R2);
        when "11" =>
          R1 <= ADD8(R1,INC8(not(R2)));
        end case;
      end if;
    end process;

  end ALG;
```

Behavioral vs Dataflow, cont.

- Dataflow model
 - More signals (many for communication)
 - Operations are registers, multiplexes, or arithmetic/logic operations
 - Global decoding using signals D00 to D11
 - Corresponds to a data flow graph

Behavioral vs Dataflow, cont.

```

architecture DF1 of REG_SYS is
  signal MUX_R1, R1, R2, R2C, R2TC, MUX_ADD, SUM:
    BIT_VECTOR(0 to 7);
  signal D00, D01, D10, D11, R1E: BIT;
begin
  D00 <= not COM(0) and not COM(1);
  D01 <= not COM(0) and COM(1);    ---Command Decoder
  D10 <= COM(0) and not COM(1);
  D11 <= COM(0) and COM(1);
  MUX_R1 <= SUM when D00 = '0' else INP; --Reg 1 Mux
  R1E <= D00 or D10 or D11;

  R1_REG: process(C)    -- Register 1
  begin
    if (C='1') and C'EVENT) then
      if (R1E = '1') then
        R1 <= MUX_R1;
      end if;
    end if;
  end process;

```

```

R2_REG: process(C)    --Register 2
begin
  if (C='1') and C'EVENT) then
    if (D01 = '1') then
      R2 <= INP;
    end if;
  end if;
end process;


R2C <= not R2;          ---Complement
R2TC <= INC8(R2C);     ---Increment
MUX_ADD <= R2TC when D11 = '1' else R2; ---Adder Mux
SUM <= ADD8(R1, MUX_ADD); ---Adder

end DF1;

```

Described Dataflow implementation

- One-to-one mapping

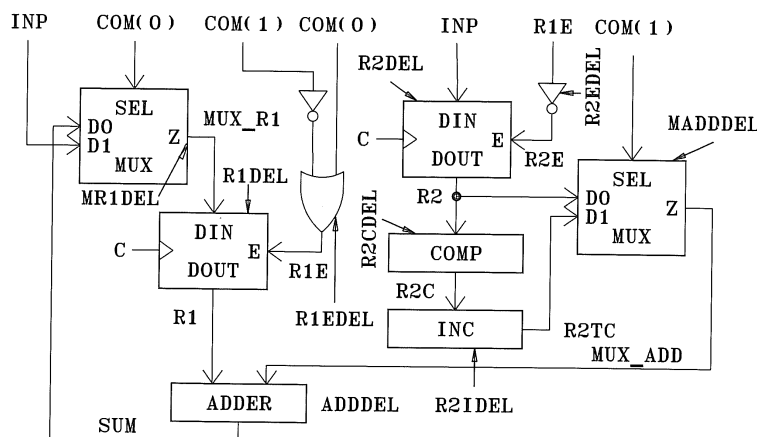

```

MUX_R1 <= SUM when D00 = '0'
  else INP;
R1E <= D00 or D10 or D11;
R1_REG: process(C) begin
  if (C='1') and C'EVENT and
    (R1E='1') then
    R1 <= MUX_R1;
  end if; end process;
R2_REG: process(C) begin
  if (C='1') and C'EVENT and
    (D01='1') then
    R2 <= INP;
  end if; end process;
R2C <= not R2;
R2TC <= INC8(R2C);
MUX_ADD <= R2TC when D11 = '1'
  else R2;
SUM <= ADD8(R1, MUX_ADD);


```

Control units

- Hard wired
 - Moore (output only dependent on state)
 - Mealy (output dependent on state and input)
 - Fast
 - Custom designed
- Microcoded
 - Cheap
 - Standardized (easy to reuse)

Microcoded control unit

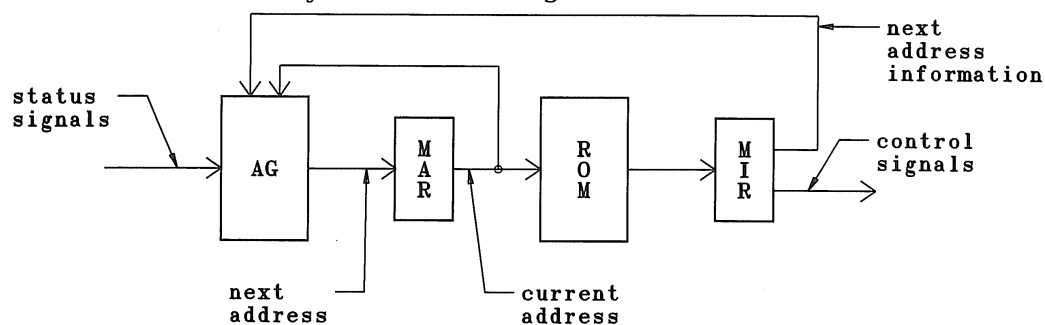- General structure
 - AG = Adress generator
 - MAR = Memory Address Register
 - MIR = Memory Instruction register




Microcoded control unit

- Advantages
 - Easy to create a generic design
 - Only ROM contents needs to be replaced
 - Easy to change existing design
 - Short design time (low design cost)
 - May use compiler to create ROM contents
- Drawbacks
 - Slower in many cases (ROM must be read)
 - Only Moore type of controllers
 - Small controllers are more expensive due to extra register and ROM
 - Must be designed for worst case regarding required features


Microcoded control unit, example

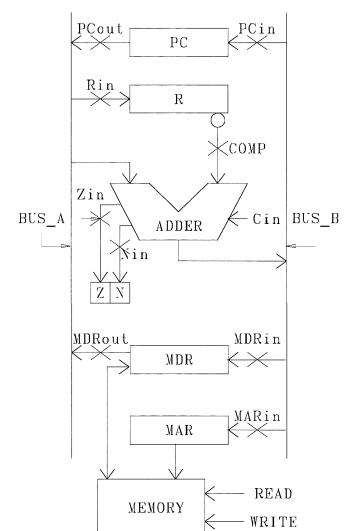- Controller for an extremely small RISC processor
 - 4 register (PC, R, MDR, MIR)
 - 1 subtraction unit
 - Some multiplexers and busses
 - Use the same add unit both for instruction operation and PC update
 - Cost: 9 clock cycles per instruction
- Only one instruction: subtract with branch on negative result
 - 3 byte instruction
 - 1st operand address, 2nd operand address, branch address



Controller for structure

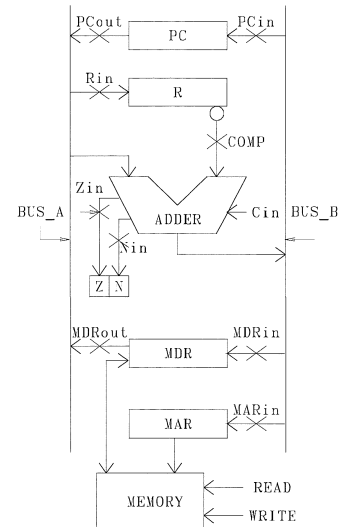- One instruction execution
 0. PCout,Zin,MARin,READ,ZEND
 1. MDRout,MARin,READ
 2. MDRout,Rin
 3. Pcout,Cin,PCin,MARin,READ
 4. MDRout,MARin,READ
 5. MDRout,COMP,Cin,Nin,MDRin,WRITE
 6. PCout,Cin,PCin,MARin,READ
 7. PCout,Cin,PCin,NNEND
 8. MDRout,Pcin
- 2 loops, 0-7 or 0-8



Control with two jumps, microcoded

- All control steps described in a ROM table
- Easy to understand
- Easy to redesign

```

----- The microinstructions ROM -----
ROM: process(C)
  type SQ_ARRAY is array(0 to 8,0 to 8) of BIT;
  constant MEM : SQ_ARRAY:=
-- 0      1      2      3      4      5      6      7      8      COLUMN
MDR_OUT,MAR_IN,N_IN,R_IN,PC_IN,ZEND,C_IN,WRITE,NNEND,micins
(('0',  '1',  '0',  '0',  '0',  '1',  '0',  '0',  '0'), --0
 ('1',  '1',  '0',  '0',  '0',  '0',  '0',  '0',  '0'), --1
 ('1',  '0',  '0',  '1',  '0',  '0',  '0',  '0',  '0'), --2
 ('0',  '1',  '0',  '0',  '1',  '0',  '1',  '0',  '0'), --3
 ('1',  '1',  '0',  '0',  '0',  '0',  '0',  '0',  '0'), --4
 ('1',  '0',  '1',  '0',  '0',  '0',  '1',  '1',  '0'), --5
 ('0',  '1',  '0',  '0',  '1',  '0',  '1',  '0',  '0'), --6
 ('0',  '0',  '0',  '0',  '1',  '0',  '1',  '0',  '1'), --7
 ('1',  '0',  '0',  '0',  '1',  '0',  '0',  '0',  '0'));--8
begin
  MDR_OUT <= MEM(INTVAL(C),0) after ROM_DEL;
  MAR_IN  <= MEM(INTVAL(C),1) after ROM_DEL;
  N_IN    <= MEM(INTVAL(C),2) after ROM_DEL;
  R_IN    <= MEM(INTVAL(C),3) after ROM_DEL;
  PC_IN   <= MEM(INTVAL(C),4) after ROM_DEL;
  ZEND   <= MEM(INTVAL(C),5) after ROM_DEL;
  C_IN    <= MEM(INTVAL(C),6) after ROM_DEL;
  WRITE  <= MEM(INTVAL(C),7) after ROM_DEL;
  NNEND  <= MEM(INTVAL(C),8) after ROM_DEL;
end process ROM;

```

URISC controller, Mealy

- Inclear sequence
- Hard to modify
- Faster

```

--Hard Wired Control Unit
--Decoder
--First Stage Decoding
ST0 <= not C(2) and not C(1) and not C(0) after AND_DEL;
ST1 <= not C(2) and not C(1) and C(0) after AND_DEL;
ST2 <= not C(2) and C(1) and not C(0) after AND_DEL;
ST3 <= not C(2) and C(1) and C(0) after AND_DEL;
ST4 <= C(2) and not C(1) and not C(0) after AND_DEL;
ST5 <= C(2) and not C(1) and C(0) after AND_DEL;
ST6 <= C(2) and C(1) and not C(0) after AND_DEL;
ST7 <= C(2) and C(1) and C(0) after AND_DEL;
--Second Stage Decoding
ST07 <= ST0 or ST7 after OR_DEL;
ST25 <= ST2 or ST5 after OR_DEL;
ST36 <= ST3 or ST6 after OR_DEL;
ST57 <= ST5 or ST7 after OR_DEL;
ST78 <= ST7 or C(3) after OR_DEL;
--Control signals
PC_OUT <= (ST07 or ST36) and not C(3)
        after (OR_DEL + AND_DEL);
C_IN <= ST36 or ST57 after OR_DEL;
PC_IN <= ST36 or ST78 after OR_DEL;
MAR_IN <= not(ST25 or ST78) after (OR_DEL + INV_DEL);
MDR_OUT <=not PC_OUT after INV_DEL;
READ <= MAR_IN; COMP <= ST5; N_IN <= ST5; MDR_IN <= ST5;
WRITE <= ST5; R_IN <= ST2; ZIN <= ST0; ZEND <=ST0;
NNEND <= ST7;

```

More on microcoded controllers

- Lecture 11 will cover more details on microcoded controller structures
 - Introduces also lab 3
- Lab 3 includes an example of a microcoded controller structure
 - Controller used to control a user interface and a datapath
 - Y and D program students have seen this approach in computer technology courses
 - Used there for creating machine instruction implementations

Gate level simulation

- All designs will eventually reach the gate level
- Need accuracy to allow check of timing requirements
 - Setup time on flip-flops
 - Clock signals
 - Races, hazards
 - Glitch example (inverter + and with rising edge input)
- Models must be efficient
 - Large number of gates
 - Slow simulation due to accuracy
 - Still much faster than spice simulation

How accurate can a gate model be?

- Example: 2 input OR-gate

```
Entity OR2 IS
  Port (I1, I2 : in bit; O : out bit);
END OR2;
Architecture DELTA_DEL of OR2 IS
BEGIN
  O <= I1 OR I2;
END DELTA_DEL;
Architecture FIXED_DEL OF OR2 IS
BEGIN
  O <= I1 OR I2 after 3 ns;
END FIXED_DEL;
```

```
ENTITY OR2G IS
  Generic (DEL: TIME)M
  Port (I1, I2 : in bit; O : out
  bit);
END OR2G;
Architecture GNR_DEL of
  OR2G IS
BEGIN
  O <= I1 OR I2 after DEL;
END GNR_DEL;
```

Model accuracy

- Models are better and better, but not good enough
 - Multiple timing models required
 - typical delay, max, min
- Want single model, only changing one constant
 - Timing_CONTROL
 - Set one constant to define type of timing (min, max, typical)

Code example

```
use work.TIMING_CONTROL.all;
entity OR2_TV is
  generic(TMIN,TMAX,TTYP: TIME);
  port(I1,I2: in BIT; O: out BIT);
end OR2_TV;

architecture VAR_T of OR2_TV is
begin
  O <= I1 or I2 after T_CHOICE(TIMING_SEL,
    TMIN,TMAX,TTYP);
end VAR_T;
```

```
package TIMING_CONTROL is
  type TIMING is (MIN,MAX,TYP,DELTA);
  constant TIMING_SEL: TIMING := TYP;
  function T_CHOICE(TIMING_SEL: TIMING;
    TMIN,TMAX,TTYP: TIME)
    return TIME;
end TIMING_CONTROL;
```

```
package body TIMING_CONTROL is
  function T_CHOICE(TIMING_SEL: TIMING;
    TMIN,TMAX,TTYP: TIME)
    return TIME is
  begin
    case TIMING_SEL is
      when DELTA => return 0 ns;
      when TYP => return TTYP;
      when MAX => return TMAX;
      when MIN => return TMIN;
    end case;
  end T_CHOICE;
end TIMING_CONTROL;
```

Additional timing details

- Timing is asymmetric
 - Different rise and fall times
 - Needs modeling

```
entity OR2GV is
  generic(TPLH,TPHL: TIME);
  port(I1,I2: in BIT; O: out BIT);
end OR2GV;
```

```
architecture VAR_DEL of OR2GV is
begin
  process(I1,I2)
    variable OR_NEW,OR_OLD:BIT;
  begin
    OR_NEW := I1 or I2;
    if OR_NEW = '1' and OR_OLD = '0' then
      O <= OR_NEW after TPLH;
    elsif OR_NEW = '0' and OR_OLD = '1' then
      O <= OR_NEW after TPHL;
    end if;
    OR_OLD := OR_NEW;
  end process;
end VAR_DEL;
```

Load dependency


- Every attached gate input slows the output speed
 - Large fan-out
 - Load is gate dependent
 - Number of transistor gates connected
 - Size of transistors on input gate
- Each connection corresponds to a small delay
 - Model each individual input wire delay
 - Gate delay included in output wire delay
- Not good enough still
 - Delay depends on edge slope, temperature, etc.

Common model used in synopsis library compiler

- $D_{TOTAL} = D_I + D_S + D_T + D_C$
- D_I = Intrinsic delay inherent in gate and independent of where/how it is used
- D_S = Slope delay caused by ramp time of the input signal
- D_T Transition delay caused by loading of the output pin (approx $R_{driver} (C_{wire} + C_{pin})$)
- D_C Connect media delay to an input pin (wire delay).

Different max and min

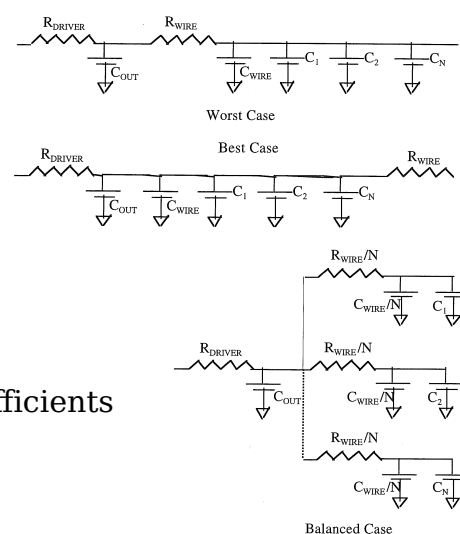- Wire delay (D_C) more complicated
 - Worst case
 - Best case
 - Balanced
- Technology library
 - Large amount of information
 - Usually described as tables
 - Sometimes described as polynomial coefficients



Back annotation

- The process of abstraction
 - adding more details to a high level model by analyzing a lower abstraction level model
 - Example: Layout information used to generate timing information in a gate netlist
- Standardized way: SDF
 - Add timing info from layout to gate level
 - Useful for general timing requirements and properties)
 - Delays module path, device, interconnect, and port

SDF file format

- Timing checks: setup, hold, recovery, removal, skew, width, period, and no change
- Timing constraints: path, skew, period, sum, and diff
- Each trippel defines min, typical, and max delay
 - One for positive edge
 - One for negative edge

```
(CELL
  (CELLTYPE "DFF")
  (INSTANCE top/b/c)
  (DELAY
    (ABSOLUTE
      (IOPATH (posedge clk) q (2:3:4) (5:6:7))
      (PORT clr (2:3:4) (5:6:7))
    )
  )
  (TIMINGCHECK
    (SETUPHOLD d (posedge clk) (3:4:5) (-1:-1:-1))
    (WIDTH clk (4.4:7.5:11.3))
  )
)
```

SDF File format, cont.

- Design/instance-specific or type/library-specific data
- Timing environment:
 - intended operating timing environment
 - Scaling, environmental, and technology parameters
- Incremental delay builds on the previous models timing by adding/subtracting timing information
- Absolute replaces timing information

Gate models of increasing complexity

- Creating accurate library models is time consuming
- Delay, timechecks etc. can be done in many different ways
- A standard has evolved that defines what parameters to use
 - Simplifies back annotation
 - Allows for accelerated models (hard-coded)

VITAL models of gates

- Three parts: Input delay, Functional and Path delay

```

library IEEE;
use IEEE.VITAL_Primitives.all;
library LIBVUOF;
use LIBVUOF.VTABLES.all;
architecture VITAL of ONAND is
  attribute VITAL_LEVEL1 of VITAL : architecture is TRUE;
  SIGNAL A_ipd : STD_ULOGIC := 'X';
  SIGNAL B_ipd : STD_ULOGIC := 'X';
  SIGNAL C_ipd : STD_ULOGIC := 'X';
  SIGNAL D_ipd : STD_ULOGIC := 'X';
begin
  -- INPUT PATH DELAYS
  WireDelay : block
  begin
    VitalWireDelay (A_ipd, A, tpd_A);
    VitalWireDelay (B_ipd, B, tpd_B);
    VitalWireDelay (C_ipd, C, tpd_C);
    VitalWireDelay (D_ipd, D, tpd_D);
  end block;

  -- BEHAVIOR SECTION
  VITALBehavior : process (A_ipd, B_ipd, C_ipd, D_ipd)
  -- functionality results
  VARIABLE Results: STD_LOGIC_VECTOR(1 to 1):=(others => 'X');
  ALIAS Y_zd : STD_LOGIC is Results(1);
  -- output glitch detection variables
  VARIABLE Y_GlitchData : VitalGlitchDataType;
  begin
    -- Functionality Section
    Y_zd := (NOT ((D_ipd) AND ((B_ipd) OR (A_ipd) OR C_ipd)));
    -- Path Delay Section
    VitalPathDelay01 (
      OutSignal => Y,
      GlitchData => Y_GlitchData,
      OutSignalName => "Y",
      OutTemp => Y_zd,
      Paths => (0 => (A_ipd'last_event, tpd_A_Y, TRUE),
                1 => (B_ipd'last_event, tpd_B_Y, TRUE),
                2 => (C_ipd'last_event, tpd_C_Y, TRUE),
                3 => (D_ipd'last_event, tpd_D_Y, TRUE)),
      Mode => OnDetect,
      Xon => Xon,
      MsgOn => MsgOn,
      MsgSeverity => WARNING);
  end process;
end VITAL;

```

Detection of timing errors

- Input path delay: Transport delay dependent on previous value and wire delay
- Functional part. Boolean expression or lookup tables for fast simulation
- Path delay: output delay, glitch handling
- Models often includes error detection
 - Short spikes, short setup/hold timing etc.
 - Unacceptable values (Z or X)
 - Unacceptable input combinations (both set and reset active on SR flipflop)

