

# Multiplication

## TSTE18 Digital Arithmetic Seminar 4

Oscar Gustafsson

- ▶ **Partial product generation**
- ▶ **Partial product accumulation**
- ▶ **Final adder**
- ▶ Squarers
- ▶ Constant multiplication


# Multiplication

## Partial product generation

- ▶ Multiplying two unsigned binary numbers  $X$  and  $Y$  can be written as

$$Z = XY = \sum_{i=-L}^{M-1} x_i 2^i \sum_{j=-L}^M y_j 2^j = \sum_{i=-L}^{M-1} \sum_{j=-L}^M x_i y_j 2^{i+j}$$

 - ▶ The resulting partial product array is




- ▶ Multiplication can typically be separated into three sub-problems
  - ▶ Generating partial products
  - ▶ Adding the partial products using a redundant number representation
  - ▶ Converting the redundant number representation to non-redundant form (commonly using a vector merging adder, VMA)





 
## Partial product generation

- ▶ Only half the number of partial product rows are now required
- ▶ Must be one bit wider to allow shifts
- ▶ Also, to possibly subtract a row, a partial product for adding the LSB must be included
- ▶ Resulting partial products array


 
## Partial product generation

- ▶ One possible realization of the modified radix-4 Booth encoding partial product generation



## Partial product generation


- ▶ Possible to define Booth encoding for higher radices
- ▶ For radix-8 the digits are  $x_i \in \{-4, -3, -2, -1, 0, 1, 2, 3, 4\}$
- ▶ Multiplication by 3 require one adder in the pre-computation part
- ▶ The number of rows are now  $\frac{M+L}{3}$  instead of  $\frac{M+L}{2}$  for radix-4
- ▶ Example: derive a truth table for Radix-8 Booth encoding

## Partial product accumulation

- ▶ Three general ways of adding the partial products
  - ▶ Sequential – some of the partial products are added in each cycle
  - ▶ Array – regular structure
  - ▶ Tree – smallest logic depth but irregular structure
 
## Partial product accumulation – Sequential


- ▶ Add one row or column in each cycle, shift the result and add one more row or column
- ▶ Five-bits row-wise sequential accumulator



- ▶ Commonly used structure for bit-serial/parallel multipliers
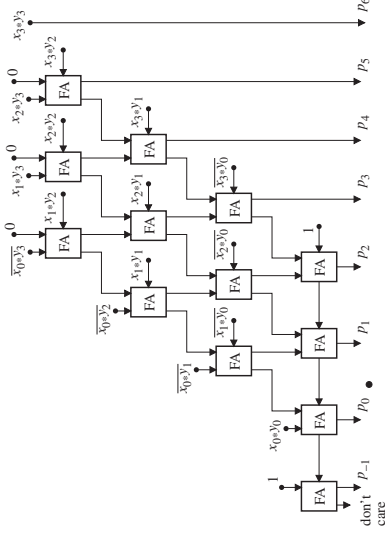
## Partial product accumulation – Array

- ▶ Use an array of almost identical cells for generation and accumulation of the partial products
- ▶ Array multiplier with multiplication time proportional to  $2W$




## Partial product accumulation – Tree

- ▶ The partial product accumulation tree should add a number of bits
- ▶ Convenient to represent these using dot diagrams
- ▶ Example of partial products from a  $6 \times 6$  multiplication



 
## Partial product accumulation – Tree

- ▶ Array accumulation gives high regularity, but at the same time the delay increase linearly with the wordlength
- ▶ Instead, we can just add all the partial products using simple building blocks such as half and full adders
- ▶ A full adder will take three partial products and output two partial products
- ▶ A full adder will take two partial products and output two partial products


 
## Partial product accumulation – Tree

- ▶ The approach to add all partial products as fast as possible by first adding as many full adders as possible and then as many half adders as possible is known as the Wallace multiplier
- ▶ The drawback of the Wallace multiplier is the excessive use of half adders
  - ▶ Half adders does not decrease the number of partial products, it only moves them to different columns



## Partial product accumulation – Tree


- ▶ An alternative approach is to try to balance the height of the columns first to later reduce as much as possible
- ▶ This approach is called the Dadda multiplier
- ▶ The sequence of wanted number of partial products is the same as the maximum number of partial products that can be reduced using a given number of levels

Levels	Partial products
1	3
2	4
3	6
4	9
5	13
6	19
7	28
8	42

- ▶ The drawback is that it hardly use any half adders and, hence, the carry-propagation may become longer

## Partial product accumulation – Tree


- ▶ Dadda tree

 

## Partial product accumulation – Tree


- ▶ The reduced area tree tries to use the best of both algorithms, fastest possible reduction, but considering half adders
- ▶ Works as follows

 1. Use as many full adders as possible for each level
2. Use half adders if (a) will result in a number of bits equal to the Dadda sequence or (b) to reduce the right-most column containing exactly two bits


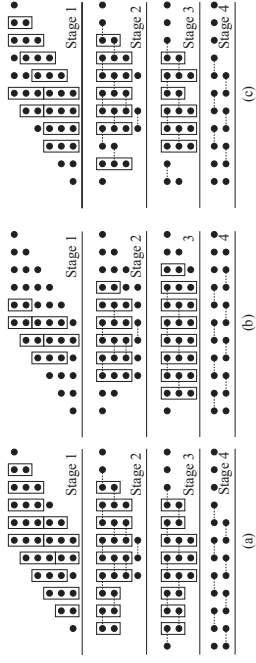
## Partial product accumulation – Tree

- ▶ Example reduction steps of the discussed algorithms: (a) Wallace, (b) Dadda, and (c) Reduced area




Tree structure	Full adders	Half adders	VMA length
Wallace	16	13	8
Dadda	15	5	10
Reduced area	18	5	7

## Counters and compressors

- ▶ A full adder counts three bits and produce a result with two bits
- ▶ Hence, this can be called a 3:2-counter
- ▶ Similarly, a half adder can be called a 2:2-counter
- ▶ This is useful when looking at alternative cells to accumulate partial products
- ▶ A  $n : k$  counter adds  $n$  bits and produce a result with  $k$  bits
- ▶ Clearly  $k \geq \log_2(n + 1)$
 
## Counters and compressors

- ▶ A compressor does not produce a valid binary count of the number of input bits
- ▶ Instead, it reduces the number of bits while having several input and output carries
- ▶ However, the output carries does not depend on the input carries
- ▶ A commonly used compressor is the 4:2 compressor as illustrated below



$$x_1 + x_2 + x_3 + x_4 + c_{in} = s + 2c + 2c_{out} \quad (1)$$

- ▶ The 4:2 compressor implemented using full adders may not have any significant advantages
- ▶ However, there are other realizations possible
- ▶ These should satisfy


- ▶ with  $c_{out}$  independent of  $c_{in}$
- ▶ Example: determine Boolean equations for a 4:2 compressor

## Vector merging adder

- ▶ Most partial products accumulation schemes results in a redundant representation
- ▶ This must be converted to non-redundant form, typically by addition
- ▶ All carry-propagation schemes from earlier seminars can be used
 
## Vector merging adder

- ▶ Often, the arrival time of the bits differ
- ▶ Shown below are the arrival times for the bits of the earlier accumulation schemes assuming unity delay for full adders



- ▶ Can use this information to optimize the vector merging adder

## Fixed-width multiplication

- ▶ Multiplying two  $N$ -bit numbers results in a  $2N$ -bit number
- ▶ Often, only  $N$  bits are of interest
- ▶ This can be utilized to simplify the multiplication
- ▶ Remove less significant partial products and possibly compensate for the error
- ▶ Commonly referred to as a fixed-width multiplication
- ▶ Example: Design a  $4 \times 4$ -bit unsigned fixed-width multiplier with 5-bit output and static compensation