

## Solution to lecture 7 exercises

7-100

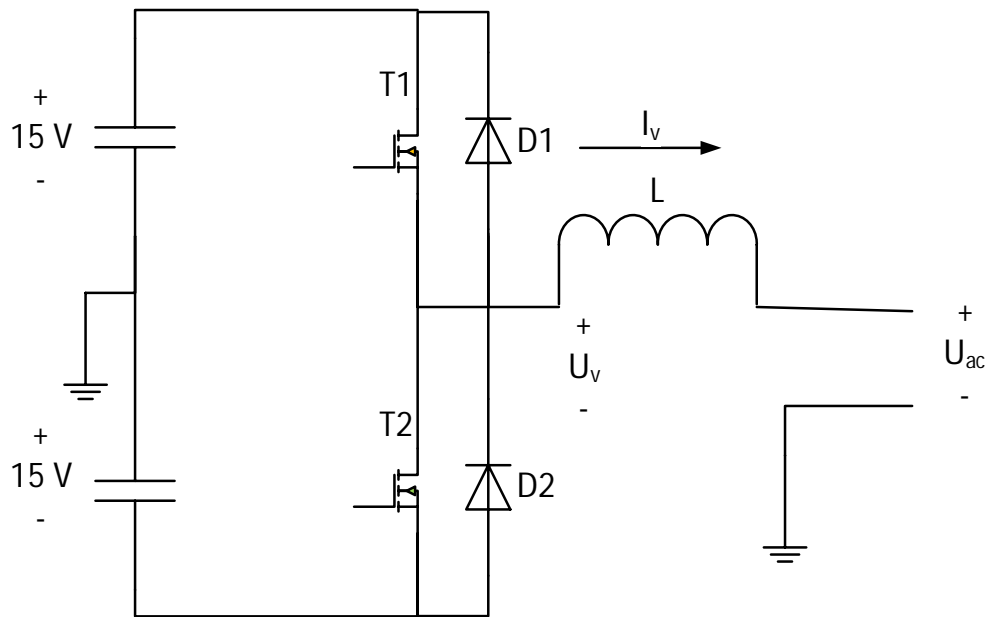


Figure 1

- $m_f=19$ ,  $f_s=19*50 = 950$  Hz
- $L = 1.0$  mH
- $I_{vpk} = 8$  A
- $m_a = 0.9$
- $P_{ac}=U_{ac}*I_v*\cos(\phi_i)=13.2*8/2=52$  W,  
 $Q_{ac}= U_{ac}*I_v*\sin(\phi_i)=0$  VAR.
- $\text{angle}(I_{v1}-U_{v1})=15$  deg
- $P_v= U_{v1}*I_v*\cos(\phi_{iv})=13.5*8/2*\cos(15\text{deg})=52$  W  
 $Q_v = U_{v1}*I_v*\sin(\phi_{iv})=13.5*8/2*\sin(15\text{deg})=14$  Var
- Switch utilization ratio =  $U_{v1}*I_v/2/(4*30*8)=5.6\%$

Tomas Jonsson