

## Exercise 1-5 RMS current calculation

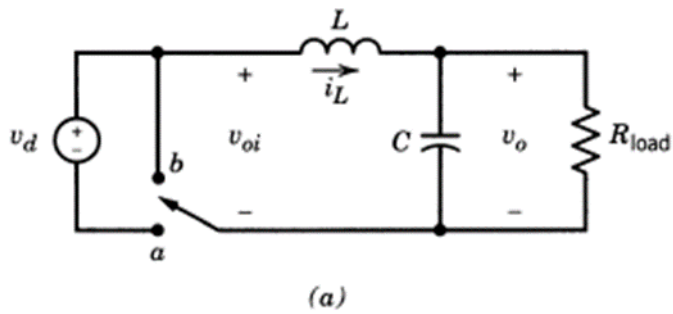


Figure 1

$V_d = 20V$   
 Duty cycle  $D = 0.75$   
 $f_s = 300kHz$   
 $L = 1.3 \mu H$   
 $C = 50 \mu F$   
 $P_{load} = 240W$   
 $V_o = 15V$

The inductor current is defined with an average value given by  $P_{load}$  and  $V_o$ :  $I_{L_{av}} = 240/15 = 16A$ .

The switched voltage  $v_{oi}$  is defined by the duty cycle  $D$  as shown below.

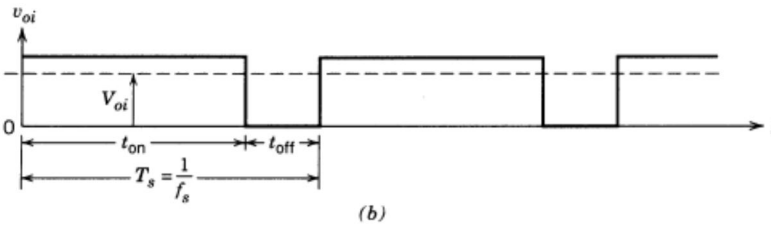


Figure 2

$$T_s = 1/300kHz = 3.33 \mu s$$

$$T_{on} = D * T_s = 0.75 * 3.33 \mu s = 2.5 \mu s$$

The ripple current is defined by the voltage across the inductor,  $v_L = v_{oi} - v_o$

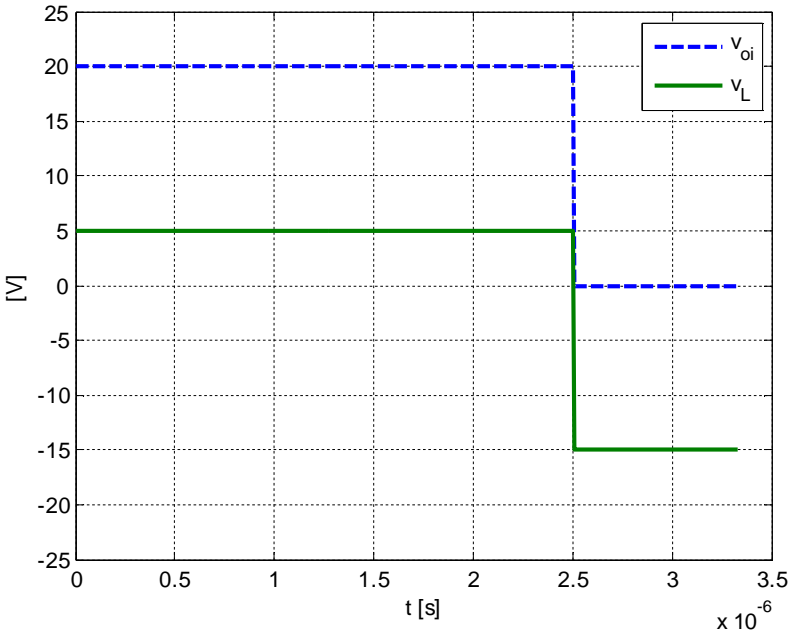


Figure 3

The current gets two slopes:

- Rising slope with a  $di_1/dt = v_{L1}/L = 5/1.3$  [A/μs]
- Dropping slope  $di_2/dt = v_{L2}/L = -15/1.3$  [A/μs]

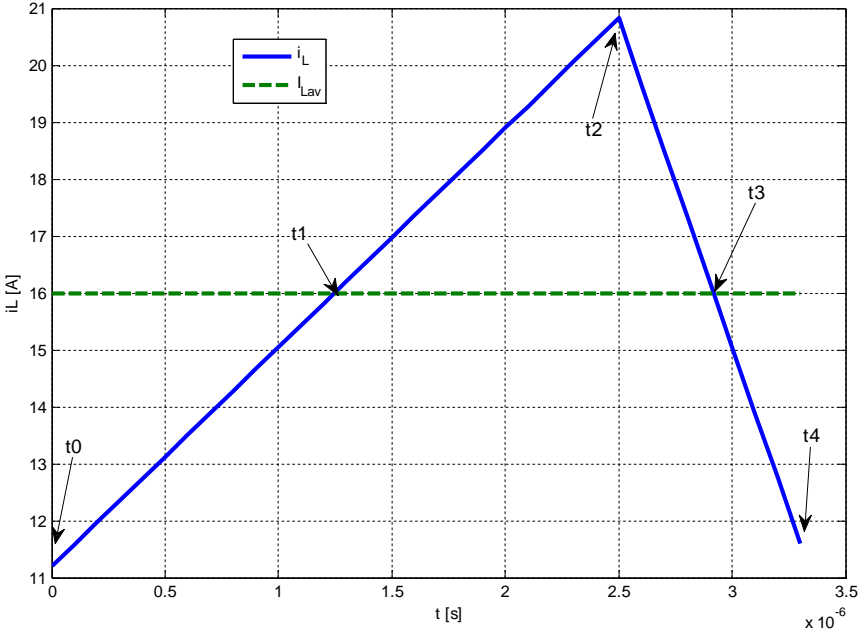


Figure 4

t1=1.25μs, t2=2.5μs, t3=2.9μs, t4=3.3μs

The RMS current of the inductor current can be divided in a dc-part ( $I_{Lav}$ ) and a ripple-part ( $i_{Lr}$ ). The total rms is defined as:

$$I_{LRMS} = \sqrt{I_{Lav}^2 + i_{LrRMS}^2}$$

The general formula for the RMS current is.

$$I = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

The ripple current RMS can be calculated by considering the four separate triangles, each with a magnitude of  $\Delta I$ , for the time intervals ( $t_0..t_1$ ), ( $t_1..t_2$ ), ( $t_2..t_3$ ), ( $t_3..t_4$ ).

$$\Delta I = \frac{dI}{dt} t_1 = \frac{5}{1.3} 1.25 = 4.8A$$

Considering the triangle ( $t_1..t_2$ ) where we shift the time to get a zero point at  $t_1$ , gives:

$$\begin{aligned} I_{LrRMS2} &= \sqrt{\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \left( \Delta I \cdot \frac{t - t_1}{t_2 - t_1} \right)^2 dt} = \{\tilde{t} = t - t_1\} = \sqrt{\frac{1}{t_2 - t_1} \int_0^{t_2 - t_1} \left( \Delta I \cdot \frac{\tilde{t}}{t_2 - t_1} \right)^2 dt} \\ &= \sqrt{\frac{\Delta I^2}{(t_2 - t_1)^3} \left[ \frac{\tilde{t}^3}{3} \right]_0^{t_2 - t_1}} = \frac{\Delta I}{\sqrt{3}} \end{aligned}$$

The total RMS for the ripple current becomes the same since it is the sum of the four triangles divided by 4 to get the total RMS for a full cycle.

$$I_{LrRMS} = \frac{\Delta I}{\sqrt{3}} = \frac{4.8}{\sqrt{3}} = 2.8A$$

The total RMS current;

$$I_{LRMS} = \sqrt{I_{Lav}^2 + i_{LrRMS}^2} = \sqrt{16^2 + 2.8^2} = 16.2A$$