
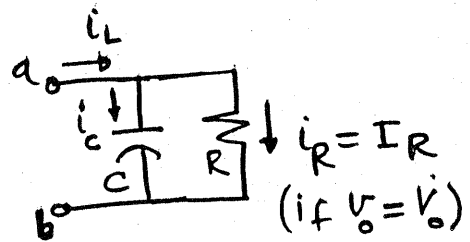


# Problem 1-5

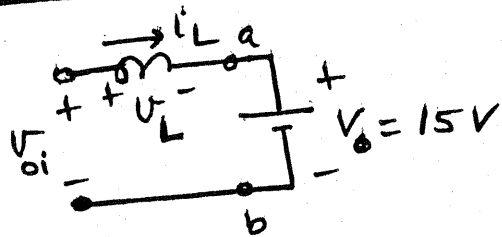

$$T_s = \frac{1}{f_s} = 3.33 \mu s$$

$$DT_s = 0.75 \times T_s = 2.5 \mu s$$


$$I_R = \frac{240W}{15V} = 16A$$

$$i_L = i_c + i_R$$

$$\therefore I_L = I_R \text{ (since } I_c = 0)$$

$$= 16A \text{ average}$$

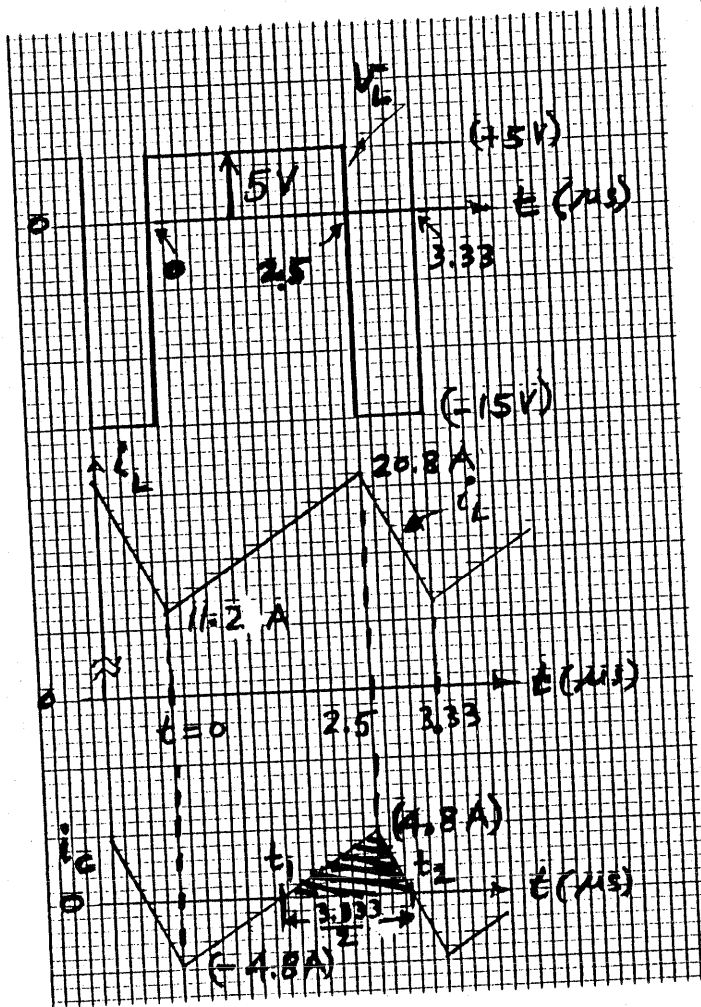During  $0 < t < 2.5 \mu s$  when the switch is ON,  $V_L = V_d - V_o = 20 - 15 = 5V$ . The waveforms are shown below. The peak-to-peak ripple  $(\Delta i_L)_{pp}$



in the inductor current  $i_L$  can be calculated during this interval,  $2.5 \mu s$

$$(\Delta i_L)_{pp} = \frac{1}{L} \int_0^{2.5 \mu s} V_L \cdot dt$$

$$= \frac{5 \times 2.5}{1.3}$$

$$\approx 9.6 A$$

$$\& \frac{(\Delta i_L)_{pp}}{2} = 4.8 A$$

$$\therefore I_{L, \min} = I_L - 4.8$$

$$= 11.2 A$$

and

$$I_{L, \max} = I_L + 4.8$$

$$= 20.8 A$$

$$i_c(t) = i_L(t) - I_R \quad [\text{assuming } i_R \approx I_R]$$

The  $i_c$  waveform is shown. Due to  $i_c$ , the capacitor voltage  $V_c$  will be at its minimum at  $t_1$  and its maximum at  $t_2$ , where  $(t_2 - t_1) = \frac{T_s}{2} = \frac{3.33}{2} \mu\text{s}$ .

$$\begin{aligned} \therefore (\Delta V_c)_{pp} &= \frac{1}{C} \int_{t_1}^{t_2} i_c \cdot dt = \frac{1}{C} [\text{Area shown under } i_c \text{ waveform}] \\ &= \frac{1}{50} \cdot \left[ \frac{4.8 \times 3.33}{2} \right] \\ &\approx 80 \text{ mV} \end{aligned}$$