

Problem 7-1

$$V_o = 5 \text{ V}, \quad V_d = 10 \text{ V to } 40 \text{ V}, \quad P_o \geq 5 \text{ W}, \quad f_s = 50 \text{ kHz}$$

Find the minimum inductance to keep the converter in the continuous conduction mode under all conditions.

Solution: For a given load and output voltage, the likelihood that the inductor current will fall to zero is increased by lowering the duty ratio and thus increasing the OFF time. The duty ratio is lowest when $V_d = 40\text{V}$. $P_o/V_o = 5\text{W}/5\text{V} = I_o = 1\text{A}$

For continuous conduction from Eq. 7-5, $I_o \geq \frac{D}{2f_s L} [V_d - V_o]$

$$D = \frac{5}{40} = 0.125; \quad L = \frac{D}{2f_s I_o} [V_d - V_o] = \frac{0.125}{2 \cdot 50,000 \cdot 1} [40 - 5]$$

$$\boxed{L = 43.75 \mu\text{F}}$$