

Problem 7-8


$$V_d = 12V, V_o = 24V, I_o = 0.5A, L = 150\mu H, C = 470\mu F, f_s = 20kHz.$$

Find  $\Delta V_o$ .

Solution: Initially, assume that the converter is in a continuous-conduction mode.

$$\frac{24}{12} = \frac{1}{1-D} \therefore D = 0.5; \text{ From Eq. 7-29 } I_{oB} = \frac{24 \cdot 0.5 (0.5)^2}{2 \cdot 20,000 \cdot 150 \cdot 10^{-6}} = 0.5 \text{ A}$$

Boundary case since  $I_o = I_{oB}$ .

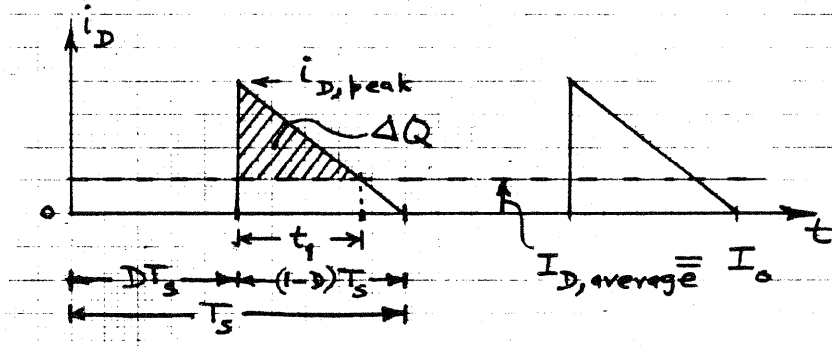

$$i_{D,peak} = i_{L,peak} = \frac{V_d}{L} DT_s = \frac{12 \cdot 0.5}{150 \times 10^{-6} \cdot 20,000} = 2A$$

$$\text{during off time: } \frac{di_D}{dt} = \frac{V_d - V_o}{L} = \frac{12 - 24}{150 \times 10^{-6}} = -80,000 \text{ A/s}$$

$$\text{Therefore, } \left( -\frac{di_D}{dt} \right) = \frac{i_{D,peak} - I_o}{t_1} = 80,000; \therefore t_1 = \frac{2-0.5}{80,000} = 18.75 \times 10^{-6}$$

$$\Delta V_o = \frac{\Delta Q}{C} = \frac{1}{2} \frac{(i_{D,peak} - I_o)t_1}{C} = \frac{1}{2} \cdot \frac{(2-0.5)18.75 \times 10^{-6}}{470 \times 10^{-6}} = \boxed{\Delta V_o = 29.92 \text{ mV}}$$

Note that the expression for  $\Delta V_o$  given by Eqs. 7-39 and 7-40 is valid only if the minimum value of  $i_L$  is greater than  $I_o$  in the continuous-conduction mode of operation (as shown in Fig. 7-17 a).